


EE 140

MOS Source-Coupled Pair

CTN

10

MOSFET Source-Coupled Pair

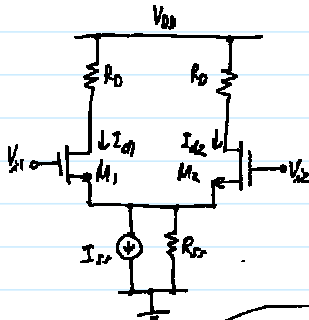

Assume:  $M_1, M_2$  are identical.

Find  $\Delta I_D = I_{D1} - I_{D2} = f(V_{id})$ .

$\rightarrow$  approach: get  $V_{id} = f(\Delta I_D) \rightarrow$  then invert to get  $\Delta I_D = f(V_{id})$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS1} - V_t)^2 \Rightarrow V_{GS1} = V_t + \sqrt{\frac{2I_{D1}}{k}}$$

$$\therefore V_{id} = V_{GS1} - V_{GS2} = \sqrt{\frac{2I_{D1}}{k}} - \sqrt{\frac{2I_{D2}}{k}}$$

$$\text{Define: } \begin{cases} \Delta I_D = I_{D1} - I_{D2} \\ I_D = \frac{I_{D1} + I_{D2}}{2} \end{cases} \Rightarrow \begin{cases} I_{D1} = I_D + \frac{\Delta I_D}{2} \\ I_{D2} = I_D - \frac{\Delta I_D}{2} \end{cases}$$

$$V_{id} = \sqrt{\frac{2(I_D + \frac{\Delta I_D}{2})}{k}} - \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_D + \frac{\Delta I_D}{2} - 2\sqrt{I_D^2 - (\frac{\Delta I_D}{2})^2} + I_D - \frac{\Delta I_D}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_D - 2\sqrt{I_D^2 - (\frac{\Delta I_D}{2})^2}$$

$\Rightarrow$  now rearrange to get  $\Delta I_D$  (algebra)

Solve for  $\Delta I_D$ :  $\Delta I_D = \frac{k}{2} V_{id} \left( \frac{2I_{SS}}{k} - V_{id}^2 \right)^{\frac{1}{2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left( \frac{2I_{SS}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_D$

Large Signal Equation for Differential Output Current

Valid so long as the devices stay saturated:


$$|V_{id}| \leq \sqrt{\frac{2I_{SS}}{k}} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

$V_{GS}$  for  $I_D = \frac{I_{SS}}{2}$

if true then input devices are both saturated

Thus, to extend the linear input range:

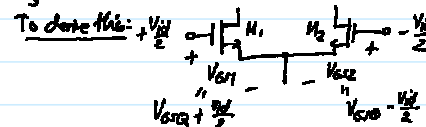- ①  $I_{SS} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ②  $W/L$
- ③  $L \uparrow$



When  $V_{id} \geq V_{GS} - V_t$  or  $V_{id} \leq -V_{GS} + V_t$  then  $M_2$  will cut-off


$\therefore |V_{id}| \leq 2(V_{GS} - V_t) \rightarrow$  to maintain saturation

$$V_{GS} - V_t = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$


Then plug in  $\Delta I_D$  + solve for  $V_{id}$

EE 140 Diff. Pair w/ Current Mirror Load CTN 11

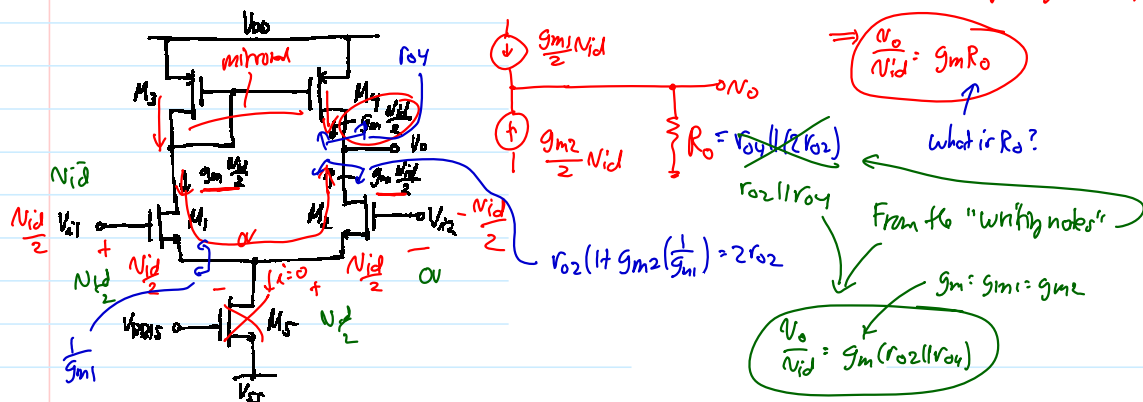MOS Differential Stage w/ Current Mirror Load



CMRR-

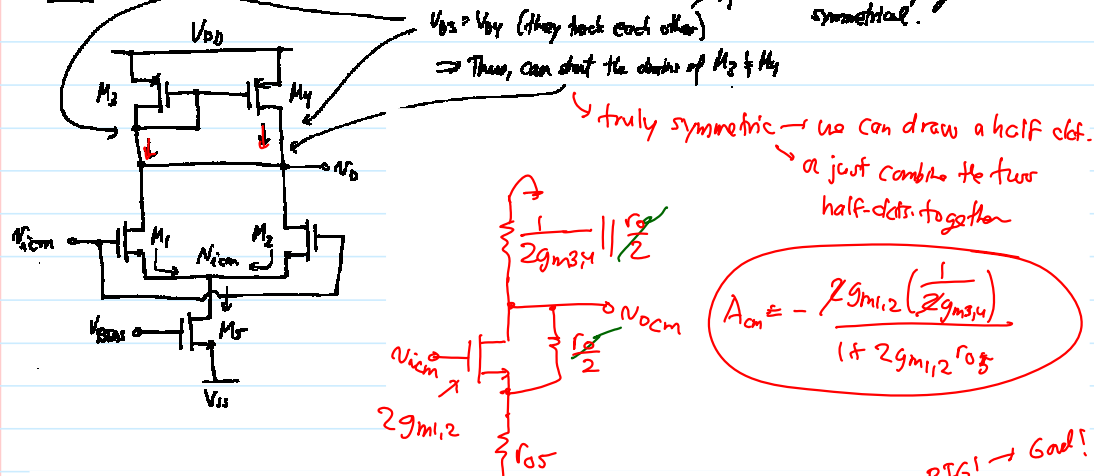

Thus:

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1,2} (r_{o1,2} || r_{o3,4}) (1 + 2g_{m1,2} r_{o5}) \left( \frac{g_{m3,4}}{g_{m1,2}} \right) \rightarrow CMRR = (1 + 2g_{m1,2} r_{o5}) g_{m3,4} (r_{o1,2} || r_{o3,4})$$

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep  $M_5$  saturated

$$V_{icm(min)} = CMR^- = V_{S1} + V_{ovs} + V_{ovs1,2}$$


$$CMR^- = V_{S1} + \sqrt{\frac{2I_{D5}}{\mu_n C_{ox}(W/L)_5}} + V_{E1,2} + \sqrt{\frac{I_{D1,2}}{\mu_n C_{ox}(W/L)_{1,2}}}$$

EE 140

Diff. Pair w/ Current Mirror Load

CTN

12

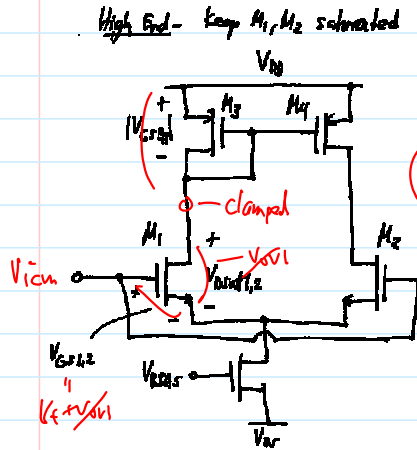

$$V_{icm(max)} = CMR+ = V_{DD} - |V_{GS3,4}| - V_{GS1,2} + V_{GS1,2}$$

$$V_{icm(max)} = CMR+ = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox}(W/L)_{3,4}}} - |V_{GS3,4}| + V_{GS1,2}$$