

Lecture 14: Source Coupled Pairs & Vos

• Announcements:

- I am on travel this week
 - ↳ This is a video recorded lecture
 - ↳ Please watch the online lecture videos before the week after
- Pre-Lecture materials online
- HW#6 online ... now due this Friday
- HW#1A online 240A folks
- Should have turned in returned HW#5 on Monday morning
- Midterm is three weeks away, Oct. 29, in the evening


• Lecture Topics:

- ↳ Emitter Coupled Pair Example
- ↳ Source Coupled Pair
- ↳ Current Mirror Load
- ↳ Offset Voltage

• Last Time:


- In the middle of the Pre-Lecture handout ... continue with this

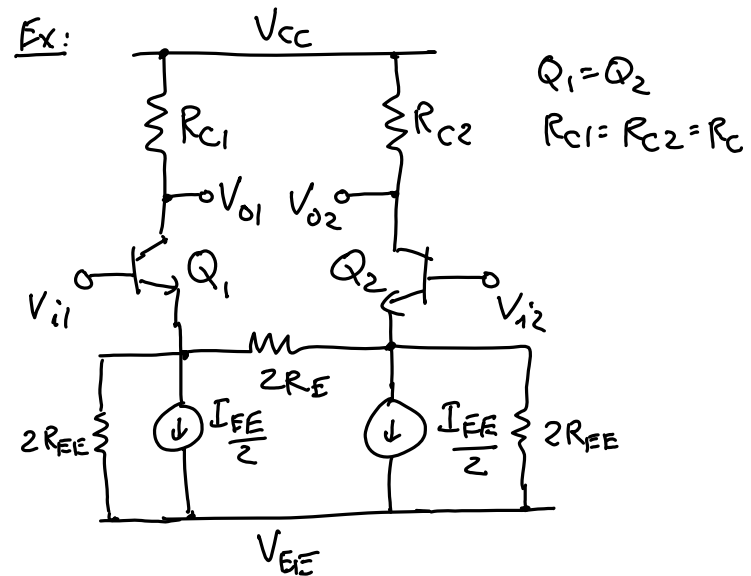- -----
- Last Time:
- Going through op amp handout; continue this



(1) Find the differential gain (A_{dm})



S.S. Ckt:

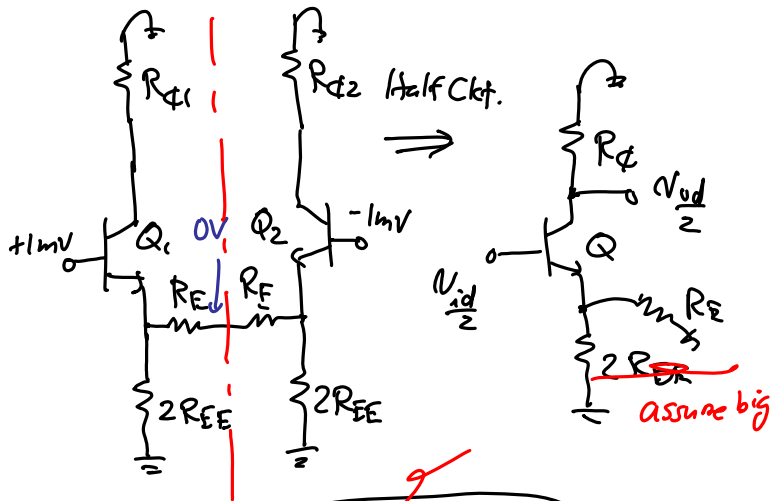


$$\frac{(V_{od}/2)}{(V_{id}/2)} = \frac{-g_m(V_o(1+g_m R_E) || R_c)}{1+g_m R_E}$$

$$A_{dm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}} = \frac{V_{od}}{V_{id}}$$

(2) Find the common-mode gain: (A_{cm})

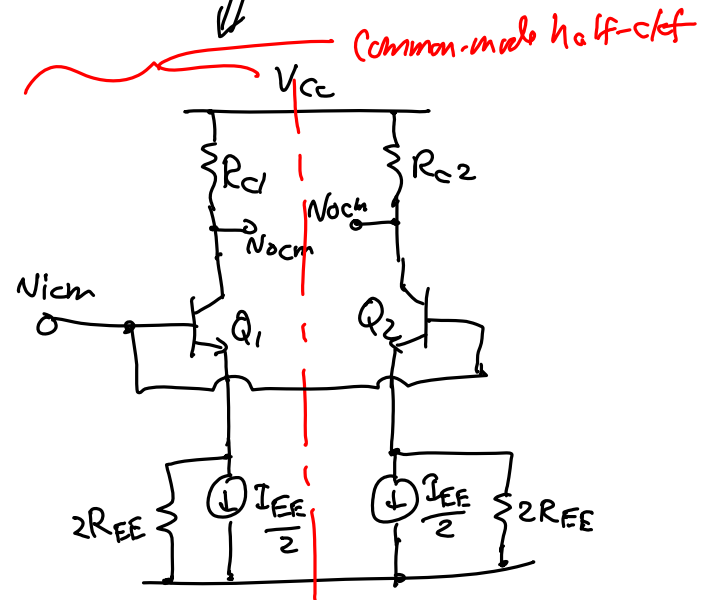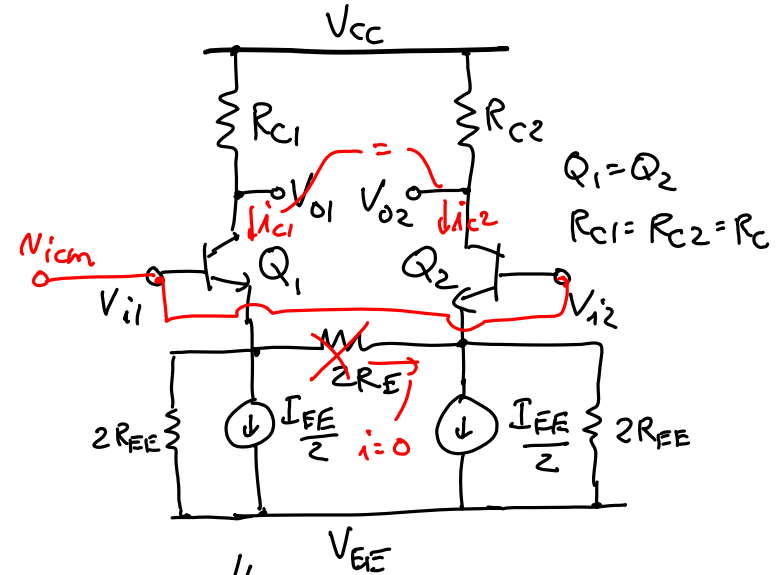

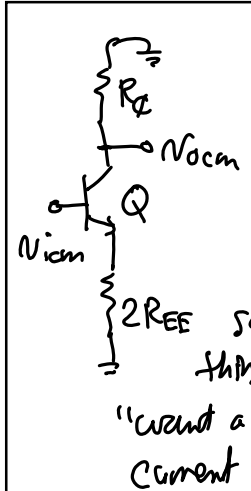

$$A_{cm} = \frac{v_{ocm}}{v_{icm}} = \frac{-g_m R_C}{1 + g_m (2R_{EE})} \approx -\frac{R_C}{2R_{EE}}$$

Want $2R_{EE} \gg R_C$
 "want a good current source"
 $A_{cm} \downarrow \rightarrow$ reject noise better!


If there is a mismatch in the load, e.g., $R_{C1} \neq R_{C2}$, then we can also define:

$A_{cm-dm} \triangleq$ common-mode input to differential-mode output gain
 $= \frac{v_{od}}{v_{ic}} = \frac{v_{o1} - v_{o2}}{v_{i1}} = \frac{v_{o1} - v_{o2}}{v_{i2}}$ (w/ $v_{i1} = v_{i2}$)

$A_{dm-cm} \triangleq$ differential-mode input to common-mode output gain
 $= \frac{v_{oc}}{v_{id}} = \frac{v_{oc}}{v_{i1} - v_{i2}}$ [w/ $v_{oc} = \frac{1}{2}(v_{o1} + v_{o2})$]

You will be experiencing these in a future trv.


What is R_o ?

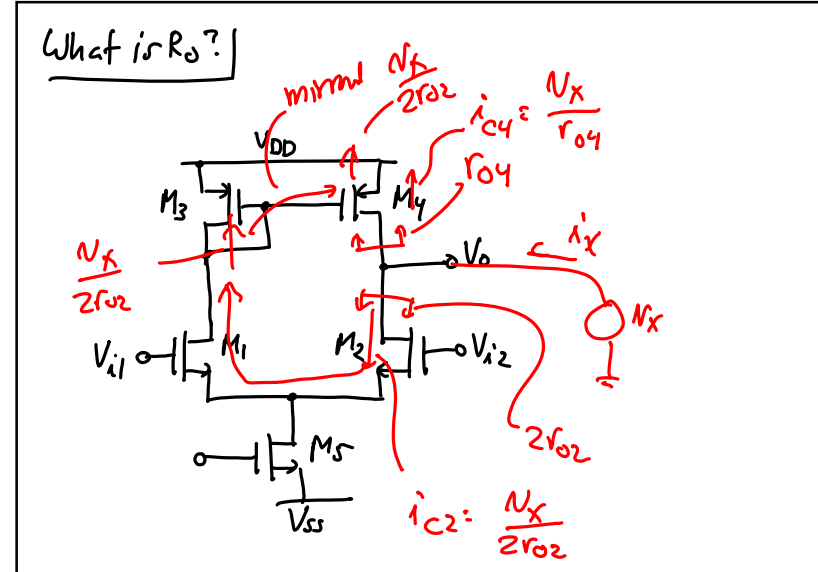

Handwritten notes on the diagram:
 - $i_{c4} = \frac{N_X}{r_{O4}}$
 - $i_{c2} = \frac{N_X}{2r_{O2}}$
 - $i_X = \frac{N_X}{r_{O4}} + \frac{N_X}{2r_{O2}} + \frac{N_X}{2r_{O2}} = \left(\frac{1}{r_{O4}} + \frac{1}{r_{O2}}\right) N_X$
 - mirroring (FB)
 - $\frac{N_X}{i_X} = R_o = (r_{O2} || r_{O4})$

V_{os} of a Mismatched SCP

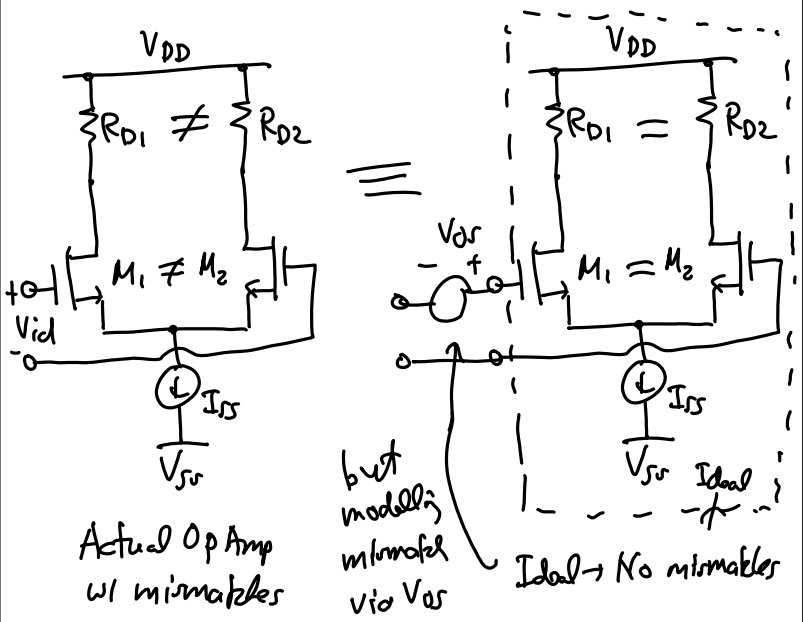
Objective: Determine an expression for V_{os} .



V_{os} arises due to variations in:

- ① $X_{ratio} = M_1 / M_2 \rightarrow \frac{W}{L} \neq V_t$ vary
- ② $R_{D1} \neq R_{D2} \rightarrow$ cause variations in gain

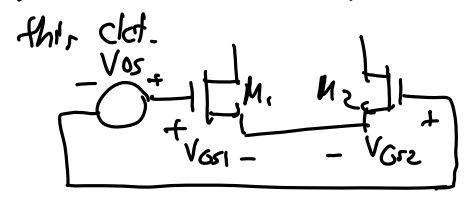Definition. $V_{os} = V_{id}$ needed to get $V_{od} = 0V$ in



KVL: $V_{os} - V_{GS1} + V_{GS2} = 0$

$$\begin{aligned} \therefore V_{os} &= V_{GS} - V_{GS2} \\ &= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} (W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} (W/L)_2}} \\ V_{os} &= V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} (W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} (W/L)_2}} \quad (1) \end{aligned}$$

Define difference and average quantities:

$\Delta I_D = I_{D1} - I_{D2}$	$\Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$
$I_D = \frac{I_{D1} + I_{D2}}{2}$	$\left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$
$\Delta V_t = V_{t1} - V_{t2}$	$\Delta R_D = R_{D1} - R_{D2}$
$V_t = \frac{1}{2} (V_{t1} + V_{t2})$	$R_D = \frac{1}{2} (R_{D1} + R_{D2})$

Rearranging:

$$\begin{aligned} I_{D1} &= I_D + \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} & V_{t1} &= V_t + \frac{\Delta V_t}{2} \\ I_{D2} &= I_D - \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_2 &= \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} & V_{t2} &= V_t - \frac{\Delta V_t}{2} \end{aligned}$$

Substituting into (1): $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}}$$

$$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right] \cdot \frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right]$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1+x)^m \rightarrow 1+mx \quad \eta = \text{small}$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{x + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} - 1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2}$

mismatch in I_D must be opposite that of R_D

$$\therefore \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D}$$

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ - \frac{\Delta R_D}{R_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Mismatch
↑
Bicr Indep.

Geometric Variations
(i.e., layout)
↓
scale cr overdrp

Again, signs mean nothing as could have

$$\frac{\Delta R_D}{R_D} = (-) \quad \frac{\Delta(W/L)}{(W/L)} = (-)$$

Take the worst case by convention → add everything