


Lecture 15: High Gain Op Amps

- Announcements:
  - I am still on travel today
    - ↳ This is a video recorded lecture
    - ↳ Please watch the online lecture videos before next week
  - Pre-Lecture materials online (for Vos)
  - HW#6 online ... now due this Friday, 10/16
  - HW#1A online 240A folks
  - Midterm is getting closer: Oct. 29, in the evening
  - Lecture Topics:
    - ↳ Finish offset Voltage (bipolar)
    - ↳ Finite Gain BW
    - ↳ Effect of FB (a first pass)
    - ↳ High Gain Op Amps
- 
- Last Time:
  - SCP input offset voltage
  - Go through offset voltage handout (skim in lecture, then you should go through it more slowly later)

over

Finite Op Amp Gain & Bandwidth

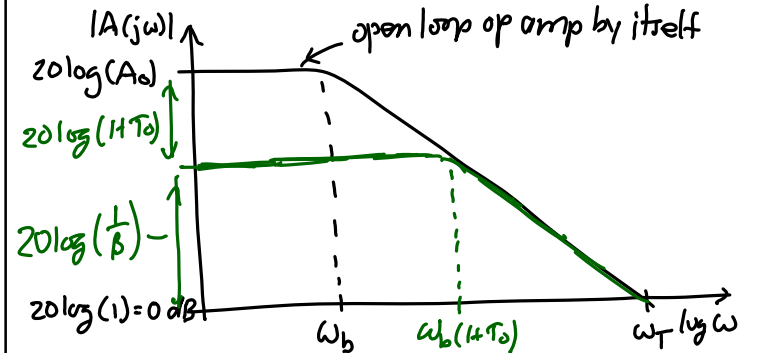For an ideal op amp,  $A = \infty$ .  
 In reality, the gain is given by:  $A(s) = \frac{A_0}{1 + s/\omega_b}$



$\omega_T \triangleq$  unity gain frequency = freq. @ which  $|A(j\omega)| = 1$  (= 0dB)

At  $\omega_T$ :

$$|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}}$$

$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\omega_T} = 1 \rightarrow \omega_T = A_0 \omega_b$   
 Gain-Bandwidth Product


For  $\omega \gg \omega_b$ :

$$A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f} \left[ \begin{array}{l} \text{Integrate w/ time} \\ \text{Constant } C = \frac{1}{\omega_T} \end{array} \right]$$

The unity gain bandwidth  $f_T$  is usually specified on op amp data sheets. Knowing  $f_T$ , one can easily determine the op amp gain at a given frequency  $f$ .

Frequency Response of Closed Loop Amplifiers

Example. Non-Inverting Amplifier

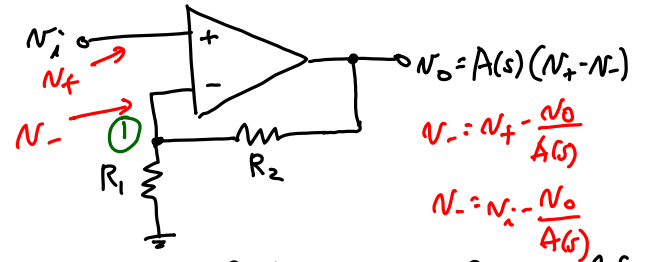

$$V_- = V_+ - \frac{V_o}{A(s)}$$

$$V_- = V_i - \frac{V_o}{A(s)}$$

Find an expression for the gain as a function of frequency.


① Brute force derivation:

$$\text{KCL } \textcircled{1}: \frac{V_o - V_-}{R_2} = \frac{V_-}{R_1} \rightarrow \frac{V_o}{R_2} = V_- \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\frac{V_o}{R_2} = \left( V_i - \frac{V_o}{A(s)} \right) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{V_o}{V_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left( 1 + \frac{R_2}{R_1} \right)}$$

$$\left[ A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{V_o}{V_i}(s) = \left( 1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b} \left( \frac{R_1 + R_2}{R_1} \right)}$$

② More insightful way to do this:

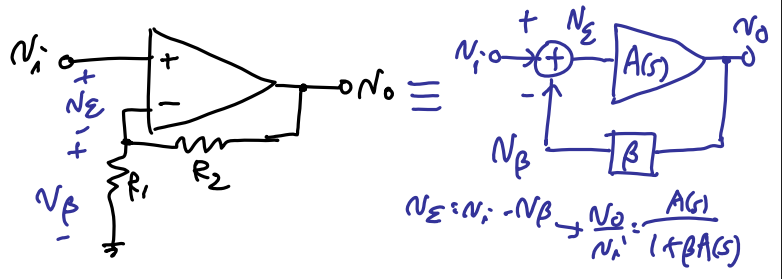

What is  $\beta$ ?

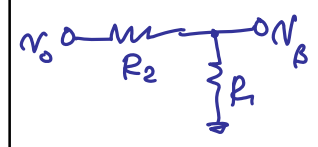


$$\beta = \frac{V_\beta}{V_o} = \frac{R_1}{R_1 + R_2}$$

feedback factor

Recall f/ previous FB analysis:

$$\frac{V_o}{V_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$
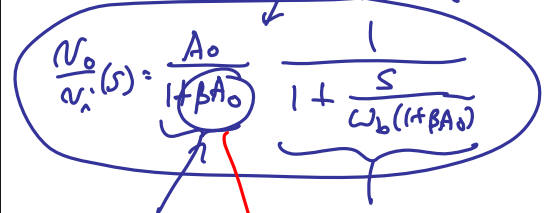
$$\left[ A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \rightarrow \frac{V_o}{V_i}(s) = \frac{A_0}{1 + \frac{s}{\omega_b} \left( 1 + \beta \frac{A_0}{1 + \frac{s}{\omega_b}} \right)}$$



closed loop dc gain term

frequency shaping term

If  $A_0 \rightarrow \infty$ ,  
or if  $\beta A_0 \gg 1 \Rightarrow \text{dc gain} = \frac{1}{\beta}$   $T_0 = \beta A_0 \hat{=} \text{"loop gain" @ } \omega=0$   
(i.e., @ dc)

Plug in  $\beta$ : [for  $\beta A_0 \gg 1$ ]

$$\frac{V_o}{V_i}(s) \cong \frac{1}{\beta} \frac{1}{1 + \frac{s}{\omega_b \beta A_0}} = \left( 1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{\omega_b A_0} \left( \frac{R_1 + R_2}{R_1} \right)}$$

Observations:


- ① Closed loop DC gain =  $\frac{A_o}{1+\beta A_o} = \frac{A_o}{1+T_o} \approx \frac{A_o}{T_o}$   
 i.e., the closed loop gain is reduced from the open loop gain by  $1+T_o \rightarrow$  show this on graph [  $T_o \gg 1$  ]
- ② Alternatively, closed loop DC gain  $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta}$  [  $T_o \gg 1$  ]
- ③  $\omega_{-3dB}$  has increased from  $\omega_b \rightarrow \omega_b(1+A_o\beta) = \omega_b(1+T_o)$   
 To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!
- ④ Gain-BW Product =  $\frac{A_o}{1+\beta A_o} \omega_b(1+\beta A_o) = A_o \omega_b = \omega_T$   
 $\therefore$  the Gain-BW product remains the same for the open & closed loop FB cases!

High Gain Op Amps

How can we increase gain?

- ① Cascode
- ② Cascode Amplifier

Telescopic Op Amp w/ Single-Ended Output

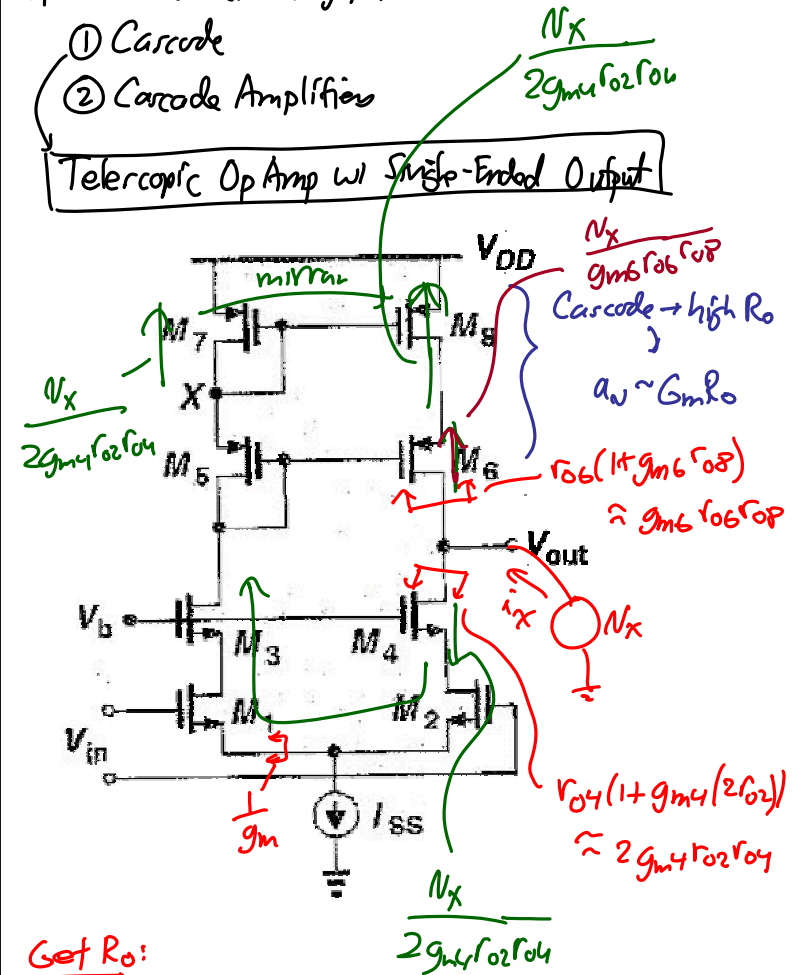

Get  $R_o$ :

$$i_{N_x} = \frac{N_x}{g_{m6} r_{o6} r_{o8}} + \frac{N_x}{2g_{m4} r_{o2} r_{o4}} + \frac{N_x}{2g_{m4} r_{o2} r_{o4}}$$

$$R_o = \frac{V_x}{i_x} = (g_{m6} r_{o6} r_{o8}) \parallel (g_{m4} r_{o2} r_{o4})$$

$$= (g_{mp} r_{op}^2) \parallel (g_{mn} r_{on}^2)$$

Get Gm!

$$i_o = g_m \frac{V_{in}}{2} + g_m \frac{V_{in}}{2} \Rightarrow G_m = \frac{i_o}{V_{in}} = g_m$$

$$\therefore \text{Gain} \cdot A_v = g_{mN} \left[ (g_{mN} r_{oN}^2) \parallel (g_{mP} r_{oP}^2) \right]$$

$$\text{gain will be } \underline{\underline{BIG!}}$$

Freq. Response:

$$\omega_H = \frac{1}{R_o C_L}$$

This contributes the dominant pole since  $R_o \sim \mu\text{sec}$ :

Problem/Issue:

① Limited output swing:  

$$V_{omax} = V_{DD} - |V_{t7}| - |V_{ov7}| - |V_{t5}| - |V_{ov5}| + |V_{t6}| + |V_{ov6}| - |V_{ov6}|$$

$$V_{omin} = V_{ovSS} + V_{ov2} + V_{ov4}$$

$$V_{swing} = V_{omax} - V_{omin}$$

Problem: Not so large!

