

Lecture 17: Slew Rate & Output Stages

Announcements:

- ↪ HW#7 due Monday, Oct. 26, at ~~8 a.m.~~ ^{12 noon}
- ↪ 240A students should be working on HW#1A, too, due Friday, Nov. 6
- ↪ I will be traveling again this Friday, returning next Monday - should be back in time for office hours, depending on flight arrival time
- ↪ Midterm will be on the date specified in your syllabus: Thursday, Oct. 29, 6-8 p.m. in 141 McCone

Lecture Topics:



- Slew Rate (a 1st pass)
- Output Stages

Last Time:

- Telescopic op amps
- For the compensation part of your lab, just assume the load is the oscilloscope input, which is probably 1MΩ

over

Slew Rate ← unity gain FB

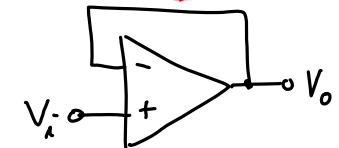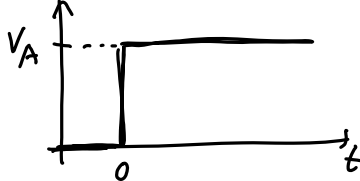Using Laplace Xform Theory:


$$\frac{V_o}{V_i}(s) = \frac{1}{1 + \frac{s}{\omega_i}} = \frac{1}{1 + s\tau_i}$$

← single (dominant) pole


$$V_i(s) = \frac{V_A}{s}$$

$$V_o(s) = \frac{V_A}{s(1 + s\tau_i)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_i}}$$


↕ Inverse Laplace Xform
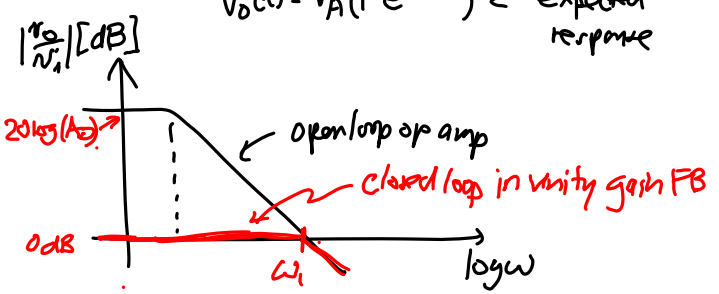
$$V_o(t) = V_A(1 - e^{-t/\tau_i}) \leftarrow \text{expected response}$$

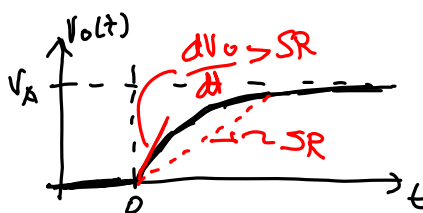
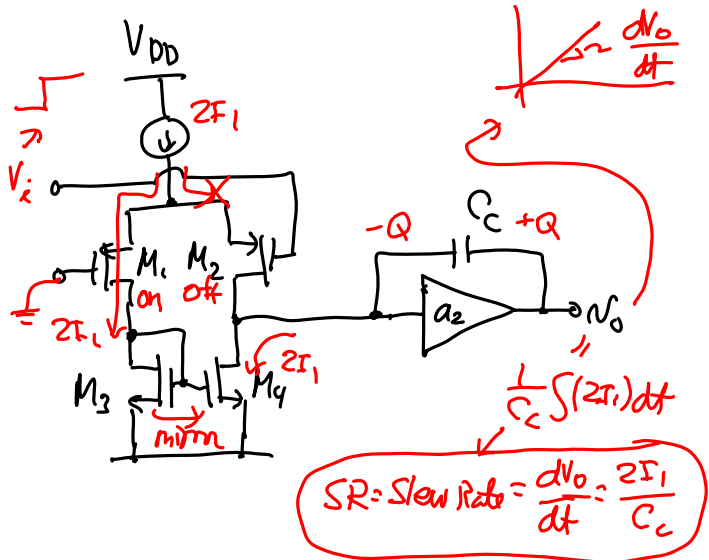
Theoretical Expectation





Reality (Why?)




Reason: 1st or 2nd stage of op amp cannot source enough current to mimic the slope (or speed) of a fast rising theoretical output waveform



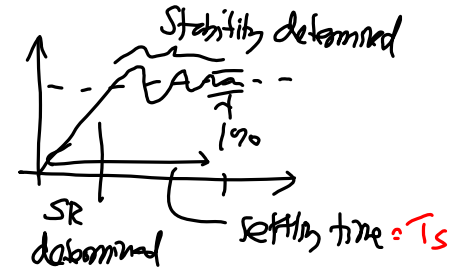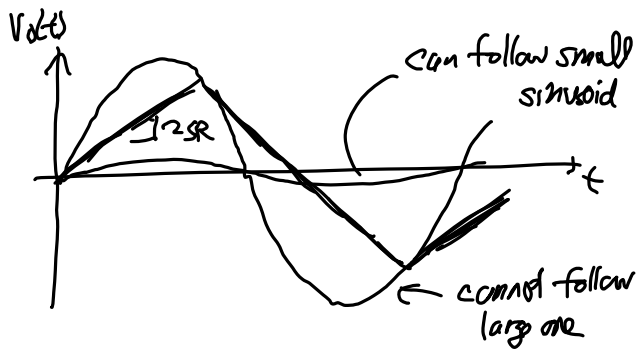Ex. Apply a fast (i.e., high freq., large amplitude) sinusoid



Your Lab

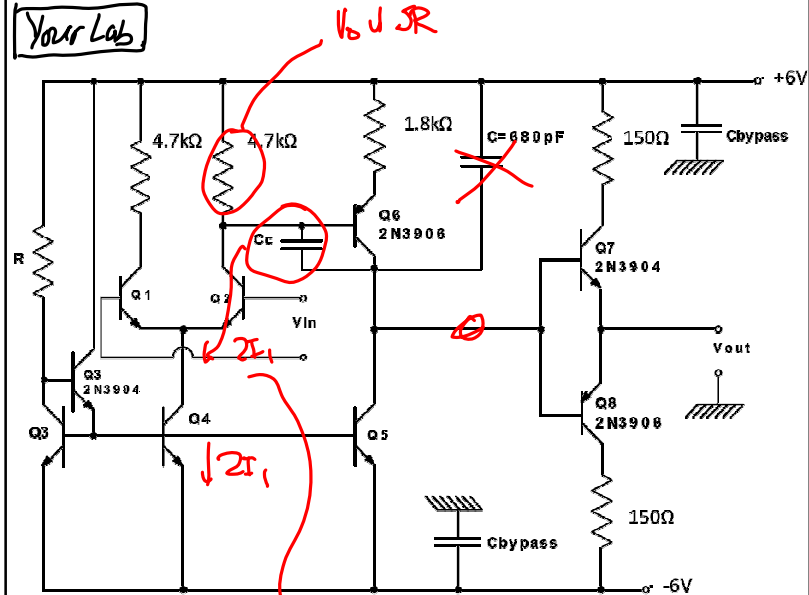

Output Stages

- Class A (Emitter or Source Follower)
- Class B
- Class AB (we'll do this one later)


Purpose: Drive Loads

- ① Deliver power w/ small distortion.
- ② Minimize output impedance \rightarrow so that the amplifier gain is insensitive to the load.

Desirable Attributes:

- ① High R_{in} ; Low R_{out} . \rightarrow *assumes voltage application*
- ② Low quiescent power.
- ③ Minimal effect on the amplifier freq. response.
- ④ Should be able to handle large input/output swings. (i.e., V_i may be $> V_T$, invalidating small-signal approximations)

Emitter Follower (Class A)

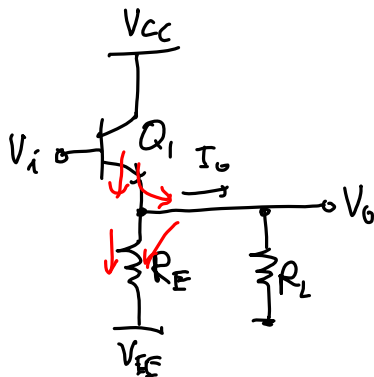

Two Main Cases:

- ① $I_o > 0, V_o > 0$:
 I_o comes from Q_1
 \Rightarrow adequate I_o can be delivered so long as Q stays forward-active


② $I_o < 0: (V_o < 0)$

I_o must be sunk through R_E to V_{EE} .

$$I_o = \frac{V_o - V_{EE}}{R_E} \Rightarrow \text{Issue: } I_o = f(V_o)$$

$\rightarrow I_o \uparrow$ as $V_o \downarrow \rightarrow$ Problem!

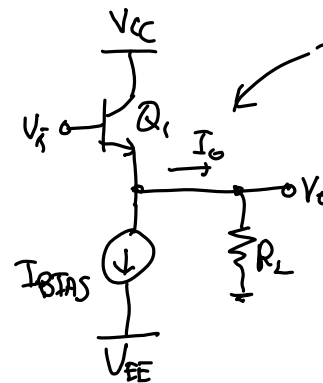Solution: Replace R_E w/ a current source.



for V_i going V_o can source I_o thru Q_1

\bar{Q} can sink I_o thru

$$I_{BIAS} = I_o \text{ (less)}$$

\uparrow
w/ competing w/ Q_1

I_{BIAS} does not get smaller as V_o decreases

\therefore can maintain drive power as V_o Δ 's!

Actual Implementation:

More Accurate:

$V_{BE1} \neq \text{const.} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$ (Q_1 in FAR)

$I_{C1} = I_Q + I_o = I_Q + \frac{V_o}{R_L}$

$\therefore V_i = V_o + V_T \ln\left(\frac{I_Q + V_o/R_L}{I_{S1}}\right) \rightarrow$ for large power

Two Cases: (depending on the size of R_L)

Case ①: $R_L = \text{large}$ ($I_o < I_Q$)

$\Rightarrow I_o$ not Δ 'ing much $\rightarrow I_{C1}$ not Δ 'ing much

For $V_i = \text{large and (+)}$: Q_1 must source $I_o + I_Q$

$V_o = V_i - V_{BE1}$ at some pt., Q_1 will saturate as $V_o \uparrow$

Get $V_{omax} = V_{CC} - V_{CE1(sat)}$

$\hookrightarrow V_i = V_{CC} - V_{CE1(sat)} + V_{BE1} (\geq V_{CC})$

For $V_i = \text{large and (-)}$: V_o follows V_i until Q_2 saturates

$V_{omin} = V_{EE} + V_{CE2(sat)}$

$\hookrightarrow V_i = V_o + V_{BE1} = V_{EE} + V_{CE2(sat)} + V_{BE1}$

Case ②: $R_L = \text{small}$ \rightarrow thus, I_o can be large!

For $V_i = (+)$ and large: Q_1 can source as much current as needed until it either saturates or it fries

For $V_i = (-)$ and large: $V_o = I_o R_L \rightarrow \text{min. } V_o = -I_Q R_L$

$\Rightarrow Q_1$ cut-off ($I_{C1} = 0$) further decrease in V_i yields no ΔV_o

$\Rightarrow V_o$ clamps @ $-I_Q R_L$


If must drive R_L : small \rightarrow need large I_Q

Problem: too much power consumption

$P_Q = (V_{CC} - V_{EE}) I_Q \rightarrow$ DC quiescent power consumption

If want large output swing w/ small $R_L \rightarrow$ must consume power!

Solution: **Class B Output Stage**

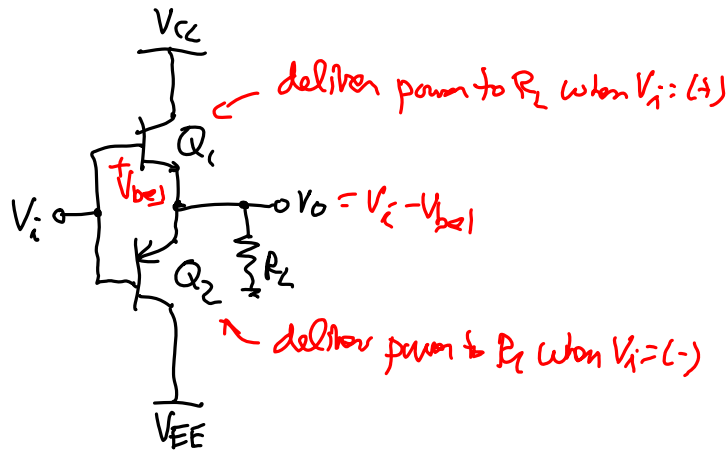

Operation:

$Q_1 \& Q_2$ cut-off

$|V_i| < V_{BE(on)} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_o = 0V$

$V_{CC} > (V_i) > V_{BE(on)} \rightarrow V_o \cong V_i - V_{BE(on)}$

$V_{o,max} = V_{CC} - V_{CE1(sat)}, V_{o,min} = V_{EE} + V_{CE2(sat)}$

