

Lecture 18: Stability

• Announcements:



- ↪ Midterm: Thursday, Oct. 29, 6-8 p.m. in 141 McCone (this coming Thursday)
- ↪ No lecture this coming Thursday -> Prof. Nguyen will hold office hours, instead
- ↪ Midterm info sheet online (indicates extra office hours this week)
- ↪ Solutions to all HW's through HW#7 online (except 1A)
- ↪ Review Session on Tuesday evening, 6-8 p.m., in 293 Cory
- ↪ 240A students: HW#1A due Friday, Nov. 6

• Lecture Topics:

- ↪ Finish output stages
- ↪ Stability

• Last Time:

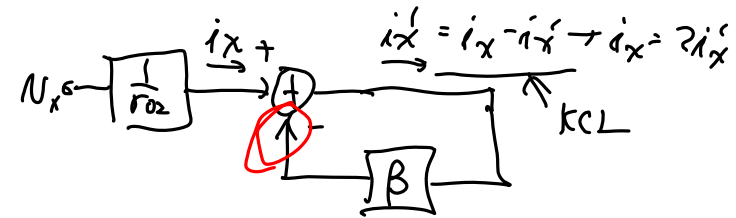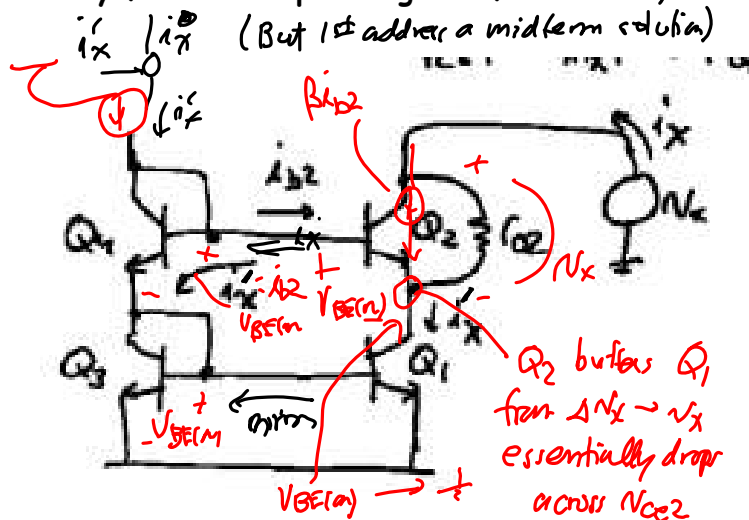Nearly finished output stages ... finish now <sup>from Spring 2013</sup>



$$\frac{v_x}{i_x} = (\beta+1)r_{o2} \rightarrow \frac{v_x}{i_x} = \frac{1}{2}(\beta+1)r_{o2} = \frac{1}{2}\beta r_{o2} \checkmark$$

$$i_x = \frac{v_x}{r_{o2}} - \beta i_x' \rightarrow i_x'(\beta+1) = \frac{v_x}{r_{o2}}$$


$$\frac{v_x}{i_x'} = (\beta+1)r_{o2}$$

⇒ above done by essentially "following the currents" through the feedback ckt.

⇒ Can also do this using full hybrid-π circuit analysis → get the same answer

↳ this is how most did it on the Spring 2013 Midterm

Class A Output Stage (last time)

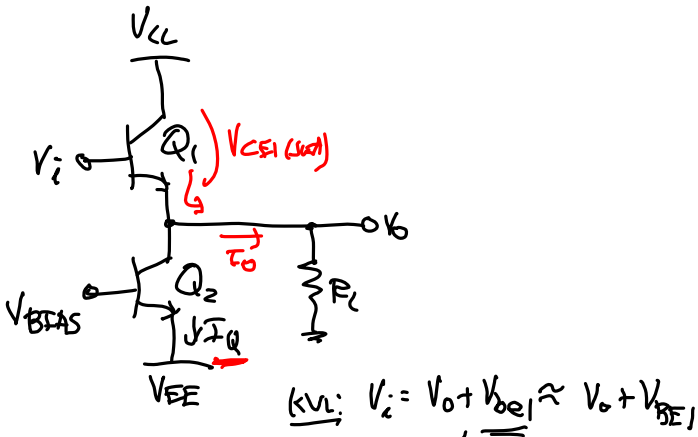


More Accurate:

$$V_{be1} \neq \text{const.} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) \quad (Q_1 \text{ in F.A.R.})$$

$$I_{C1} = I_Q + I_o = I_Q + \frac{V_o}{R_L}$$
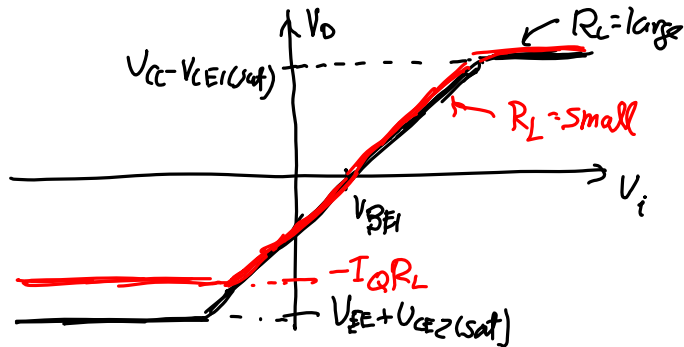
$$\therefore V_i = V_o + V_T \ln\left(\frac{I_Q + V_o/R_L}{I_{S1}}\right) \rightarrow \text{for large power}$$




If must drive  $R_L = \text{small} \rightarrow$  need large  $I_Q$

Problem: too much power consumption

$$P_Q = (V_{CC} - V_{EE}) I_Q \rightarrow \text{DC quiescent power consumption}$$

If want large output swing w/ small  $R_L \rightarrow$  must consume power!

Solution: Class B Output Stage

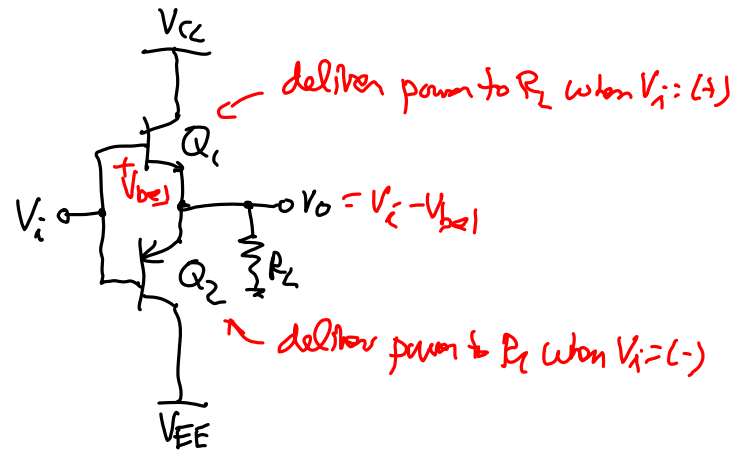



Operation:

$Q_1$  &  $Q_2$  cut-off

$$|V_i| < V_{BE(on)} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_o = 0V$$

$$V_{CC} > |V_i| > V_{BE(on)} \rightarrow V_o \cong V_i - V_{BE(on)}$$

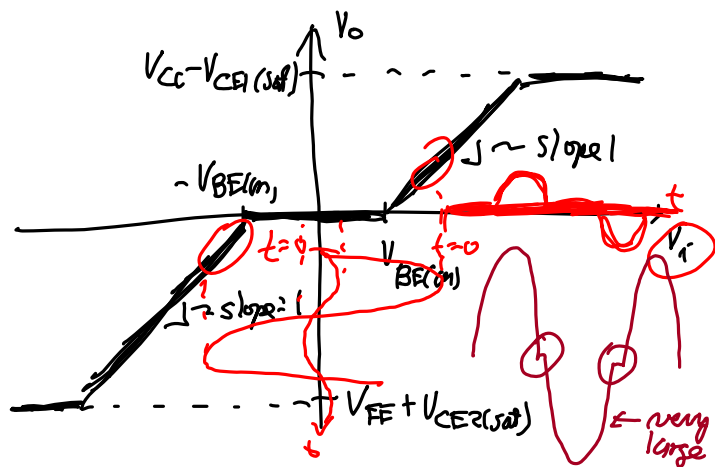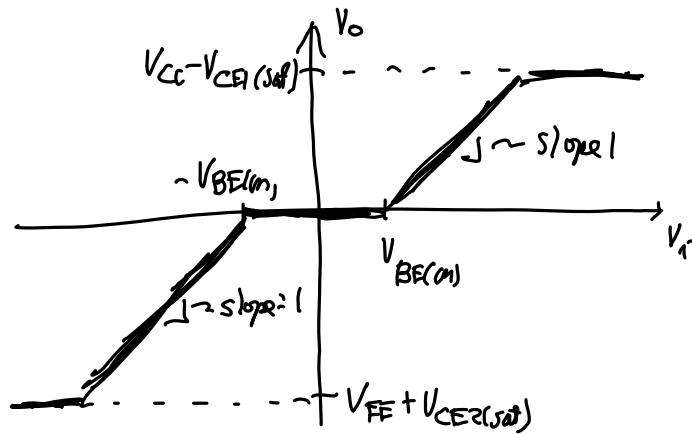
$$V_{o,max} = V_{CC} - V_{CE1(sat)}, V_{o,min} = V_{EE} + V_{CE2(sat)}$$



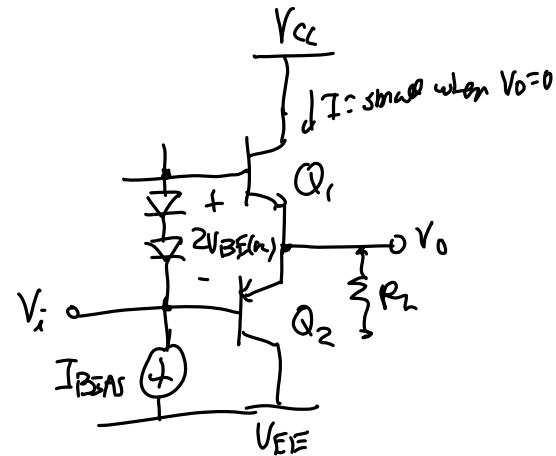Problem: Distorted output due to the dead zone.



Solution: **Class AB Amplifier**

use diodes to supply enough voltage to keep  $Q_1$  &  $Q_2$  on w/ small current



⇒ you will see this on a future HW

**Settling Time**

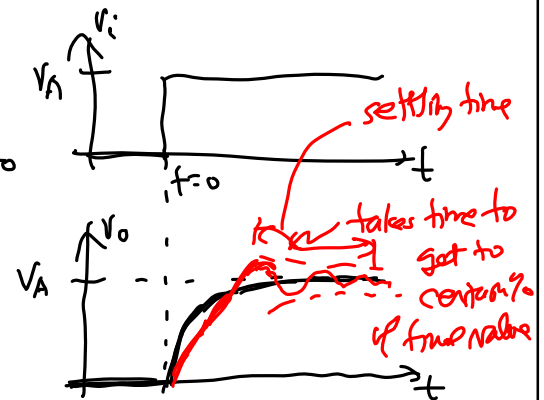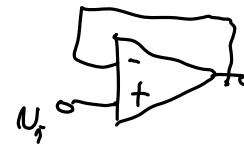


Stability & Compensation in Op Amps

In general, op amps are used in neg. FB loops.

Reasons:


- ① Feedback sets the biasing → no large coupling or bypass caps needed.
- ② FB increases BW.
- ③ FB increases linearity or input range.  
(eg., emitter degeneration is a type of FB)
- ④ Gain determined by external FB components → more accurate than op amp gain.
- ⑤ FB sets  $R_i$  and  $R_o$ .
- ⑥ FB can improve temperature stability.

Stability & Compensation

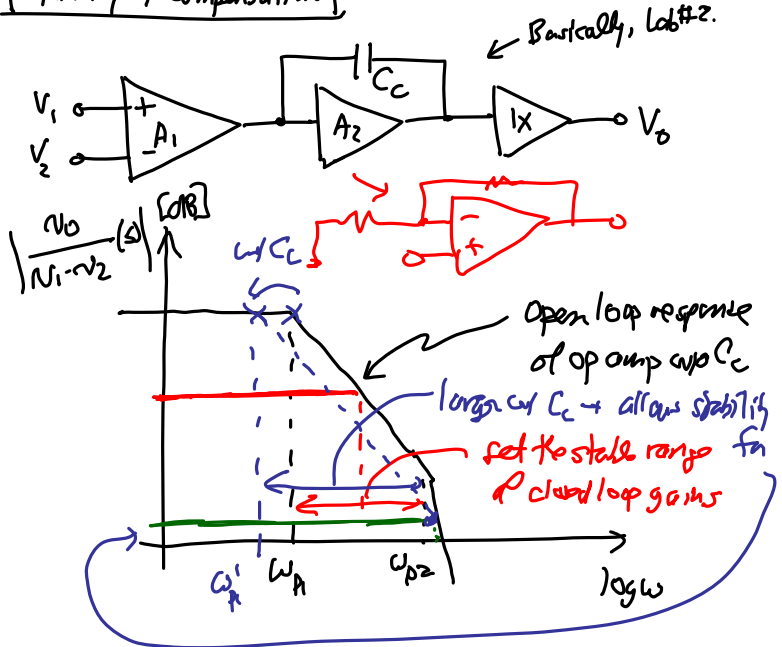

⇒ Problem: any FB loop can become unstable under certain conditions → ∴ must compensate to suppress instability!

Ex. Non-inverting Amplifier

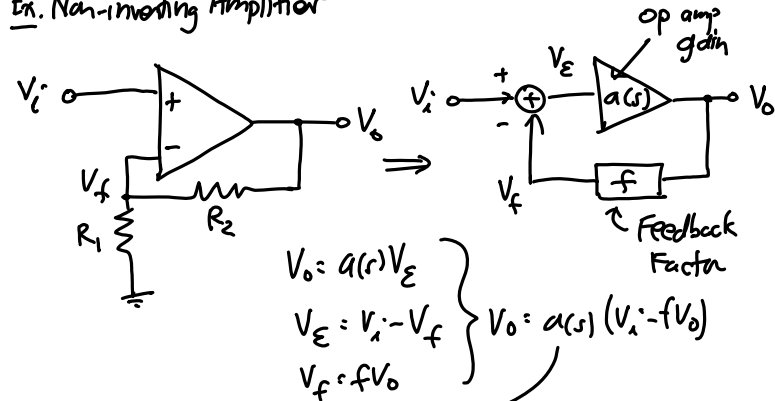

$$\begin{aligned} V_o &= a(s)V_E \\ V_E &= V_i - V_f \\ V_f &= fV_o \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} V_o = a(s)(V_i - fV_o)$$

$$\underline{A(s)} = \frac{V_o(s)}{V_i(s)} = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)}$$

closed loop gain

Loop Transmission =  $T(s) = a(s)f$   
↙ ⇒ fun of freq.

e.g., loop gain =  $a(j\omega=0)f = a_0f = T_0$

Instability occurs when  $A(s) \rightarrow \infty$ !

$$\Rightarrow A(s) = \frac{a(s)}{1 + a(s)f} \rightarrow A(s) = \frac{a(s)}{1 - 1} = \frac{a(s)}{0} \rightarrow \infty$$

$a(s)f = -1$   
loop transmission will also go unstable if denominator is (-)

In General: ✓ ✓

If  $|a(s)f| \geq 1$  when  $\angle a(s)f = -180^\circ \Rightarrow$  unstable

This is a simplified form of the Nyquist criterion.

Stability of a FB Ckt. Using a Single-Pole Op Amp

For a single-pole op amp:  $a(s) = \frac{a_0}{1 - \frac{s}{P_1}}$  open-loop op amp Xfer Fcn.

Thus: (close to loop)

$$A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0 f} \frac{1}{1 - \frac{s}{A(1 + a_0 f)}}$$

closed-loop Xfer Fcn

$A_0 =$  closed-loop dc gain


if  $a_0 f \gg 1 \rightarrow \approx \frac{1}{f}$

BW increases by  $1 + a_0 f$

$T_0 = a_0 f =$  loop gain (defined @ DC)


$T(s) = a(s)f =$  loop transmission (defined for general freqs.)

Bode Plot:  $\rightarrow$  use to determine  $\angle a(s)f$  when  $|a(s)f| = 1 = 0 \text{ dB}$

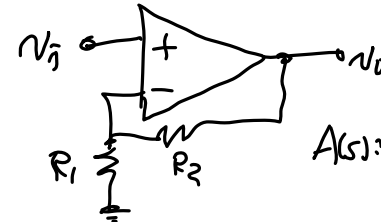

then can determine stability
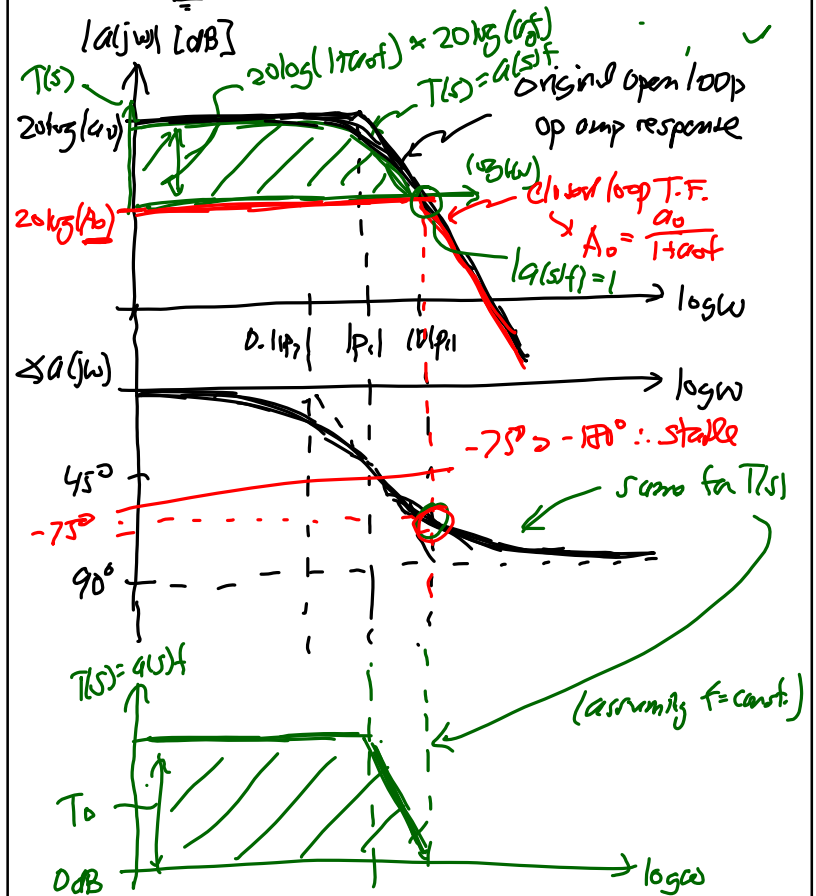
$$A(s) = \frac{V_o}{V_i}(s) = \frac{a(s)}{1 + a(s)f}$$



Remarks:

w/  $f = \text{const}$

① For the case of a single-pole op amp,  $\text{FB}^{\uparrow}$  can never reach  $\angle a(s)f = -180^\circ$ . ( $90^\circ$  is the limit.)

② Thus, a single-pole op amp in FB w/  $f = \text{const}$ , i.e.,  $f \neq$  function of  $s = j\omega$ , is always stable!

↓  
But in reality, any op amp will have more

than one pole  $\rightarrow$  two poles get to

$$\angle a(s)f = -180^\circ$$

↓  
instigate instability

↓  
use a Bode plot  
to investigate