

Welcome to EE 140/240A
Analog Integrated Circuits
Prof. Clark Nguyen


Lecture 1: Admin & Overview

- Announcements:
- EE 140/240A: Analog Integrated Circuits
- Instructor: Prof. Clark T.-C. Nguyen
- -----
- Go though
 - ↪ Course information sheet
 - ↪ Syllabus
 - ↪ Grading Information and Policy
- Hand out class account sheets → *Not yet... will do this next week!*
- About Me:
- Education: Ph.D., University of California at Berkeley, 1994
- 1995: joined the faculty of the Dept. of EECS at the University of Michigan
- 2006: (came back) joined the faculty of the Dept. of EECS at UC Berkeley
- Research: microelectromechanical systems (MEMS) that employ transistor-level circuit design
- Teaching: (at the UofM) mainly transistor circuit design courses; (UC Berkeley) 140, 143, 240A, 243, 245
- 2001: founded Discera, the first company to commercialize vibrating RF MEMS technology
- Mid-2002 to 2005: DARPA MEMS program manager
 - ↪ ran 10 different MEMS-based programs
 - ↪ topics: power generation, chip-scale atomic clock, gas analyzers, nuclear power sources, navigation-grade gyros, on-chip cooling, micro environmental control
- -----

- For the course website, just google ee140
 - ↳ The website is already up and running
- This course will be screencast
 - ↳ EE 140 screencast previously, so you can actually view previous year lectures, too
 - ↳ If you miss a lecture ... can watch the video, if successfully recorded
 - ↳ Won't be able to view lectures on itunes or youtube as in the past due to new rules
 - ↳ But can still see lectures from previous years
 - ↳ Warning: It's a very bad idea not to come to lecture in person
 - ↳ People who think they will watch the videos, often don't get time to do so
- This course now "contains" EE 240A
 - ↳ EE 240A same as 140, but with additional material for graduate students
 - ↳ Additional homework problems
 - ↳ Additional project specs or a different project altogether
- Office Hour Changes?:
- Discussion sections start week after next
- -----
- Lecture Topics:
 - ↳ Review
 - Op Amp Examples
 - Ideal Op Amps
 - Non-Ideal Op Amps
- -----

- Look at op amp usage examples using prepared pages

Review of Op Amps

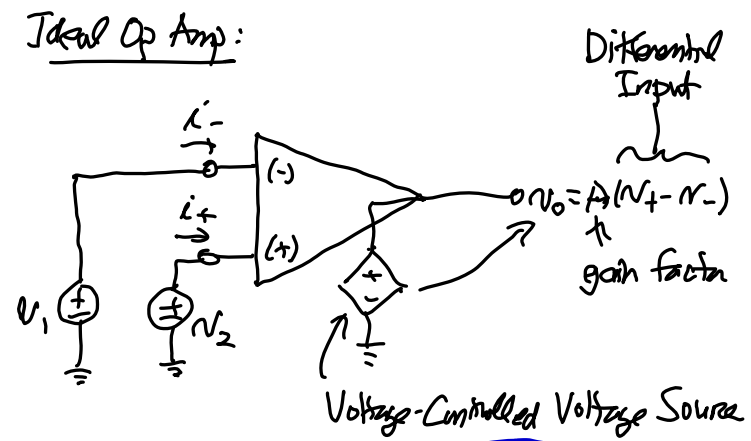

Properties of Ideal Op Amps: (given neg. FB)

- ① $A = \infty \rightarrow v_+ = v_-$ (in a neg. FB ckt.)
 - ② $R_i = \infty \rightarrow i_+ = i_- = 0$
 - ③ $R_o = 0$
 - ④ $BW = \infty$
- $v_O = A(v_+ - v_-)$
 ↑ ↓
 finite ∞ $0 \rightarrow v_+ = v_-$

Inverting Amplifier

Get the gain, $\frac{V_o}{V_i}$.

- Verify that we have neg. FB.
- So $v_o = \text{finite} \rightarrow v_+ = v_-$
- $i_- = 0$

$$i_i = \frac{v_i - 0}{R_1} = \frac{v_i}{R_1} \quad ; \quad v_o = 0 - i_i R_2$$

$$v_o = -\frac{v_i}{R_1} R_2 \rightarrow \boxed{\frac{v_o}{v_i} = -\frac{R_2}{R_1}}$$

Positive FB Example

$\times \rightarrow$ pos. FB
 can't say $v_+ = v_-$

- **Non-Ideal Op Amps:**
- Actual op amps, of course, are not ideal; rather, they ...
 - ↳ Have finite gain, A_o
 - ↳ Have finite bandwidth, BW
 - ↳ Have finite input resistance, R_i
 - ↳ Have finite input capacitance, C_i
 - ↳ Have finite output resistance, R_o
 - ↳ Generate noise
 - ↳ Have input bias currents (because R_i is not infinite)
 - ↳ Have input offset currents and voltages
 - ↳ Have finite slew rate
 - ↳ Have finite output swing
- All of the above can be temperature dependent!
- A major objective of this class is to understand what gives rise to the above non-idealities and to teach design strategies to get around them

- Then, start going through the Device Modeling Handout, on BJT modeling