


EE 140

Review of Pole/Zero Plots

CTN

94

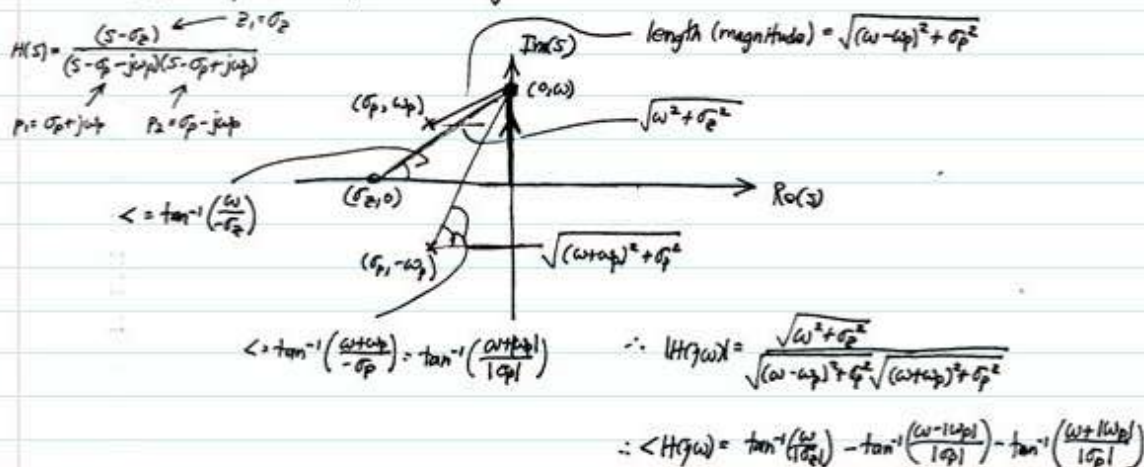The frequency response of a given system is completely characterized by knowledge of the poles, zeros, and dc gain factor (H_0) of the system in question. In fact, the magnitude & phase of the network can be determined graphically from a pole/zero diagram.




In general:

$$|H(j\omega)| = H_0 \frac{\prod_{j=1}^m (\text{mag. of vectors from zeros to } j\omega)}{\prod_{i=1}^n (\text{mag. of vectors from poles to } j\omega)} = H_0 \frac{\prod_{j=1}^m |j(\omega - \omega_{zj}) - \sigma_{zj}|}{\prod_{i=1}^n |j(\omega - \omega_{pi}) - \sigma_{pi}|}$$

$\angle H(j\omega) = \sum \text{angles from zeros} - \sum \text{angles from poles} + \angle H_0$
 $z_j = \sigma_{zj} + j\omega_{zj}$
 $p_i = \sigma_{pi} + j\omega_{pi}$
 could be 0° or 180°
 $(-)$ $(+)$

Precise Determination of Phase

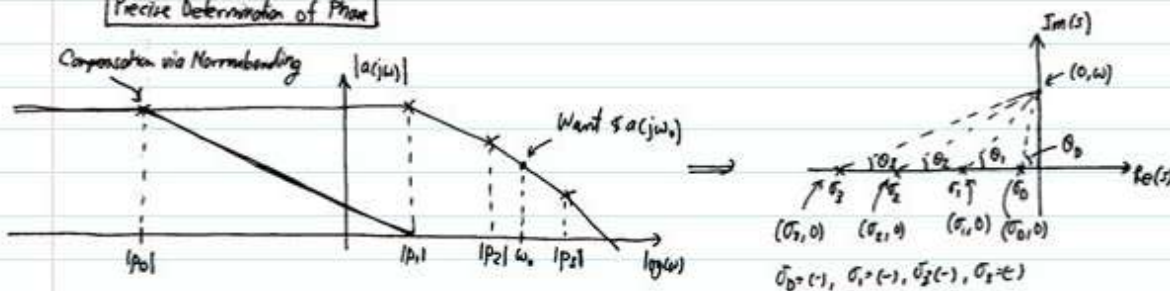

$$\angle a(j\omega) = -\theta_0 - \theta_1 - \theta_2 - \theta_3$$

$$= -\tan^{-1}\left(\frac{\omega}{\sigma_0}\right) - \tan^{-1}\left(\frac{\omega}{\sigma_1}\right) - \tan^{-1}\left(\frac{\omega}{\sigma_2}\right) - \tan^{-1}\left(\frac{\omega}{\sigma_3}\right)$$

$$\therefore \angle a(j\omega) = -90^\circ - 90^\circ - \tan^{-1}\left(\frac{\omega\omega_0}{|p_0|}\right) - \tan^{-1}\left(\frac{\omega\omega_0}{|p_3|}\right)$$

since $\omega_0 \gg |p_0| \ll |p_3|$


EE 140

Review of Pole/Zero Plots

CTN

95

Ex. System w/ 2 poles & 1 RHP zero

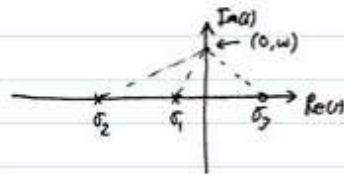

$\sigma_1 < -1$ $\sigma_2 < -1$ since it's a zero!

$$\angle H(j\omega) = -\tan^{-1}\left(\frac{\omega}{-\sigma_1}\right) - \tan^{-1}\left(\frac{\omega}{-\sigma_2}\right) + \tan^{-1}\left(\frac{\omega}{-\sigma_3}\right)$$

$$= -\tan^{-1}\left(\frac{\omega}{|\sigma_1|}\right) - \tan^{-1}\left(\frac{\omega}{|\sigma_2|}\right) + \tan^{-1}\left(-\frac{\omega}{|\sigma_3|}\right)$$

$$\angle H(j\omega) = -90^\circ - 90^\circ + (-90^\circ) \Rightarrow \angle H(j\omega) = -270^\circ$$


$\omega \rightarrow \infty$

$$|H(j\omega)| = \frac{\sqrt{\omega^2 + \sigma_3^2}}{\sqrt{\omega^2 + \sigma_1^2} \sqrt{\omega^2 + \sigma_2^2}}$$

Note: The RHP zero contributes a (-) phase shift!



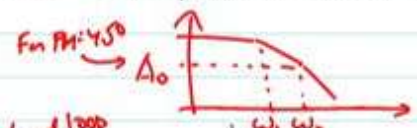Choosing C_c (assuming no RHP zero & $p_3 \gg p_2$)
 \Rightarrow for cases where $\frac{1}{sC_c} \ll$ (surrounding node resistance), can write simple expression for C_c in terms of ω_c
 very often the case



① Case: Two-Stage Amplifier, Miller Compensation

of op amp

closed loop gain

the say that $\omega_u \approx \omega_c$

To compensate for a closed-loop gain A_0 :

For $PM=45^\circ$: $\left| \frac{N_0}{N_1}(j\omega_u) \right| = A_0 = \frac{G_{m1}}{\omega_u C_c} \Rightarrow C_c = \frac{G_{m1}}{\omega_u A_0}$

$\omega_u = \omega @ |T(j\omega)| = 1 = \frac{\omega_u}{1.73}$

2nd pole \rightarrow for 45° PM

For $PM=60^\circ$: $\left| \frac{N_0}{N_1}(j\omega_u) \right| = A_0 = \frac{G_{m1}}{1.73 C_c} \Rightarrow C_c = \frac{1.73 G_{m1}}{\omega_u A_0}$

For $PM=45^\circ$ (provided high- ω poles are far away) ($p_3 \gg p_2$)

$N_0 = \frac{i_x}{sC_c}$
 $i_x = G_{m1} N_1$
 $N_0 = \frac{G_{m1} N_1}{sC_c}$
 $\therefore \frac{N_0}{N_1}(s) = \frac{G_{m1}}{sC_c}$

② Case: Two-Stage Amplifier, Shunt C_c Compensation

of op amp

To compensate for a closed-loop gain A_0 : ($PM=45^\circ$; p_2 and above far away)

For $PM=45^\circ$: $\left| \frac{N_0}{N_1}(j\omega_u) \right| = A_0 = \frac{G_{m1} a_2}{\omega_u C_c} \Rightarrow C_c = \frac{G_{m1} a_2}{\omega_u A_0}$

$\left(\frac{N_0}{N_1}(s) = -\frac{G_{m1} a_2}{sC_c} \right)$ ends up (+) since $a_2 = (-)$

$a_2 \times$ bigger than (consistent w previous analysis)

For $PM=60^\circ$: $C_c = \frac{1.73 G_{m1} a_2}{\omega_u A_0}$

③ Case: Single-Stage Amplifier, Shunt C_c Compensation \Rightarrow we will see this case often in CMOS

again, (+) term/w/ op amp!

$N_0 = \frac{i_x}{sC_c}$
 $i_x = G_{m1} N_1$
 $\frac{N_0}{N_1}(s) = \frac{G_{m1}}{sC_c}$

To compensate for a closed-loop gain A_0 : ($PM=45^\circ$ w/ $p_2 \gg p_2$)

For $PM=45^\circ$: $\left| \frac{N_0}{N_1}(j\omega_u) \right| = A_0 = \frac{G_{m1}}{\omega_u C_c} \Rightarrow C_c = \frac{G_{m1}}{\omega_u A_0}$

For $PM=60^\circ$: $C_c = \frac{1.73 G_{m1}}{\omega_u A_0}$