

Lecture 21: CMOS Op Amp Compensation



- Announcements:
 - HW#8 due Wednesday at 8 a.m.
 - HW#9 online soon
 - Lab#3 (Design Project) in progress
 - Design Project Checkpoint:
 - ↳ Due Tuesday, Nov. 17, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (or linear if an MOS resistor)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
 - Thursday (next week) I'll be traveling
 - ↳ Lecture by videotape
 - ↳ People seemed to like this last time
 - Handout on pole/zero plots online
 - Lecture Topics:
 - ↳ Choosing C_c
 - ↳ CMOS Op Amp Compensation
-
- Last Time: Choosing C_c

over

Choosing C_c (assume no RHP zeros & $|P_3| \gg |P_2|$)

\Rightarrow assume $\frac{1}{sC_c} \ll$ surrounding impedance @ high freq.

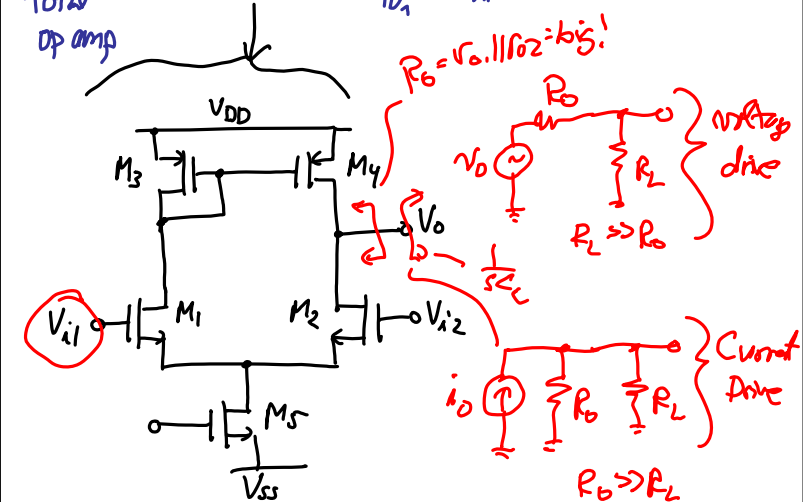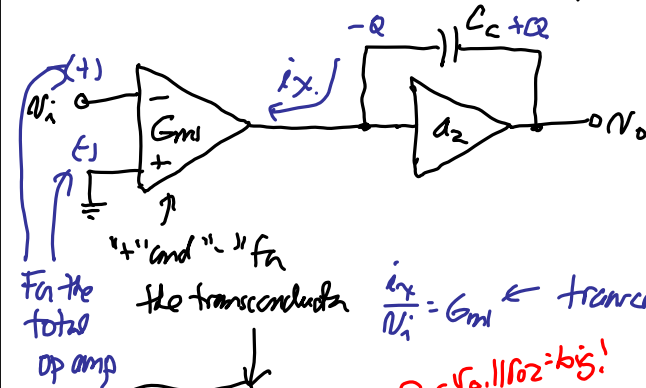Case D: Two Stage Amplifier w/ Miller Compensation



$$i_x = G_{m1} v_i$$

$$v_o = \frac{i_x}{sC_c} \Rightarrow v_o = \frac{G_{m1}}{sC_c} v_i \Rightarrow \frac{v_o}{v_i}(s) = \frac{G_{m1}}{sC_c}$$

Really care most about freqs. around this point, since the PM determined here

$$\left| \frac{v_o}{v_i}(j\omega) \right| = \frac{G_{m1}}{\omega C_c} \Rightarrow \text{this should equal } A_0 \text{ @ the freq. corresponding to the target phase margin (PM)}$$

Define: $\omega_{u1t} = \omega @ |a(j\omega)| = 1$
 ↳ "u1t": "unity loop transmission"

For PM = 45°:

$\omega_{u1t} = \omega_2$
 ↳ freq of the 2nd pole of the open loop $a(j\omega)$ transfer function

$$\left| \frac{v_o}{v_i}(j\omega_2) \right| = A_0 = \frac{G_{m1}}{\omega_2 C_c} \rightarrow C_c = \frac{G_{m1}}{\omega_2 A_0}$$

$$a(j\omega) = \frac{A_0}{(1 - \frac{s}{p_1})(1 - \frac{s}{p_2})}$$

For PM = 60°:

$$\angle a(j\omega) = -\tan^{-1}\left(-\frac{\omega}{p_1}\right) - \tan^{-1}\left(-\frac{\omega}{p_2}\right) = -120^\circ \text{ (for PM = 60°)}$$


$$\omega_{u1t} = \frac{|p_2|}{\sqrt{3}} = \frac{\omega_2}{1.73}$$

$$\left| \frac{v_o}{v_i}(j \frac{\omega_2}{1.73}) \right| = A_0 = \frac{G_{m1}}{(\frac{\omega_2}{1.73}) C_c} \rightarrow C_c = \frac{1.73 G_{m1}}{\omega_2 A_0}$$

Remarks:

- ① Smaller A_0 requires larger C_c .
- ② Dependence on G_{m1} .

② Case: Two-Stage Amplifier w/ Shunt C_c

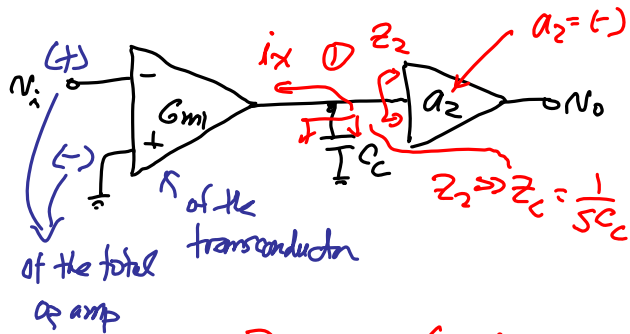

$$N_o = -\frac{G_{m1} N_i}{s C_c}$$

$$N_o = a_2 N_o$$

$$N_o = -\frac{G_{m1} a_2 N_i}{s C_c}$$

$$\therefore \frac{N_o}{N_i}(s) = -\frac{G_{m1} a_2}{s C_c}$$

Closed-loop gain A_o must again intersect this curve @ the right ω_{uH} for the desired PM

For PM = 45° :

$$\left| \frac{N_o}{N_i}(j\omega) \right| = A_o = \frac{G_{m1} a_2}{\omega_2 C_c} \rightarrow C_c = \frac{G_{m1} a_2}{\omega_2 A_o}$$

For PM = 45°


For PM = 60° :

$$C_c = \frac{1.73 G_{m1} a_2}{\omega_2 A_o}$$

For PM = 60°

Case ③: Single-Stage Amplifier w/ Shunt C_c

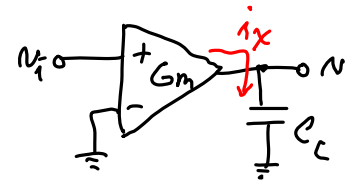e.g., telescopic cascode op amp w/ C_c at the output node



$$N_o = \frac{i_x}{s C_c}$$

$$i_x = G_m N_i$$

$$\frac{N_o}{N_i}(s) = \frac{G_m}{s C_c} \rightarrow \text{Same as Case ① (Miller cap.)}$$

Thus:

$$C_c = \frac{G_{m1}}{\omega_2 A_o}$$

For PM = 45°

$$C_c = \frac{1.73 G_{m1}}{\omega_2 A_o}$$

For PM = 60°

CMOS 2-Stage Op Amp Compensation

$g_{mI} = g_{m2}$
 $g_{mII} = g_{m6}$
 $R_I = r_{o2} || r_{o4}$
 $R_{II} = r_{o6} || r_{o7}$

$KCL \textcircled{1}: i_s = \frac{v_i}{R_I} + sC_I v_i + (v_i - v_o) sC_C$
 $KCL \textcircled{2}: g_{mII} v_i + \frac{v_o}{R_{II}} + sC_{II} v_o + (v_o - v_i) sC_C = 0$

$\frac{v_o}{i_s} = \frac{(g_{mII} - sC_C) R_I R_{II}}{1 + s[(C_{II} + C_C) R_{II} + (C_I + C_C) R_I + g_{mII} R_I R_{II} C_C] + s^2 R_I R_{II} (C_I C_{II} + C_C C_I + C_C C_{II})}$

$D(s)$

$\frac{v_o}{i_s}(s) = \frac{N(s)}{D(s)} \rightarrow$ This xfer fun has 2 poles & one zero.

The zero: $N(s) = 0 \rightarrow z = \frac{g_{mII}}{C_C}$ ← (H) & real
 $z = s$ ↑ RHP in the complex plane

Re Poles:

$D(s) = (1 - \frac{s}{p_1})(1 - \frac{s}{p_2}) = 1 - s(\frac{1}{p_1} + \frac{1}{p_2}) + \frac{s^2}{p_1 p_2}$

$[|p_2| \gg |p_1|] \rightarrow \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$
 ↑ i.e., there is a dominant pole

$p_1 = - \frac{1}{(C_I + C_C) R_I + (C_I + C_C) R_{II} + g_{mII} R_I R_{II} C_C}$
 as $C_C \uparrow \rightarrow |p_1| \downarrow \rightarrow$ pole-splitting

↑ Miller multiplied term \rightarrow others

$p_1 \approx - \frac{1}{g_{mII} R_I R_{II} C_C}$

Fin the 2nd Pole:

$p_{1p2} = \frac{1}{R_I R_{II} (C_I C_{II} + C_C C_I + C_C C_{II})}$

*

$$P_2 = - \frac{g_{mII} C_c}{C_I C_{II} + C_c C_I + C_c C_{II}} \rightarrow P_2 \approx - \frac{g_{mII}}{C_I + C_{II}}$$

\downarrow
 as $C_c \uparrow \rightarrow |P_2| \uparrow$

ω_2 by Inspection


When C_c = big @ high freq.
 (ground ω_2), $C_c \rightarrow$ short

M_6 becomes "diode-connected"

$$\omega_2 = \frac{1}{\tau} = \frac{1}{\left(\frac{1}{g_{mII}}\right)(C_I + C_{II})} = \frac{g_{mII}}{C_I + C_{II}}$$

$[g_{m6} = g_{mII}]$

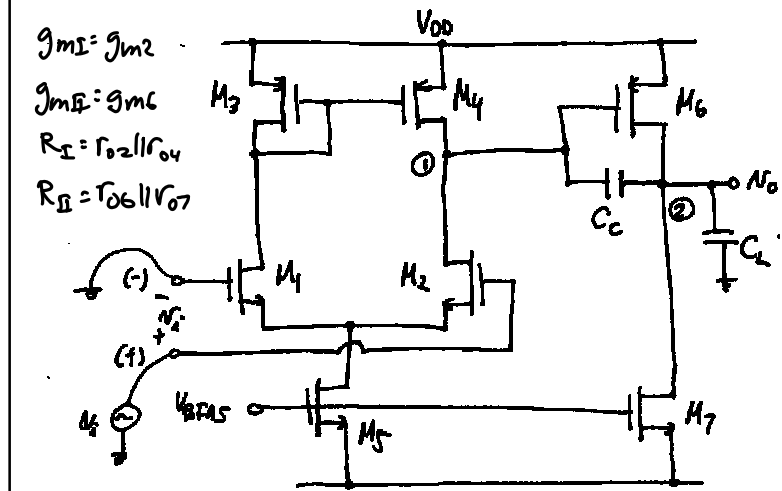CMOS 2-Stage OpAmp Compensation (Summary)



From our previous analysis:

$$P_1 = - \frac{1}{g_{mI} R_I R_{II} C_c} \quad [C_c \gg C_I \approx C_{II}] \quad [C_c \gg C_I]$$

$$P_2 = - \frac{g_{mII} C_c}{C_I C_{II} + C_c(C_I + C_{II})} \approx - \frac{g_{mII}}{C_I + C_{II}} \approx - \frac{g_{m6}}{C_L}$$

$$z = + \frac{g_{mII}}{C_c} \leftarrow \text{RHP zero (this will cause problems)}$$

Remarks:

- ① Note that as $C_c \uparrow \rightarrow |P_1| \downarrow$
- ② As $C_c \uparrow \rightarrow |P_2| \uparrow \rightarrow |P_2| = \frac{g_{mII}}{C_I + C_{II}}$
- ③ With $C_c = 0$ (i.e., before compensation)

$$P_1 = - \frac{1}{R_I C_I}, \quad P_2 = - \frac{1}{R_{II} C_{II}}$$

