

Lecture 23: MOS R & Slew Rate (revisited)

- Announcements:
 - HW#9 due tomorrow at 8 a.m.
 - HW#10 online soon
 - Lab#3 (Design Project) in progress
 - Design Project Checkpoint:
 - ↳ Due today at 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (or linear if an MOS resistor)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
 - I'll be traveling this coming Thursday
 - ↳ Lecture by videotape
 - Lecture Topics:
 - ↳ Nulling the RHP Zero (actual implementation)
 - ↳ Lab#3 Procedure
 - ↳ Slew Rate (revisited)
-
- Last Time: Nulling the RHP Zero

over

Actual Implementation of Buffer-Based Cancellation

$R_{op} = \frac{1}{g_{m8}} = \frac{1}{\sqrt{2\mu_n C_{ox}(W/L)_8 I_{D8}}} \rightarrow$ want this sufficiently small to drive LP3/1P

increase I_{D8} or increase $(W/L)_8$

↓

more power X more area → cost! X

Problem

Solution: Nulling Resistor in Series w/ C_c

Doing KCL:

$$p_1 = -\frac{1}{g_{mII} R_2 C_C} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{Same as before}$$

$$p_2 = -\frac{g_{mII} C_C}{C_I C_{II} + C_C(C_I + C_{II})} \approx -\frac{g_{mII}}{C_{II}}$$

$$p_3 = -\frac{1}{R_2 C_I} \quad \leftarrow \text{pole due to } R_2$$

$$z = \frac{1}{C_C \left(\frac{1}{g_{mII}} - R_2 \right)} \quad \leftarrow \text{relocated zero (function of } R_2 \text{)}$$

Note: The position of the zero depends upon the value of "nulling resistor" R_2 .

If $R_2 < \frac{1}{g_{mII}}$ then z is in the RHP

If $R_2 > \frac{1}{g_{mII}}$ then " " " LHP!


→ This is great! → can convert the RHP zero to a LHP one!

can even stick the zero on top of a pole to eliminate it!

$$H(s) = \dots \frac{(s - z_1)}{(s - p_1)}$$

↑
if $z_1 = p_1$

The Root Locus:

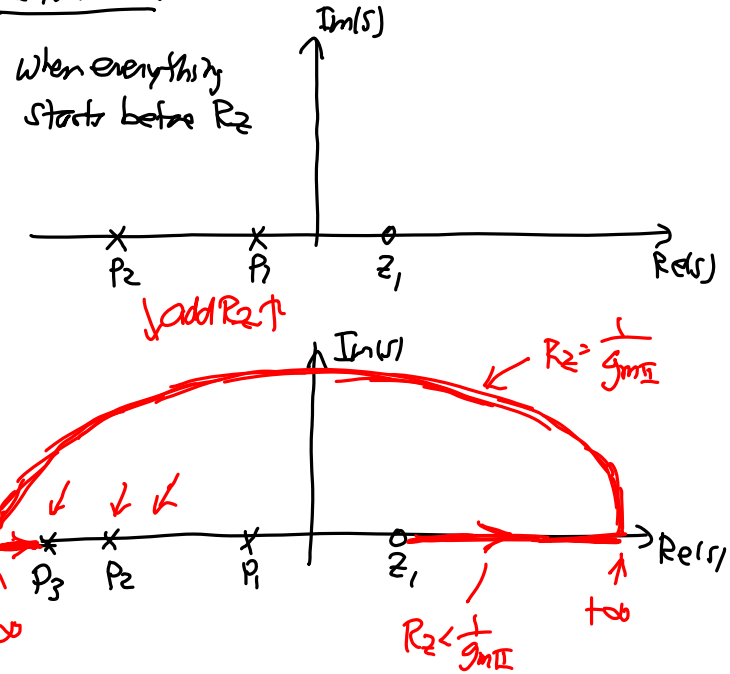

Zero Placement Strategies

① Eliminate z_1 → move it to ∞ :

$$z_1 = \frac{1}{C_C \left(\frac{1}{g_{mII}} - R_2 \right)} \rightarrow \infty \quad \text{when} \quad \boxed{R_2 = \frac{1}{g_{mII}}}$$

→ After doing this: $p_3 \approx -\frac{g_{mII}}{C_I}$
 $p_2 \approx -\frac{g_{mII}}{C_{II}}$

↓ Low Cap.
 Usually $C_{II} \gg C_I$
 so these poles are far apart... but be careful

This is good, but we can do better:

② Eliminate p_3 by placing z_1 on top of it:

$$z_1 = p_3 \Rightarrow \frac{1}{C_c \left(\frac{1}{g_{mF}} - R_2 \right)} = - \frac{1}{R_2 C_I}$$

$$R_2 = \frac{1}{g_{mII} \left(1 - \frac{C_I}{C_c} \right)}$$

After this: ① p_3 gone; p_1 & p_2 left

② Now, can place w_{u1f} @ $|p_2|$ and really get $PM = 45^\circ \rightarrow$ don't have to worry about phase influence of p_3 !


But can still do better

③ Eliminate p_2 by placing z_1 on top of it:

$\Rightarrow p_3$ becomes the 'new' p_2 ! (higher freq., higher T_{max})

$$z_1 = p_2 \Rightarrow \frac{1}{C_c \left(\frac{1}{g_{mF}} - R_2 \right)} = - \frac{g_{mII}}{C_{II}}$$
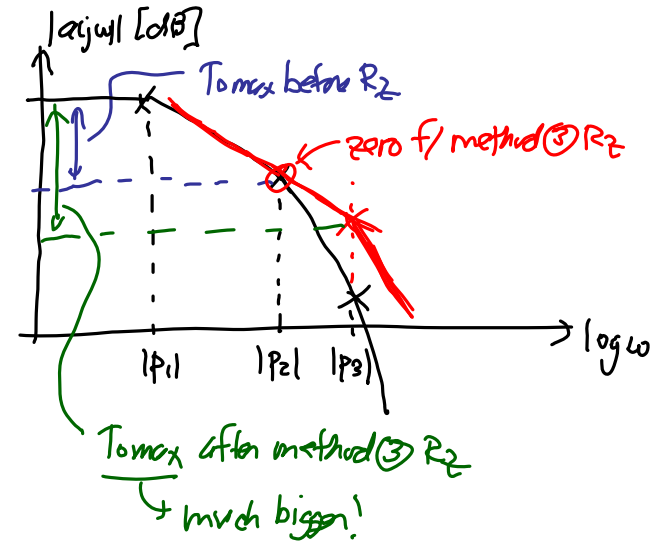
$$R_2 = \left(\frac{C_c + C_{II}}{C_c} \right) \left(\frac{1}{g_{mII}} \right) = \frac{1}{g_{mII}} \left(1 + \frac{C_{II}}{C_c} \right)$$



W/ this choice of R_2 :

$$p_3 = - \frac{1}{R_2 C_I} = - \frac{1}{\left(\frac{C_c + C_{II}}{C_c} \right) \left(\frac{1}{g_{mII}} \right) C_I}$$

$$p_3 = \frac{g_{mII} C_c}{C_I (C_c + C_{II})}$$

This becomes the new p_2 !

For $PM = 45^\circ$:

$$C_c = \frac{g_{mII}}{|p_3| A_0} = \frac{g_{mII}}{g_{mI}} \frac{C_I (C_c + C_{II})}{C_c A_0}$$

↑ the 'new' $|p_2|$ ↓ Solve for C_c : ← For $PM = 45^\circ$

$$C_c \approx \sqrt{\frac{g_{mF}}{g_{mII}} \frac{C_I C_{II}}{A_0}}$$

For $PM=60^\circ$:

$$C_c = \frac{1.73 g_{mII}}{\omega_{3dB} A_o} \rightarrow C_c = \sqrt{\frac{1.73 g_{mII} C_I C_{II}}{g_{mII} A_o}}$$

$[C_I \ll C_{II}]$ For $PM=60^\circ$

Remark. If settling time is important, then approach ③ may not be the best approach. The reason is that if the zero is not exactly equal to the pole, the a "doublet" ensues, which actually can hurt the settling time.

Discussed in a handout to be posted on the course website. → also, discussed in Razavi, problem 10.19.

Actual Implementation

⇒ resistors are too big. ∴ implement using a much smaller MOS resistor

MOS Resistor: just an MOS transistor operated in the linear region

uniform inversion charge → just like n⁺ material
 central effective sheet R by dividing the gate voltage V_G

In the linear region:

$$I_d = \mu_n C_{ox} \frac{W}{L} [(V_{gs} - V_t) V_{ds} - \frac{1}{2} V_{ds}^2]$$

$$\frac{\partial I_d}{\partial V_{ds}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t - V_{ds})$$

$$R_{s.s.} = \left[\frac{dI_d}{dV_{ds}} \right]^{-1}_{V_{gs}=V_{GS}, V_{ds}=V_{DS}} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t - V_{DS})} = \frac{1}{g_{ds}}$$

Variable resistor controllable by V_{GS} !

Actual Implementation

$$V_{DSB} = 0V \Rightarrow R_p = \frac{1}{\mu_p C_{ox} (w/L)_p (|V_{GSB}| - |V_{tsp}|)}$$

Design:

Need $V_A = V_B \rightarrow |V_{GS11}| = |V_{GS6}|$, know $|V_{t11}| = |V_{t6}|$

$$\sqrt{\frac{2I_{D1}}{\mu_p C_{ox} (w/L)_{11}}} = \sqrt{\frac{2I_{D6}}{\mu_p C_{ox} (w/L)_6}}$$

$$\left(\frac{w}{L}\right)_{11} = \left(\frac{w}{L}\right)_6 \frac{I_{D11}}{I_{D6}} = \left(\frac{w}{L}\right)_6 \frac{I_{D10}}{I_{D6}}$$

Also, need $|V_{GS10}| = |V_{GS8}|$.

Because $V_A = V_B \rightarrow V_{S10} = V_{S8} \rightarrow |V_{t10}| = |V_{t8}|$

$$\therefore |V_{D10}| = |V_{D8}| = \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} (w/L)_{10}}}$$

Thus:

$$R_p = \frac{1}{\mu_p C_{ox} (w/L)_p \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} (w/L)_{10}}}} = \frac{\sqrt{\mu_p C_{ox} (w/L)_{10}}}{\mu_p C_{ox} (w/L)_p \sqrt{2I_{D10}}}$$

Case: Eliminate p_2 by placing z on top of it.

$$R_z = \frac{C_c + C_L}{g_{m6} C_c} = \frac{\sqrt{\mu_p C_{ox} (w/L)_{10}}}{\mu_p C_{ox} (w/L)_p \sqrt{2I_{D10}}}$$

$$\sqrt{2\mu_p C_{ox} (w/L)_6 I_{D6}} \downarrow$$

$$\left(\frac{w}{L}\right)_p = \sqrt{\left(\frac{w}{L}\right)_6 \left(\frac{w}{L}\right)_{10} \frac{I_{D6}}{I_{D10}} \cdot \left(\frac{C_L}{C_c + C_L}\right)}$$

Case: Move $z_1 \rightarrow \infty$.

$$R_z = \frac{1}{g_{m6}} \rightarrow \left(\frac{w}{L}\right)_p = \sqrt{\left(\frac{w}{L}\right)_6 \left(\frac{w}{L}\right)_{10} \frac{I_{D6}}{I_{D10}}}$$

Project Design → Lab 3



Ad Hoc Procedure:

- Write down all equations for all needed specs.
 ↓ Then, study the dependencies, e.g.,
 $a_0 = \text{gain} = f(I_D, \lambda, \dots) \sim \frac{1}{\sqrt{I_D}}$
- Choose C_L
 $\omega_u = \text{unity gain freq.} = \frac{g_{mE}}{C_L} \sim \sqrt{I_D}$
 $|p_2| \cong + \frac{g_{mE}}{C_L} \rightarrow \text{For PM} = 60^\circ: \omega_u = \frac{|p_2|}{\sqrt{3}}$
- Choose I_D 's → SR
- Determine μ 's (governed by swing & input range)

Rule of Thumb:
 $SR \cong \frac{V_o}{\frac{T_s}{10}} = \frac{10V_o}{T_s}$

Fn 240A:

Slew Rate (f/ before)

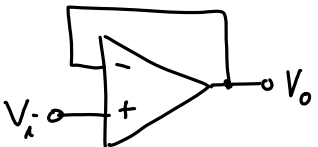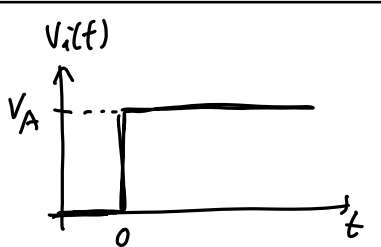Using Laplace Xform Theory:


$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + \frac{s}{\omega_i}} = \frac{1}{1 + s\tau_i}$$

← single (dominant) pole

$$V_i(s) = \frac{V_A}{s}$$


$$V_o(s) = \frac{V_A}{s(1 + s\tau_i)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_i}}$$

↕ Inverse Laplace Xform

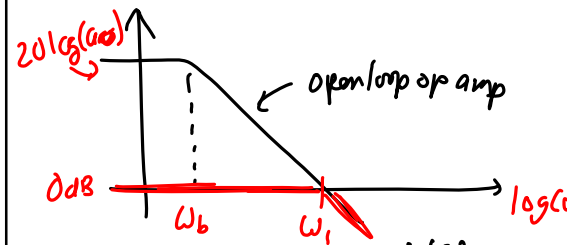
$$V_o(t) = V_A(1 - e^{-t/\tau_i}) \leftarrow \text{expected response}$$


open loop op amp

Expectation

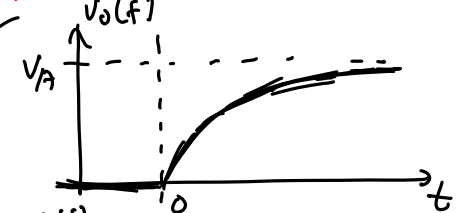


What we really see from a real op amp

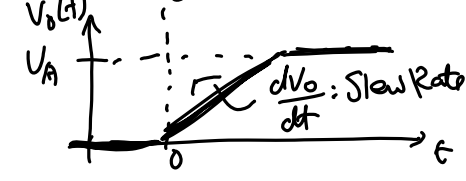

$\frac{dV_o}{dt} = \text{Slew Rate}$

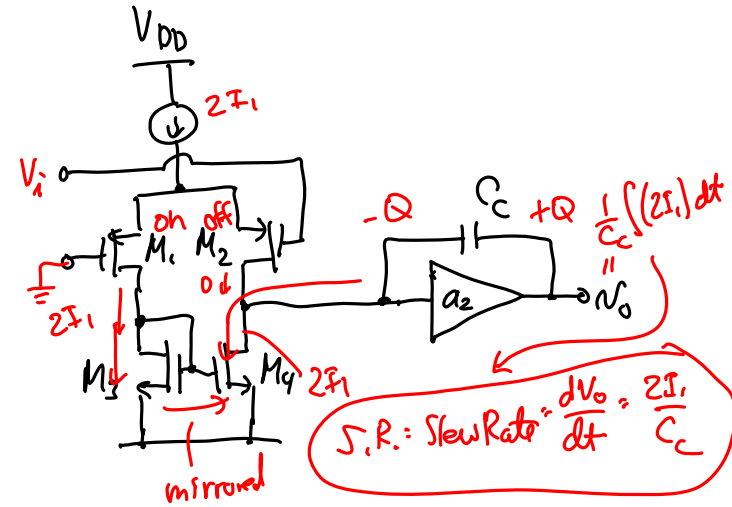Reasons: 1st or 2nd stage of op amp cannot source enough current to mimic the slope (or speed) of a fast rising input signal



If apply a very fast (i.e., high frequency), large amplitude sinusoid:

