

Lecture 26: Feedback By Inspection

- Announcements:
- HW#11 online soon, due 12/9 @ 8 a.m.
- Pre-Lecture Feedback Loading Handout online
- "Inspection Analysis of Feedback Circuits" Handout online
- Lab#3 (Design Project) due Friday, Dec. 11, at 11:59 p.m. in the 140/240a homework box
  - ↳ For 240A: use resistor temperature coefficients previously given in lecture
  - ↳ Best to be finished with design by next Monday, so you have plenty of time to write the report
  - ↳ Make sure the report is good, since it is what is graded in the end
- Will discuss Final Exam next lecture
- Lecture Topics:
  - ↳ Effect of FB on  $Z_i$  and  $Z_o$
  - ↳ Feedback Loading
  - ↳ Feedback By Inspection

- 
- Last Time:
  - Effect of FB on  $Z_i$  and  $Z_o$
  - Continue with this


over

Effect of FB on  $Z_i$  &  $Z_o$

Ex. Series-Shunt FB

Assumption: FB network has ideal impedances

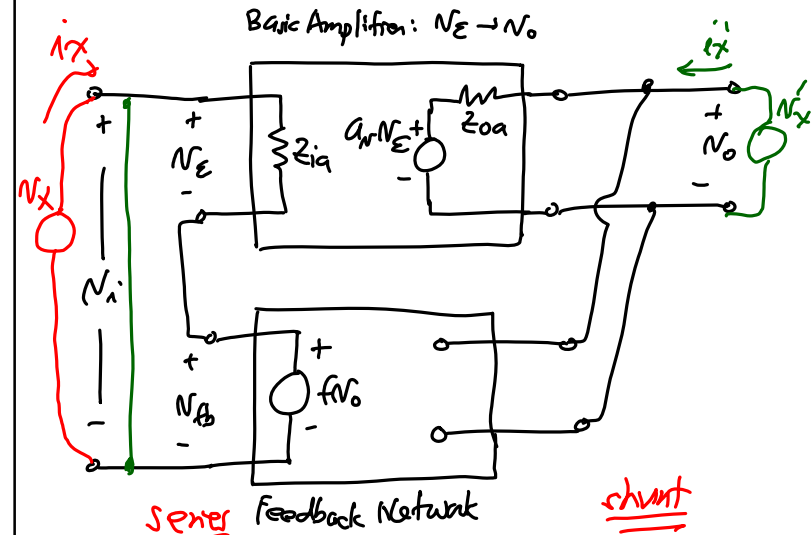↳ i.e., it does not load the basic amplifier



Find the T.F.:

$$\begin{aligned}
 v_E &= v_i - v_{fb} \\
 v_o &= a_v v_E \\
 v_{fb} &= f v_o
 \end{aligned}
 \left. \vphantom{\begin{aligned} v_E \\ v_o \\ v_{fb} \end{aligned}} \right\} \Rightarrow v_i = a_v (v_i - f v_o)$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{a_v}{1 + a_v f} \quad \checkmark$$

(as expected)

Find  $Z_i = \frac{V_x}{i_x}$ :

$$V_x = V_\Sigma + V_{fb}$$

$$= V_\Sigma + fV_o = V_\Sigma + fA_{OL}V_\Sigma = V_\Sigma(1 + A_{OL}f)$$

$i_x = \frac{V_\Sigma}{Z_{io}}$

$$Z_i = \frac{V_x}{i_x} = \frac{V_\Sigma(1 + A_{OL}f)}{\frac{V_\Sigma}{Z_{io}}} = Z_{io}(1 + A_{OL}f) = Z_i$$

closed loop input impedance

original open-loop impedance of op amp

loop gain!

When we series connect @ input } Closed loop input impedance raised by  $(1 + A_{OL}f)$ !

If  $Z_i \uparrow \rightarrow$  better voltage amplifier!  
 at least it accepts a voltage input better

Find  $Z_o = \frac{V_x'}{i_x'}$ : (w input shorted)

$$V_\Sigma + V_o = 0 = V_\Sigma + fV_x' \rightarrow V_\Sigma = -fV_x'$$

$$i_x' = \frac{V_x' - A_{OL}V_\Sigma}{Z_{oa}} = \frac{V_x' + A_{OL}fV_x'}{Z_{oa}}$$

orig. amplifier open-loop output impedance

$$\frac{V_x'}{i_x'} = \frac{Z_{oa}}{1 + A_{OL}f} = Z_o$$

closed-loop output impedance is lowered by a factor  $(1 + A_{OL}f)$

loop gain

Again, makes for a better voltage-to-voltage amplifier!

Overall, series-shunt FB improves the impedance characteristics of a  $v \rightarrow v$  amplifier!  $\rightarrow Z_i \uparrow, Z_o \downarrow$  due to FB

Ex. Shunt-Series FB

⇒ Again, assume the FB network does not load the amplifier

Basic Amplifier:  $i_i \rightarrow i_o$

Feedback Network:  $i_o \rightarrow i_{fb}$

shunt series

Find the T.F.:

$i_o = a_i i_i$   
 $i_i = i_x - i_{fb} = i_x - f_v i_o$

$$\frac{i_o}{i_x} = \frac{a_i}{1 + a_i f}$$

↑ open loop  $i \rightarrow i$  gain

↑ loop gain

Similar to the  $V \rightarrow V$  case, except now  $i \rightarrow i$

Find  $Z_i = \frac{V_x}{i_x}$ : open-loop input impedance

$$\frac{V_x}{i_x} = \frac{Z_{ig}}{1 + a_i f} = Z_i$$

⇒ Again, a shunt connection reduces impedance by a factor of  $(1 + a_i f)$ !

expect a  $i$  input!

Find  $Z_o = \frac{V_x'}{i_x'}$ :

$$\frac{V_x'}{i_x'} = Z_{oc} (1 + a_i f) = Z_o$$

↳ series connection raises the impedance by a factor  $(1 + a_i f)$ !

Summary: Shunt-Series makes for a better  $i \rightarrow i$  amplifier!

Summary,  $T = \text{loop gain}$

↓


① series connection:  $Z \rightarrow Z(1+T)$

② shunt connection:  $Z \rightarrow \frac{Z}{(1+T)}$

- Now go through the "Loading from the FB Network" Handout

Determine the FB loading of an Amplifier


Example: Non-Inverting Amplifier

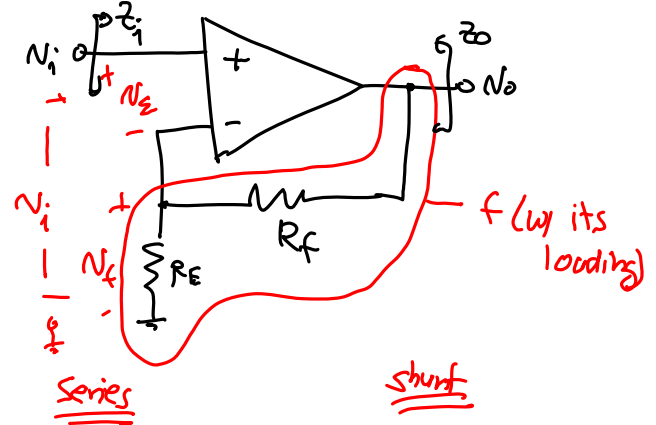


Objective: Use  $A_o = \frac{a_v}{1 + a_v f}$  to get  $A_o$ .

- In order to use this equation, we must know
- (i)  $a_v \hat{=}$  gain of the amplifier
  - (ii)  $f \hat{=}$  gain of the feedback (also, called the feedback factor)

In general:

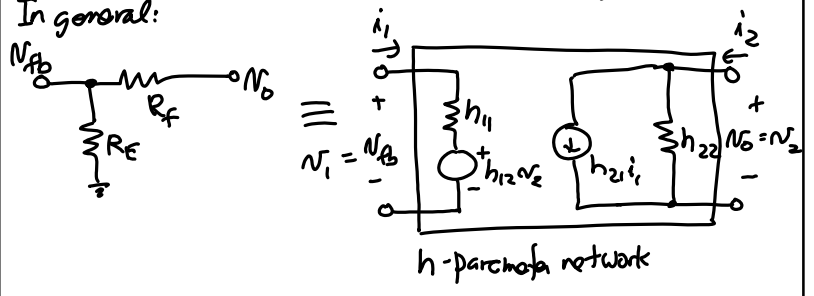


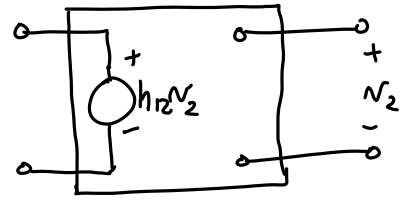But to simplify things, we would like to be able to represent the feedback network by just:




- Where:
- ① The small  $h_{21}$  is neglected.
  - ② All impedances have been moved out of the f-network and moved to the  $a_v$ -network.

Pictorially:

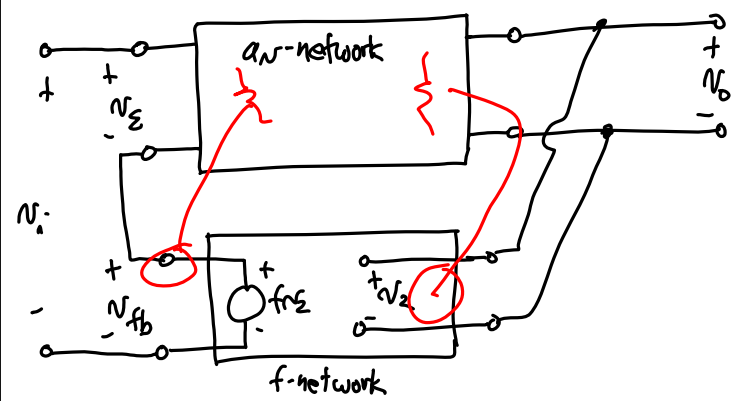

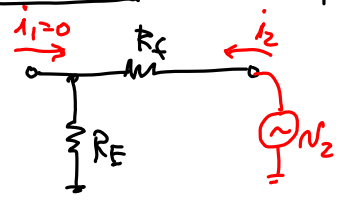The FB Network: (find the h-parameter representation)



h-parameter Network (just a reminder)

Port Equations:

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$i_2 = h_{21}i_1 + h_{22}V_2$$

Elements:

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

$h_{22f} = \left. \frac{i_2}{V_2} \right|_{i_1=0} = \frac{1}{R_E \parallel R_f}$  ← This is the loading @ port 2, i.e., at the amplifier output port.

↑  
conclusion

$h_{12f} = \left. \frac{V_1}{V_2} \right|_{i_1=0} = \frac{R_E}{R_E \parallel R_f} = f$  (feedback gain factor)

$h_{11f} = \left. \frac{V_1}{i_1} \right|_{V_2=0} = R_E \parallel R_f$  ← This is the loading @ port 1, i.e., at the amplifier input

↑  
resistance

So we have:

open loop amp w/ FB loading

new simpler FB network

Want  $A_o = \frac{A_{ol} \text{ w/ FB loading}}{1 + A_{ol} \text{ w/ FB loading} \times f}$

Determine  $A_{ol} \text{ w/ FB loading}$ :

$N_o = A_{N_E} \left\{ \frac{(R_E + R_F) \parallel Z_L}{(R_E + R_F) \parallel Z_L + Z_o'} \right\}$ ;  $N_E = N_i \left\{ \frac{Z_i'}{Z_i' + R_E \parallel R_F} \right\}$

$\left. \frac{v_o}{v_i} \right|_{ol, w/ FB \text{ loading}} = \left( \frac{Z_i'}{Z_i' + R_E \parallel R_F} \right) \times \left( \frac{(R_E + R_F) \parallel Z_L}{(R_E + R_F) \parallel Z_L + Z_o'} \right) = (A_{ol})_{ol, w/ FB \text{ loading}}$

we have:  $f = \frac{R_E}{R_E + R_F}$

Get closed-loop gain  $A_o$ : if  $A_{ol} \text{ w/ FB loading} = \text{large load}$

$A_o = \frac{N_o}{N_i}$

$1 + A_{ol} \text{ w/ FB loading} \times f$  —  $R_E$

must use if  $A_{ol} \text{ w/ FB loading}$  not large

What about  $Z_i$  &  $Z_o$ ?

⇒ For the open-loop op amp w/ FB loading:

$Z_{ia} = Z_i' + R_E \parallel R_F$  } open-loop amp w/ FB loading

$Z_{oa} = Z_o' \parallel (R_E + R_F) \parallel Z_L$  }

⇒ For closed-loop, just multiply or divide by  $(1 + A_{ol} f)$  depends on the type of FB connection

series:  $Z_i = Z_{ia} (1 + A_{ol} f) = (Z_i' + R_E \parallel R_F) (1 + A_{ol} f)$


shunt:  $Z_o = \frac{Z_{oa} \text{ w/ FB loading}}{1 + A_{ol} \text{ w/ FB loading} \times f} = \frac{Z_o' \parallel (R_E + R_F) \parallel Z_L}{1 + A_{ol} \text{ w/ FB loading} \times f}$

What about  $\omega_{-3dB}$ ?


$\omega_{-3dB} \text{ closed-loop} = \left[ \omega_{-3dB} \text{ w/ FB loading} \right] \times (1 + A_{ol} \text{ w/ FB loading} \times f)$

To determine loading by FB:

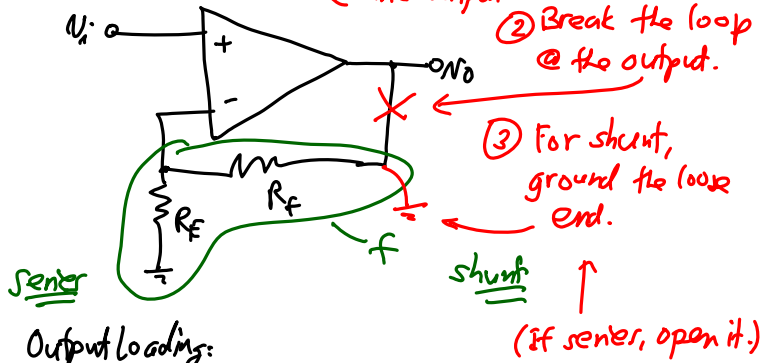Input Loading: ① Determine the feedback type @ the output. (Here, it's shunt.)  
 ② Break the loop @ the output.



Output Loading:

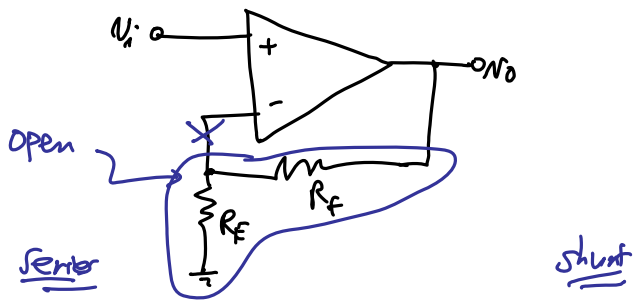

① Determine the feedback type @ the input.  
 (Here, it's series.)  
 ② Break the loop @ the input.  
 ③ For series, open the loose end.  
 ↓  
 (If shunt, short it.)

- Go through the "Inspection Analysis of Feedback Circuits" Handout
- In the end, if one can determine the open loop gain with FB loading and feedback factor, then the rest of the problem becomes simple
- Study the table in the handout
  - ↳ Be able to fluently go between different types of gain, from  $v \rightarrow v$ , to  $i \rightarrow v$ , etc.