

EE 140

BJT Modeling



CTN

1



Modeling the Bipolar Junction Transistor (BJT)

→ physically, BJTs are just back-to-back pn junctions

npn bipolar X-section

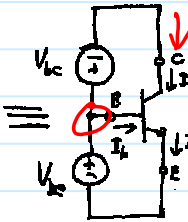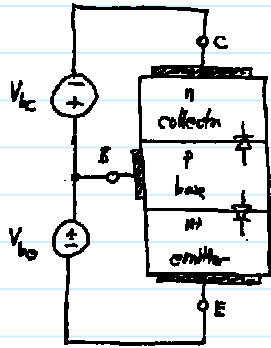

ppn bipolar X-section

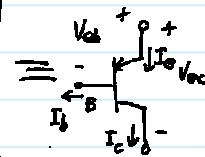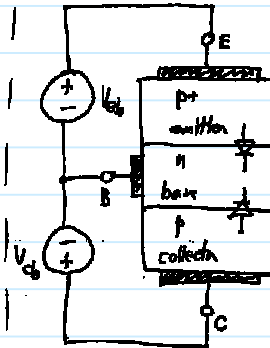

Regions of Bipolar X-section Operation

EBJ

CBJ

Mode
R = reverse-biased
F = forward-biased

R

R

Cut-off (both diodes off)

F

R

Forward Active (widely used in analog amplifier ckt)

R

F

Reverse Active


F

F

Saturation

⇒ can also think of this in a convenient graphical sense:

→ for npn (ppn):

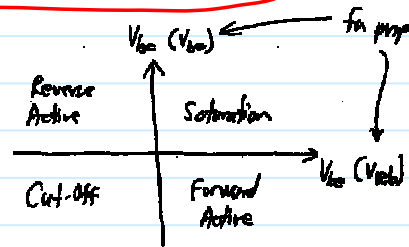


① Cut-off region - (npn transistor)

⇒ both diodes reverse-biased

⇒ no current flows:

$$I_B = 0, I_C = 0, I_E = 0$$

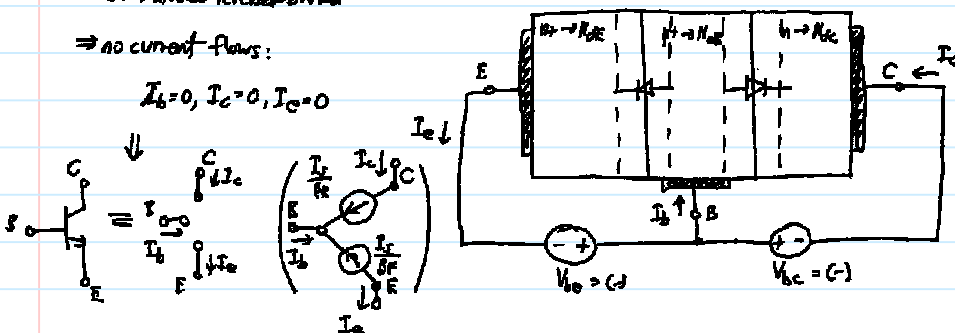

EE 140




BJT Forward-Active

CTN

2

② Forward-Active Region - (npn transistor)

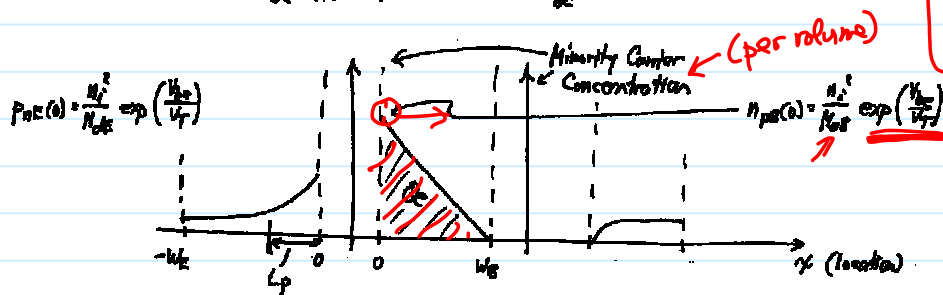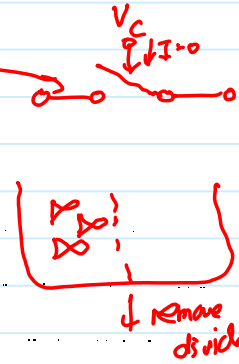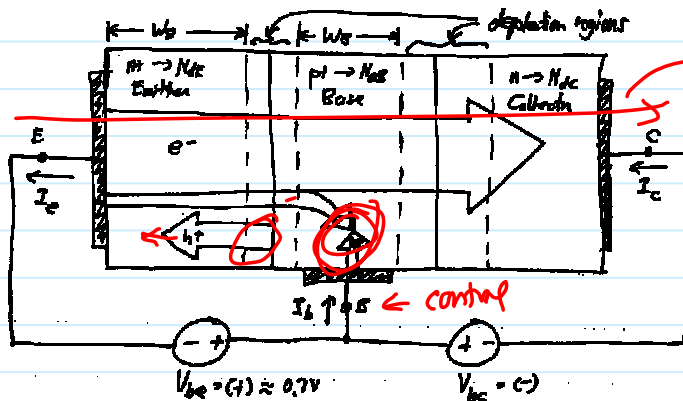⇒ BJT Forward-Biased (i.e., diode on), BJT Reverse-Biased (i.e., diode off)



Forward biasing of the BJT generates three current components:

- ① e⁻s injected from emitter to base: $I_{nE} = -A J_{nE}^{diff}$
 - ② h⁺s injected from base to emitter: $I_{pE} = A J_{pE}^{diff}$
 - ③ recombination of e⁻s & h⁺s in base: I_{rB}
- $$I_C = I_{nE} = 0$$
- $$I_E = I_{nE} + I_{pE} + I_{rB} = 0 + ② + ③$$
- $$I_B = I_{pE} + I_{rB} = ② + ③$$

$$I_{nE} = -A J_{nE}^{diff} = -A q D_{nE} \frac{dn_p(x)}{dx} = -q A D_{nE} \frac{[n_{pE}(W_B) - n_{pE}(0)]}{W_B} = q A D_{nE} \frac{n_i^2}{N_B W_B} \exp\left(\frac{V_{BE}}{V_T}\right) = ① *$$

diffusion constant for e⁻s in E

diffusion constant for h⁺s in E

$$\left[\begin{aligned} n_{pE}(W_B) &= \frac{n_i^2}{N_B} \exp\left(\frac{V_{BC}}{V_T}\right) \approx 0 \\ n_{pE}(0) &= \frac{n_i^2}{N_B} \exp\left(\frac{V_{BE}}{V_T}\right) \end{aligned} \right] \quad I_C = I_{nE} \exp\left(\frac{V_{BC}}{V_T}\right)$$

$$I_{pE} = A J_{pE}^{diff} = A q D_{pE} \frac{dp_p(x)}{dx} = q A D_{pE} \frac{[p_{pE}(0) - p_{pE}(-W_E)]}{W_E} = q A D_{pE} \frac{n_i^2}{N_E W_E} \exp\left(\frac{V_{BE}}{V_T}\right) = ② *$$

could also replace by diffusion length, L_p (for h⁺ in n-type material)

$$\left[\begin{aligned} p_{pE}(0) &= \frac{n_i^2}{N_E} \exp\left(\frac{V_{BE}}{V_T}\right) \\ p_{pE}(-W_E) &= 0 \end{aligned} \right]$$

EE 140

BJT Forward-Active

CTN

3

minority-carrier charge in base

$$I_{B5} = \frac{Q_{B5}}{\tau_b} = \frac{1}{\tau_b} \left[\frac{1}{2} n_{p0}(0) W_b q A \right] = \frac{1}{2} \frac{A^2 n_i^2 W_b q A}{N_B \tau_b} \exp\left(\frac{V_{BE}}{V_T}\right) = \textcircled{3} \quad *$$

minority carrier lifetime in base

Define Forward Current Gain = β_F :

$$\beta_F = \frac{I_C}{I_B} = \frac{\textcircled{1}}{\textcircled{3} + \textcircled{2}} = \frac{\frac{qADn_i^2}{N_B W_B}}{\frac{I_A W_B q A}{2 N_B \tau_b} + \frac{qADn_i^2}{N_{DE} W_E}} = \left[\frac{W_B^2}{2\tau_b D_{nB}} + \frac{D_{nE} W_B N_D}{D_{pE} W_B N_D} \right]^{-1}$$

N_{DE}

L_p

- To maximize β_F , want:
- ① W_B = small
 - ② $N_{DE} \gg N_{DB}$ (this is why emitter is n) \rightarrow also leads to $D_{pE} \ll D_{nE}$ which we also want
 - ③ τ_b = large (since Si must be free of impurities/defects to prevent recombination)

More Complete Expression for β_F :

$$\beta_F = \underbrace{\frac{N_{DE} W_B}{D_{nE}} \frac{D_{nE}}{N_D L_p}}_{\text{Injection Efficiency}} + \underbrace{\frac{1}{2} \left(\frac{W_B}{L_{nB}} \right)^2}_{\text{Volume Recombination}} + \underbrace{s \left(\frac{A_E}{A_B} \right) \left(\frac{W_B}{D_{nB}} \right)}_{\text{Surface Recombination}} + \underbrace{\frac{W_E N_D W_B}{2 D_{nE} \tau_{nE}} e^{-\frac{V_{BE}}{V_T}}}_{\text{Recombination in the BE Depletion Region} \leftarrow \text{Significant @ low current levels}}$$

where: s = Surface Recombination Velocity

D_i = Diffusion constant

n_i = intrinsic carrier concentration

N_i = carrier concentration


A_E = total emitter area

A_B = sidewall emitter area

τ = minority carrier lifetime

L_i = diffusion length ($L_i = \sqrt{D_i \tau}$)

W_b = active base width

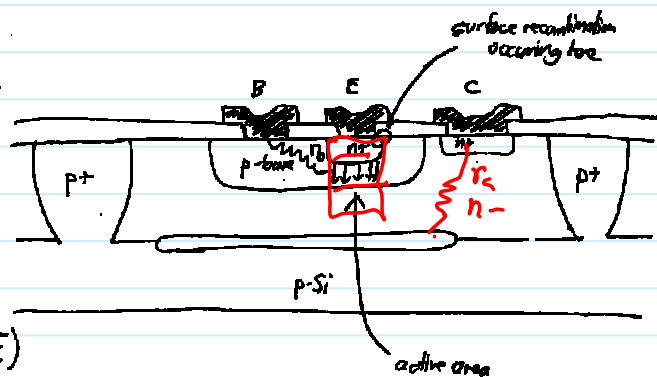


EE 140

Forward-Active LS Models

CTN

4

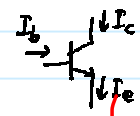So β relates I_b to I_c . To relate I_c to I_e , use KCL:






$$I_e = I_c + I_b = I_c + \frac{I_c}{\beta} = \left(1 + \frac{1}{\beta}\right) I_c$$

$$\Rightarrow I_c = \left(\frac{1}{1 + \frac{1}{\beta}}\right) I_e = \left(\frac{\beta}{\beta + 1}\right) I_e = \alpha I_e, \text{ where } \alpha = \frac{\beta}{\beta + 1} \Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$


$\frac{100}{101} = \beta \alpha$

Equivalent Large Signal Ckt. Models for Forward-Active BJTs

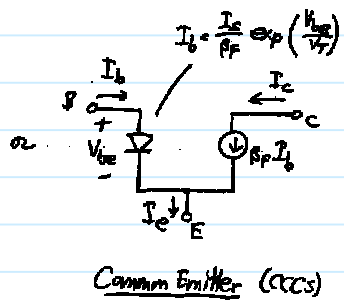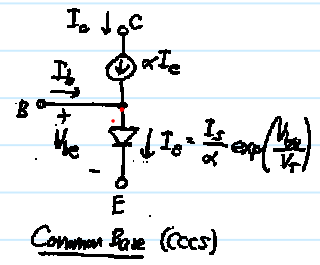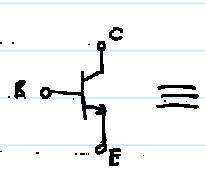
There are several of them. The most useful ones are:



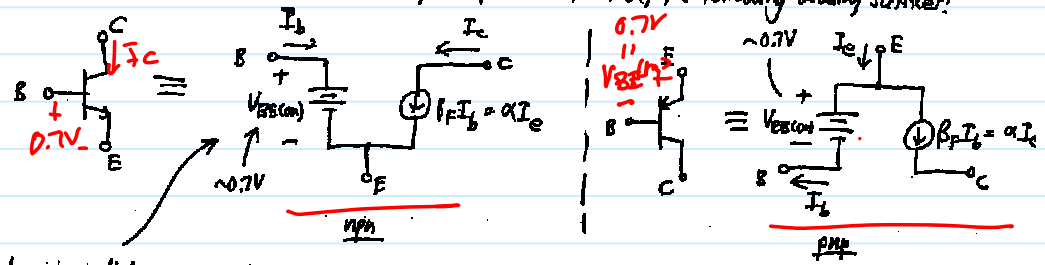But usually one doesn't have to use those complicated models. Rather, the following usually suffices:



Just as in a diode:

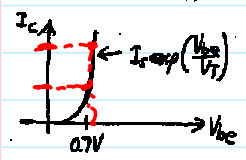

You should already be used to using approximate models like this
 \Rightarrow the more complicated models are a waste of time in comparison.

③ Reverse-Active Region -

\Rightarrow very similar to forward-active region except now:

BEJ reverse-biased
 BCJ forward-biased

\Rightarrow one important difference:

$$\beta_R \propto \frac{N_{ac} W_B D_B}{N_{ae} W_E D_E}$$

$$\rightarrow N_{ac} \ll N_{ae} \rightarrow D_B \ll D_E$$

$$\therefore \beta_R \text{ is much smaller than } \beta_F$$

$$\Rightarrow \text{poor device performance}$$

EE 140

BJT Saturation LS Models

CTN


5

④ Saturation Region-

BEJ forward-biased $\rightarrow V_{BE(sat)} \sim 0.8V$ (higher than 0.7V in saturation)

BCJ forward-biased $\rightarrow V_{BC(sat)} \sim 0.6V$

Result

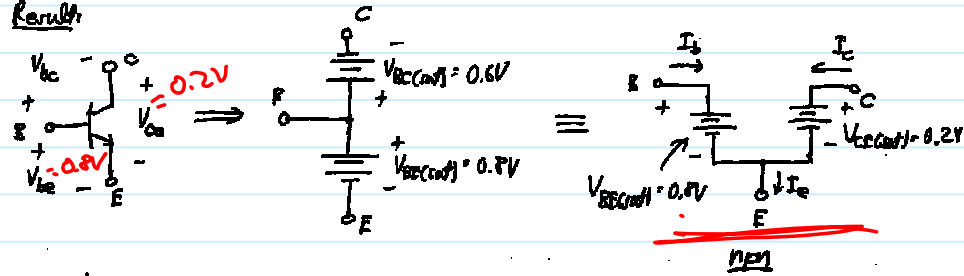

\Rightarrow currents now determined by the attached elements & KCL:



$$I_e = I_b + I_c ; \text{ no longer have } I_b = \frac{I_c}{\beta} \text{ or } I_c = \alpha I_e$$

These no longer apply when BJT is in saturation.

When determining DC operating point:


- ① Assume forward-active \rightarrow check for cut-off (enough V_{be} ?)
- ② Determine V_{ce} .
- ③ If $V_{ce} > V_{ce(sat)} = 0.2V$, then ok (i.e., it's forward-active) ... otherwise, must do the analysis over assuming saturation.

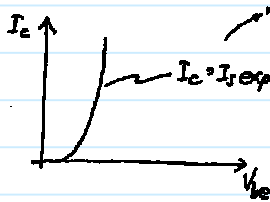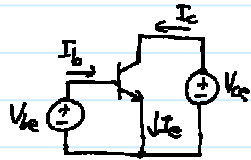IV Characteristics of Bipolar Junction Transistors



realities \rightarrow not easy to work with since we can't use Ohm's law theory \rightarrow then real life circuits!
 (a diode-like characteristic)
 digital etc \rightarrow present the only case \rightarrow small signal models

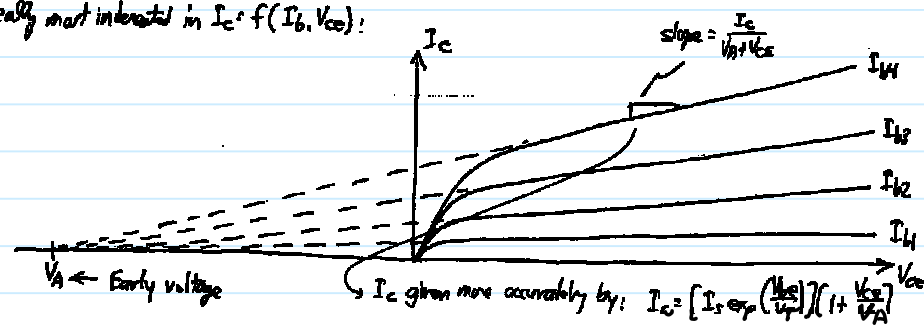\Rightarrow really most interested in $I_c = f(I_b, V_{ce})$:



$$I_c \text{ given more accurately by: } I_c = [I_s \exp(\frac{V_{be}}{V_T})] (1 + \frac{V_{ce}}{V_A})$$


EE 140

BJT Early Effect


CTN

6


What is happening physically?

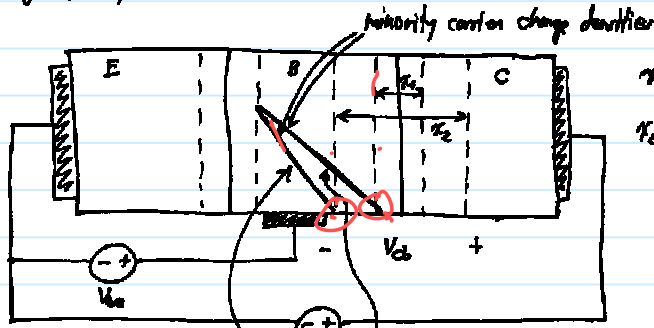

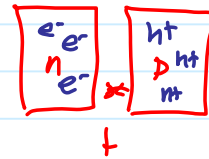$x_1 \approx$ depl. region width for $V_{CE} = V_{CE1}$
 $x_2 \approx$ depl. region width for $V_{CE} = V_{CE2} > V_{CE1}$



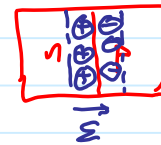- ① Case: $V_{CE} = V_{CE1} \rightarrow x_1 \rightarrow I_{C1} \propto$ slope of this curve
- ② Now, increase $V_{CE1} \rightarrow V_{CE2} \rightarrow V_{CB} \uparrow \rightarrow x_2 \rightarrow I_{C2} \propto$ slope of this line
 $\therefore I_{C2} > I_{C1}$




Thus, $V_{CE} \uparrow \rightarrow I_C \uparrow$ due to $x_{depl} \uparrow$

Result: $I_C = f(I_B, V_{CE})$ in forward-active!


$$I_C = \left[I_S \exp\left(\frac{V_{BE}}{V_T}\right) \right] \left[1 + \frac{V_{CE}}{V_A} \right]$$

This, V_{CE} , is a more accurate I_C equation.

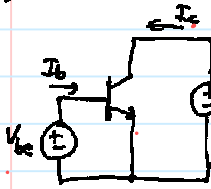
Small-Signal Model for Forward-Active Bipolar Xsistors



S.S. Ckt
Zero out all DC sources

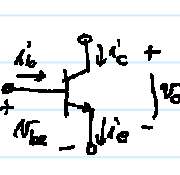


Y-parameter Model

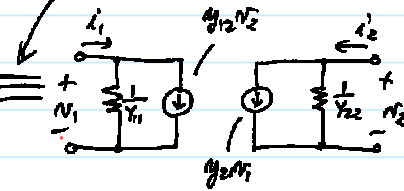


$$Y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0} \quad Y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}$$

$$Y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0} \quad Y_{22} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

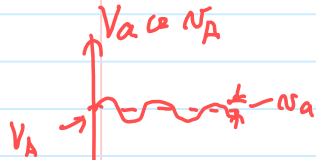

If only interested in the forward direction

Hybrid- π Model

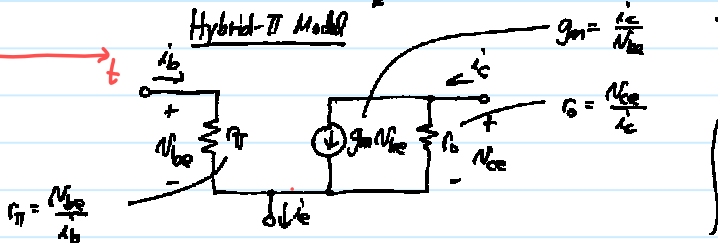

Specified by the bias point.

EE 140


BJT Small-Signal Model

CTN

7


Determine the S.S. elements

$$g_m = \frac{i_c}{v_{be}} = \frac{\partial I_c}{\partial v_{be}} \Big|_{Qpt.} = \frac{\partial}{\partial v_{be}} \left[I_s \exp\left(\frac{v_{be}}{V_T}\right) \right] \Big|_{v_{be} = V_{be}} = \frac{I_c}{V_T} \exp\left(\frac{V_{be}}{V_T}\right) \Rightarrow \boxed{g_m = \frac{I_c}{V_T}}$$

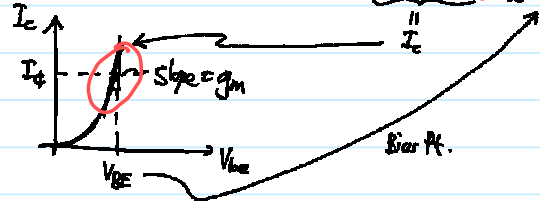

Note: function of the DC operating pt.

$$r_{\pi} = \frac{V_{be}}{I_b}$$

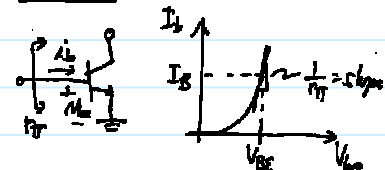


$$r_{\pi} = \frac{V_{be}}{I_b} = \frac{V_{be}}{\frac{I_c}{\beta}} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_c}{V_T}} = \frac{\beta V_T}{I_c}$$

$$\therefore \boxed{r_{\pi} = \frac{\beta}{g_m} = \frac{\beta V_T}{I_c}}$$

Again, function of the DC operating pt.

$$r_o = \frac{V_{ce}}{I_c}$$

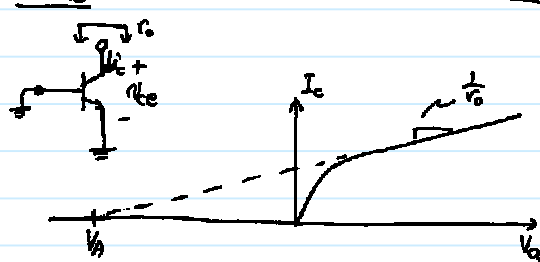


$$r_o = \frac{\partial v_{ce}}{\partial I_c} = \left[\frac{\partial I_c}{\partial v_{ce}} \Big|_{Qpt.} \right]^{-1} = \left[\frac{\partial}{\partial v_{ce}} \left(I_s \exp\left(\frac{v_{be}}{V_T}\right) \left[1 + \frac{v_{ce}}{V_A} \right] \right) \Big|_{v_{be} = V_{be}} \right]^{-1}$$

$$= \left[\frac{I_s \exp\left(\frac{V_{be}}{V_T}\right)}{V_A} \right]^{-1} = \left[\frac{I_c}{V_A + V_{ce}} \right]^{-1} = \frac{V_A + V_{ce}}{I_c}$$

$$\therefore \boxed{r_o = \frac{V_A + V_{ce}}{I_c} \approx \frac{V_A}{I_c} \quad (V_A \gg V_{ce})}$$

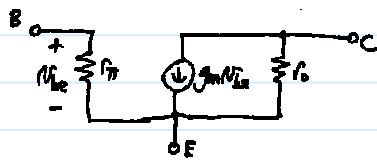... and thus, we have the hybrid- π model:



$$\boxed{\begin{aligned} r_{\pi} &= \frac{\beta}{g_m} = \frac{\beta V_T}{I_c} \\ g_m &= \frac{I_c}{V_T} \\ r_o &= \frac{V_A + V_{ce}}{I_c} \approx \frac{V_A}{I_c} \end{aligned}}$$

Remarks:

- ① g_m is independent of device specifics; depends only on temperature (thru V_T) and biasing I_c
- ② small-signal model valid for $v_{be} \ll V_T \leftarrow \approx 26mV @ 300K$

quite different from MOS as we'll see