

Lecture 2: Device Models I (Bipolar Review)

• Announcements:

- The course website was up and running last week
 ↳ Just google ee140 to get to it
- HW#1 online last week ... due next week
 Wednesday, at 8 a.m., in the 140/240A box on 1st floor (near the TI lab)
- My Monday Office Hours updated to 2-3 p.m.

• Lecture Topics:

↳ Review (fast)


↳ Bipolar Junction Transistor Modeling

- Basic Structure & Physics
- Large Signal Models
- DC Operating Point
- Small Signal Models
- Frequency Shaping Elements
- Layout
- Unity Gain Frequency

- Last Time: Reviewed op amps and started into BJT modeling using the module handout
- Continue with the handout

↪ over

Simple Biasing Example

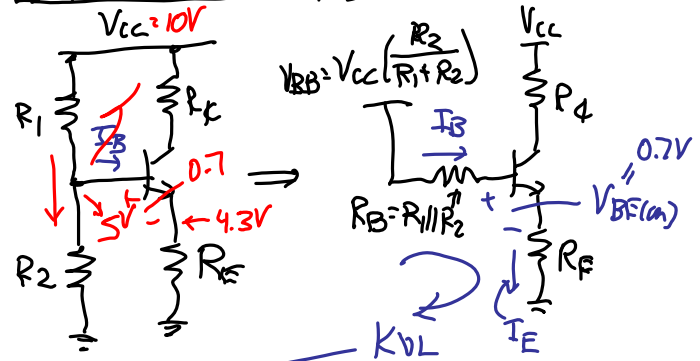

$$\rightarrow V_{BB} = I_B R_B + V_{BE(on)} + I_E R_E$$

$$\rightarrow I_C = \frac{V_{BB} - V_{BE(on)}}{\frac{R_E}{\alpha} + \frac{R_B}{\beta}}$$

Ex. $V_{CC} = 10V$, $V_{BE(on)} = 0.7V$, $R_E = 5k\Omega$, $R_1 = R_2 = 20k\Omega$
 $\beta = 200 \rightarrow \alpha = \frac{200}{201} = 0.995$ $V_{BB} = 5V$


$$\therefore I_C = \frac{5 - 0.7}{\frac{5k}{0.995} + \frac{10k}{200}} = 0.85mA$$

Ignore I_B : $I_C \approx I_E = \frac{4.3}{5k} = 0.86mA$ \rightarrow Same!

Example: Find the DC operating pt.


→ want the I_C 's of all Xistors → g_m for...

small-signal
elements

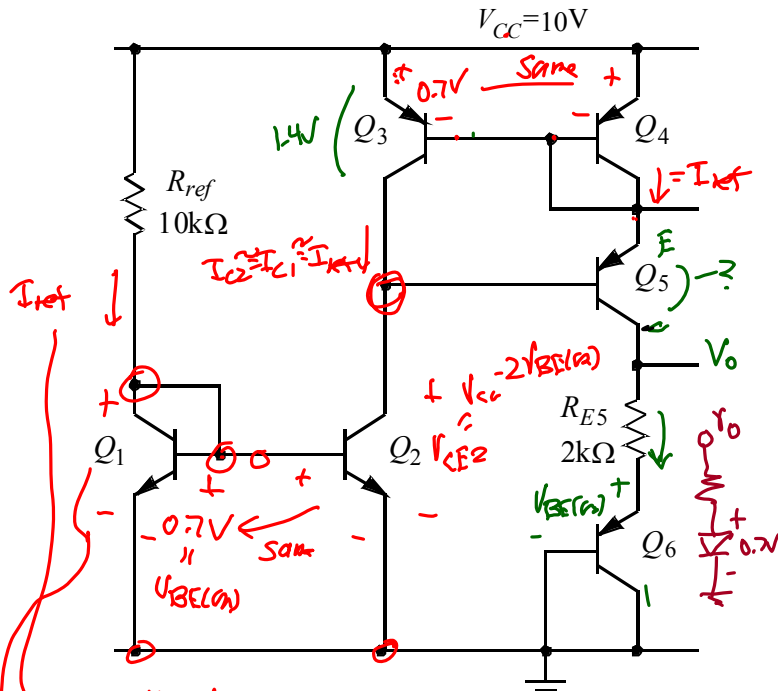


$$I_{ref} = \frac{V_{CC} - V_{BE(on)}}{R_{ref}} = \frac{10 - 0.7}{10k} = 0.93 \text{ mA}$$

$$V_{CE} = V_{BE(on)} = 0.7 \text{ V}$$

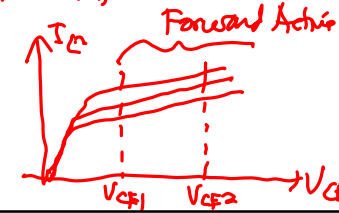


$$V_0 = V_{BE6(on)} + I_{ref} R_{E5} = 0.7 + (0.93 \text{ mA})(2k) = 2.56 \text{ V}$$

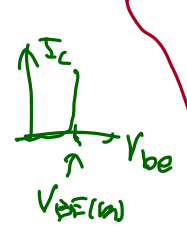In biasing: V_{BE} 's are well-defined
 $V_{BE(on)}$



② V_{CE} 's not well-defined

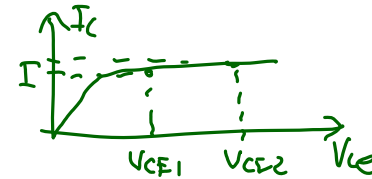

For Q_5 to be FA, need: ~ need $V_{CE5} > 0.2 \text{ V}$

$$V_0 < V_{CC} - V_{BE(on)4} - V_{CE(sat)5}$$

$$10 - 0.7 - 0.2 = 9.1 \text{ V}$$

What if $R_{E5} = 20k\Omega$?

$$V_0 = 0.7 + (0.93 \text{ mA})(20k) = 19.3 \text{ V} \rightarrow \text{X}$$

Q_5 is saturated!

$$V_0 = V_{CC} - V_{BE4(on)} - V_{CE(sat)} = 9.1 \text{ V}$$

$$I_{E5} = \frac{V_0 - V_{BE6(on)}}{R_{E5}} = \frac{9.1 - 0.7}{20k} = \underline{\underline{0.42 \text{ mA}}}$$