

Lecture 4: Inspection Analysis



- Announcements:
- Inspection formula sheet online in "Handouts" link
- HW#1 due tomorrow at 8 a.m. in the EE140/240A box near 140 Cory
- No labs this week
- EE 240A lecture increased to accommodate all
- Need to equalize labs, so go to the lab that is available if you still must get into the class

Lecture Topics:

- ↳ Procedure for Small Signal Analysis
- ↳ Inspection Formulas
- ↳ 1-Tx Amplifier Example
- ↳ Multi-Tx Amplifier Examples


Last Time:

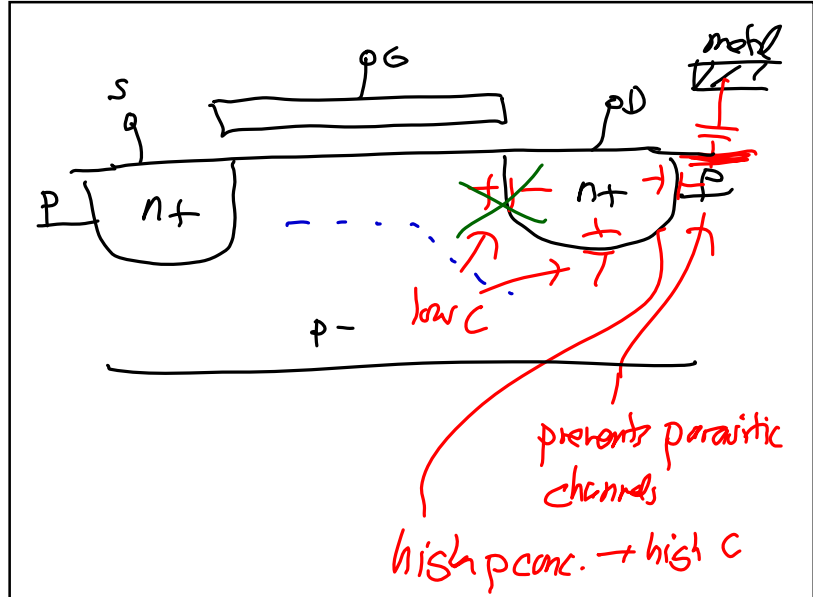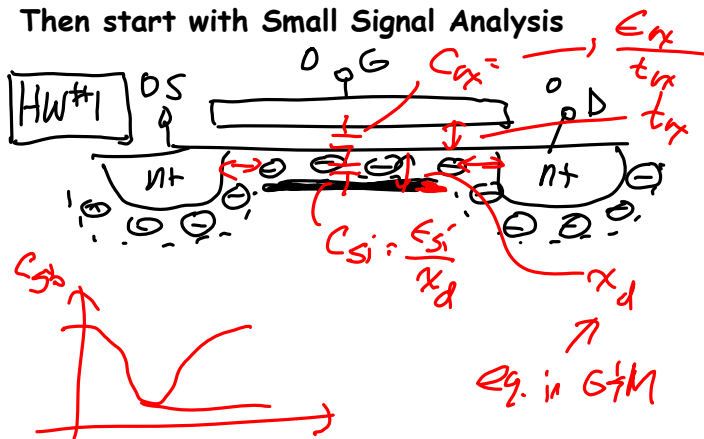- Going through MOS device modeling
- Finish this now
- Then start with Small Signal Analysis




Procedure for Small-Signal Analysis


Ex. Discrete Common-Emitter Ckt.

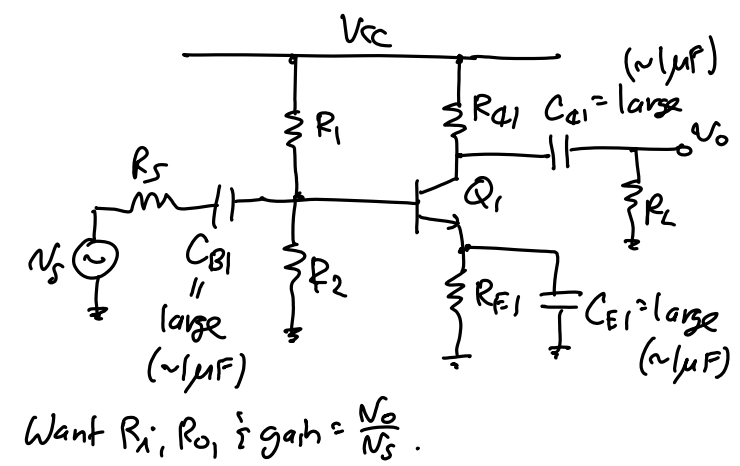


Procedure:

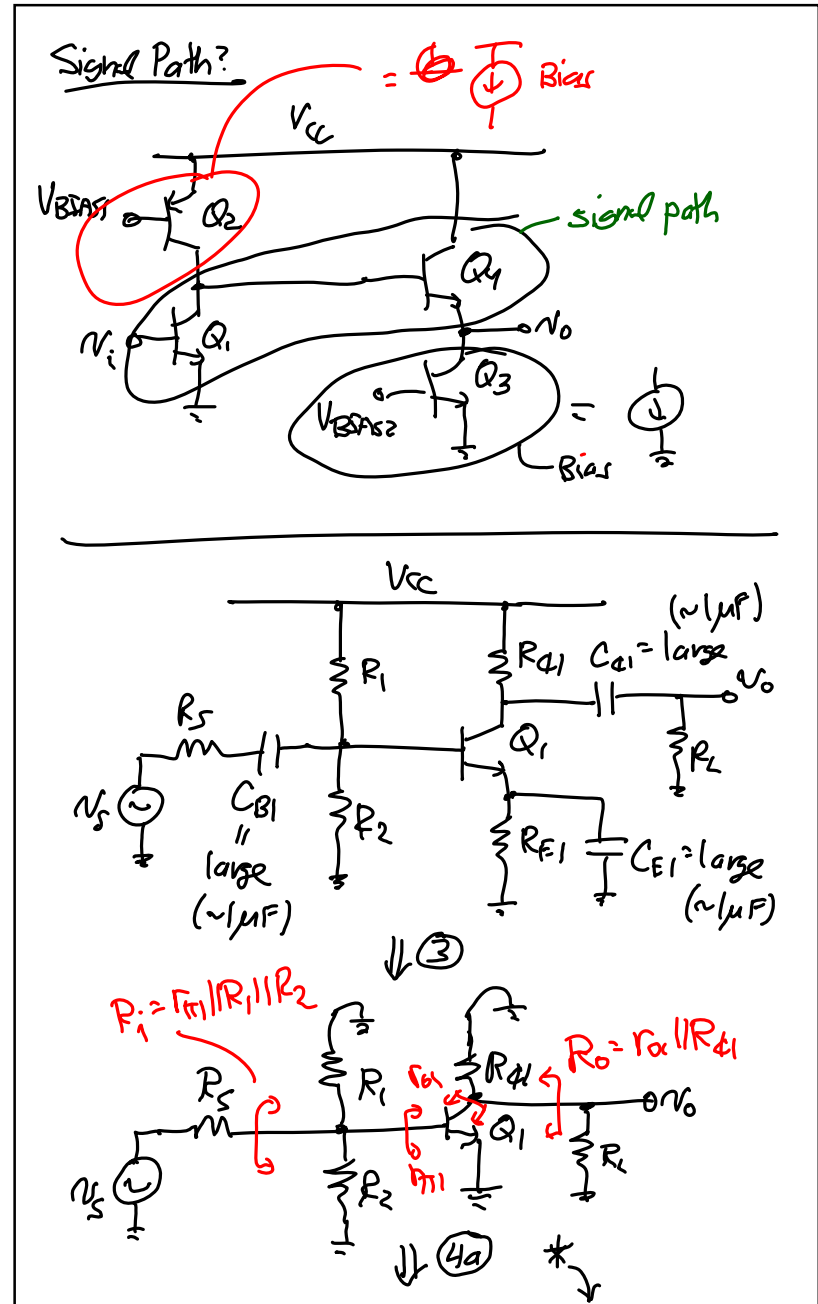1. Find the DC operating point
 - Get all the voltages & currents at all nodes & branches, respectively
2. Determine S.S. parameters for devices in the signal path (e.g., g_m , r_π , r_o , ...)
3. Convert the full circuit to the S.S. circuit
 - Zero out DC sources
 - Short out large capacitors (e.g., with values greater than nF's)
4. (a) If needed, replace transistor with its S.S. model (e.g., hybrid- π , T-model, ...)
 - This should NOT be needed often!
 - When is it needed? \rightarrow generally in cases where there is feedback
4. (b) Analyze by inspection based on prior S.S. analysis experience! (This should be 99% of the time.)




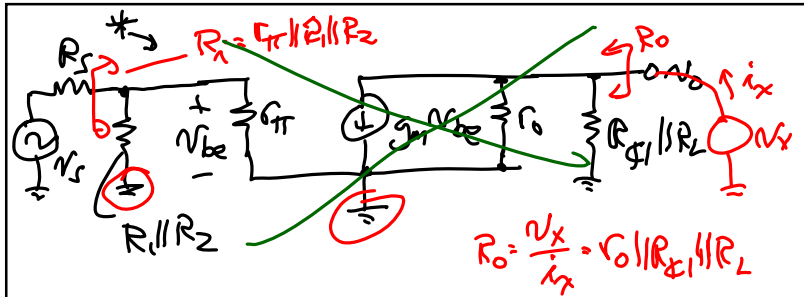

Get Gain: (by inspection)

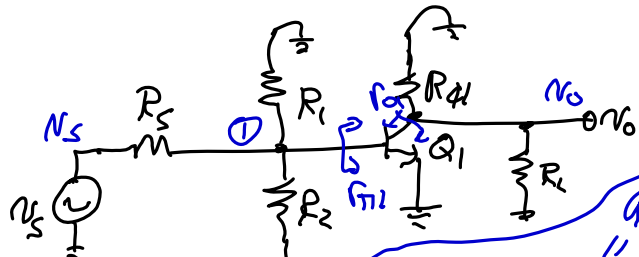

$$A_{v_r} = \frac{v_o}{v_s} = \frac{v_o}{v_{\pi}} \cdot \frac{v_{\pi}}{v_s} = - \left(\frac{R_D || R_L || R_2}{R_1 || R_2 || R_2 + R_s} \right) g_m (R_D || R_L)$$

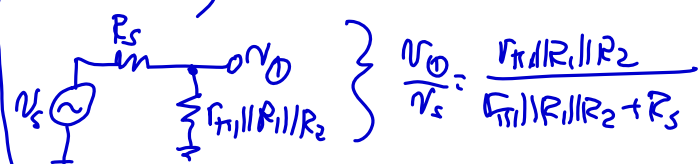


$$\frac{v_o}{v_{\pi}} = \frac{R_D || R_L || R_2}{r_{\pi} || R_1 || R_2 + R_s}$$

base-to-collector gain (with emitter grounded)

$$\frac{v_o}{v_o} = -G_m R_o = -g_m (r_o || R_C || R_L) \approx -g_m (R_C || R_L)$$

[$r_o \Rightarrow R_C || R_L$]

Ex. Common-Collector

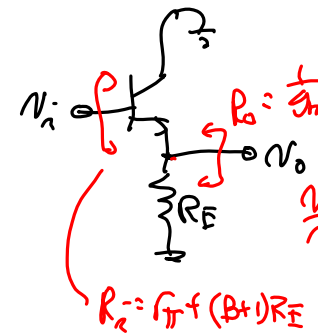

$$R_o = \frac{1}{g_m} || (r_o || R_E) \approx \frac{1}{g_m} || R_E$$

$$\frac{v_o}{v_i} = \frac{R_E}{r_{\pi} + R_E} = \frac{(B+1)R_E}{r_{\pi} + (B+1)R_E}$$

$\frac{1}{g_m}$ $r_{\pi} = \frac{B}{g_m}$