

Lecture 5: MOS Inspection Analysis

- Announcements:
- HW#2 already online and due next week on Wednesday at 8 a.m.
- EE 240A lecture increased again to accommodate all who want in
- Need to equalize labs, so go to the lab that is available if you still must get into the class
- If you still cannot get into the class, go and see Lydia in 205 Cory
- Room Change Verdict: 19 for 521 Cory, 12 for 289 Cory ... in the end, we need 521 Cory, since it can properly fit the class
- Class accounts passed out

Lecture Topics:


- ↳ Procedure for Small Signal Analysis
- ↳ Inspection Formulas
- ↳ 1-Tx Amplifier Example
- ↳ Multi-Tx Amplifier Examples
- ↳ MOS Inspection Analysis

- Last Time:
- Small Signal Analysis procedure
- Continue with examples

over

Procedure:

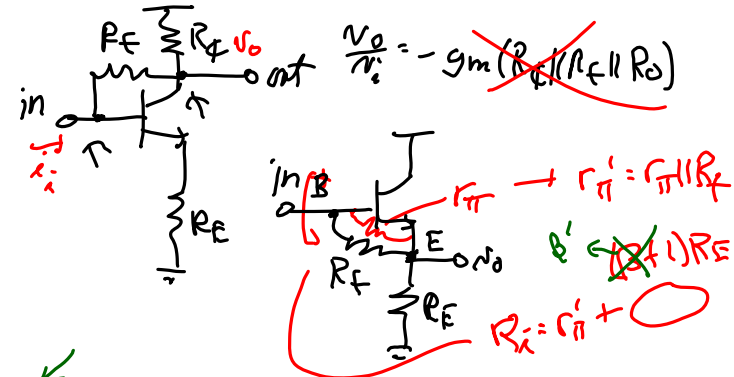1. Find the DC operating point
  - Get all the voltages & currents at all nodes & branches, respectively
2. Determine S.S. parameters for devices in the signal path (e.g.,  $g_m$ ,  $r_{\pi}$ ,  $r_o$ , ...)
3. Convert the full circuit to the S.S. circuit
  - Zero out DC sources
  - Short out large capacitors (e.g., with values greater than nF's)
4. (a) If needed, replace transistor with its S.S. model (e.g., hybrid- $\pi$ , T-model, ...)
  - This should NOT be needed often!
  - When is it needed?  $\rightarrow$  generally in cases where there is feedback



4. (b) Analyze by inspection based on prior S.S. analysis experience! (This should be 99% of the time.)

Ex. Common-Collector

$R_o = \frac{1}{g_m} \parallel (r_o \parallel \beta R_E) \approx \frac{1}{g_m} R_E$

$R_i = r_{\pi} \parallel (\beta + 1) R_E$

$\frac{v_o}{v_i} = \frac{R_E}{r_e + R_E} = \frac{(\beta + 1) R_E}{r_{\pi} + (\beta + 1) R_E}$

$r_e = \frac{1}{g_m}$ ,  $r_{\pi} = \frac{\beta}{g_m}$

Ex. Common-Base

$R_o = r_o \parallel R_C \approx R_C$  [ $r_o \gg R_C$ ]

$R_i = \frac{1}{g_m}$

$\frac{v_o}{v_i} = g_m (r_o \parallel R_C) \approx g_m R_C$

$\Rightarrow$  so far, we've been focused on "midband" analysis

$\Rightarrow$  Bode plot: (for the discrete amp f/ last time)

low frequency range

midband

high frequency range

-20 dB/dec

$\omega_L$ ,  $\omega_H$ ,  $\log \omega$

Inspection Analysis of a Multi-Transistor Ckt.

$R_s = 100 \Omega$

$R_{C2} = 1 k\Omega$

$R_{EE} = 10 k\Omega$

$V_{BE1} = V_{BE2} = -0.7V$

$-V_{BE(ON)} = 0.7V$

$I_{C1} = I_{C2} = \frac{I_{EE}}{2}$

Assume  $Q_1$  &  $Q_2$  identical.

Want  $R_i, R_o, g_{m1}$ .



First, set the DC operating point.

$V_{BE1} = V_{BE2} \rightarrow V_{E1} = V_{E2} = -V_{BE(ON)} = -0.7V$

$I_{EE} = \frac{-V_{BE(ON)} - V_{EE}}{R_{EE}} \rightarrow I_{C1} = I_{C2} = \frac{I_{EE}}{2}$


$r_{\pi 1} = r_{\pi 2}, r_{o 1} = r_{o 2}, g_{m 1} = g_{m 2}$

$\Downarrow$  S. & AC Ckt.

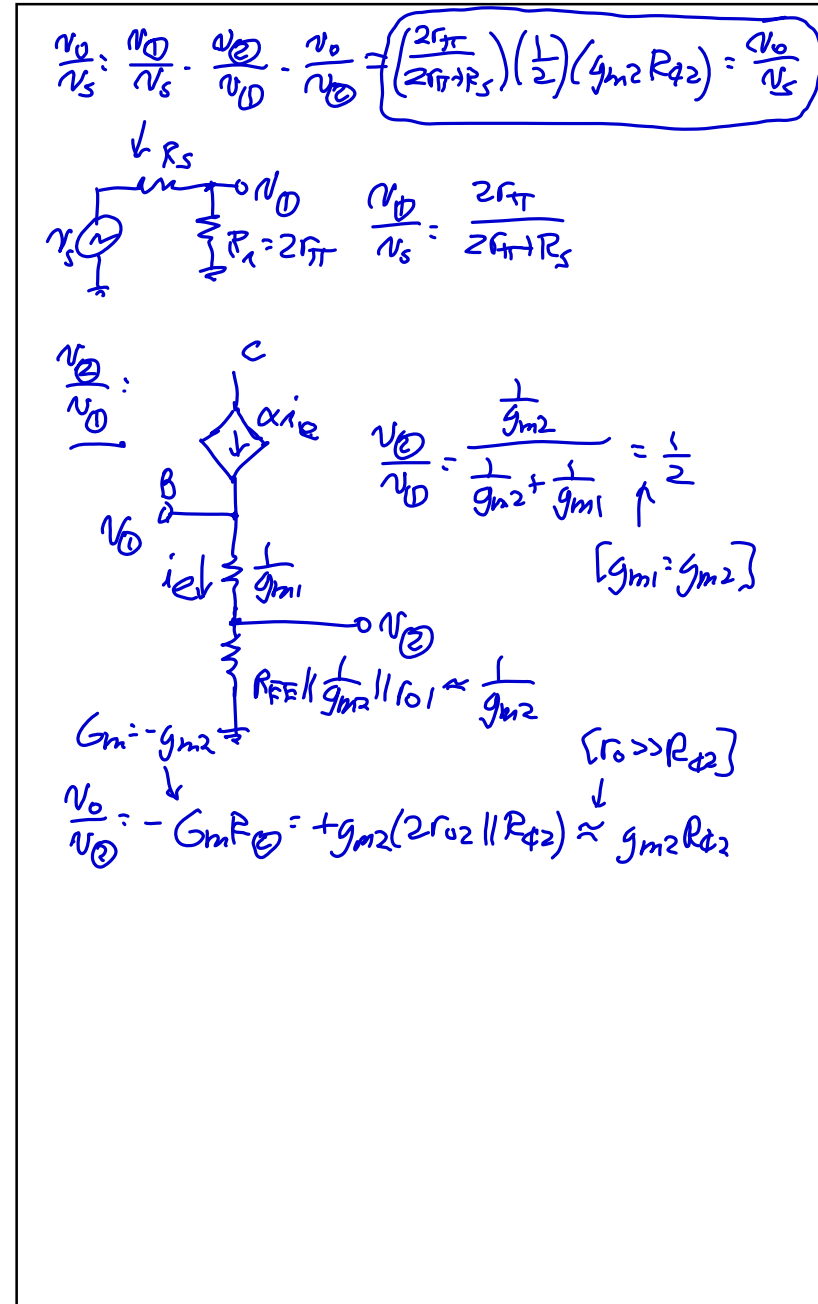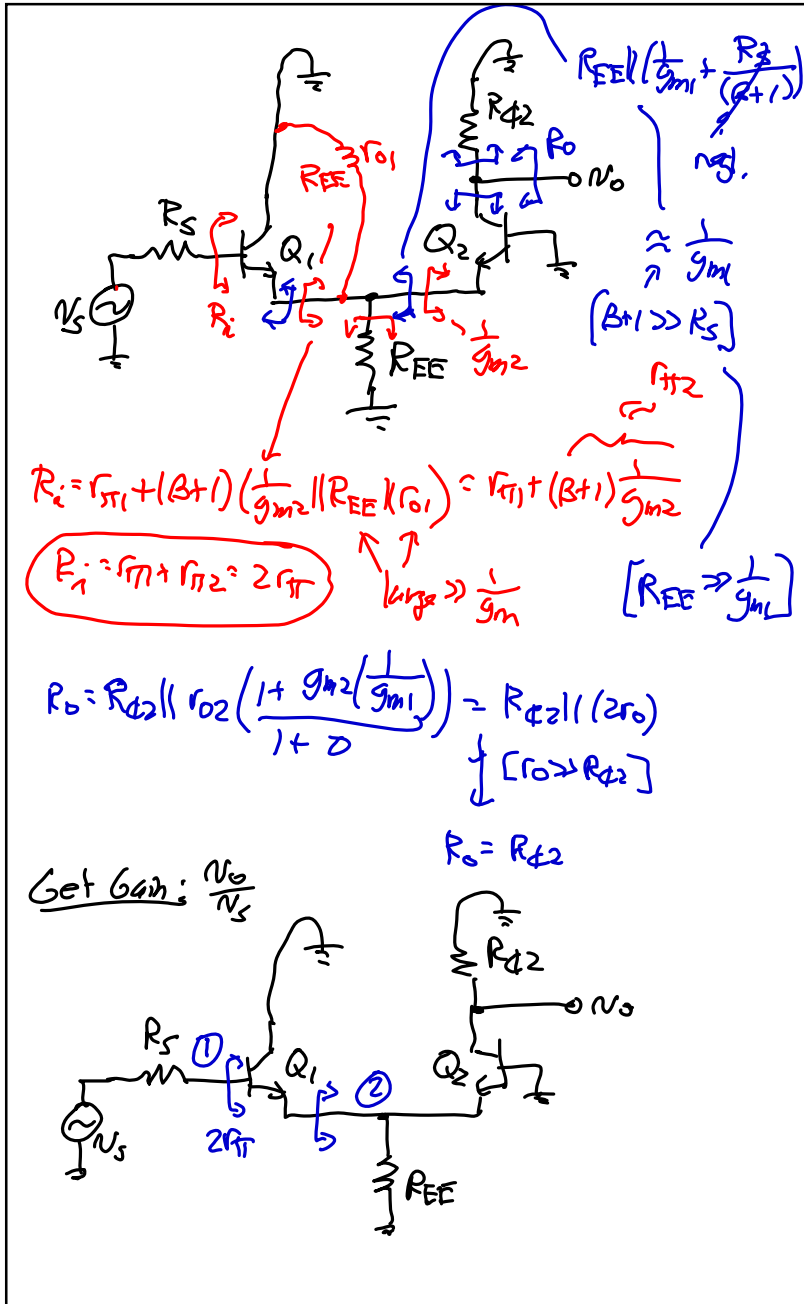

MOS Xistor Ckts

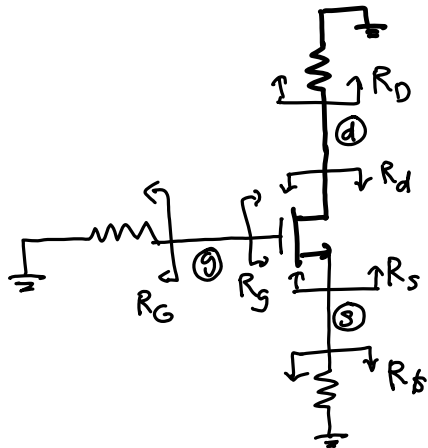⇒ for n/w, ignore Body effect (i.e., ignore  $g_{mb}$ )  
 ↪ use the same inspection formulas as bipolar,  
 but  $\beta \rightarrow \infty$ ,  $r_{\pi} = \frac{\beta}{g_m} \rightarrow \infty$



⇒ referring to the bipolar inspection formula sheet:



<u>Bipolar</u>	$\xrightarrow{\beta \rightarrow \infty}$	<u>MOS</u>
$R_b = (\frac{1}{g_m} + R_E)(\beta + 1)$	$\xrightarrow{\beta \rightarrow \infty}$	$R_g = \infty$
$R_e = \frac{1}{g_m} + \frac{R_B}{\beta + 1}$	$\xrightarrow{\beta \rightarrow \infty}$	$R_s = \frac{1}{g_m}$
$R_c = r_o \left[ 1 + \frac{g_m R_E}{1 + R_B/r_{\pi}} \right]$	$\xrightarrow[\beta \rightarrow \infty]{r_{\pi} \rightarrow \infty}$	$R_d = r_o (1 + g_m R_E)$

$$\frac{v_d}{v_g} = -G_m R_D, \quad G_m = \frac{g_m}{1 + g_m R_E}$$

$$\frac{v_d}{v_s} = -G_m R_D, \quad G_m = -g_m$$

$$\frac{v_s}{v_g} = \frac{g_m R_E}{1 + g_m R_E} = \frac{R_E}{\frac{1}{g_m} + R_E}$$

MOS Inspection Analysis

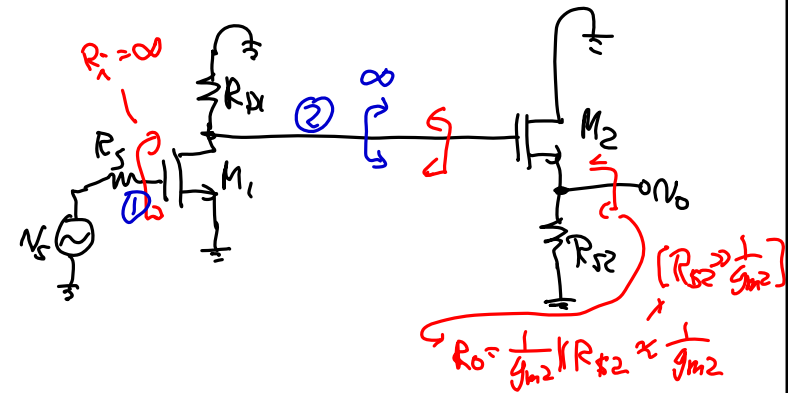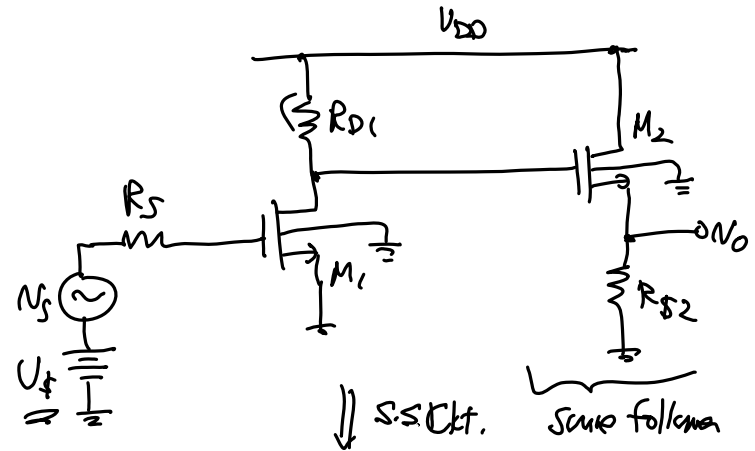

$$\frac{v_o}{v_s} = \frac{v_D}{v_s} \cdot \frac{v_D}{v_D} \cdot \frac{v_o}{v_D}$$

$$= (1)(-g_m R_D) \left( \frac{R_{S2}}{R_{S2} + \frac{1}{g_{m2}}} \right) = \frac{v_o}{v_s}$$

**Problem:** Simulate in SPICE → the  $g_m$  will be 80-90% of what is calculated using the problem is we ignored  $g_{mb}$  (should do this for a source follower)

this is the difference between the bipolar & MOS hybrid- $\pi$  models

**Source Follower:**

$v_{gs} = v_i - v_o$   
 $v_{bs} = -v_o$   
 $R_S = \frac{1}{G_S}$   
 $g_{ds} = \frac{1}{r_o}$

$$g_m(v_i - v_o) = v_o(g_{ds} + G_S + g_{mb})$$

$$\Rightarrow \frac{v_o}{v_i} = a_v = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_S}$$

$R_S = \infty \rightarrow G_S = 0$   
 $g_{ds} \ll g_m + g_{mb}$

← Body factor

$$a_v \approx \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}, \quad \eta = \frac{g_{mb}}{2\sqrt{V_{SB} + 2\phi_f}}$$

$\neq 1$

To make it '1', can do this:

$\Rightarrow$  not usually practical

washed out → costly X

MOS Inspection Formulas w/ Substrate Grounded

↳ only difference from "substrate tied to source" case is that  $g_m$  is replaced by  $g_m + g_{mb}$  in some of the formulas  
 particularly over where the source is involved!

$$R_g = \infty$$

$$R_s = \frac{1}{g_m + g_{mb}}$$

$$R_d = r_o [1 + (g_m + g_{mb}) R_s]$$

$$\frac{N_d}{N_g} = -G_m R_{(a)}, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_s}$$

$$\frac{N_d}{N_s} = -G_m R_{(a)}, \quad G_m = -(g_m + g_{mb})$$

$$\frac{N_s}{N_{\theta}} = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s}$$

Remark: When the substrate is tied to the source,  $g_{mb} = 0$ .