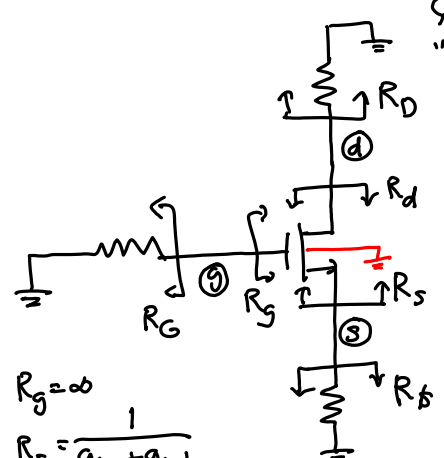


Lecture 6: Frequency Response Inspection Analysis

- Announcements:
- HW#2 due tomorrow at 8 a.m.
- Lab#1 is online; HW#3 online soon
- Lecture Topics:
 - ↳ Amplifier Bode plot
 - ↳ Open Circuit Time Constant (OCTC) Analysis
 - ↳ Frequency Response Inspection Analysis

• Last Time:

Mos Inspection Formulas w/ Substrate Grounded



↳ only difference from substrate tied to source case is that g_m is replaced by $g_m + g_{mb}$ in some of the formulas particularly over where the source is involved!

$R_g = \infty$
 $R_s = \frac{1}{g_m + g_{mb}}$

$R_d = r_o [1 + (g_m + g_{mb}) R_B]$


$\frac{v_s}{v_o} = \frac{g_m R_B}{1 + (g_m + g_{mb}) R_B}$

$\frac{v_d}{v_g} = -G_m R_D$, $G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_B}$


$\frac{v_d}{v_s} = -G_m R_D$, $G_m = -(g_m + g_{mb})$

Remark: When the substrate is tied to the source, $g_{mb} = 0$.

Effect of g_{mb} on Impedance

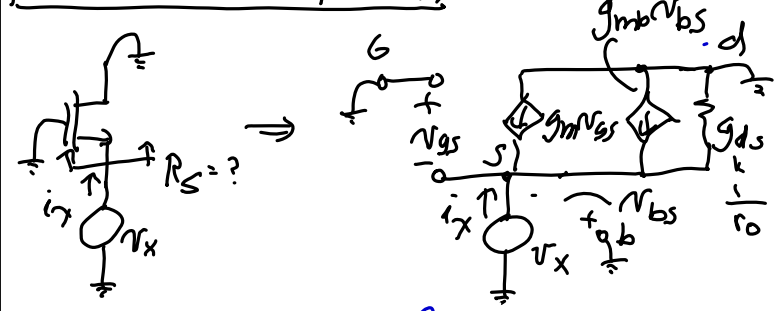

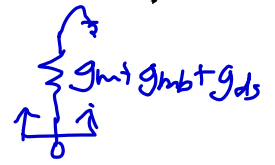$v_{gs} = -v_x = v_{bs}$
 $v_{ds} = -v_x$




$R_s = \frac{1}{g_m + g_{mb} + g_{ds}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel \frac{1}{g_{ds}}$
 $\frac{1}{r_o} \Rightarrow \frac{1}{g_m} \parallel \frac{1}{g_{mb}}$

$R_s \approx \frac{1}{g_m} \parallel \frac{1}{g_{mb}} = \frac{1}{g_m + g_{mb}}$

If continue to analyze all quantities,

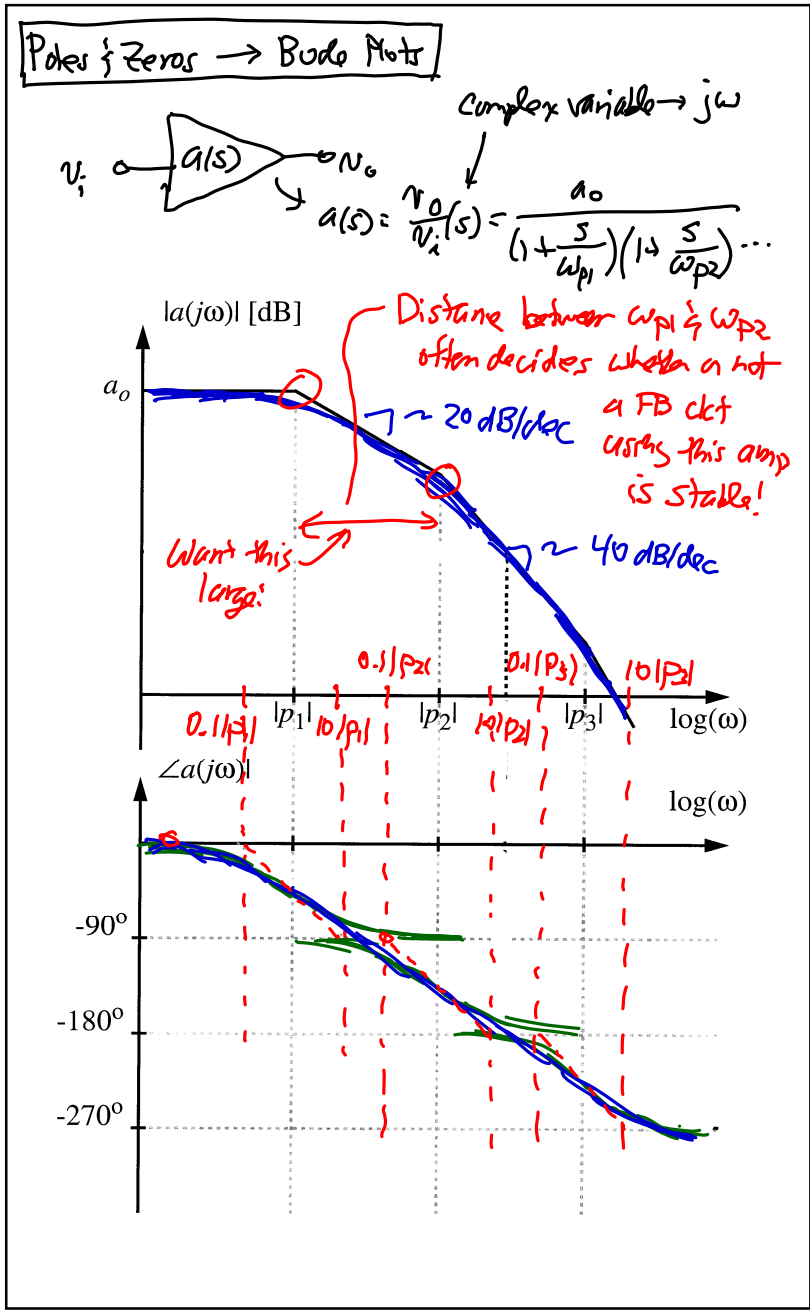
" g_m " \rightarrow " $g_m + g_{mb}$ " (for all denominators) (but not some numerators)



Freq. Response

Recall that the transfer function of a general amplifier can be expressed as a function of frequency via:
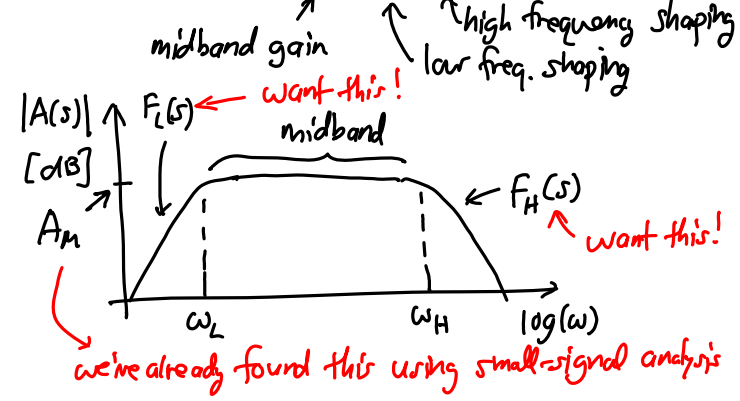
$$A(s) = A_M F_L(s) F_H(s) \quad s = j\omega$$




High Freq. Response Determination Using Open Ckt. Time Constant (OCTC) Analysis

In general:

$$F_H(s) = \frac{1 + a_1 s + a_2 s^2 + \dots + a_{n_z} s^{n_z}}{1 + b_1 s + b_2 s^2 + \dots + b_{n_p} s^{n_p}} \quad n_p > n_z$$
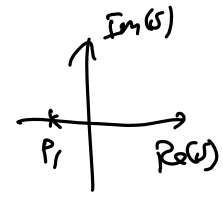
$$= \frac{\prod_{j=1}^{n_z} (1 - \frac{s}{z_j})}{\prod_{i=1}^{n_p} (1 + \frac{s}{\omega_{pi}})}$$



from which:

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn_p}} = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{k=1}^{n_p} \tau_{pk}$$

↑
coeff. of the 1st order term

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{np} \tau_{pi} = \sum_j C_j R_{j0} = \sum_j \tau_{j0}$$

where C_j are capacitors in the H.F. ckt., i.e., small ones
 $R_{j0} \hat{=}$ driving pt. resistance seen between the terminals of C_j determined with

- ① all small (< 1nF) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e., > 1μF or > 1nF)

In calculating the H.F. response, we use the dominant pole approximation:

(i) $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pn}$
 (ii) $F_H(s) \cong \frac{1}{1 + \frac{s}{\omega_H}}$
 (iii) $b_1 \cong \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \cong \frac{1}{b_1} = \frac{1}{\sum_j \tau_{j0}} = \frac{1}{\sum_j C_j R_{j0}}$


When there is no dominant pole, an approximate expression for ω_H is:

$$\omega_H \approx \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots - \frac{1}{\omega_{z1}^2} - \frac{1}{\omega_{z2}^2} \dots}}$$


(just FYI)

• Now, go to inspection formula sheet and go over how to use the frequency response parts

Ex: H.F. Analysis (C.F. Ckt.)

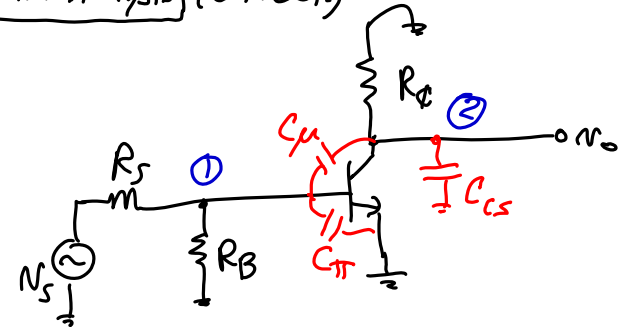


Find τ_{D1} :

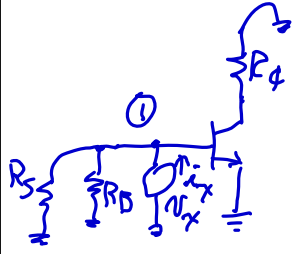

$$R_{D1} = \frac{v_x}{i_x} = R_S || R_B || R_L$$

$$\tau_{D1} = C_{\pi} (R_S || R_B || R_L)$$

Find τ_{D2} :

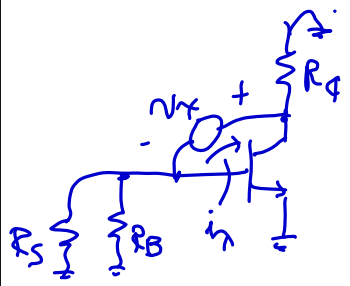

$$R_{D2} = \frac{v_x}{i_x} = R_O + R_L + g_m R_O R_L$$

$$R_{D2} = (R_S || R_B || R_{\pi}) + (R_O || R_L)$$

$$+ g_m (R_S || R_B || R_{\pi}) (R_O || R_L)$$

$$\tau_{D2} = C_{\mu} R_{D2}$$

Find T_{out} : $T_{\text{out}} = C_{cs}(r_{o1} || R_d) \approx C_{cs} R_d$

$\omega_H = \frac{1}{T_{\text{out}} + T_{\text{out}0} + T_{\text{out}2}$

Now, use Miller's Theorem:

$C_M = (1 - a_v) C_{u1} = (1 + g_m R_d) C_{u1}$

$T_{\text{out}} = (R_S || R_B || r_{\pi}) (C_{\pi} + C_M (1 + g_m R_d))$

$T_{\text{out}} = R_d (C_u + C_{cs})$

$\omega_H = \frac{1}{T_{\text{out}} + T_{\text{out}2}}$

Exactly the same as before!

Ex. Multi-Transistor Cks.

$T_{\text{out}} = (R_S || 2r_{\pi1}) C_{u1}$

$T_{\pi} = C_{\pi1} \left(r_{\pi1} || \left[\frac{R_S + \frac{1}{g_{m2}}}{1 + g_m \left(\frac{1}{g_{m2}} \right)} \right] \right)$

$T_{\text{out}} = C_{\pi2} \left[\left(\frac{1}{g_{m1}} + \frac{R_S}{\beta + 1} \right) || \frac{1}{g_{m2}} || R_{EE} \right]$

$T_{\text{out}} = (C_{cs2} + C_{u2}) R_d$

$\omega_H = \frac{1}{T_{\text{out}} + T_{\text{out}2} + T_{\text{out}3} + T_{\pi}}$

$R_{EE} = \text{very large}$

Ex. MOS Two-Stage Amplifier

$C_{\mu} = C_{gd1}(1 + g_{m1}R_{D1})$
 $\tau_{\text{O1}} = [C_{gd1}(1 + g_{m1}R_{D1}) + C_{gs1}]R_{S}$
 $\tau_{\text{O2}} = [C_{db1} + C_{gd1} + C_{gd2}]R_{D1}$
 $\tau_{\text{O3}} = C_{sb2} \left(R_{S2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$
 ~~$\tau_{gs2} = C_{gs2} \left(\frac{R_{D1} + R_{S2}}{1 + (g_{m2} + g_{mb2})R_{S2}} \right)$~~

Same voltage (w/ unity gain)
 $\tau_{gs2} \approx \frac{C_{gs2}R_{S2}}{1 + (g_{m2} + g_{mb2})R_{S2}}$
 No voltage drop across C_{gs2} \therefore it's effectively not there!

$\omega_H = \frac{1}{\tau_{\text{O1}} + \tau_{\text{O2}} + \tau_{\text{O3}} + \tau_{gs2}}$