

Lecture 8: Active Loads II & Current Sources

• Announcements:


- ↳ HW#3 due tomorrow at 8 a.m.
- ↳ HW#4 will be online soon
- ↳ Videos of recorded lectures accessible by the lecture table on the website (soon)

• Lecture Topics:

- ↳ Analysis of actively loaded circuits (continued)
- ↳ Current Sources

• Last Time:

Ex. Multi-Stage Actively-Loaded MOS Ckt.

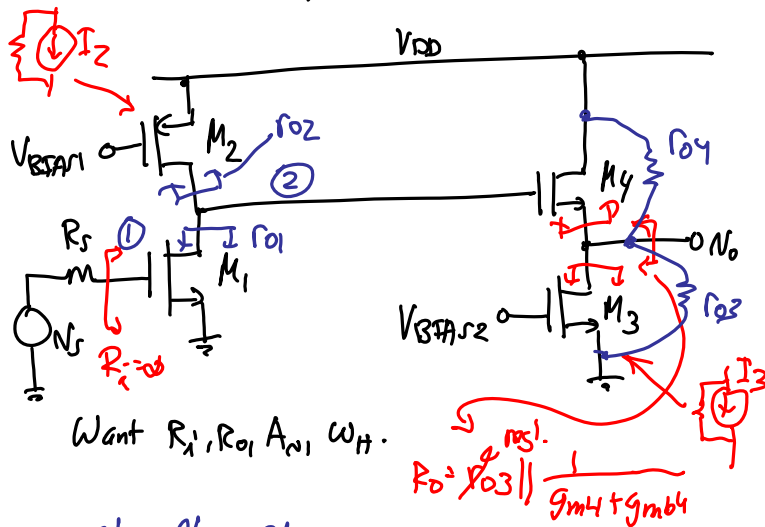


Want R_i, R_o, A_v, ω_H .

$$a_v = \frac{v_o}{v_s} = \frac{v_{o1}}{v_s} \cdot \frac{v_{o2}}{v_{o1}} \cdot \frac{v_o}{v_{o2}}$$

$$= (1 - g_{m1}(r_{o1} || r_{o2})) \cdot \frac{g_{m4}(r_{o3} || r_{o4})}{(1 + g_{m4} + g_{m4})(r_{o3} || r_{o4})}$$

$$a_v \approx -g_{m1}(r_{o1} || r_{o2}) \left(\frac{g_{m4}}{g_{m4} + g_{mb4}} \right)$$

Now, tackle freq. response:

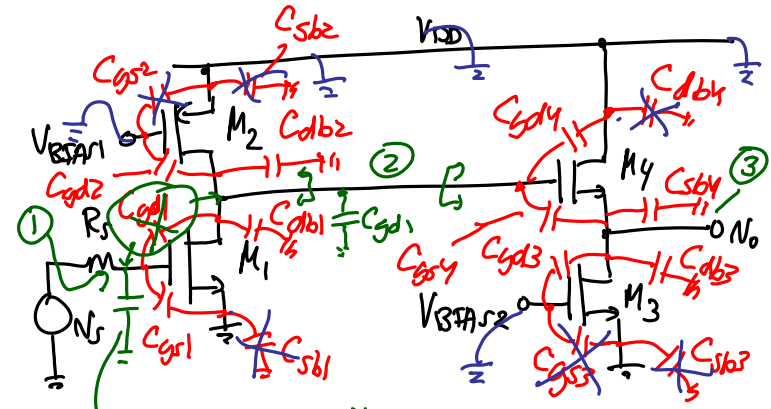

$$C_{u1} = (1 + g_{m1}(r_{o1} || r_{o2})) C_{gd1}$$

$$\tau_{D1} = \{ C_{gs1} + C_{gd1}(1 + g_{m1}(r_{o1} || r_{o2})) \} R_s$$

$$\tau_{D2} = \{ C_{db1} + C_{db2} + C_{gd1} + C_{gd2} + C_{gd4} \} (r_{o1} || r_{o2})$$

$$\tau_{D3} = \{ C_{gd3} + C_{db3} + C_{sb4} \} \left(\frac{1}{g_{m4} + g_{mb4}} \right) \times$$

$$\tau_{gs4} = C_{gs4} \left\{ \frac{(r_{o1} || r_{o2}) + (r_{o3} || r_{o4})}{1 + (g_{m4}(r_{o2} || r_{o4}) + g_{mb4})} \right\} \approx C_{gs4} \left(\frac{2}{g_{m4} + g_{mb4}} \right)$$

