
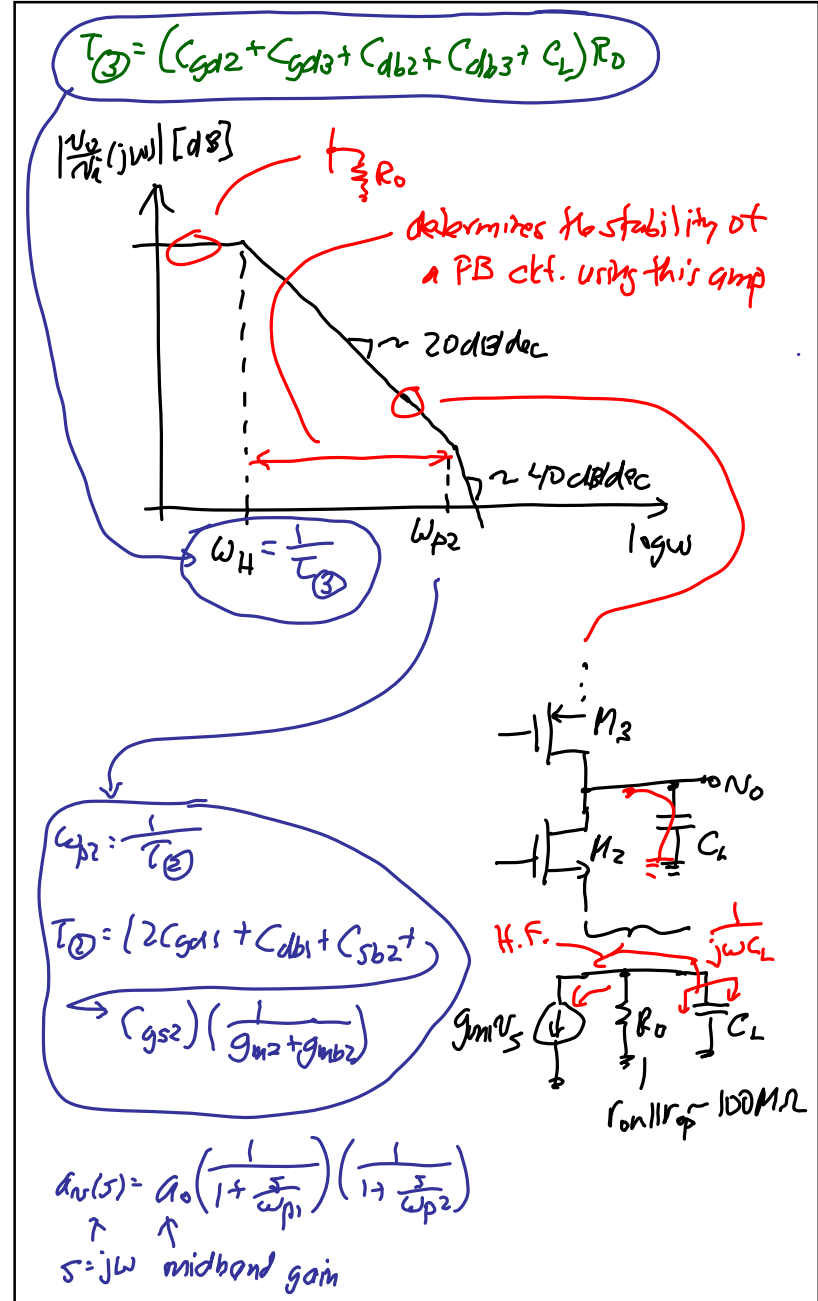


Lecture 9: Current Sources

- Announcements:
 - ↳ HW#4 online
- Lecture Topics:
 - ↳ Analysis of actively loaded circuits (continued)
 - ↳ Current Sources
 - ↳ Widlar Current Source
 - ↳ Supply & Temperature Independent Biasing

• Last Time:

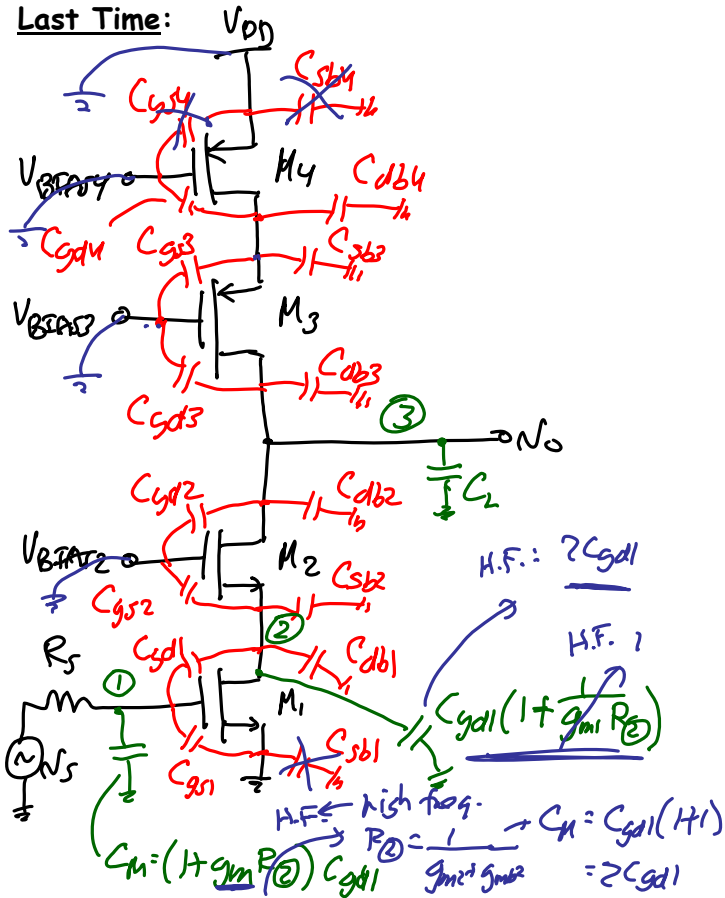

Transistor Current Sources

How can a transistor implement a current source?

I_0 \Rightarrow I_0 R_0 \Rightarrow bipolar \Rightarrow $R_0 = \infty \rightarrow$ ideal

Ideal Current Source Actual Current Source

Bipolar Forward-Active Xsistor Current Source

$$I_0 = I_c = I_s \exp\left(\frac{V_{BIAS}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$\phi_0 = V_0 = \frac{V_A}{I_c}$

Very stable if $V_{BIAS} = \text{const.}$ & $V_A = \text{large}$

Note that V_{BIAS} must be very accurate due to exponential \rightarrow to several sig. figs.

e.g., $V_{BIAS} = 0.68745V$

MOS Saturated MOS Xsistor Current Source

Problem: hard to specify R_1 & R_2 so exactly that they set the voltage to this precision

$$I_0 = I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{BIAS} - V_t)^2 (1 + \lambda V_{DS})$$

Again, very stable if $V_{BIAS} = \text{const.}$ & $\lambda = \text{small}$

Problem: need to generate a stable V_{BIAS}


We now focus on methods for generating V_{BIAS} . But how do we get this degree of precision using a transistor ckt?

Solution: \rightarrow

Replica Biasing (a simple & effective approach)

- ① Generate the desired current.
- ② Push the current through a Xsistor and allow it to reach a stable bias pt.
- ③ Use this stable bias pt. as V_{BIAS} \rightarrow this can be very precise!

One simple approach:

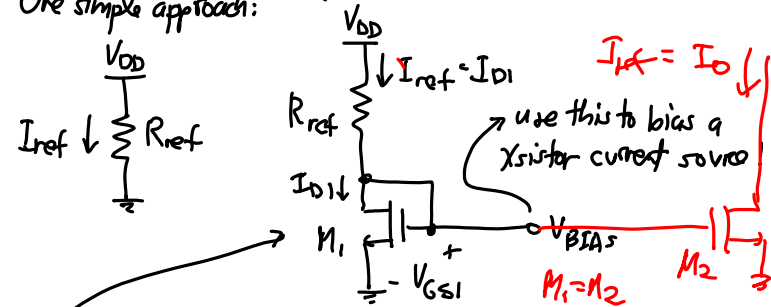


A diode-connected Xsistor is always in saturation and will basically bias itself to support the needed current!

$$I_{ref} = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$$

V_{BIAS}

Now, can distribute this V_{BIAS} to the gates of many MOS transistor current sources!

Ex. Simple MOS Current Source

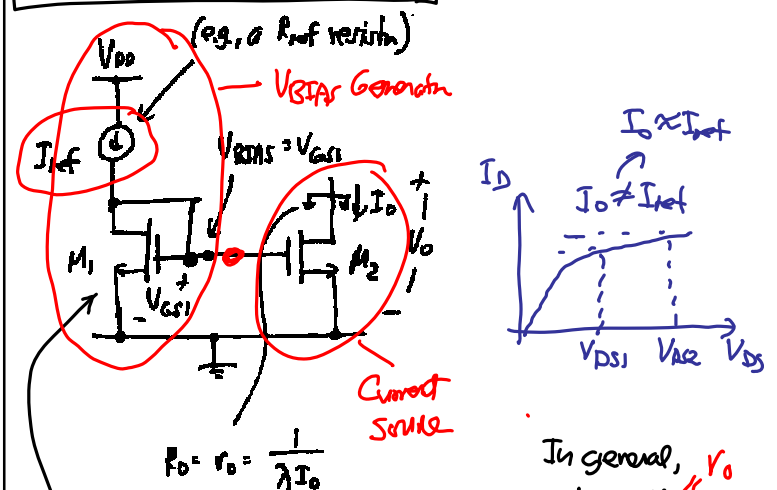

(eg, a R_{ref} resistor) V_{BIAS} Generator
 I_{ref}
 $V_{GS1} = V_{GS2}$
 I_D
 $I_0 \propto I_{ref}$
 $I_0 \neq I_{ref}$
 V_{DS1} V_{DS2} V_{DS}
 Current Source
 $P_0 = r_o = \frac{1}{\lambda I_0}$
 Diode-connected transistor \rightarrow saturation:
 $I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{BIAS} - V_t)^2 (1 + \lambda V_{DS1})$
 $I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{BIAS} - V_t)^2 (1 + \lambda V_{DS2})$
 In general, V_0
 $V_{DS1} \neq V_{DS2}$, but
 if λ is small, then
 little difference
 in I_{D1} & I_{D2}


① Case: matched M_1 & $M_2 \Rightarrow I_0 = I_{ref}$

② Case: M_1 & M_2 scaled w.r. to each other
 $\Rightarrow I_0 = I_{ref} \frac{(W/L)_2}{(W/L)_1}$
 \Rightarrow use $L_1 = L_2$ for better accuracy, then:


$$\frac{I_0}{I_{ref}} = \frac{W_2}{W_1}$$

Note: for better accuracy, should use multiple copies of one device when scaling currents \rightarrow reduces edge effects!

EX: Layout for a Doubling Current Source

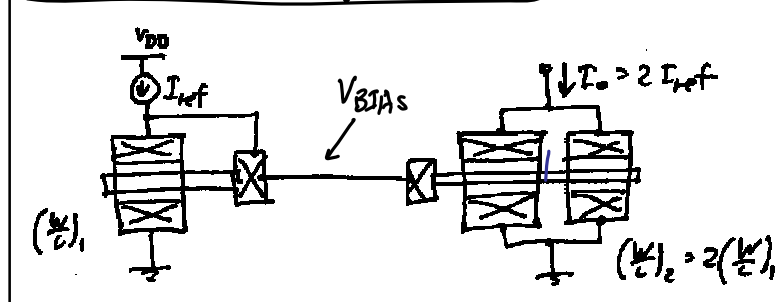


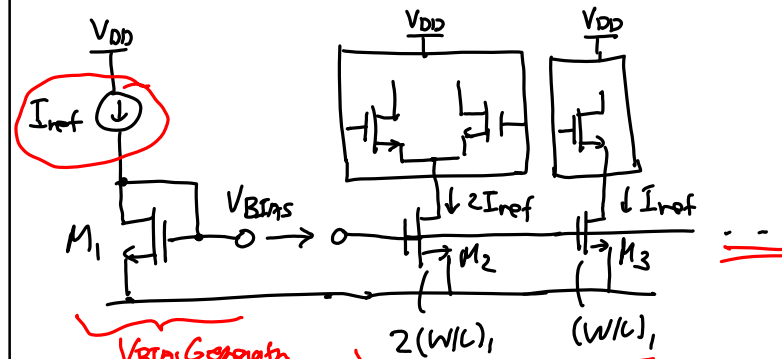A single V_{BIAS} generator can now serve numerous current sources:



How about bipolar?

Simple Bipolar Current Source

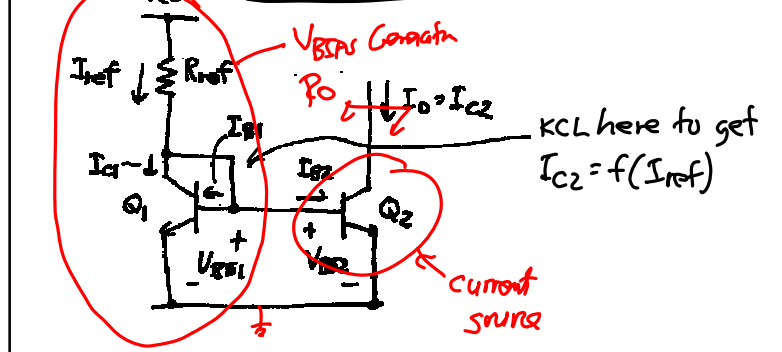

Assume Q_1 & Q_2 are matched. i.e., $V_A = \infty$


$V_{BE1} = V_{BE2} \rightarrow I_{C1} = I_{C2} = I_0$ (neglecting V_A 's)

KCL: $I_{ref} = I_{C1} + I_{B1} + I_{B2} = I_{C1} \left(1 + \frac{2}{\beta}\right)$

$\therefore I_{C1} = I_{C2} = I_0 = \frac{I_{ref}}{1 + \frac{2}{\beta}} \rightarrow I_0 \approx I_{ref}$

and $I_{ref} = \frac{V_{CC} - V_{BE(on)}}{R_{ref}}$ $R_0 = r_{o2}$ can say $\approx \frac{2}{\beta}$

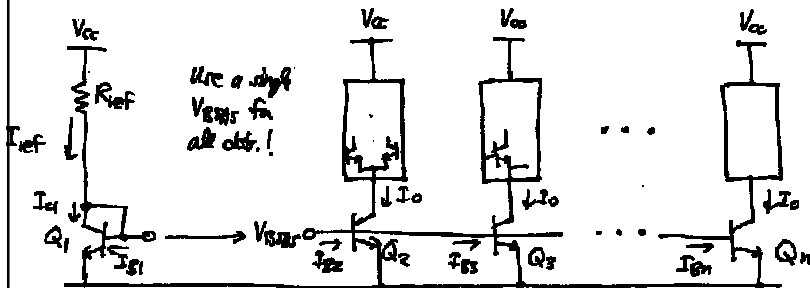Again, a single V_{BES} generator can serve many current sources throughout the IC chip:



$I_{ref} = I_{C1} + I_{B1} + I_{B2} + I_{B3} + \dots + I_{Bn}$

[Identical Xistors] $\rightarrow I_{ref} = I_{C1} \left(1 + \frac{n}{\beta}\right)$


$\Rightarrow I_0 = I_{C1} = \frac{I_{ref}}{\left(1 + \frac{n}{\beta}\right)}$

Problem: error $\sim \frac{n}{\beta}$ increases as n (I_0 deviates from I_{ref} , and the deviation depends on n .)

How can one reduce the error?

To reduce the error term, use a

Buffered V_{BES} -Generator

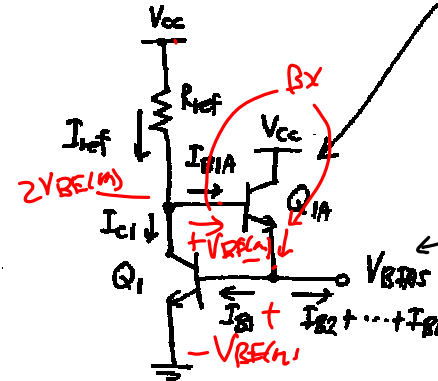

Add a buffer Xistor to attenuate base currents from Xistor current sources.

This can now drive the base currents of many bipolar-transistor current sources (i.e., active loads).

$I_{ref} = I_{C1} + I_{BIA}$

$I_{BIA} = \frac{I_{B1} + I_{B2} + \dots + I_{Bn}}{\beta + 1} = \frac{n I_{C1}}{\beta(\beta + 1)}$


[Assuming identical Xistors]

$I_{ref} = I_{C1} \left(1 + \frac{n}{\beta(\beta + 1)}\right)$

$\rightarrow I_0 = I_{C2} = \frac{I_{ref}}{1 + \frac{n}{\beta(\beta + 1)}} \approx I_{ref} \left(1 - \frac{n}{\beta^2}\right)$

Note: Now, $I_{ref} = \frac{V_{CC} - 2V_{BE(on)}}{R_{ref}}$

Problem: For power savings reasons, oftentimes very small bias currents are needed, on the order of $5\mu A$. This might force for large an R_{ref} in the above bipolar V_{BES} generator.

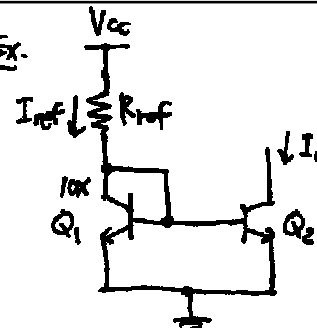Ex. 

$V_{BE1} = V_{BE2} + V_{R2} = V_{BE2} + \frac{1}{\alpha} I_{C2} R_2 \approx V_{BE2} + I_{C2} R_2$

$I_{C2} R_2 = V_{BE1} - V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$

$I_{C2} R_2 = V_T \ln \frac{I_{C1}}{I_{S2}}$ [Assuming $\alpha_1 \neq \alpha_2$ are matched]

$I_0 R_2 = V_T \ln \frac{I_{ref}}{I_0}$

Rule of Thumb: $V_{R2} = I_{C2} R_2$ $\frac{I_{C2} \cdot I_0}{\frac{1}{2} I_{ref}}$
 18mV $\frac{1}{2} I_{ref}$
 42mV $\frac{1}{5} I_{ref}$
 60mV $\frac{1}{10} I_{ref}$
 120mV $\frac{1}{100} I_{ref}$

→ Sub example again

Ex. scale by 100x using Widlar source

$V_{BE1} - V_{BE2} = 120mV \rightarrow R_2 = \frac{120mV}{5\mu A} = 24k\Omega$

$I_{ref} = 500\mu A \rightarrow R_{ref} = \frac{30V}{500\mu A} = 60k\Omega$

More accurate than 600kΩ before.
If want smaller, scale by 100x instead.


Another advantage of the Widlar: larger R_0 : a more ideal current source:


$R_0 = r_{o2} (1 + g_{m2} R_2)$

IF Q_1 is 10x larger than Q_2 .
 $\therefore I_{S1} = 10 I_{S2} \rightarrow I_0 \approx I_{ref}/10$
 $\therefore I_0 = \frac{(V_{CC} - V_{BE(on)})}{10 R_{ref}} \rightarrow R_{ref} = \frac{V_{CC} - V_{BE(on)}}{10 I_0}$
 ↑ this helps to lower R_{ref} , but is it enough?

Ex. $I_0 = 5\mu A$, $V_{CC} = 30V$
 $R_{ref} \approx \frac{30}{5\mu} = 600k\Omega$ ← That's way too big!
 (Yes, there's only one of them on the chip, but this takes up too much space!)

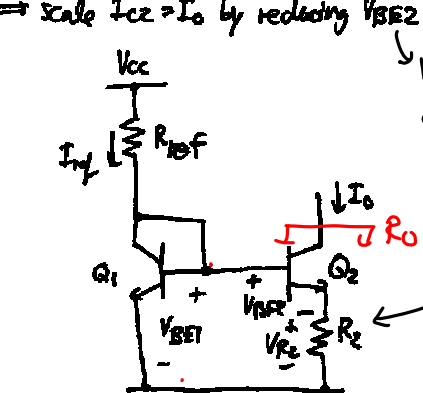The Low Current Solution: **Widlar Current Source**
 \Rightarrow scale $I_{C2} = I_0$ by reducing V_{BE2} (relative to V_{BE1}):
 Do this by emitter degenerating Q_2 via R_2



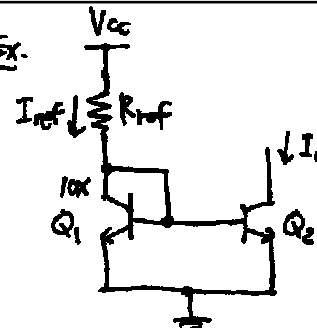Ex. 

$V_{BE1} = V_{BE2} + V_{R2} = V_{BE2} + \frac{1}{\alpha} I_{C2} R_2 \approx V_{BE2} + I_{C2} R_2$

$I_{C2} R_2 = V_{BE1} - V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}}$

$I_{C2} R_2 = V_T \ln \frac{I_{C1}}{I_{S2}}$ [Assuming $\alpha_1 \neq \alpha_2$ are matched]

$I_0 R_2 = V_T \ln \frac{I_{ref}}{I_0}$

Rule of Thumb: $V_{R2} = I_{C2} R_2$ $\frac{I_{C2} \cdot I_0}{\frac{1}{2} I_{ref}}$
 18mV $\frac{1}{2} I_{ref}$
 42mV $\frac{1}{5} I_{ref}$
 60mV $\frac{1}{10} I_{ref}$
 120mV $\frac{1}{100} I_{ref}$

→ Sub example again

Ex. scale by 100x using Widlar source

$V_{BE1} - V_{BE2} = 120mV \rightarrow R_2 = \frac{120mV}{5\mu A} = 24k\Omega$

$I_{ref} = 500\mu A \rightarrow R_{ref} = \frac{30V}{500\mu A} = 60k\Omega$

More accurate than 600kΩ before.
If want smaller, scale by 100x instead.


Another advantage of the Widlar: larger R_0 : a more ideal current source:

$R_0 = r_{o2} (1 + g_{m2} R_2)$

Supply & Temperature Independent Biasing

- Why is it necessary?
- For battery-operated systems, battery voltages vary over time
 - ↳ Amplifier gains change
 - ↳ Power consumption changes
 - ↳ Frequency of oscillators changes
 - ↳ In summary: long-term stability degrades
 - ↳ Large uncertainty in biasing translates to overdesign that wastes power
- Same issues as above when temperature varies with time
- Short-term supply variations
 - ↳ In mixed signal circuits, i.e., both analog and digital together, digital switching generates noise on the supply lines
 - ↳ Noise can couple to analog circuits, reducing their dynamic range

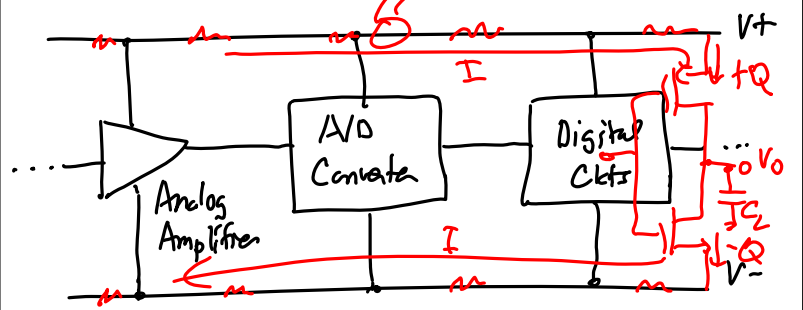$N_{TP} - V_{TH} \approx 10mV \rightarrow 100mV$
~~XXXXXXXXXX~~




Definition: Sensitivity of Y to X

$$S_x^y = \frac{\frac{\Delta Y}{Y}}{\frac{\Delta X}{X}} = \frac{X}{Y} \frac{\Delta Y}{\Delta X} = \frac{X}{Y} \frac{\partial Y}{\partial X}$$

For supply independence, we want $S_{V_{CC}}^{I_0} = 0$.

Simple Current Source

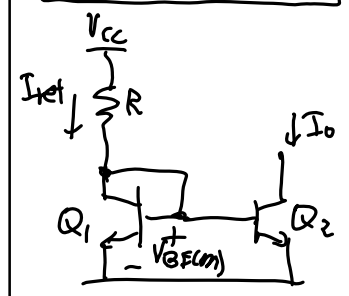

Neglecting base current:

$$I_0 = I_{ref} = \frac{V_{CC} - V_{BE(m)}}{R}$$

$$I_0 \approx \frac{V_{CC}}{R} \quad [V_{CC} \gg V_{BE(m)}]$$

Thus:

$$S_R^{I_0} = \frac{R}{I_0} \frac{\partial I_0}{\partial R} = \frac{R^2}{V_{CC}} \left(-\frac{V_{CC}}{R^2} \right) \Rightarrow S_R^{I_0} = -1$$

$$S_{V_{CC}}^{I_0} = \frac{V_{CC}}{I_0} \frac{\partial I_0}{\partial V_{CC}} = R \left(\frac{1}{R} \right) \Rightarrow S_{V_{CC}}^{I_0} = 1$$

∴ 10% change in Vcc leads to 10% change in I0!

(terrible!)

Widlar Current Source (Any better?)

$V_T \ln \frac{I_{ref}}{I_0} = I_0 R_2$
 $V_T (\ln I_{ref} - \ln I_0) = I_0 R_2$
 Differentiate w.r.t to V_{cc} :

$\Rightarrow V_T \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} - \frac{1}{I_0} \frac{\partial I_0}{\partial V_{cc}} \right) = R_2 \frac{\partial I_0}{\partial V_{cc}}$
 rearrange
 $\frac{\partial I_0}{\partial V_{cc}} = \frac{V_T}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \frac{I_0}{(R_2 + \frac{V_T}{I_0})}$
 $\therefore S_{V_{cc}}^{I_0} = \frac{V_{cc}}{I_0} \frac{\partial I_0}{\partial V_{cc}} = \frac{V_T \left(\frac{V_{cc}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \right)}{I_0 R_2 + V_T}$
 $\Rightarrow S_{V_{cc}}^{I_0} = \left(\frac{1}{1 + \frac{I_0 R_2}{V_T}} \right) S_{V_{cc}}^{I_{ref}}$

Since $I_{ref} = \frac{V_{cc} - V_{BE(1)}}{R_1} \approx \frac{V_{cc}}{R_1} \Rightarrow S_{V_{cc}}^{I_{ref}} \approx 1$

$\therefore S_{V_{cc}}^{I_0} = \frac{1}{1 + \frac{I_0 R_2}{V_T}}$

For $I_{ref} = 1\text{mA}$, $I_0 = 10\mu\text{A}$, $R_2 = 11.9\text{k}\Omega$, then
 $10\% \Delta$ in $V_{cc} \rightarrow 1.39\% \Delta$ in I_0
 (better than a simple current source)

How can we do better? \rightarrow use another voltage reference!

- ✓ ① $V_{BE(1)}$ \rightarrow bjt emitter junction voltage
- ✓ ② V_Z \rightarrow Zener diode
- ✓ ③ V_T \rightarrow threshold voltage (MOS)
- ✓ ④ $V_T = \frac{kT}{q}$ \rightarrow thermal voltage
- ✓ ⑤ E_g \rightarrow bandgap