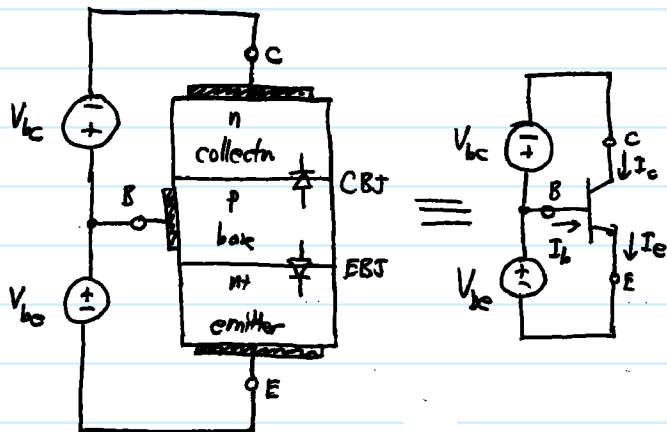



Modeling the Bipolar Junction Transistor (BJT)

⇒ physically, BJT's are just back-to-back pn junctions

npn bipolar Xistor



ppn bipolar Xistor

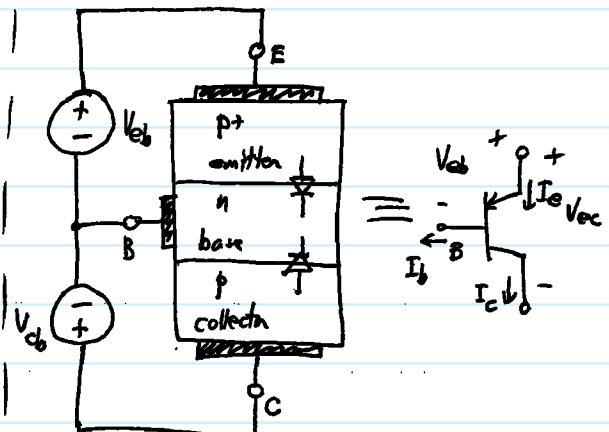

Regions of Bipolar Xistor Operation


EBJ	CBJ
R	R
F	R
R	F
F	F

Key: R = reverse-biased, F = forward-biased

- Cut-off (both diodes off)
- Forward Active (widely used in analog amplifier ckt)
- Reverse Active
- Saturation

⇒ can also think of this in a convenient graphical sense:

→ for npn (pnp):


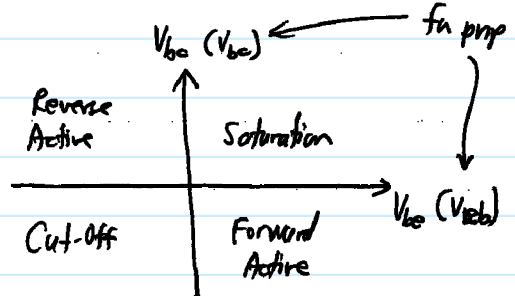


① Cut-off Region - (npn transistor)

⇒ both diodes reverse-biased



⇒ no current flows:

$I_b = 0, I_c = 0, I_e = 0$

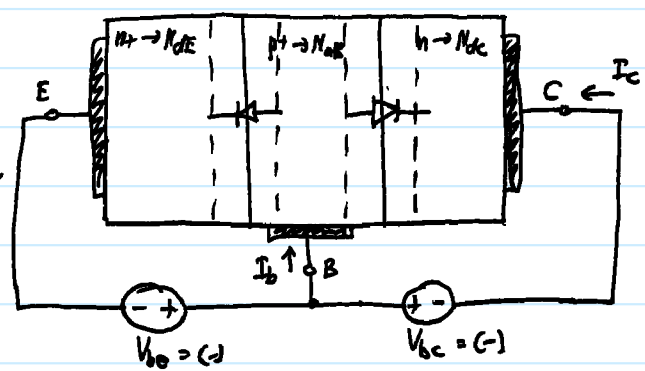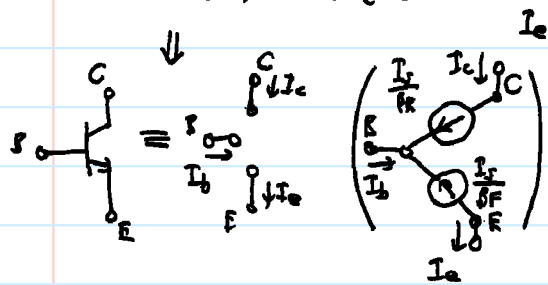

② Forward-Active Region - (npn transistor)

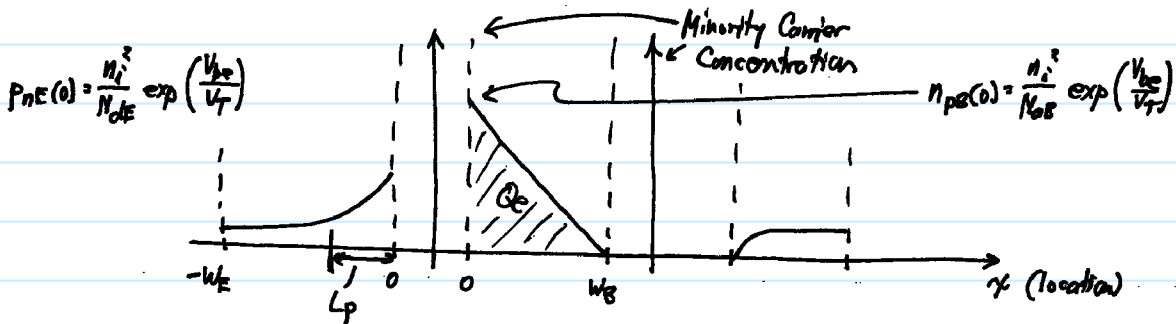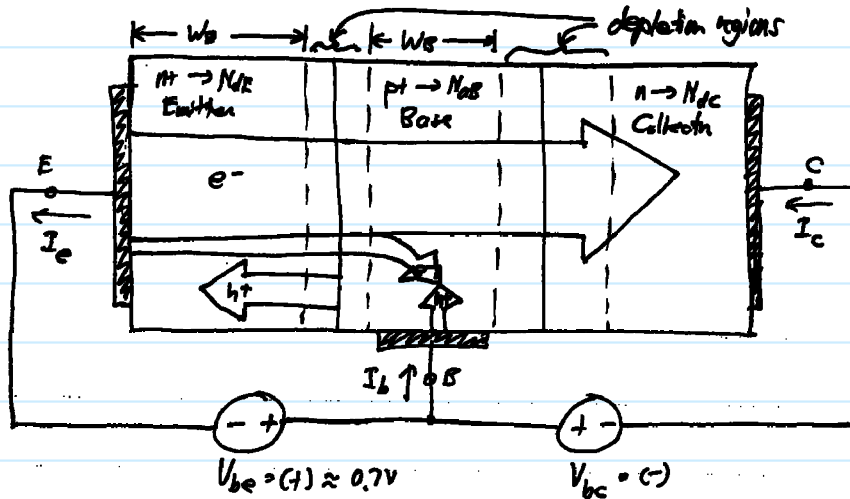⇒ BEJ Forward-Biased (i.e., diode on), BCJ Reverse-Biased (i.e., diode off)



Forward biasing of the BEJ generates three current components:

- ① \$e^-\$'s injected from emitter to base : \$I_{nB} = -A J_{nB}^{diff}\$
 - ② \$h^+\$'s injected from base to emitter : \$I_{pE} = A J_{pE}^{diff}\$
 - ③ recombination of \$e^-\$'s & \$h^+\$'s in base : \$I_{rB}\$
- $I_C = I_{nB} = ①$
 $I_E = I_{nB} + I_{pE} + I_{rB} = ① + ② + ③$
 $I_B = I_{pE} + I_{rB} = ② + ③$

$$I_{nB} = -A J_{nB}^{diff} = -A q D_{nB} \frac{dn_p(x)}{dx} = -q A D_{nB} \frac{[n_{pB}(W_B) - n_{pB}(0)]}{W_B} = \boxed{q A D_{nB} \frac{n_i^2}{N_{DB} W_B} \exp(\frac{V_{BE}}{V_T}) = ①} *$$

Diffusion constant for \$e^-\$'s in B
 Diffusion constant for \$h^+\$'s in E

$n_{pB}(W_B) = \frac{n_i^2}{N_{DB}} \exp(\frac{V_{BC}}{V_T}) \approx 0$
 $n_{pB}(0) = \frac{n_i^2}{N_{DB}} \exp(\frac{V_{BE}}{V_T})$

$I_C = I_S \exp(\frac{V_{BE}}{V_T})$

$$I_{pE} = A J_{pE}^{diff} = A q D_{pE} \frac{dp_n(x)}{dx} = q A D_{pE} \frac{[p_{nE}(0) - p_{nE}(-W_E)]}{W_E} = \boxed{q A D_{pE} \frac{n_i^2}{N_{DE} W_E} \exp(\frac{V_{BE}}{V_T}) = ②} *$$

$p_{nE}(0) = \frac{n_i^2}{N_{DE}} \exp(\frac{V_{BE}}{V_T})$
 $p_{nE}(-W_E) \approx 0$

could also replace by diffusion length, \$L_p\$ (for \$h^+\$ in n-type material)

minority-carrier charge in base

$$I_{B1} = \frac{Q_E}{\tau_b} = \frac{1}{\tau_b} \left[\frac{1}{2} n_{pe}(0) W_B qA \right] = \frac{1}{2} \frac{n_i^2 W_B qA}{N_B \tau_b} \exp\left(\frac{V_{BE}}{V_T}\right) = \textcircled{3} \quad *$$

minority carrier lifetime in base

Define Forward Current Gain = β_F :

$$\beta_F = \frac{I_C}{I_B} = \frac{\textcircled{1}}{\textcircled{3} + \textcircled{2}} = \frac{\frac{qADn_{pi}^2}{N_B W_B}}{\frac{1}{2} \frac{n_i^2 W_B qA}{N_B \tau_b} + \frac{qADn_{pi}^2}{N_{DE} W_E}} = \left[\frac{W_B^2}{2\tau_b D_{nB}} + \frac{D_{nE} W_B N_A}{D_{nB} W_E N_D} \right]^{-1}$$

which we also want

To maximize β_F , want:

① $W_B = \text{small}$

② $N_{DE} \gg N_B$ (this is why emitter is n+) \rightarrow also leads to $D_{pE} \ll D_{nE}$

③ $\tau_b = \text{large}$ (base Si must be free of impurities/defects to prevent recombination)

More Complete Expression for β_F :

$$\beta_F = \underbrace{\frac{N_B W_B}{D_{nB}} \cdot \frac{D_{pE}}{N_D L_{pE}}}_{\text{Injection Efficiency}} + \underbrace{\frac{1}{2} \left(\frac{W_B}{L_{nB}}\right)^2}_{\text{Volume Recombination}} + \underbrace{s \left(\frac{A_s}{A_E}\right) \left(\frac{W_B}{D_{nB}}\right)}_{\text{Surface Recombination}} + \underbrace{\frac{W_E N_B W_B}{2 D_{nB} \tau_{n1}} e^{-\frac{V_{BE}}{2V_T}}}_{\text{Recombination in the BE Depletion Region} \leftarrow \text{Significant @ low current levels}}$$

where: $s =$ Surface recombination velocity

$D_i =$ Diffusion constant

$n_i =$ intrinsic carrier concentration

$N_i =$ carrier concentration


$A_E =$ total emitter area

$A_s =$ sidewall emitter area


$\tau =$ minority carrier lifetime

$L_i =$ diffusion length ($L_i = \sqrt{D_i \tau}$)

$W_B =$ active base width

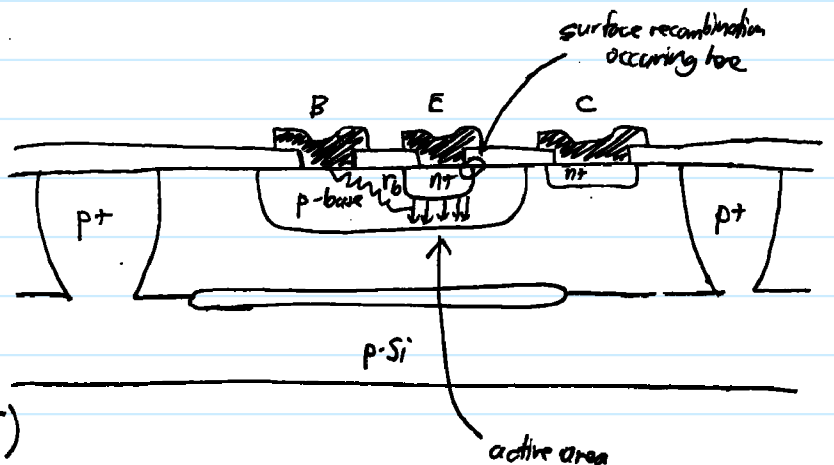

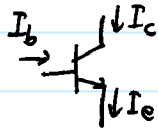So β relates I_b & I_c . To relate I_c & I_e , use KCL:





$$I_e = I_c + I_b = I_c + \frac{I_c}{\beta} = \left(1 + \frac{1}{\beta}\right) I_c$$


$$\Rightarrow I_c = \left(\frac{1}{1 + \frac{1}{\beta}}\right) I_e = \left(\frac{\beta}{\beta + 1}\right) I_e = \alpha I_e, \text{ where } \boxed{\alpha = \frac{\beta}{\beta + 1}} \Rightarrow \boxed{\beta = \frac{\alpha}{1 - \alpha}}$$

Equivalent Large Signal Ckt. Models for Forward-Active BJTs

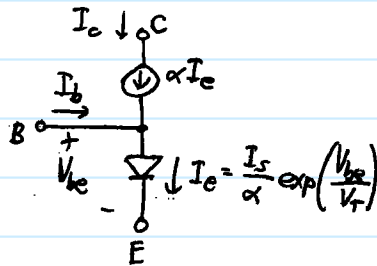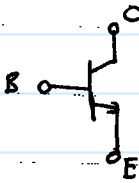There are several of them. The most useful ones are:





Common Base (CCCS)

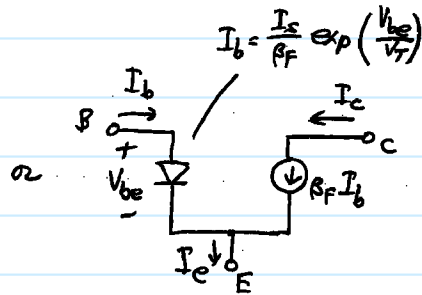


Common Emitter (CCCS)

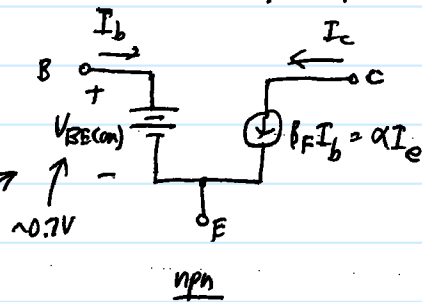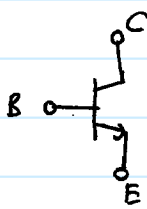But usually one doesn't have to use those complicated models. Rather, the following usually suffices:




nPN

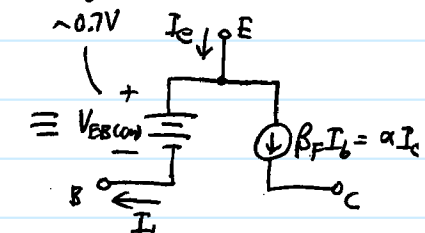

pNP

Just as in a diode:

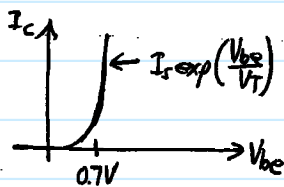

You should already be used to using approximate models like this
 \Rightarrow the more complicated models are a waste of time in comparison

③ Reverse-Active Region -

\Rightarrow very similar to forward-active region except now: BEJ reverse-biased

BCJ forward-biased

\Rightarrow one important difference: $\beta_R \propto \frac{N_{dcb} W_b D_{nb}}{N_{ab} W_B D_{pe}}$

$N_{dc} \ll N_{ab} \rightarrow D_{nb} \ll D_{pc}$


$\therefore \beta_R$ is much smaller than β_F
 \Rightarrow poor device performance

④ Saturation Region -

BEJ forward-biased $\rightarrow V_{BE(sat)} \sim 0.8V$ (higher than 0.7V in saturation)

BCJ forward-biased $\rightarrow V_{BC(sat)} \sim 0.6V$

Result:

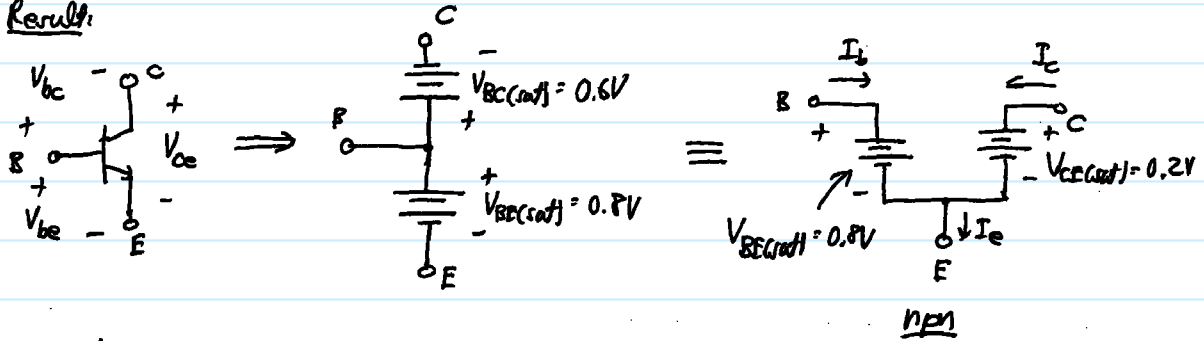

\Rightarrow currents now determined by the attached elements & KCL:



$$I_e = I_b + I_c ; \text{ no longer have } I_b = \frac{I_c}{\beta} \text{ or } I_c = \alpha I_e$$

These no longer apply when BJT is in saturation.

When determining DC operating point:


- Pass $\left\{ \begin{array}{l} \text{① Assume forward-active} \rightarrow \text{check for cut-off (enough } V_{be}?) \\ \text{② Determine } V_{ce} \\ \text{③ If } V_{ce} > V_{ce(sat)} = 0.2V, \text{ then ok (i.e., it's forward-active) ... otherwise, must do the} \\ \text{analysis over assuming saturation.} \end{array} \right.$

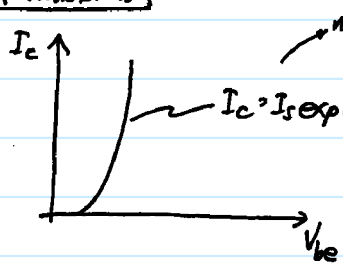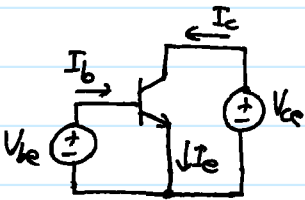IV Characteristics of Bipolar Junction Transistors




nonlinear \rightarrow not easy to work with since we can't use linear system theory \rightarrow this real life behavior!
 (a diode-like characteristic)
 digital ctr. \rightarrow piecewise linear analysis ok. \rightarrow small-signal models

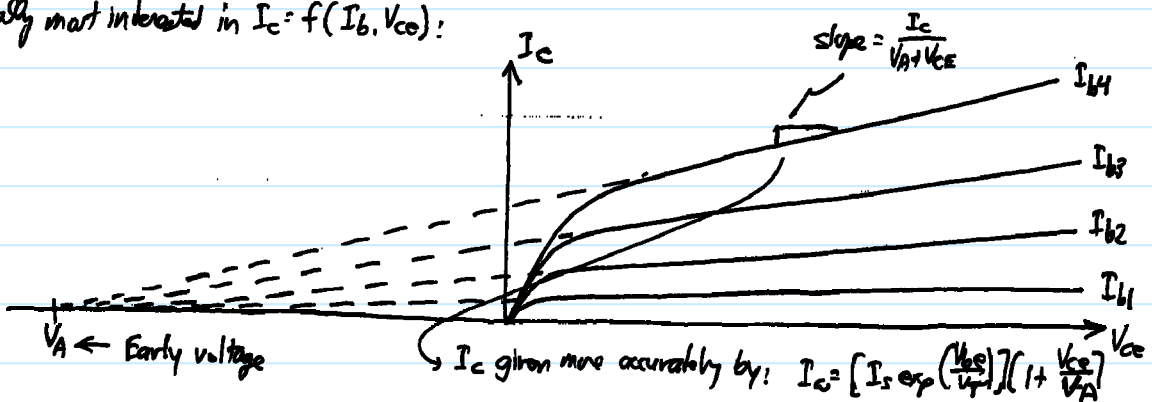\Rightarrow really most interested in $I_c = f(I_b, V_{ce})$:



What is happening physically?

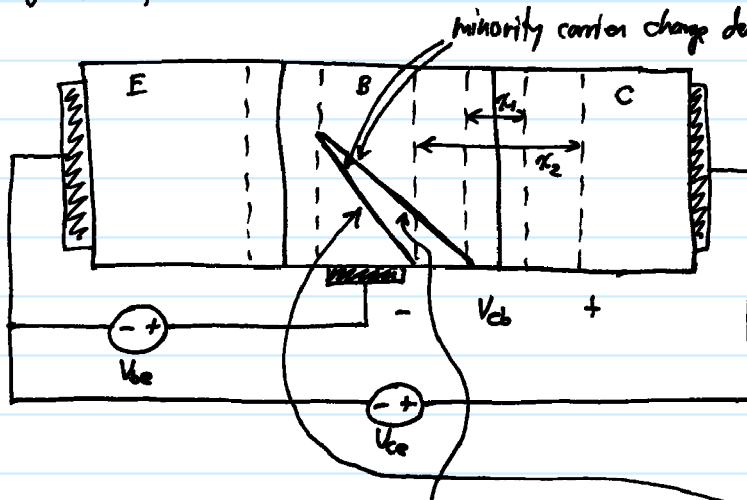

$x_1 \triangleq$ depl. region width for $V_{ce} = V_{ce1}$

$x_2 \triangleq$ depl. region width for $V_{ce} = V_{ce2} > V_{ce1}$

① Case: $V_{ce} = V_{ce1} \rightarrow x_1 \rightarrow I_{c1} \propto$ slope of this carrier line

② Now, increase $V_{ce1} \rightarrow V_{ce2} \rightarrow V_{cb} \uparrow \rightarrow x_1 \uparrow$ to $x_2 \rightarrow I_{c2} \propto$ slope of this line

$\therefore I_{c2} > I_{c1}$


Thus, $V_{ce} \uparrow \rightarrow I_c \uparrow$ due to $x_{depl.} \uparrow$

Result: $I_c = f(I_b, V_{ce})$ in forward-active!


$$I_c = \left[I_s \exp\left(\frac{V_{be}}{V_T}\right) \right] \left[1 + \frac{V_{ce}}{V_A} \right]$$

← This, V_{ce} , is a more accurate I_c equation.

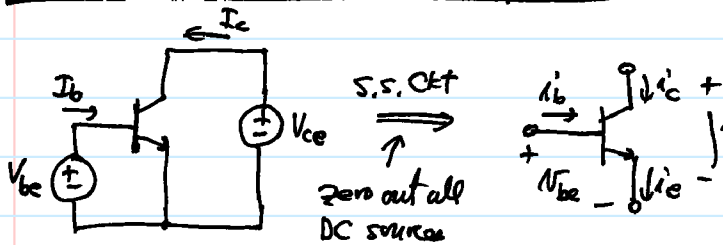Small-Signal Models for Forward-Active Bipolar Xsistors



Y-parameter Model

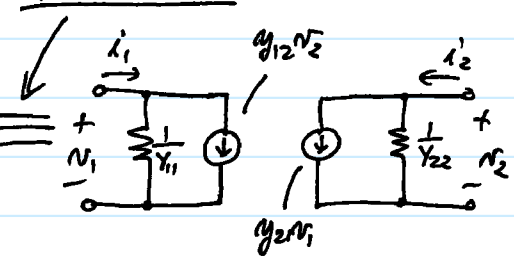


If only interested in the forward direction

$$Y_{11} = \frac{i_1}{V_1} \Big|_{V_2=0} \quad Y_{21} = \frac{i_2}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{i_1}{V_2} \Big|_{V_1=0} \quad Y_{22} = \frac{i_2}{V_2} \Big|_{V_1=0}$$

Hybrid- π Model

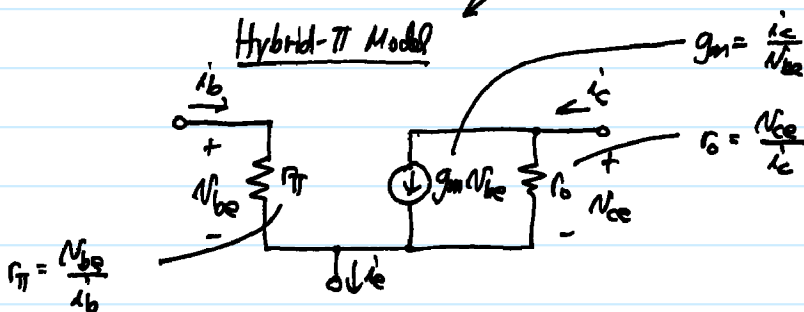

Specified by the bias point.


$$r_{\pi} = \frac{V_{be}}{I_b}$$

$$g_m = \frac{I_c}{V_{be}}$$

$$r_o = \frac{V_{ce}}{I_c}$$

Determine the S.S. elements



$$g_m = \frac{i_c}{v_{be}} = \frac{\partial I_c}{\partial v_{be}} \Big|_{Q-pt.} = \frac{\partial}{\partial v_{be}} \left[I_s \exp\left(\frac{v_{be}}{V_T}\right) \right] \Big|_{v_{be} = V_{BE}} = \frac{I_c}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow g_m = \frac{I_c}{V_T}$$

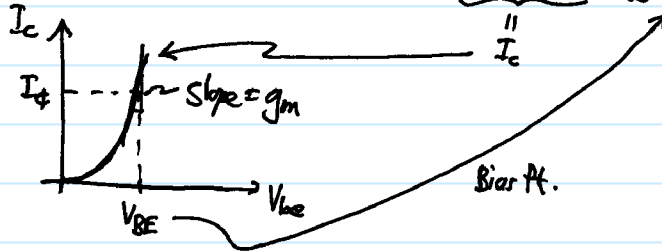

$$\frac{I_c}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow g_m = \frac{I_c}{V_T}$$

Note: function of the DC operating pt.



$$r_{\pi} = \frac{v_{be}}{i_b}$$

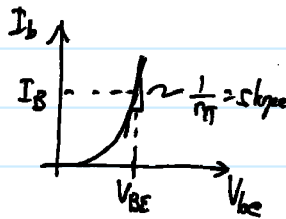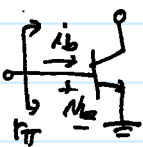

$$r_{\pi} = \frac{v_{be}}{i_b} = \frac{V_{be}}{I_b} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_c}{V_T}} = \frac{V_T}{I_B}$$

$\therefore r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$ Again, function of the DC operating pt.


$$r_o = \frac{v_{ce}}{i_c}$$

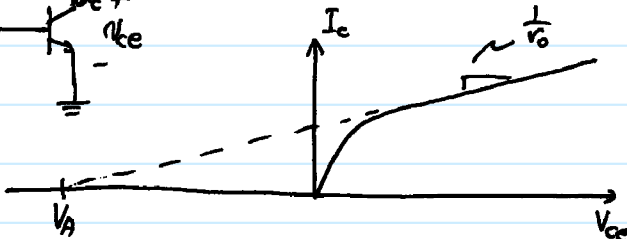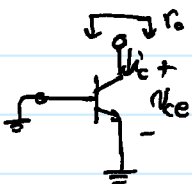

$$r_o = \frac{\partial v_{ce}}{\partial i_c} \Big|_Q = \left[\frac{\partial I_c}{\partial v_{ce}} \Big|_Q \right]^{-1} = \left[\frac{\partial}{\partial v_{ce}} \left(I_s \exp\left(\frac{v_{be}}{V_T}\right) \left[1 + \frac{v_{ce}}{V_A} \right] \right) \Big|_{v_{be} = V_{BE}} \right]^{-1} = \left[\frac{I_s \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A} \right]^{-1} = \frac{V_A + V_{CE}}{I_C}$$

$$\therefore r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \quad [V_A \gg V_{CE}]$$

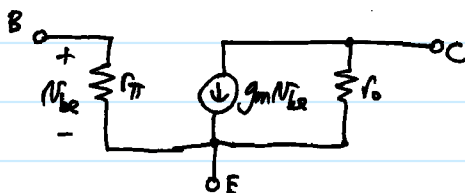... and thus, we have the hybrid- π model:



SPICE: BPF

$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{I_C}{V_A}$$

SPICE: VAF

Remarks:


i.e., β, I_s

quite different from MOS, as we'll see

① g_m is independent of device specifics; depends only on temperature (thru V_T) and biasing I_C

② small-signal model valid for $v_{be} \ll V_T \leftarrow \approx 26mV @ 300K$

What about emitter resistance?

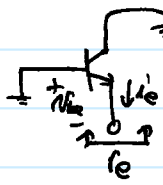


$$r_e = \frac{V_{be}}{i_e} = \frac{V_{be}}{i_c} = \frac{\alpha}{g_m} = \frac{\alpha V_T}{I_E} = \frac{V_T}{I_E}$$

$$\Rightarrow r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_E}$$

Note that although it's not explicitly shown in the hybrid- π model, r_e is present.

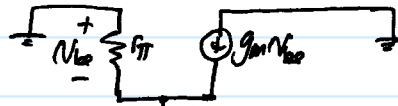
\Rightarrow i.e., if you analyze this, you find that




$$\frac{v_x}{i_x} = \frac{\alpha}{g_m} = r_e$$

To explicitly show emitter resistance, use the T-model:

T-Model: (Common Base Model)

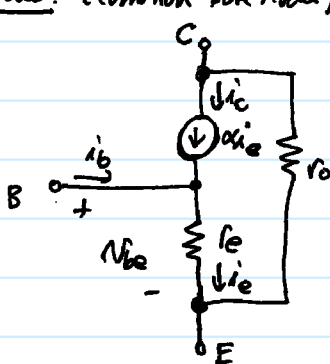

forward-active

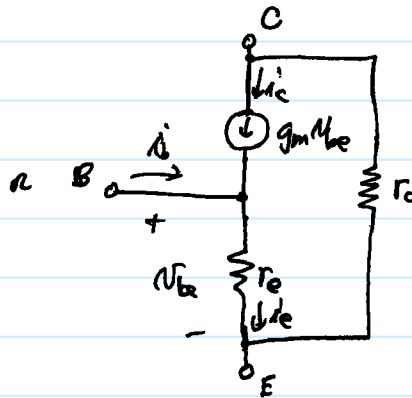

where as before:


$$g_m = \frac{I_C}{V_T}$$

$$r_e = \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

relative


Small-Signal Model for pnp Transistors

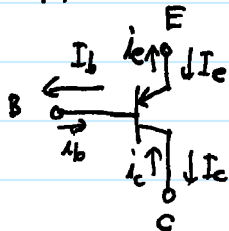For pnp transistors, use the same small-signal models as npn with no change in polarities!




Small-signal

Hybrid- π Model:

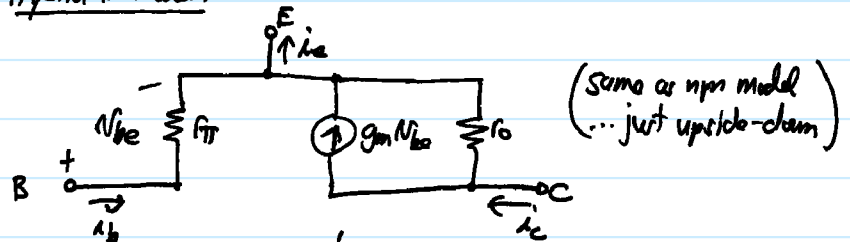

(Same as npn model ... just upside-down)

T-Model:

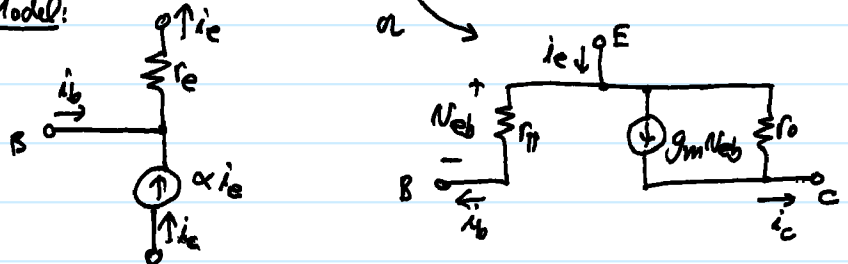


Note that in these S.S. models,

the same current directions as used for npn are used too

\Rightarrow i.e., no change in S.S. polarities


(large-signal directions, however, can be as before)

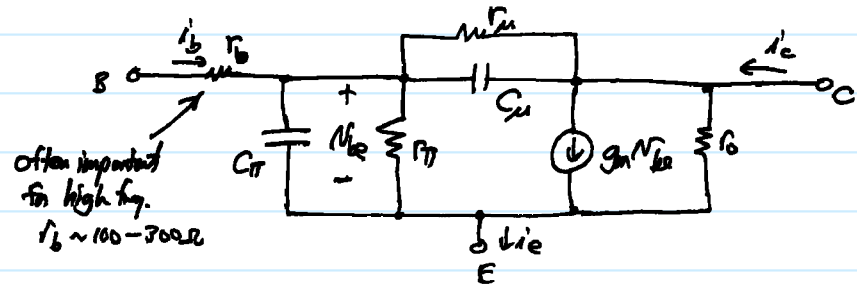More Complete Hybrid- π Model (adding frequency effects & 2nd order effects)



often important for high freq.
 $r_b \sim 100 - 300 \Omega$

C_{μ} - Base-to-Collector Capacitance

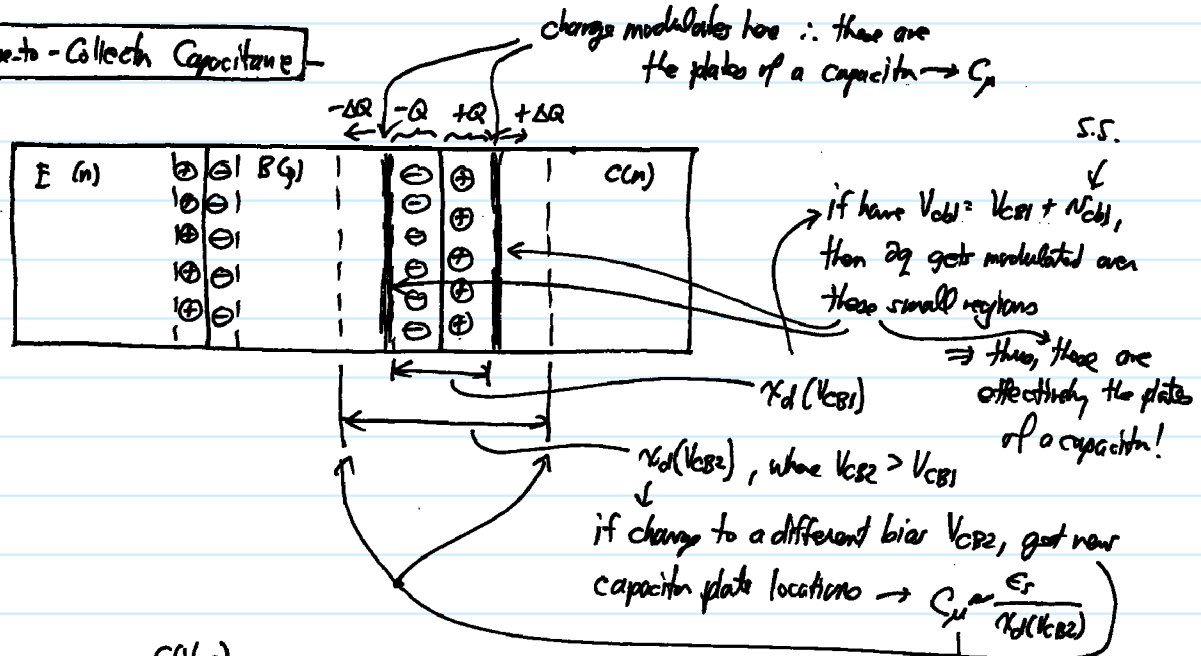

$C_{\mu} = \frac{C_{j0}}{\sqrt{1 + \frac{V_{CB}}{\phi_j}}}$ where C_{j0} = capacitance for $V_{CB} = 0$
 ϕ_j = function of the built-in potential between p and n-type semiconductors
 $\phi_j = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$
 $n_i = 1.45 \times 10^{10} \text{ cm}^{-3}$


In general:
 $C_{\mu} = \frac{C_{j0}}{\left(1 + \frac{V_{CB}}{\phi_j}\right)^m}$, where $m = \frac{1}{2}$ or $\frac{1}{3}$ depending upon how abrupt the junction is

Detailed Derivation: [FIS]

$x_d \approx x_n = \left[\frac{2\epsilon(V_0 + V_{CB})}{qN_A(1 + \frac{N_D}{N_A})} \right]^{1/2} \rightarrow Q = qN_A x_d = A \left[\frac{2\epsilon q N_A (V_0 + V_{CB})}{1 + \frac{N_D}{N_A}} \right]^{1/2}$
 $[N_A \ll N_D]$
 $C_j = \frac{dQ}{dV_{CB}} \Big|_{V_{CB}} = \left[\frac{2\epsilon q N_A}{1 + \frac{N_D}{N_A}} \right]^{1/2} \frac{A}{2} (V_0 + V_{CB})^{-1/2} = A \frac{[q\epsilon N_A N_D]^{1/2}}{[2(N_A + N_D)]^{1/2}} \frac{1}{\sqrt{V_0 + V_{CB}}} = C_j | V_{CB}$
 $C_j = \frac{\epsilon_s A}{x_d(V_{CB})}$


C_{π} - Base-to-Emitter Capacitance

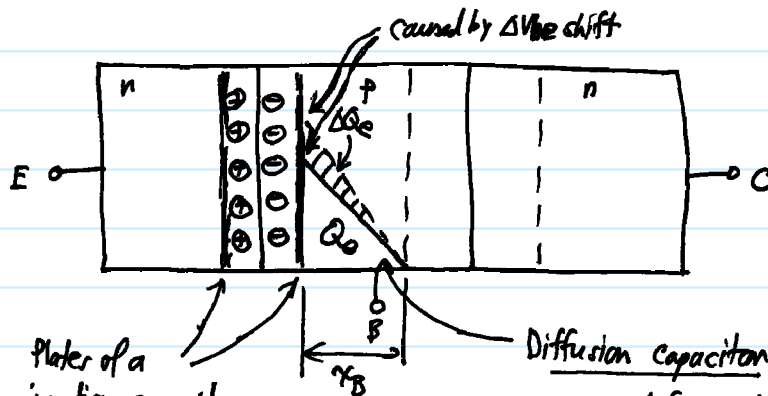Two components comprise C_{π} : ① Junction capacitance, C_{je}
 ② Diffusion capacitance, C_b



Plates of a junction capacitor:
 → bias level determines where the plates are
 In SPICE:
 CJE
 VJE
 MJE
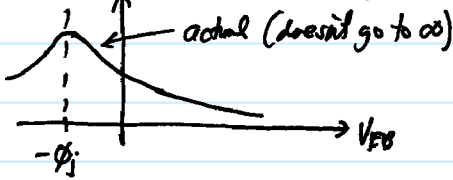
$$C_{je} = \frac{C_{je0}}{\left(1 + \frac{V_{EB}}{\phi_0}\right)^m}$$



Diffusion capacitance: (or Base Charging Capacitance)

⇒ can define a base transit time:

$$\tau_F = \frac{Q_e}{I_c} = \frac{x_B^2}{2D_n}$$

arg. time spent by carrier in crossing base
 think of I_c as the rate of x_B of charge through the base

$$Q_e = \tau_F I_c$$

$$\Delta Q_e = \tau_F \Delta I_c$$

Switch to S.S. parameters (variables):

$$q_e = \tau_F i_c$$

$$q_e = C_b \frac{dq}{dt} \rightarrow C_b = \frac{q}{i_c} = \tau_F \frac{i_c}{i_c} = \tau_F g_m = \tau_F \frac{I_c}{V_T} = C_b$$


SPICE: τ_F

$$\therefore C_b \propto I_c$$

$$C_{\pi} = C_b + C_{je} \approx 2C_{je0}$$

$$C_{\pi} = \tau_F g_m + \frac{C_{je0}}{\left(1 + \frac{V_{EB}}{\phi_0}\right)^m}$$

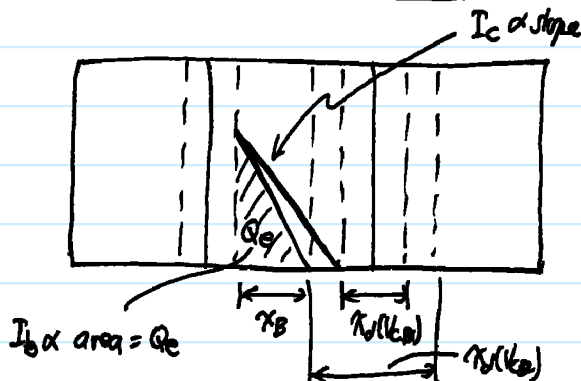
Collector-to-Base Feedback Resistor, r_{μ}




Remember, recombination base current $I_{rB} = \frac{Q_e}{\tau_b}$!

$\therefore N_{ce} \uparrow \rightarrow x_B \downarrow \rightarrow Q_e \downarrow \rightarrow i_b \downarrow$
 $\rightarrow i_c \uparrow$ (due to Early effect)

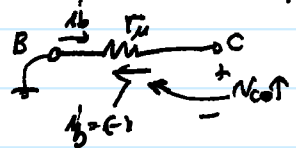$N_{ce} \uparrow \rightarrow i_b \downarrow$ can be modeled by an r_{μ} connected C-to-B



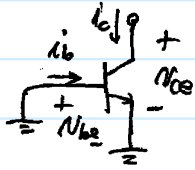

\Rightarrow here, $N_{be} = 0 \rightarrow N_{ce} = N_{cb}$

$$\therefore \frac{I_c}{N_{ce}} = \frac{1}{r_o} = \frac{I_c}{N_{cb}} = \frac{\beta I_b}{N_{cb}} \rightarrow \frac{N_{cb}}{I_b} = \beta r_o = r_{\mu}$$

assuming all of I_b is recombination current



In general, base recombination current is only part of the total base current and is the only component dependent on $V_{bc} \Rightarrow$ thus,

$r_{\mu} > \beta_0 r_o \rightarrow r_{\mu} = 2-10 \beta_0 r_o$
 (label pnp) (npn) $\rightarrow I_b$ is 10% recomb.
 where base recomb. more significant

Complete Forward Active BJT S.S. Model (including parasitics)

\Rightarrow Actual integrated BJT:

should draw this on the board

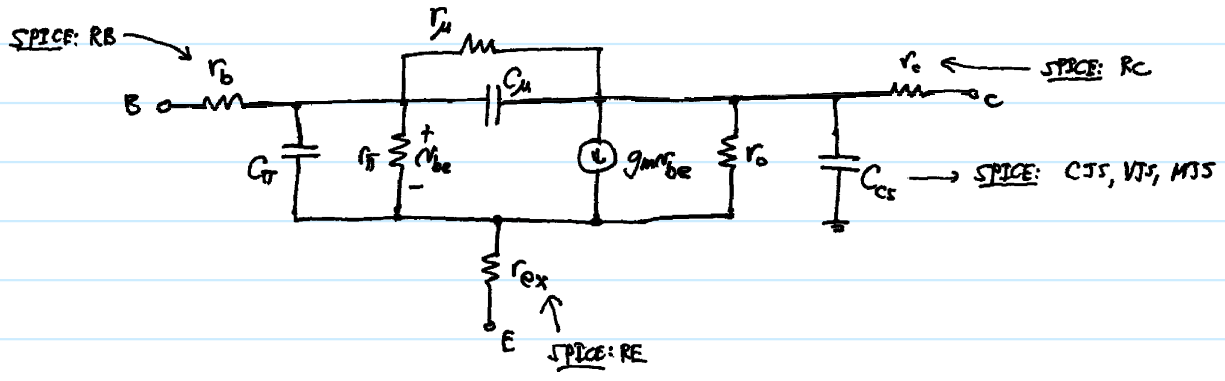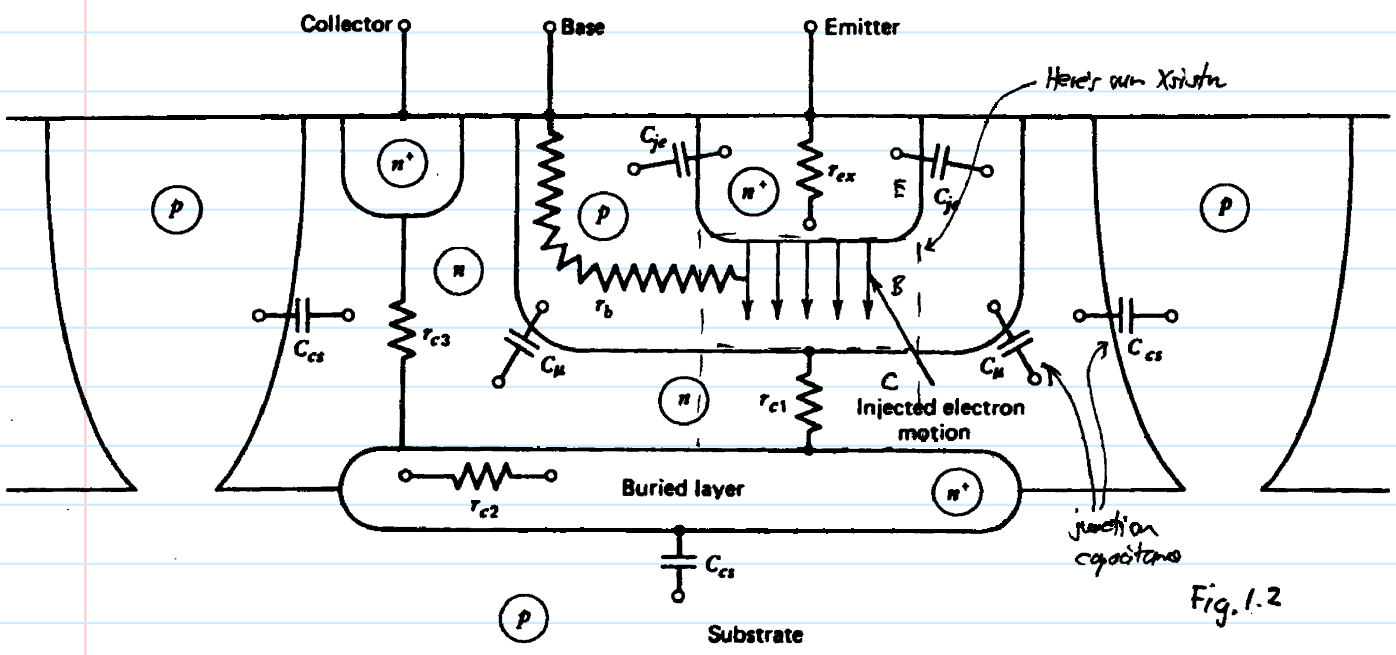


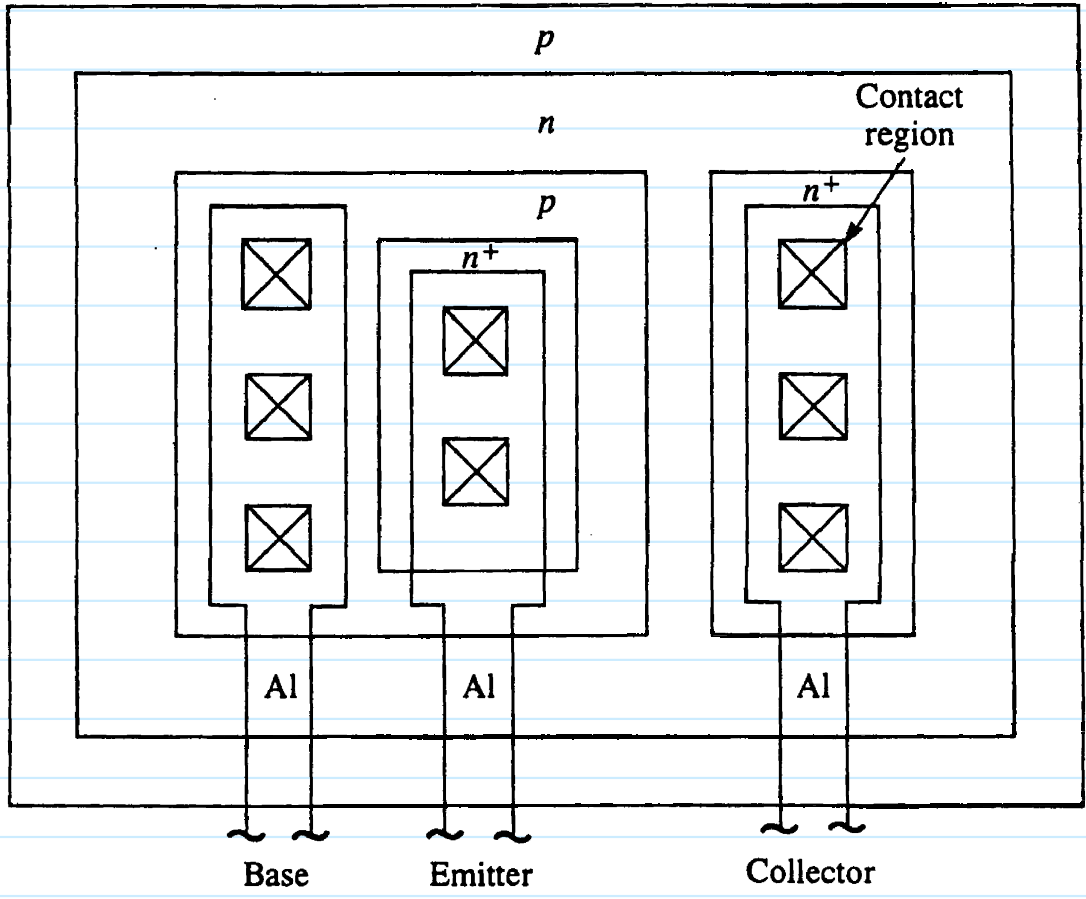
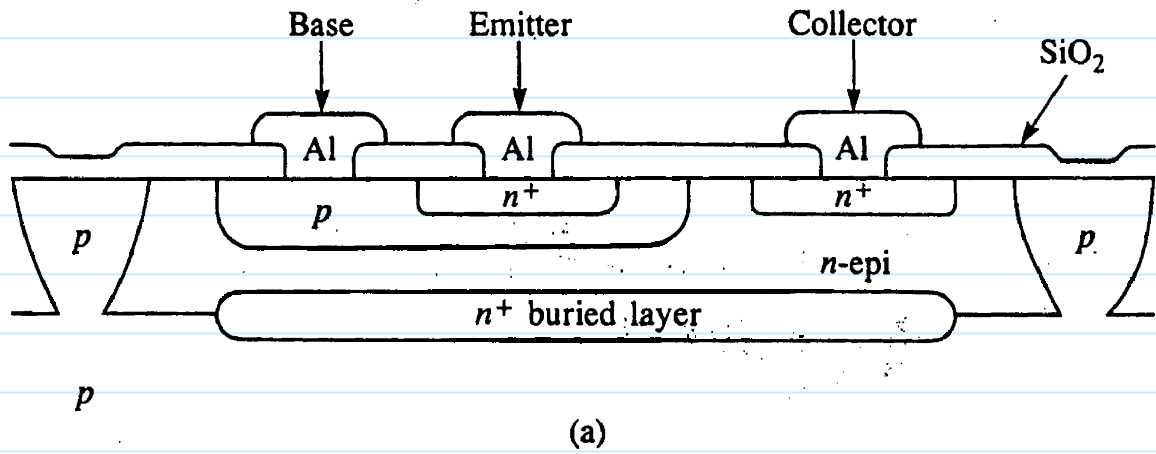


Fig. 1.1

f_T (unity gain freq. for β)

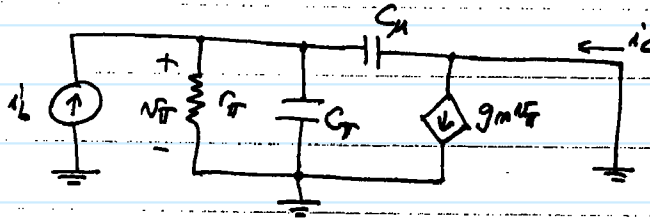Find $\beta(j\omega)$: (β as a function of freq.)



Find $\frac{i_c}{i_b} \Big|_{v_{be} \rightarrow 0}$

$$v_{\pi} = i_b \left(r_{\pi} \parallel \frac{1}{sC_{\pi}} \parallel \frac{1}{sC_{\mu}} \right)$$

$[g_m \gg sC_{\mu}]$

$$i_c = g_m v_{\pi} - sC_{\mu} v_{\pi} = (g_m - sC_{\mu}) v_{\pi} \approx g_m v_{\pi}$$

$$i_c = g_m \left(r_{\pi} \parallel \frac{1}{sC_{\pi}} \parallel \frac{1}{sC_{\mu}} \right) i_b$$


$$\frac{i_c}{i_b} = \frac{g_m}{\frac{1}{r_{\pi}} + s(C_{\pi} + C_{\mu})} = \frac{g_m r_{\pi}}{1 + s r_{\pi} (C_{\pi} + C_{\mu})} = \frac{\beta_0}{1 + s r_{\pi} (C_{\pi} + C_{\mu})}$$

$[\beta_0 = g_m r_{\pi}]$
(low freq. β)

$$\beta(j\omega) = \frac{\beta_0}{1 + \frac{j\omega}{\omega_p}}$$

$$\omega_p = \frac{1}{r_{\pi} (C_{\pi} + C_{\mu})}$$

Plot $|\beta(j\omega)|$: (Bode plot)

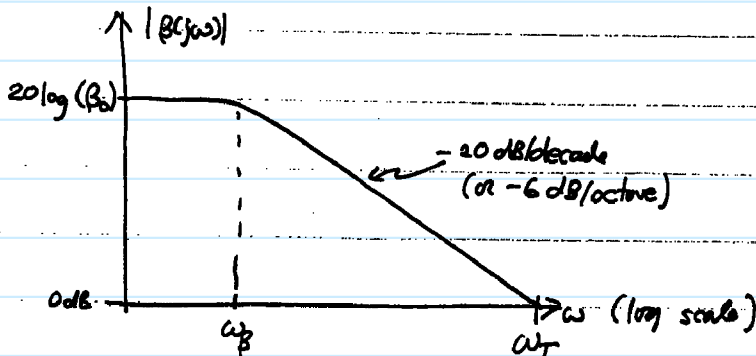

$\omega_T \triangleq$ defined as the unity radian frequency where $|\beta(j\omega)| = \beta_0$

For ω large: (eg. ω close to ω_T)

$$|\beta(j\omega)| \approx \frac{\beta_0}{\omega r_{\pi} (C_{\pi} + C_{\mu})} = 1 \rightarrow \omega_T = \frac{g_m}{C_{\pi} + C_{\mu}} \Rightarrow f_T = \frac{\omega_T}{2\pi} \text{ is a figure of merit}$$

Also, note that $\omega_T = \beta_0 \omega_p$


for the frequency performance of a transistor.

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu}$$


$f_T = 100 \text{ MHz} \rightarrow 15 \text{ GHz}$ for bipolar Xistors.

MOS Transistor

Physical Structure & Device Symbols -


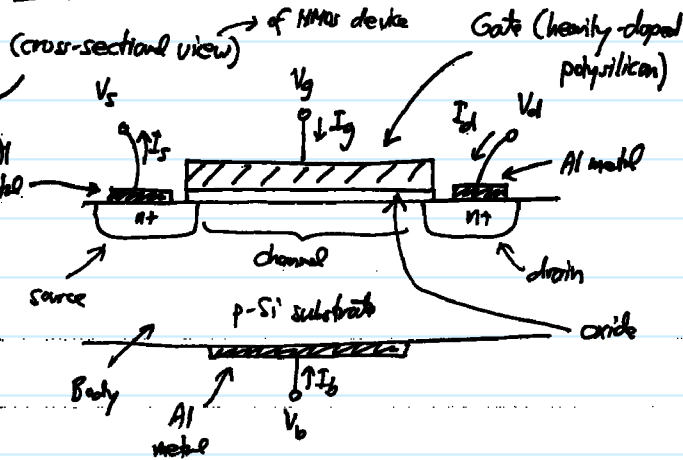


NMOS Xistor Device Symbol

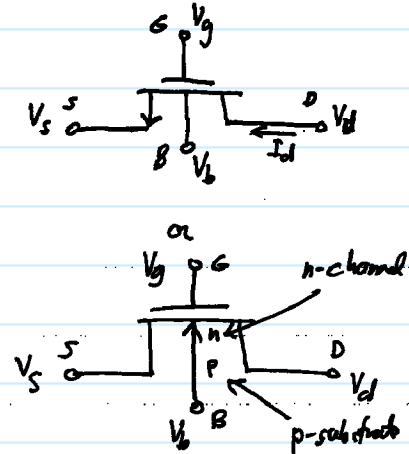


But first start w/ a perspective-view: (This also defines dimensions.)
 → use the viewgraph on next page → pg. (14a)

IV Characteristics (NMOS)

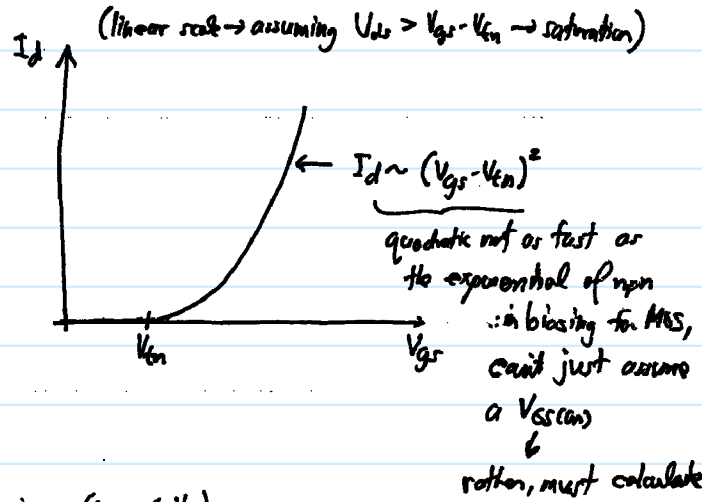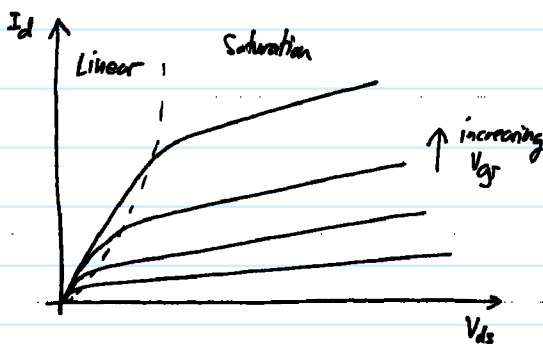

NMOS Xistor Mathematical Model

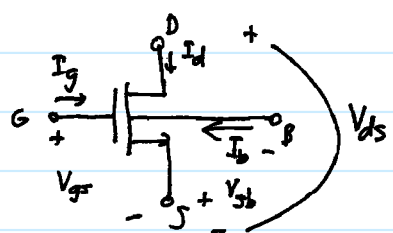


- ① Cut-Off Region: ($V_{gs} \leq V_{tn}$)
 $I_g = I_b = 0$; $I_d = 0$
- ② Linear (or Triode) Region: ($V_{gs} - V_{tn} \geq V_{ds} \geq 0$)
 $I_g = I_b = 0$; $I_d = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn} - \frac{V_{ds}}{2}) V_{ds}$
- ③ Saturation Region: ($V_{ds} \geq V_{gs} - V_{tn} \geq 0$)
 $I_g = I_b = 0$; $I_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 (1 + \lambda V_{ds})$


Body Factor $\rightarrow \gamma = \frac{1}{C_{ox}} \sqrt{2q\epsilon_s / \mu_{sub}}$ ← substrate doping conc
 permittivity in Si

General:
 $k_n = k_n' \frac{W}{L} = \mu_n C_{ox} \frac{W}{L}$
 $I_g = I_b = 0$ for all regions (at least for dc)
 $V_{tn} = f(V_{sb}) = V_{t0} + \gamma (\sqrt{|V_{sb} + \phi_{fs}|} - \sqrt{|\phi_{fs}|})$

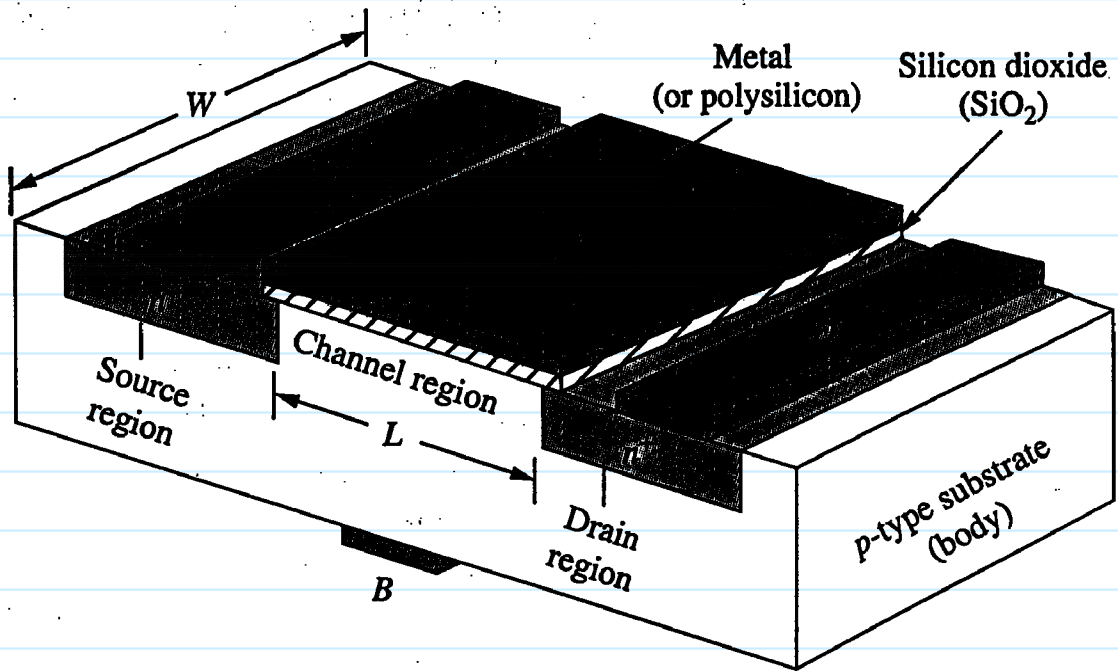
$\mu_n \triangleq$ e- mobility in the channel
 $C_{ox} \triangleq$ gate oxide capacitance per unit area



(a)

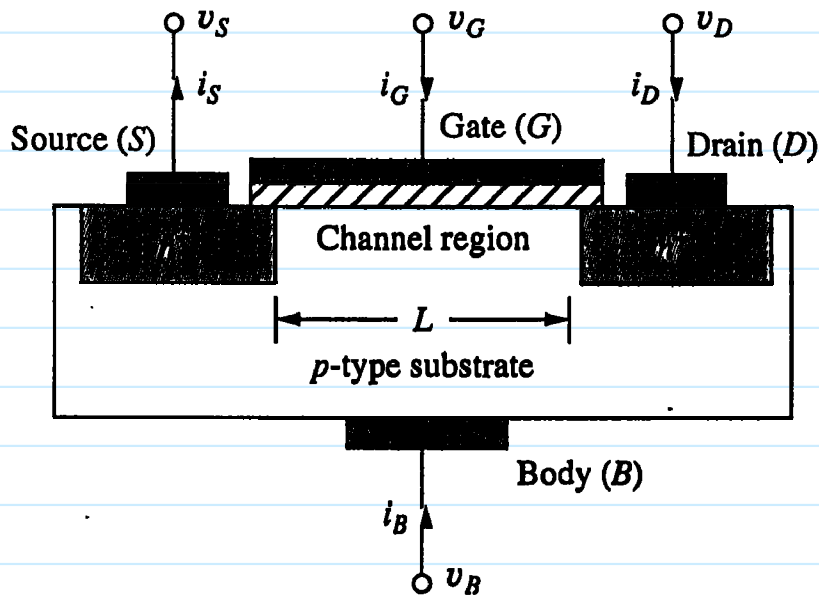


(b)

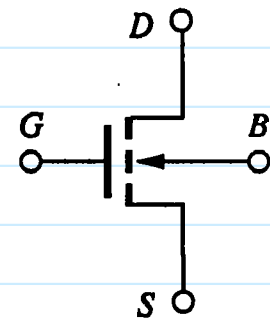

(c)

Fig. 2.1

PMOS Xiton Mathematical Model

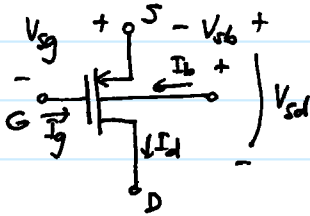

① Cut-off Region: ($V_{sg} \leq -V_{tp}$) or ($|V_{gs}| \geq |V_{tp}|$)

$$I_{sd} = 0$$

② Linear (or Triode) Region: ($V_{sg} + V_{tp} \geq V_{sd} \geq 0$; or ($|V_{gs}| - |V_{tp}| \geq |V_{ds}| \geq 0$)

$$I_{sd} = k_p (V_{sg} + V_{tp} - \frac{V_{sd}}{2}) V_{sd} = \mu_p C_{ox} \frac{W}{L} (V_{sg} + V_{tp} - \frac{V_{sd}}{2}) V_{sd}$$

$$= \mu_p C_{ox} \frac{W}{L} (|V_{gs}| - |V_{tp}| - \frac{|V_{ds}|}{2}) |V_{ds}|$$

For all regions:

$$k_p = k_p' \frac{W}{L} = \mu_p C_{ox} \frac{W}{L}$$

$$I_g = 0 \text{ and } I_b = 0 \text{ (at dc)}$$

$$V_{tp} = V_{t0} - \gamma (\sqrt{|V_{bs}| + 2\phi_f} - \sqrt{2\phi_f})$$

③ Saturation Region: ($V_{sd} \geq V_{sg} + V_{tp} \geq 0$; $|V_{ds}| \geq |V_{gs}| - |V_{tp}| \geq 0$)

$$I_{sd} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{sg} + V_{tp})^2 (1 + \lambda V_{sd}) = \frac{1}{2} k_p (V_{sg} + V_{tp})^2 (1 + \lambda V_{sd})$$

$$= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{gs}| - |V_{tp}|)^2 (1 + \lambda |V_{ds}|)$$

$\mu_p \hat{=}$ h^+ mobility in the channel

$C_{ox} \hat{=}$ gate oxide capacitance per unit area

Threshold Voltage

$$V_t = \phi_{ms} - \psi_s - \frac{Q_B}{C_{ox}} - \frac{Q_{ss}}{C_{ox}}$$

, where ϕ_{ms} = work function difference [in V] between gate material and built Si

ψ_s = surface potential in the Si @ onset of strong inversion

= $2\phi_f$ for uniformly doped substrate ($\phi_f \sim 0.3V$)

Q_{ss} = oxide charge per unit area at the oxide-Si interface [C/cm^2]

Q_B = charge stored per unit area in the depletion region (at onset of inversion)

$$\Rightarrow |Q_B| = \sqrt{2q\epsilon_s N_B (2|\phi_f| + |V_{sb}|)} \quad [C/cm^2]$$

\uparrow conc. in bulk \uparrow reverse bias

C_{ox} = gate oxide capacitance per unit area [F/cm^2]

Case: $V_{SB} = 0 \Rightarrow V_t(V_{SB} = 0) = V_{t0} = \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{B0}}{C_{ox}}$, where \downarrow

Then:

$$V_t = \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_B}{C_{ox}}$$

$$Q_{B0} = \sqrt{2q\epsilon_{si}N_B(2|\phi_f| + |V_{SB}|)}$$

$$= \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{B0}}{C_{ox}} - \frac{Q_B - Q_{B0}}{C_{ox}}$$


$\underbrace{\hspace{10em}}_{V_{t0}}$

$$V_t = V_{t0} - \gamma \left(\sqrt{2|\phi_f| + |V_{SB}|} - \sqrt{2\phi_f} \right), \quad \gamma = \frac{1}{C_{ox}} \sqrt{2q\epsilon_{si}N_B}$$

Signs in the V_t Equation:

Parameter	NMOS	PMOS
Substrate	p-type	n-type
ϕ_{ms} : metal gate	-	-
n+ Si gate	-	-
p+ Si gate	+	+
ϕ_f	-	+
Q_{B0} (or Q_B)	-	+
Q_{ss}	+	+
γ	-	+
C_{ox}	+	+

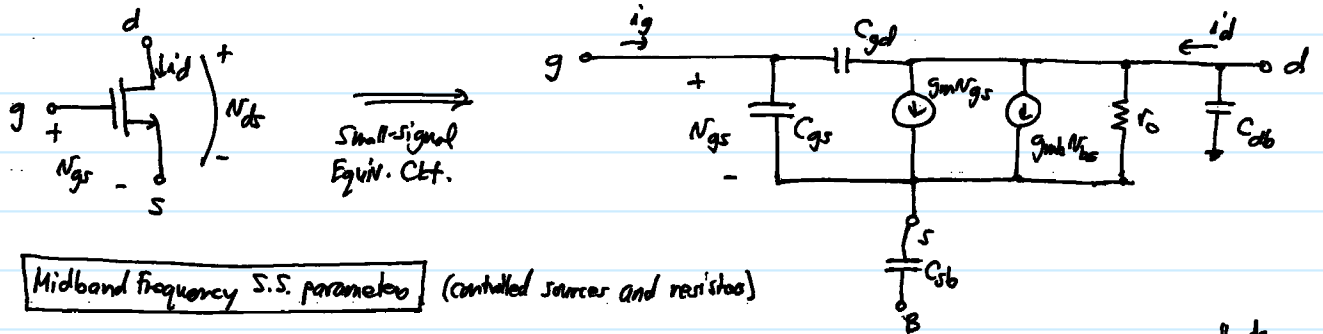MOS Small-Signal Model (for NMOS) in saturation



Midband frequency S.S. parameters (controlled sources and resistors)

Transconductance, gm:

$$g_m = \frac{i_d}{V_{gs}} = \frac{\partial I_d}{\partial V_{gs}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{gs}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 \right) \Big|_{Q_{pt}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn}) \Big|_{Q_{pt}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_{mb} = \frac{i_d}{V_{sb}} = - \frac{\partial I_d}{\partial V_{sb}} = - \left(\frac{\partial I_d}{\partial V_{tn}} \cdot \frac{\partial V_{tn}}{\partial V_{sb}} \right) \Big|_{Q_{pt}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 \rightarrow (V_{gs} - V_{tn}) = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}}$$

$$\frac{\partial V_{tn}}{\partial V_{sb}} \Big|_{Q_{pt}} = - \frac{\partial I_D}{\partial V_{gs}} \Big|_{Q_{pt}} = -g_m ; \quad \frac{\partial V_{tn}}{\partial V_{sb}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{sb}} \left[V_{t0} + \gamma \left(\sqrt{V_{sb} + 2\phi_f} - \sqrt{2\phi_f} \right) \right] \Big|_{Q_{pt}} = \frac{\gamma}{2\sqrt{V_{sb} + 2\phi_f}} \equiv \eta$$

$$g_{mb} = \eta g_m$$

Note: $V_{sb} \uparrow \rightarrow V_T \uparrow \rightarrow \eta \downarrow \rightarrow I_D \downarrow$

often neglected!

g_{mb} is minimized by maximizing η !
 V_{sb}

Output resistance, r_o : ($= \frac{1}{g_{ds}}$)

$$\Rightarrow \text{output conductance} = g_{ds} = \frac{i_d}{V_{ds}} = \frac{\partial I_d}{\partial V_{ds}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{ds}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 (1 + \lambda V_{ds}) \right) \Big|_{Q_{pt}}$$

$$= \lambda I_{Dsat} = \frac{\lambda I_D}{1 + \lambda V_{ds}} \approx \lambda I_D = g_{ds}$$

$[1 \gg \lambda V_{ds}]$

if V_{ds} is very large

$$r_o = g_{ds}^{-1} = \frac{1}{\lambda I_D} = \frac{1}{\lambda} + \frac{V_{ds}}{I_D}$$

High Frequency S.S. Parameters (capacitors)

(cross-sectional view)

C_{gs} = gate-to-source overlap capacitance

C_g = gate capacitance = $W L \epsilon_{ox} C_{ox}$

C_{gd} = gate-to-drain overlap capacitance

Sidewall High than bottom area cap.

$n+$


bulk (p)
shielded-out depletion capacitance, C_b when inversion layer present

Field-Channel Stop Implant

C_{sb} = source-bulk junction capacitance


C_{db} = drain-to-bulk junction capacitance

(layout view)

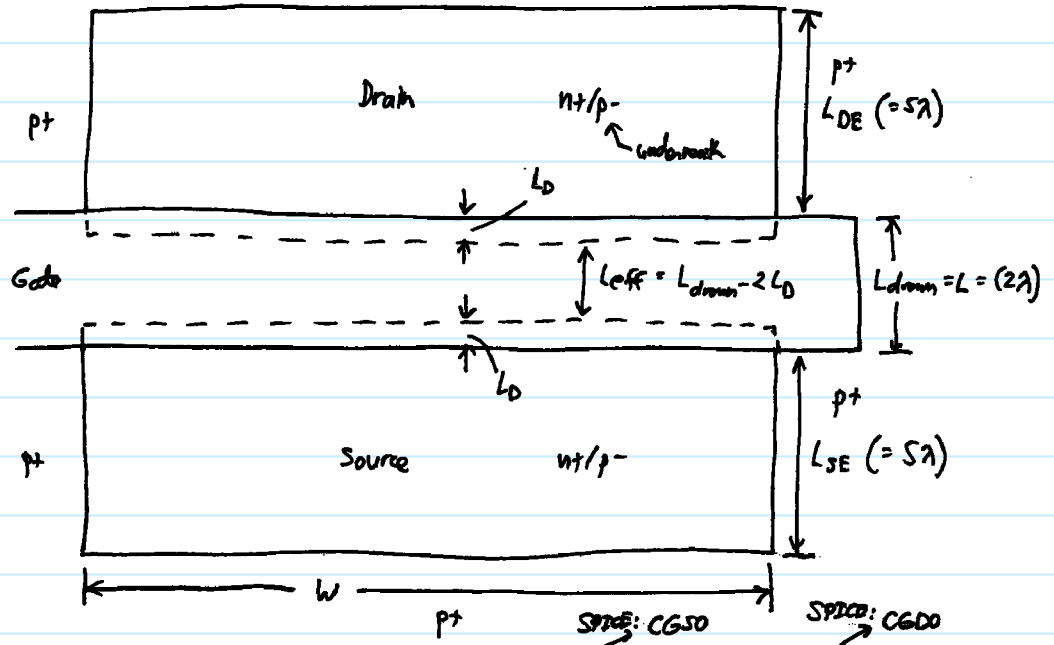

(still considering saturation region)

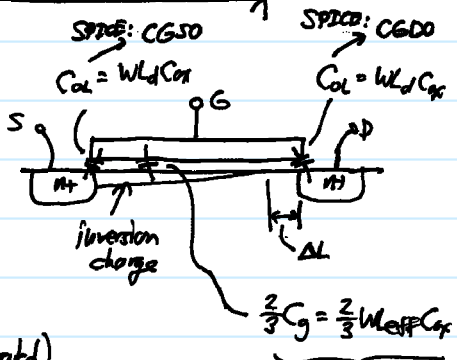In saturation, the inversion charge is not present near the drain:



Gate-to-Source Capacitor, C_{gs}:

$$C_{gs} = C_{OL} + \frac{2}{3}WLeffCox \quad (\text{inversion charge integrated})$$

Gate-to-Drain Capacitor, C_{gd}:

$$C_{gd} = C_{OL} \quad (\text{no inversion charge near the drain in saturation})$$

obtained by integrating the charge over the gate length

Source/Drain Junction Capacitance, C_{sb} & C_{db}: (must include these in SPICE simulations!)

- ⇒ there are depletion capacitors associated with the drain-to-bulk and source-to-bulk pn junctions
- ⇒ bottom-side capacitance per unit area is different from that at sidewalls due to higher doping at the sidewalls (there is higher doping in the field areas to prevent channels from forming under interconnect wires)

⇒ take drain capacitance as an example:

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DS}}{V_0}}}, \quad C_{db0} \triangleq \text{depletion capacitance with } V_{DS} = 0V$$

$$C_{j0} = \sqrt{\frac{q\epsilon_s N_A N_D}{2(N_A + N_D) V_0}} \quad \text{depl. cap. per unit area @ bottom-side w/ } V_{DS} = 0V$$

SPICE: CJ
bulk doping level

