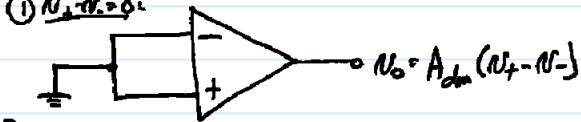


Device Mismatch Effects in Diff. Amplifiers

- ⇒ up to this point, we assumed that Q_1 & Q_2 are perfectly matched
- ⇒ in actual ckt., got device mismatches due to processing variations

The Result:

① $N_{i+} \neq 0$ → Output not zero when Input is zero → $N_{o1} \neq 0$ when $N_{id} = 0!$



Ideal Case: $N_o = 0$

Reality: $N_o \neq 0$, even w/ $(N_{i+} - N_{i-}) = 0!$

② Input $I_{B1} \neq I_{B2}$ if Q_1 & Q_2 not matched. (fn BJT & JFET only.)


To model these effects, introduce:

① Input Offset Voltage, V_{os}

② Input Offset Current, I_{os}


Typ. 1-5 mV for BJT

Typ. $I_{os} = 10$ nA for BJT

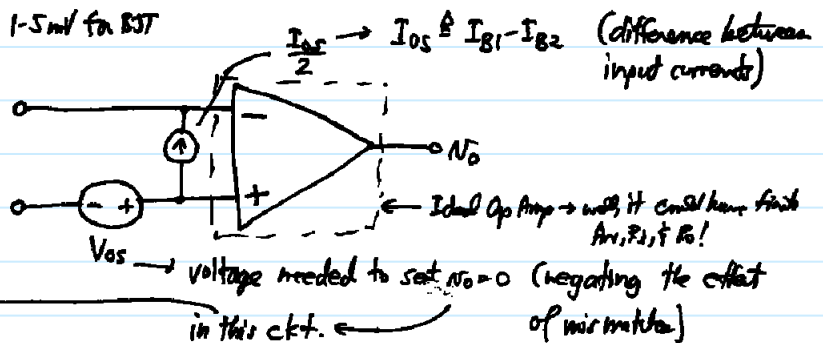

Effect of V_{os} on Op Amp Ckt. -


Example. Integrator

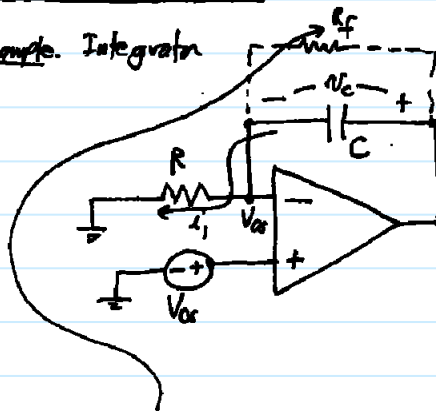

$$N_o = V_{os} + \frac{1}{C} \int_0^t i_i dt$$

$$= V_{os} + \frac{1}{C} \int_0^t \frac{V_{os}}{R} dt$$

$$= V_{os} \left(1 + \frac{t}{RC}\right) + N_o|_{t=0}$$

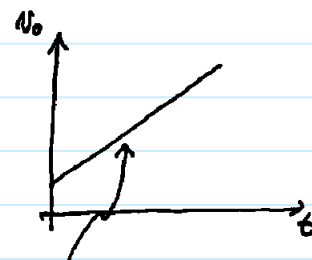

Fix: Place an R_f in shunt w/ the C

→ then $N_o = V_{os} \left(1 + \frac{R_f}{R}\right)$, and railing doesn't happen

→ but, usually R_f is large to allow the C to dominate


the integrator Xfer function ∴ $N_o = V_{os} \left(1 + \frac{R_f}{R}\right)$ can be quite large → still want $V_{os} = \text{small}$

will continue to increase until op amp hits the voltage rails

V_{os} is even more important in setting the resolution of AD converters and other precision ckt.

V_{OS} of a Mismatched SCP

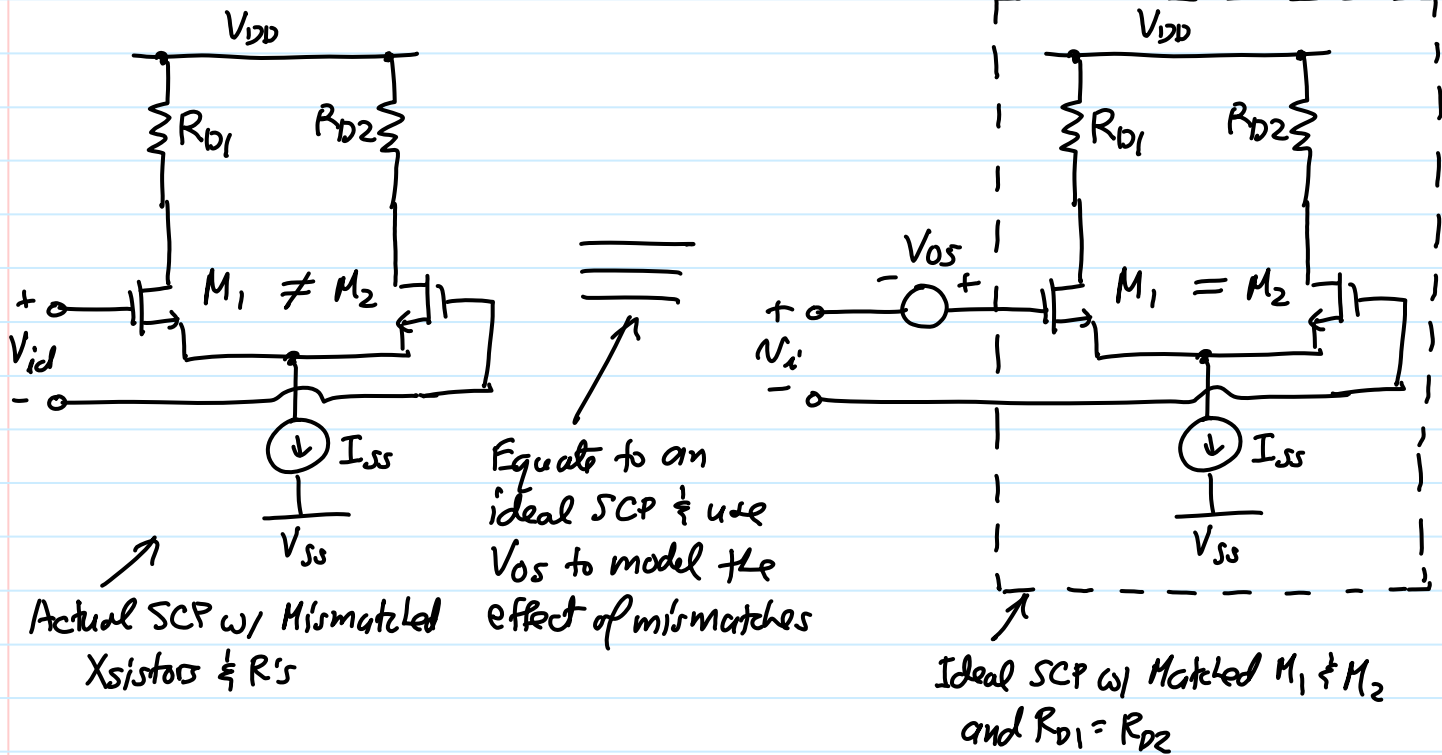Objective: Derive an expression for V_{OS}.



Input offset voltage V_{OS} arises due to variations in:

- ① Xsistors, M₁ & M₂ → $\frac{W}{L}$ and V_t vary
- ② R_{D1} ≠ R_{D2} → causes gain variation

Definition. V_{OS} = V_{id} to get V_{od} = 0 in this ckt.

KVL: V_{OS} - V_{GS1} + V_{GS2} = 0

$$\therefore V_{OS} = V_{GS1} - V_{GS2} = V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

→ $\Delta I_D = I_{D1} - I_{D2}$	$\Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$	$\Delta V_t = V_{t1} - V_{t2}$	$\Delta R_D = R_{D1} - R_{D2}$
→ $I_D = \frac{I_{D1} + I_{D2}}{2}$	$\left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$	$V_t = \frac{V_{t1} + V_{t2}}{2}$	$R_D = \frac{R_{D1} + R_{D2}}{2}$

Rearranging:

$$I_{D1} = I_D + \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} \quad V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} \quad V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Substituting into (1):

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \frac{\Delta I_D}{2})}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right)_1 + \frac{1}{2} \Delta\left(\frac{W}{L}\right) \right]}} - \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right)_2 - \frac{1}{2} \Delta\left(\frac{W}{L}\right) \right]}}$$

$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right]$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \sqrt{\frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}}} - \sqrt{\frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}}} \right\}$$

Binomial Theorem:

$$(1 + nx)^m \xrightarrow{n = \text{small}} 1 + mnx$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{OS} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2} \rightarrow$ mismatch in I_D must be opposite

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ -\frac{\Delta R}{R} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

$$\frac{\Delta I_D}{I_D} = -\frac{\Delta R_D}{R_D}$$

Threshold Mismatch


Geometric (i.e., Layout) Variation

bias independent

scale w/ overdrive


V_{OS} in a Mismatched ECP

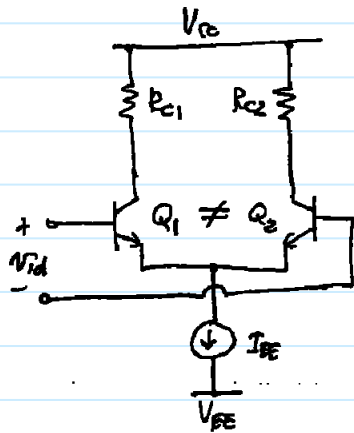Objective: Derive an expression for V_{OS} .



Actual ECP w/ Mismatched Q_1 & Q_2 & R 's

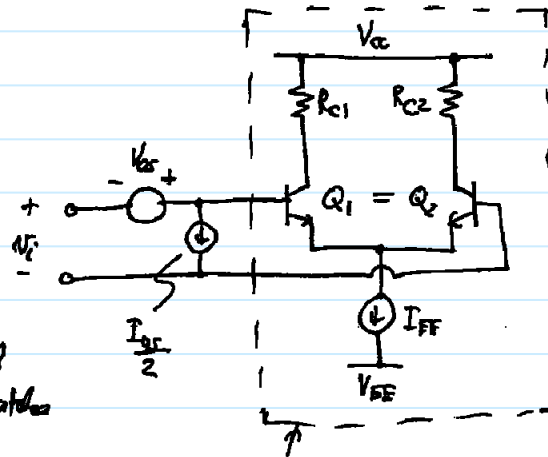Equivalent to an ideal ECP + use V_{OS} & I_{IE} to model the effect of mismatches



Ideal ECP w/ Matched Q_1 & Q_2 and $R_{c1} = R_{c2}$

Input Offset Voltage V_{OS} arises due to variations in:


① $Q_1 \neq Q_2$ → I_S & β vary: $I_S = \frac{q N_A^2 D_n A}{N_A W_B (V_{CB})}$

$I_{S1} \neq I_{S2}$ can be caused by:
 (i) $A_1 \neq A_2$ (etching tolerance limits)
 (ii) $N_{A1} \neq N_{A2}$ (doping variations of base)
 (iii) $W_B = f(V_{CB})$ (width variations exacerbated by V_{CB} diff.)

② $R_{c1} \neq R_{c2}$ → causes gain variation

Definition: $V_{OS} = V_{id}$ to get $V_{od} = 0$, which occurs when:

KVL: $V_{OS} - V_{be1} + V_{be2} = 0$

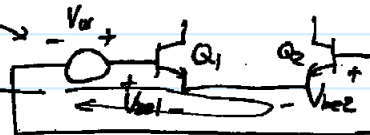

$$V_{OS} = V_{be1} - V_{be2} = V_T \ln \frac{I_{c1}}{I_{s1}} - V_T \ln \frac{I_{c2}}{I_{s2}} = V_T \ln \left(\frac{I_{c1}}{I_{c2}} \frac{I_{s2}}{I_{s1}} \right)$$

find $\frac{I_{c1}}{I_{c2}}$ in terms of design elements:

[When $V_{id} = V_{OS} \rightarrow V_{od} = 0V$] → $V_{od} = (V_{CC} - I_{c1}R_{c1}) - (V_{CC} - I_{c2}R_{c2}) = 0$

$$I_{c1}R_{c1} = I_{c2}R_{c2} \rightarrow \frac{I_{c1}}{I_{c2}} = \frac{R_{c2}}{R_{c1}}$$

$$V_{OS} = V_T \ln \left(\frac{R_{c2}}{R_{c1}} \frac{I_{s2}}{I_{s1}} \right)$$

This is an exact equation for V_{OS} . It's often more useful & intuitive to express this in terms of percent variations (and eventually standard deviations).

Convert to Percent Variation Form -

$$\text{Define: } \left. \begin{aligned} R_c &= \frac{R_{c1} + R_{c2}}{2}, \Delta R_c = R_{c1} - R_{c2} \\ I_s &= \frac{I_{s1} + I_{s2}}{2}, \Delta I_s = I_{s1} - I_{s2} \end{aligned} \right\} \text{Objective: Express Var in terms of percent variations } \frac{\Delta R_c}{R_c} \text{ \& } \frac{\Delta I_s}{I_s}.$$

$$\downarrow$$

In general: $\left. \begin{aligned} \Delta X: X_1 - X_2 \\ X = \frac{X_1 + X_2}{2} \end{aligned} \right\} \begin{aligned} X_1 &= X + \frac{\Delta X}{2} \\ X_2 &= X - \frac{\Delta X}{2} \end{aligned} \Rightarrow \text{Thus: } \begin{aligned} R_{c1} &= R_c + \frac{\Delta R_c}{2}, R_{c2} = R_c - \frac{\Delta R_c}{2} \\ I_{s1} &= I_s + \frac{\Delta I_s}{2}, I_{s2} = I_s - \frac{\Delta I_s}{2} \end{aligned}$

With these formulations:

$$V_{OS} = V_T \ln \left[\frac{R_{c2}}{R_{c1}} \frac{I_{s2}}{I_{s1}} \right] = V_T \ln \left\{ \frac{R_c - \frac{\Delta R_c}{2}}{R_c + \frac{\Delta R_c}{2}} \frac{I_s - \frac{\Delta I_s}{2}}{I_s + \frac{\Delta I_s}{2}} \right\} = V_T \ln \left\{ \frac{1 - \frac{\Delta R_c}{2R_c}}{1 + \frac{\Delta R_c}{2R_c}} \frac{1 - \frac{\Delta I_s}{2I_s}}{1 + \frac{\Delta I_s}{2I_s}} \right\}$$

$$\left[\ln(1+x) \approx x - \frac{x^2}{2} + \frac{x^3}{3} - \dots \right] \rightarrow V_{OS} \approx V_T \left[-\frac{\Delta R_c}{2R_c} - \frac{\Delta R_c}{2R_c} - \frac{\Delta I_s}{2I_s} - \frac{\Delta I_s}{2I_s} \right]$$

taking the first term assuming $\Delta R_c \ll R_c$ & $\Delta I_s \ll I_s$

$$V_{OS} = V_T \left[-\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s} \right]$$


Since $\frac{\Delta R_c}{R_c}$ and $\frac{\Delta I_s}{I_s}$ are statistically ^{varying} parameters for a given process run & layout, one usually expresses terms in the form of variances when specifying V_{OS} :

→ since $\frac{\Delta R_c}{R_c}$ & $\frac{\Delta I_s}{I_s}$ are uncorrelated, their variances add like powers:

$$\sigma_{Var} = V_T \sqrt{\sigma_{\Delta R_c/R_c}^2 + \sigma_{\Delta I_s/I_s}^2}$$

Ex: Typ. $\sigma_{\Delta R_c/R_c} \sim 0.01$, $\sigma_{\Delta I_s/I_s} \sim 0.05$
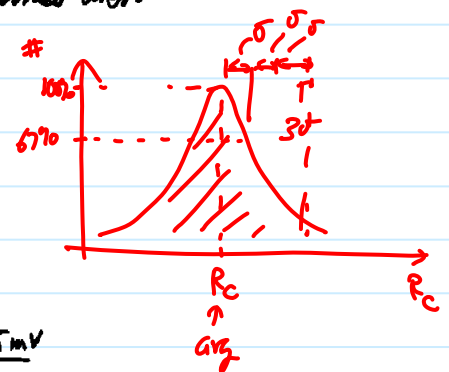
$$\therefore \sigma_{V_{OS}} = (26m) \sqrt{(0.01)^2 + (0.05)^2} = 1.3mV \quad \text{Typ. Var for BJT} \sim 1-5mV$$



V_{OS} Drift w/ Temperature

$$\frac{dV_{OS}}{dT} = \frac{kT}{q} \left\{ \underbrace{-\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s}}_{\text{indep. of } T} \right\} \frac{1}{T} = \frac{Var}{T} \quad \text{Ex: } \frac{dV_{OS}}{dT} = \frac{1.3m}{300K} = 4.3 \mu V/K \text{ around } T = 300K.$$

drift

I_{OS} in a Mismatched ECP

By Definition: $I_{OS} = I_{B1} - I_{B2} = \frac{I_{C1}}{\beta_1} - \frac{I_{C2}}{\beta_2} = I_{OS}$

To express in percent variations:

$$\begin{cases} I_{C1} = I_C + \frac{\Delta I_C}{2} \\ I_{C2} = I_C - \frac{\Delta I_C}{2} \end{cases} \quad \begin{cases} \beta_1 = \beta + \frac{\Delta \beta}{2} \\ \beta_2 = \beta - \frac{\Delta \beta}{2} \end{cases}$$

$$\therefore I_{OS} = \frac{I_C + \frac{\Delta I_C}{2}}{\beta + \frac{\Delta \beta}{2}} - \frac{I_C - \frac{\Delta I_C}{2}}{\beta - \frac{\Delta \beta}{2}} = \frac{I_C}{\beta} \left\{ \frac{1 + \frac{\Delta I_C}{2I_C}}{1 + \frac{\Delta \beta}{2\beta}} - \frac{1 - \frac{\Delta I_C}{2I_C}}{1 - \frac{\Delta \beta}{2\beta}} \right\}$$

$$\left[\frac{1}{1+x} \approx 1 - x + x^2 - \dots \right] \rightarrow = \frac{I_C}{\beta} \left\{ \left(1 + \frac{\Delta I_C}{2I_C}\right) \left(1 - \frac{\Delta \beta}{2\beta}\right) - \left(1 - \frac{\Delta I_C}{2I_C}\right) \left(1 + \frac{\Delta \beta}{2\beta}\right) \right\}$$

$$= \frac{I_C}{\beta} \left\{ 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} - \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} - 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} + \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} \right\}$$

$$I_{OS} = \frac{I_C}{\beta} \left\{ \frac{\Delta I_C}{I_C} - \frac{\Delta \beta}{\beta} \right\}$$


But for $V_{od} = 0V \rightarrow \frac{I_{C1}}{I_{C2}} = \frac{R_{C2}}{R_{C1}} \rightarrow \frac{\Delta I_C}{I_C} = - \frac{\Delta R_C}{R_C}$

$$\therefore I_{OS} = - \frac{I_C}{\beta} \left(\frac{\Delta R_C}{R_C} + \frac{\Delta \beta}{\beta} \right)$$

Ex. Typ: $\sigma_{\Delta \beta/\beta} = 0.1$, $\sigma_{\Delta R_C/R_C} = 0.01$

$$\rightarrow I_{OS} = - \frac{I_C}{\beta} \left[\sigma_{\Delta R_C/R_C}^2 + \sigma_{\Delta \beta/\beta}^2 \right]^{1/2} \approx -0.1 \frac{I_C}{\beta} \approx \textcircled{-0.1 I_B = I_{OS}}$$

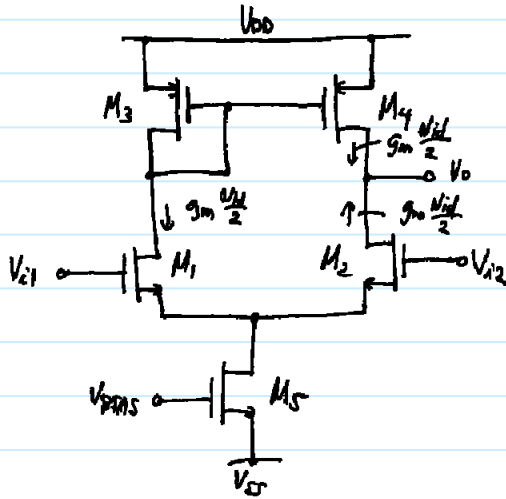MOS Differential Stage w/ Current Mirror Load



Small-Signal Gain: (similar to BJT)

$$\frac{V_o}{V_{id}} = g_{m2}(r_{o2} \parallel r_{o4}) = \frac{g_{m2}}{g_{m2} + g_{m4}} = \frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}}{\lambda_2 I_{D2} + \lambda_4 I_{D4}}$$

$$= \frac{\sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{SS}}}{\frac{I_{SS}}{2} (\lambda_2 + \lambda_4)} \Rightarrow \frac{V_o}{V_{id}} = \frac{2}{\lambda_2 + \lambda_4} \sqrt{\frac{\mu_n C_{ox} (W/L)_2}{I_{SS}}}$$

→ all the same PS effects, etc...

$$\left[\frac{\Delta(W/L)_{1,2}}{(W/L)_{1,2}} - \frac{\Delta(W/L)_{3,4}}{(W/L)_{3,4}} \right]$$

Offset Voltage - $V_{OS} = V_{GS1} - V_{GS2}$ when $V_{od} = 0V$

$$V_{OS} = \Delta V_{t1,2} + \Delta V_{E3,4} \left(\frac{g_{m3,4}}{g_{m1,2}} \right) + \frac{(V_{GS} - V_t)_{1,2}}{2} \left[\frac{\Delta k_{1,2}}{k_{1,2}} + \frac{\Delta k_{3,4}}{k_{3,4}} \right]$$

Via similar derivation to what we just did

For small V_{OS} : ① small $(V_{GS} - V_t)$

$$\text{② } g_{m3,4} < g_{m1,2} \rightarrow k_{3,4} < k_{1,2} \quad \frac{1}{2} \left(\frac{W}{L} \right)_{3,4} < \left(\frac{W}{L} \right)_{1,2}$$