

# EE 140/240A Linear Integrated Circuits

## Fall 2019

## Homework 3

### 1. Model Mania


- (a) For a quadratic model MOSFET, sketch the following curves. No units needed, but try to get the shape right with any significant points labeled, and label with something like “goes as sqrt(X)” or “linear in X”. Assume  $\lambda = 0$ .

**Solution:** We'll start with

$$I_D = \frac{1}{2} \mu C_{ox} (V_{GS} - V_t)^2$$

- i.  $g_m$  vs.  $V_{GS}$  with constant  $W/L$

**Solution:**

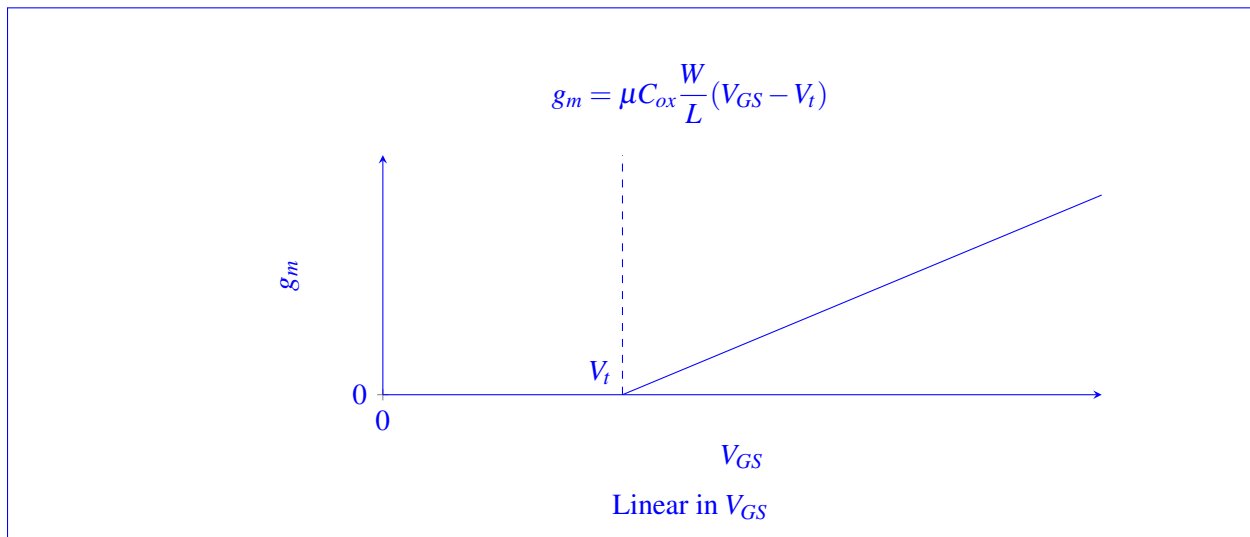


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

- ii.  $g_m$  vs.  $V_{GS}$  with constant  $I_D$

**Solution:**

$$g_m = \frac{2I_D}{V_{GS} - V_t}$$

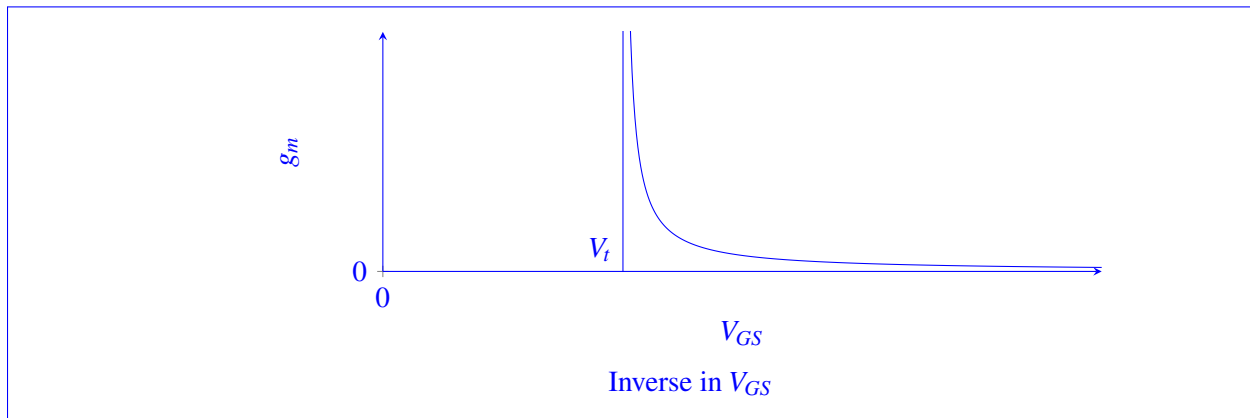


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

iii.  $g_m$  vs.  $I_D$  with constant  $W/L$

**Solution:**

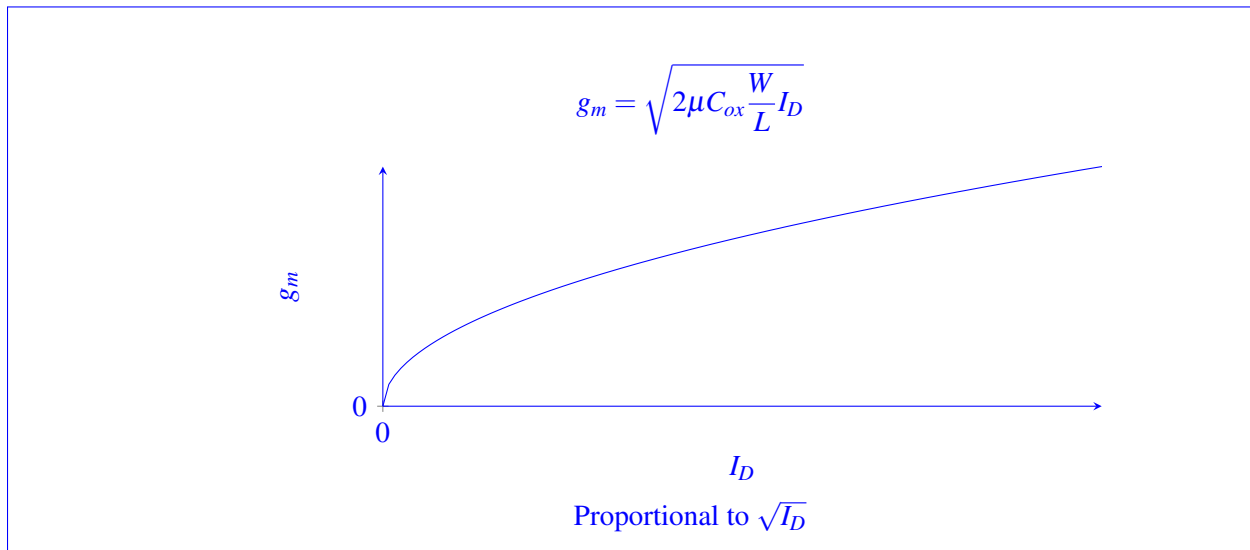


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

iv.  $g_m$  vs.  $I_D$  with constant  $V_{GS}$

**Solution:**

$$g_m = \frac{2I_D}{V_{GS} - V_t}$$

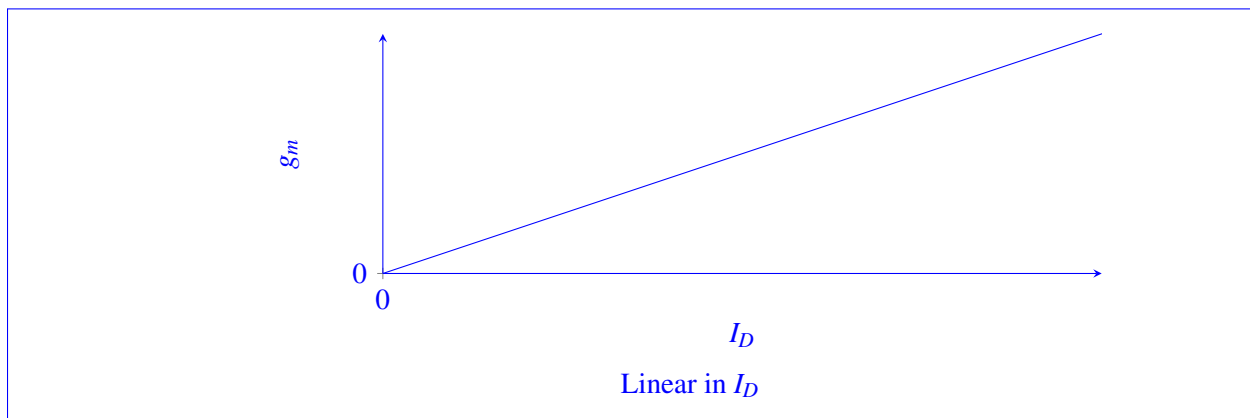


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

v.  $g_m$  vs.  $W/L$  with constant  $I_D$

**Solution:**

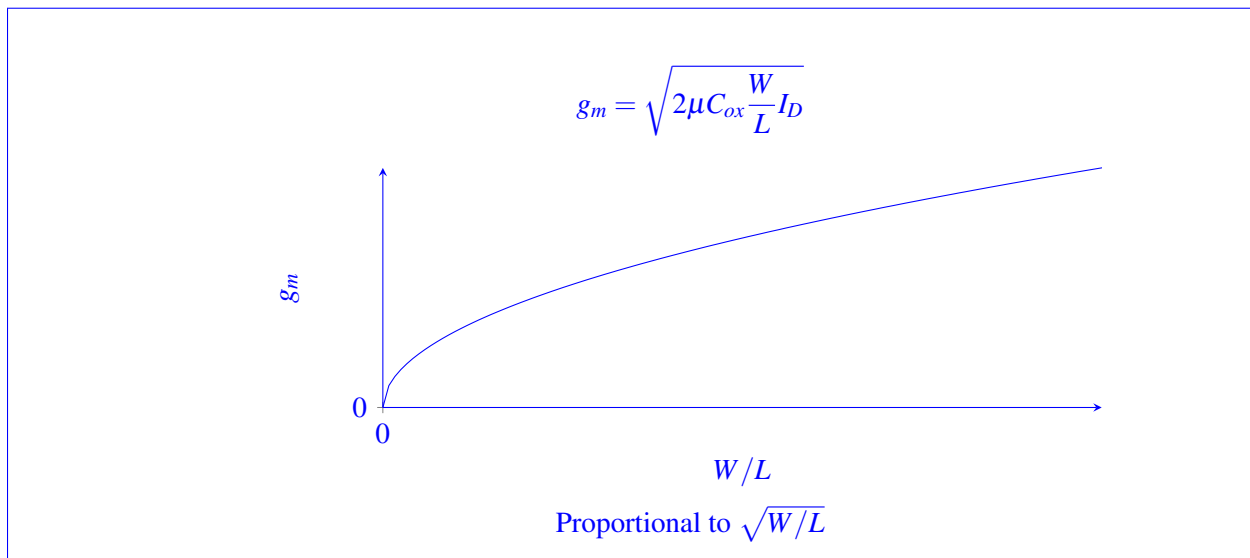


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

vi.  $g_m$  vs.  $W/L$  with constant  $V_{GS}$

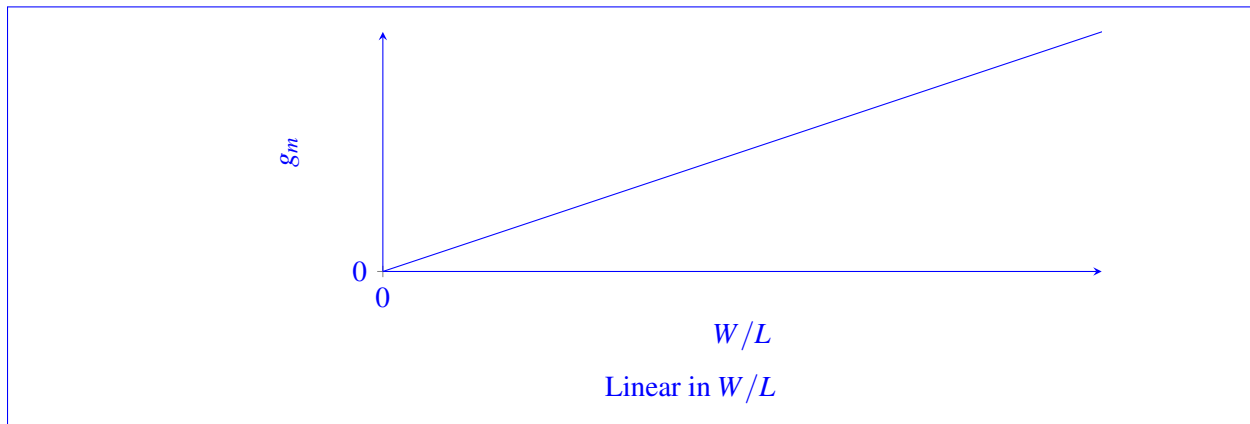**Solution:**

$$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)$$



**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Reasonable sketch

(b) **(EE240A)** Repeat questions (a)i., (a)ii., (a)iv., and (a)vi. for subthreshold. You do not need to sketch the plot. You may assume  $I_S$  is a constant in all but  $\frac{W}{L}$ . Do not assume  $n$  is necessarily a constant.

**Solution:** The equation we'll start with is

$$I_D = I_S e^{\frac{V_{GS}}{n} \cdot \frac{q}{k_B T}}$$

where  $\frac{W}{L}$  is contained within  $I_S$  (linear relationship). Finding  $g_m$ :

$$\begin{aligned} g_m &= \frac{\partial i_d}{\partial v_{gs}} \\ &= I_S e^{\frac{V_{GS}}{n} \cdot \frac{q}{k_B T}} \frac{q}{nk_B T} \\ &= I_D \cdot \frac{q}{nk_B T} \\ &= I_D \cdot \frac{\ln\left(\frac{I_D}{I_S}\right)}{V_{GS}} \end{aligned}$$

i.  $g_m$  vs.  $V_{GS}$  with constant  $W/L$

$$g_m = I_S e^{\frac{V_{GS}}{n} \cdot \frac{q}{k_B T}} \frac{q}{nk_B T}$$

Exponentially increasing in  $V_{GS}$

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

ii.  $g_m$  vs.  $V_{GS}$  with constant  $I_D$

$$g_m = I_D \cdot \frac{\ln\left(\frac{I_D}{I_S}\right)}{V_{GS}}$$

Inversely proportional to  $V_{GS}$ . Note that we want this form for  $g_m$  because none of the other elements depend on  $V_{GS}$ .

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

iii.  $g_m$  vs.  $I_D$  with constant  $V_{GS}$

$$g_m = I_D \cdot \frac{\ln\left(\frac{I_D}{I_S}\right)}{V_{GS}}$$

This is not a clean relationship.

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

iv.  $g_m$  vs.  $W/L$  with constant  $V_{GS}$

$$g_m = I_S e^{\frac{V_{GS}}{n} \cdot \frac{q}{k_B T}} \frac{q}{nk_B T}$$

Roughly linear in  $W/L$ , since it's contained within  $I_S$

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

(c) **(EE240A)** Repeat part (a), but for the linear region of operation. You do not need to plot for this subpart.

**Solution:**

$$\begin{aligned} g_m &= \frac{di_d}{dv_{gs}} \\ &= \mu C_{ox} \frac{W}{L} \\ &= \frac{I_D}{V_{GS} - V_t - \frac{1}{2}V_{DS}} \end{aligned}$$

i.  $g_m$  vs.  $V_{GS}$  with constant  $W/L$

$$g_m = \mu C_{ox} \frac{W}{L}$$

Constant! How fascinating; this means if for some reason you're in the linear region of operation, changing  $V_{GS}$  isn't going to significantly help your  $g_m$ .

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

ii.  $g_m$  vs.  $V_{GS}$  with constant  $I_D$

$$g_m = \frac{I_D}{V_{GS} - V_t - \frac{1}{2}V_{DS}}$$

Approximately inversely proportional.

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

iii.  $g_m$  vs.  $I_D$  with constant  $W/L$

$$g_m = \mu C_{ox} \frac{W}{L}$$

Constant. The takeaway here is that if you want  $g_m$  and you're in the linear region of operation, your devices will likely have to get larger.

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

iv.  $g_m$  vs.  $I_D$  with constant  $V_{GS}$

$$g_m = \frac{I_D}{V_{GS} - V_t - \frac{1}{2}V_{DS}}$$

Roughly linear

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

v.  $g_m$  vs.  $W/L$  with constant  $I_D$

$$g_m = \mu C_{ox} \frac{W}{L}$$

Linear

**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

vi.  $g_m$  vs.  $W/L$  with constant  $V_{GS}$

$$g_m = \mu C_{ox} \frac{W}{L}$$

Linear again!


**Rubric:** (3 Points)

- +1: Identifying equation
- +2: Correct relationship

## 2. Resistive Load CS Amp Biasing

A common source FET amplifier has a resistive load and  $\lambda = \frac{1}{50V}$ . The output is biased at 5V, the transistor is in saturation, and the resistive load has the same impedance as the output resistance of the transistor. What is the supply voltage?

**Solution:**

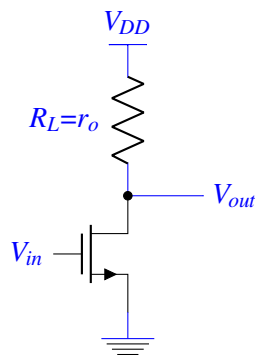

Given  $R_L = r_o$ :

$$\begin{aligned} V_{DD} &= V_{OUT} + I_D R_L \\ &= V_{OUT} + I_D r_o \\ &= V_{OUT} + I_D \frac{1}{\lambda I_D} \\ &= V_{OUT} + \frac{1}{\lambda} \\ &= 5V + 50V \\ &= 55V \end{aligned}$$

$$V_{DD} = 55V$$


**Rubric: (5 Points)**

- +1: Correct choice of circuit topology
- +2:  $V_{DD}$  Equation
- +2: Correct value of  $V_{DD}$
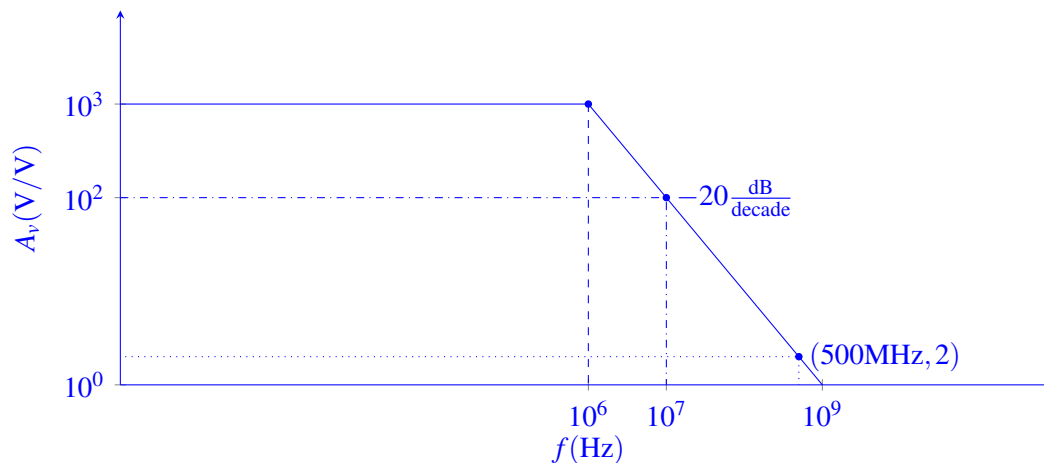
### 3. Single-Pole Amplifier

A single-pole amplifier has a low frequency gain of 1000, and a gain of 2 at 500MHz. What are the pole frequency and unity gain frequency in Hz? What is the gain at 10MHz?

**Solution:** It helps to draw this one out:



Given that this is a single-pole amplifier and the gain at 500MHz = 2, we know the unity gain frequency is roughly a third of a decade higher than 500MHz, i.e. a factor of 2, so

$$f_u = 2 \times 500\text{MHz} = 1.0\text{GHz}$$

Since gain  $\times$  bandwidth is a constant for the single-pole system,

$$\begin{aligned} f_u &= A_{v0} \times f_p \\ f_p &= \frac{f_u}{A_{v0}} \\ &= \frac{1\text{GHz}}{1000} \\ &= 1\text{MHz} \end{aligned}$$

And now we want the gain at 10MHz, i.e. one decade above the pole frequency

$$A_v(10\text{MHz}) = \frac{1000}{10} = 100\text{V/V}$$



$$f_u = 1.0\text{GHz}$$

$$f_p = 1\text{MHz}$$

$$A_V(10\text{MHz}) = 100\text{V/V}$$

**Rubric: (5 Points)**

- +1: Correct unity gain frequency equation
- +1: Correct unity gain frequency with correct units
- +1: Correct pole frequency with correct units
- +2: Correct gain with correct units

**4. Settling Time**

Write down a table of settling error vs. time for  $\frac{t}{\tau} = \{1, 3, 5, 7\}$ . Use a calculator for this one. Memorize the table to one significant digit.

**Solution:**

$t/\tau$	$v(t) = v_0(1 - e^{-t/\tau})$	% Error
1	0.632	36.8%
3	0.950	5.0%
5	0.993	0.7%
7	0.9991	0.09%


**Rubric: (4 Points)**

- +1: Correct error value ( $\times 4$ )

**5. RC Low-Pass Filter Transient**

An RC low pass filter with a time constant of  $1\mu\text{s}$  is driven with a  $0 - 1\text{V}$  square wave. Sketch the first full cycle of the input and output when the square wave is first turned on, and the frequency of the square wave is


(a)  $1\text{kHz}$

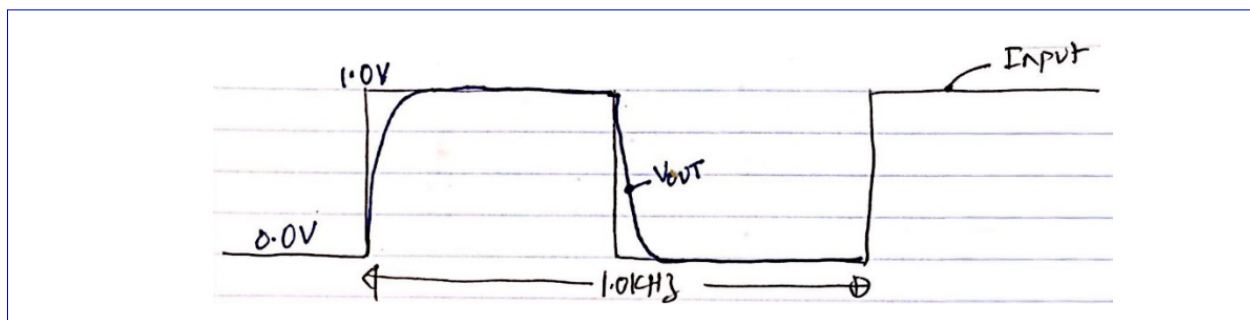**Solution:****Rubric: (3 Points)**

- +3: Correct waveform

(b) 1MHz

**Solution:**

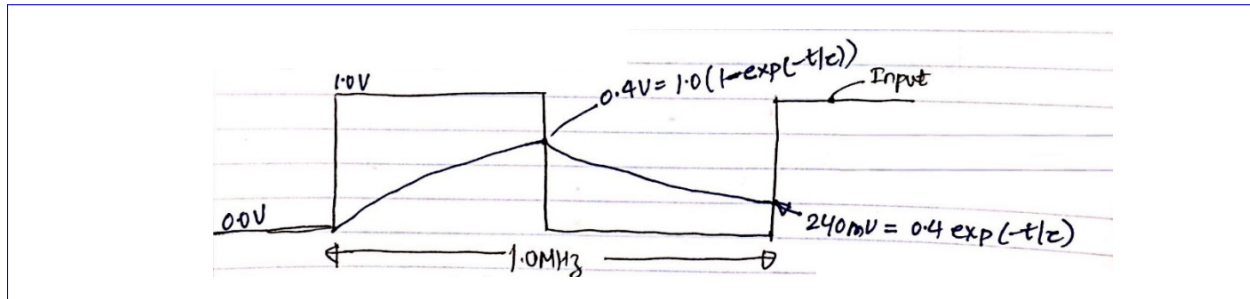


**Rubric:** (5 Points)

- +2: Correct waveform
- +3: Correct values of magnitude

(c) 1GHz

**Solution:**

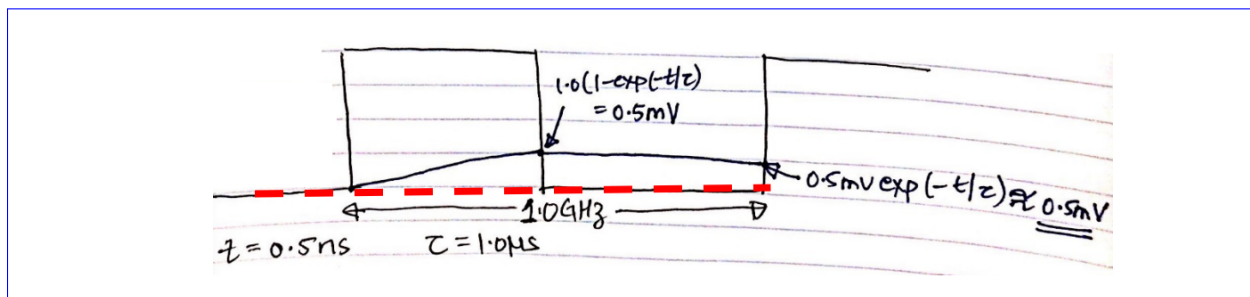

**Rubric:** (2 Points)

- +2: Correct waveform. The plot doesn't have to be to scale.

## 6. Relationships for Your Cheat Sheet

Fill in the following table for a single-transistor common-source amplifier:

$A_{v0}$ (V/V)	$\omega_p$ (rad/s)	$\omega_u$ (rad/s)	$g_m$ (1/ $\Omega$ )	$r_o$ ( $\Omega$ )	$C_L$ (F)
1000	1M				1p
	1M	0.1G		100k	
		10G		1M	20f
	10	10M			10p

**Solution:** The often-used equations of interest (that are useful for your cheat sheet):

$$A_{v0} = |g_m r_o|$$

$$\omega_p = \frac{1}{r_o C_L}$$

$$\omega_u = A_{v0} \omega_p = \frac{g_m}{C_L}$$

$A_{v0}$ (V/V)	$\omega_p$ (rad/s)	$\omega_u$ (rad/s)	$g_m$ (1/ $\Omega$ )	$r_o$ ( $\Omega$ )	$C_L$ (F)
1000	1M	<b>1G</b>	<b>1m</b>	<b>1M</b>	1p
<b>100</b>	1M	0.1G	<b>1m</b>	100k	<b>10p</b>
<b>200</b>	<b>50M</b>	10G	<b>0.2m</b>	1M	20f
<b>1M</b>	10	10M	<b>0.1m</b>	<b>10G</b>	10p

**Rubric:** (12 Points)

- +1: Each correct value ( $\times 12$ )