

EE 140/240A Linear Integrated Circuits

Fall 2019

Homework 4

This homework is due September 25, 2019, at 23:00.

Submission Format

Your homework submission should consist of **one** file.

- `hw4.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

Submit each file to its respective assignment on bCourses.

1. Single-Pole Amplifier (Spring 2015 Midterm 1 Q1)

Fill in the following table where each row is a different single-pole amplifier.

G_m (S)	R_o (Ω)	C_L (F)	$ A_{v0} $ (V/V)	ω_p (rad/s)	ω_u (rad/s)
10m			10		100G
1 μ	1M	10f			
		1p	100	10M	

2. New Transistor, Who Dis (Spring 2015 Midterm 1 Q3b)

You invent a new transistor and find the output current is given by

$$I_{xy} = KV_{zy}^3 V_{xy}^{\frac{1}{2}}$$


$$I_z = 0$$

- What are the formulas for transconductance and output resistance?
- What is the intrinsic gain when the device is biased at $V_{zy} = V_{xy} = 1V$? Give a numerical answer.

 3. (Spring 2015 Midterm 1 Q4)

You have biased the amplifier below with a particular input overdrive voltage V_{ov} . Both devices are in saturation, and the quadratic model is appropriate.

The low frequency gain is $-1000 \frac{V}{V}$. $C_{gs1} = 1pF, C_{gd1} = 0.1pF$.



- (a) What is the input capacitance? Give an exact numerical answer.
- (b) You adjust the bias voltages so that the input overdrive V_{ov1} **increases by a factor of two**. What happens to the current, small signal parameters, low frequency gain, output pole frequency, output unity gain frequency, and input capacitance? Answers should be in the form “increase $5\times$ ”, “decrease $10\times$ ”, “stay the same”, etc.

I_D	
g_m	
r_o	
$ A_{v0} $	
ω_p	
ω_u	
C_{in}	

4. RC Low-Pass Filters

An RC low pass filter has a time constant of $1\mu\text{s}$.

- (a) With an input of $1\text{V} \cdot \sin(10^7 \frac{\text{rad}}{\text{s}} \cdot t)$, draw one cycle of the input and the steady state output. Label the amplitude and phase of the output.
- (b) Draw the response to a unit step voltage on a time scale of 1ms , $1\mu\text{s}$, and 1ns .


5. (Spring 2016 Midterm 1 Q6)

The four transistors shown below are all biased at a current of $1\mu\text{A}$ at room temperature.

The NMOS device M1 is in sub-threshold, with $V_{GS} - V_t = -200\text{mV}$ and $n = 1.5$.

The NMOS device M2 is velocity saturated with $V_{GS} - V_t = 100\text{mV}$.

 
The NMOS device M3 is in saturation, with a channel field of approximately $0.1\text{V}/\mu\text{m}$ and $V_{GS} - V_t = 100\text{mV}$.



- Approximately what change in V_{BE} will cause the collector current to increase by a factor of 10?
- Approximately what change in V_{GS1} will cause the drain current in M1 to increase by a factor of 10?
- Approximately what change in V_{GS2} will cause the drain current in M2 to increase by a factor of 10?
- Approximately what change in V_{GS3} will cause the drain current in M3 to increase by a factor of 10?

6. (Fall 2009 Midterm 1 Q1)

For the following problems, the drain, gate, and source voltages are given. You may assume $V_{SB} = 0V$ and that $V_{tn} = -V_{tp} = 0.5V$. Indicate if the devices are off, in the linear or triode region, or in saturation. If the devices are in saturation, calculate $|V_{dsat}|$.

 

	(a)	(b)	(c)	(d)	(e)	(f)	(g)	(h)
Off/Lin/Sat								
V_{dsat} (if Sat)								

7. Common Source Amp Design


The parameters for a particular $0.5\mu m$ CMOS process are:

- $C_{ox} = 5 \frac{fF}{\mu m^2}$
- $\mu_n C_{ox} = 2\mu_p C_{ox} = 200 \frac{\mu A}{V^2}$
- $V_{tn} = -V_{tp} = 0.5V$
- $C_{ol} = 0.5 \frac{fF}{\mu m}$
- $\lambda = \frac{1}{10V}$ when $L = 0.5\mu m$
- $V_{DD} = 2V$

- Design an NMOS-input common source amplifier with a PMOS load with a low frequency gain of approximately $200V/V$, a unity gain frequency of 1Grad/s with a $1pF$ load, and an output swing of at least $300mV$ to $2.2V$ with a $2.5V$ single-sided supply. **Minimize power consumption.** Clearly indicate what values you are using for g_m , r_o , I_D , V_{dsat} , gate bias, W , and L for each transistor. Clearly indicate which parameters you “pick”, and which you solve for. Calculate the input capacitance.
- How much could you change the input capacitance if you were primarily optimizing to minimize that?

 8. Common Source With No Calculator

An NMOS common source amplifier has a $10V$ supply and a $1k\Omega$ load (to the supply) in parallel with $100pF$. Assume $\mu_n C_{ox} = 20\mu A/V^2$, $W/L = 10,000/1$, $V_{tn} = 1V$, and $\lambda = 0.01V$. You should be able to do all of the calculations by hand (without calculators). One-ish significant digits is fine.



- Write an expression for I_D as a function of output bias point. How much does I_D change as the output voltage varies from 9V to 1V?
- What is the change in the input and overdrive voltage as the output varies from 9V to 1V?
- Write an expression for g_m and r_o as a function of output bias point.
- Write an expression for a_{v0} —the intrinsic gain of the NMOS—as a function of output bias point.
- Fill in the following table given the output bias point. Be sure to specify your units!

Output Bias Point	I_D	g_m	r_o	A_{v0}	ω_p	ω_u
9V						
6V						
1V						