
EE 140/240A Linear Integrated Circuits

Fall 2019

Homework 6

This homework is due October 18, 2019 (late October 19, 2019 09:00).

Submission Format

Your homework submission should consist of **one** file.


- `hw6.pdf`: A single PDF file that contains all of your answers (any handwritten answers should be scanned).

1. K2-W

Check out the datasheet for the K2-W tube op-amp: http://philbrickarchive.org/k2-w_operational_amplifier_later.htm. This op-amp, released in 1952, was the first production op-amp. It runs from a $\pm 300\text{V}$ supply, and has a bandwidth of 300kHz (or k-cycles/s, as they said back then—the unit Hertz not having been established yet). There's a schematic on page 2. Pins 1, 2, and 6 on the bottom of the figure are V_+ , V_- , and V_{out} . V_{R1} and V_{R2} are neon bulbs that provide a low impedance level shift of roughly 100V to center the output between the rails. Identify (circle and label):

- input differential pair
- diff-pair load resistor
- tail current resistor
- Estimate the common mode gain and write it near the tail resistor
- Common-cathode gain stage (like CS or CE)
- Cathode-follower output stage (like source-follower or emitter follower, CD, CC)
- Miller-multiplied compensation capacitor from the output back to the input of the gain stage
- (**BONUS**) positive feedback in this amplifier, designed to increase the low frequency gain (which ended up at about 20,000)

Solution:

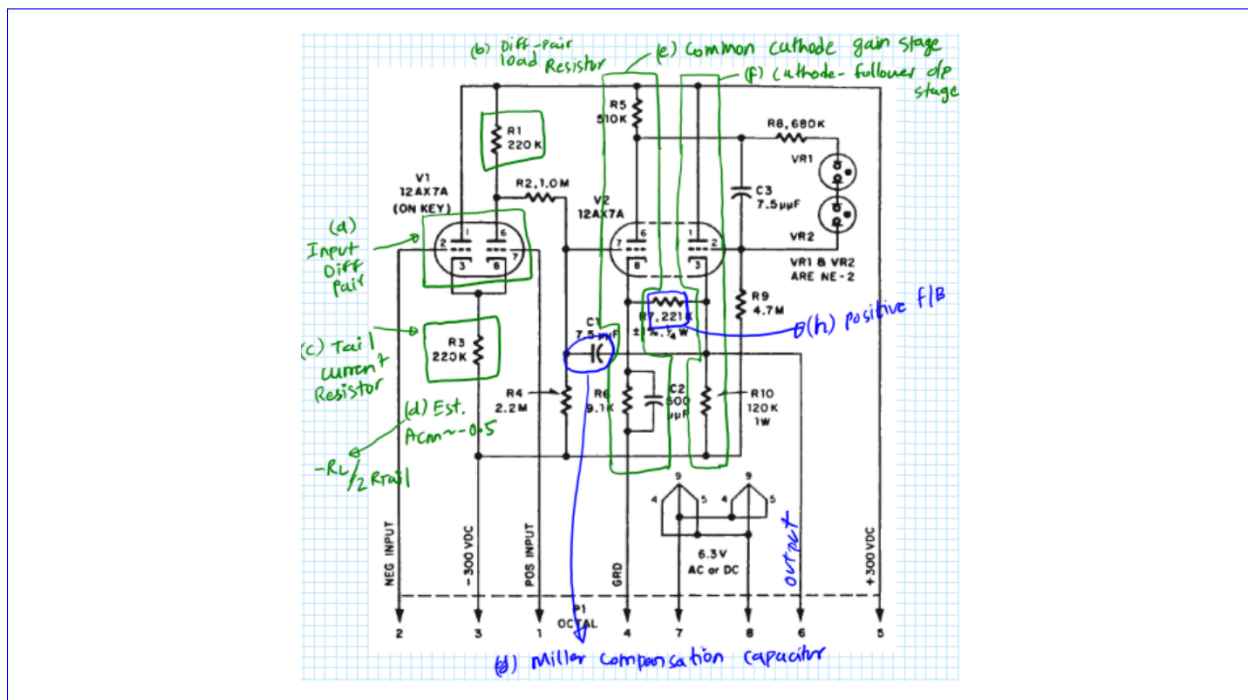

You can find more info on the K2-W here: <https://www.electronicdesign.com/analog/whats-all-k2-w-stuff-anyhow>

Rubric: (8 Points)

- +1: For each correct marking (with no extra devices)

2. More Single-Pole Amplifiers

You have an opamp with a low-frequency gain of 1000 and a single pole at 1Mrad/s. Plot the location of the pole as a function of the feedback factor f from $f = [0, 1]$.

Solution:




Rubric: (3 Points)

- +1: Pole location with $f = 0$
- +1: Pole location with $f = 1$
- +1: Trajectory of pole location correct

(a) **From now on, assume $f = 0.1$.** Sketch the Bode plot of the closed-loop amplifier.

Solution:

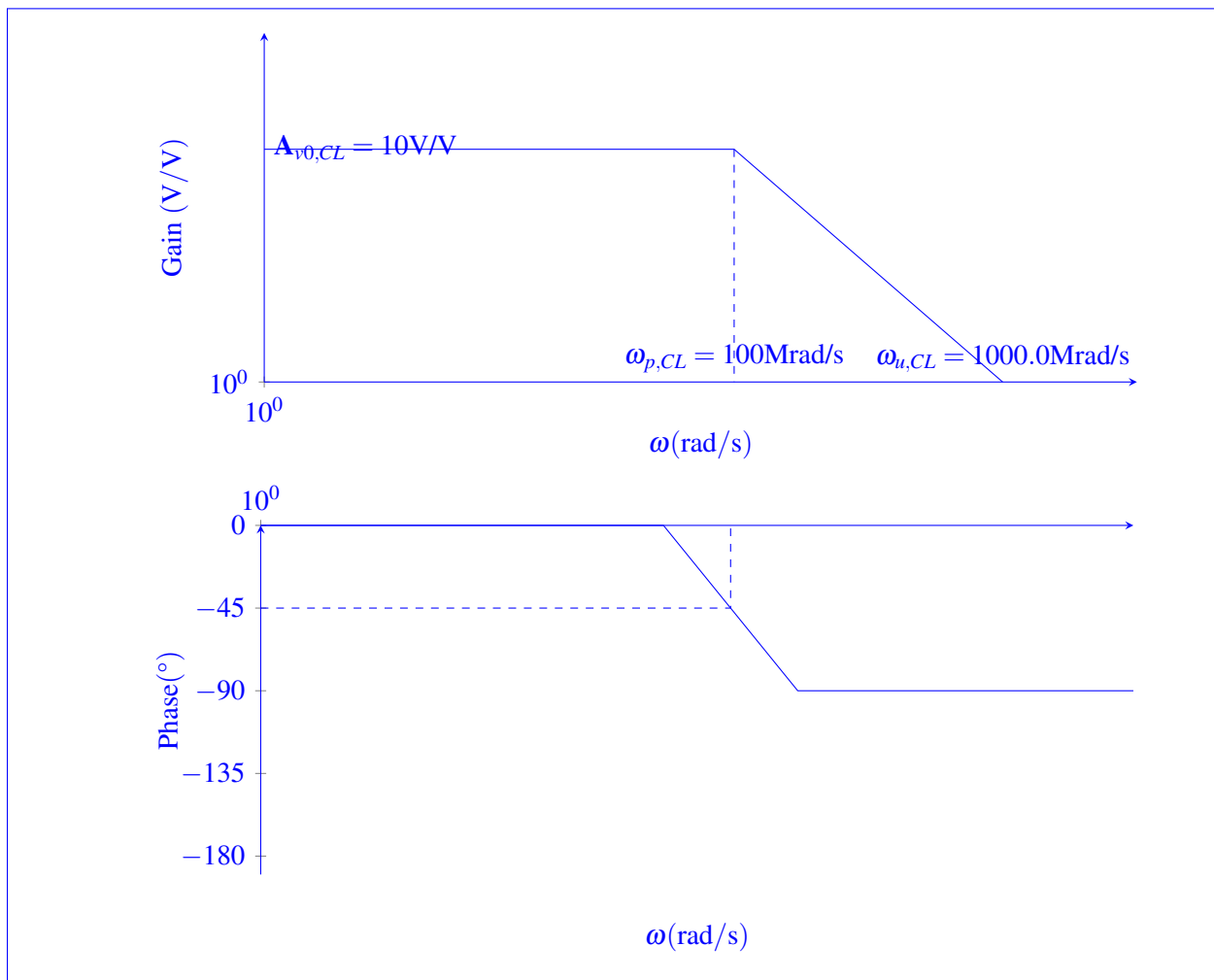

Rubric: (2 Points)

- +1: Correct 3dB frequency
- +1: Correct closed-loop gain

(b) What is the fractional gain error?

Solution: Following the equation for fractional gain error:

$$-\frac{1}{Af}$$

$$-1 \cdot 10^{-2}$$

Rubric: (2 Points)

- +1: Correct equation
- +1: Correct numerical answer

(c) What is the time constant of the step response? How does it compare to the open-loop time constant?

Solution:

$$\tau_{OL} = \frac{1}{\omega_{p,OL}}$$

$$\tau_{CL} = \frac{1}{\omega_{p,OL}A_0f}$$

$$\tau_{OL} = 1\mu\text{s}$$

$$\tau_{CL} = 1 \cdot 10^{-2}\mu\text{s}$$

The closed loop time constant is faster than the open-loop time constant by a factor of the loop gain A_0f

Rubric: (2 Points)

- +1: Correct closed-loop time constant
- +1: Correct comparison to open-loop time constant

(d) What is the unity gain frequency? How does it compare to the open-loop unity gain frequency?

Solution:

The unity gain frequency stays constant

$$\omega_u = 1000.0 \frac{\text{Mrad}}{\text{s}}$$

Rubric: (2 Points)

- +1: Correct ω_u
- +1: Correct comparison between closed-loop and open-loop unity gain frequency

3. Now With Three Poles!

You have an opamp with a low-frequency gain of 1000 and **three** poles at 1Mrad/s.

(a) Plot the location of the three poles as a function of the feedback factor f .

Solution: First, define ω_p as the open loop pole frequency.

The open-loop transfer function:

$$A_{OL}(s) = \frac{A_0\omega_p^3}{(s + \omega_p)^3}$$

And plug this into the closed loop transfer function equation:

$$A_{CL}(s) = \frac{A_{OL}(s)}{1 + A_{OL}(s)f} = \frac{A_0\omega_p^3}{(s + \omega_p)^3 + A_0f\omega_p^3}$$


The poles of the characteristic equation can be found by setting the denominator to 0:

$$(s + \omega_p)^3 + A_0 f \omega_p^3 = 0$$

$$s + \omega_p = \sqrt[3]{A_0 f \omega_p^3} \cdot \exp(j\phi_i), \phi_i = 180 \pm 60^\circ$$

$$s = -\omega_p \left(1 + \sqrt[3]{A_0 f} e^{\pm j\frac{\pi}{3}} \right)$$

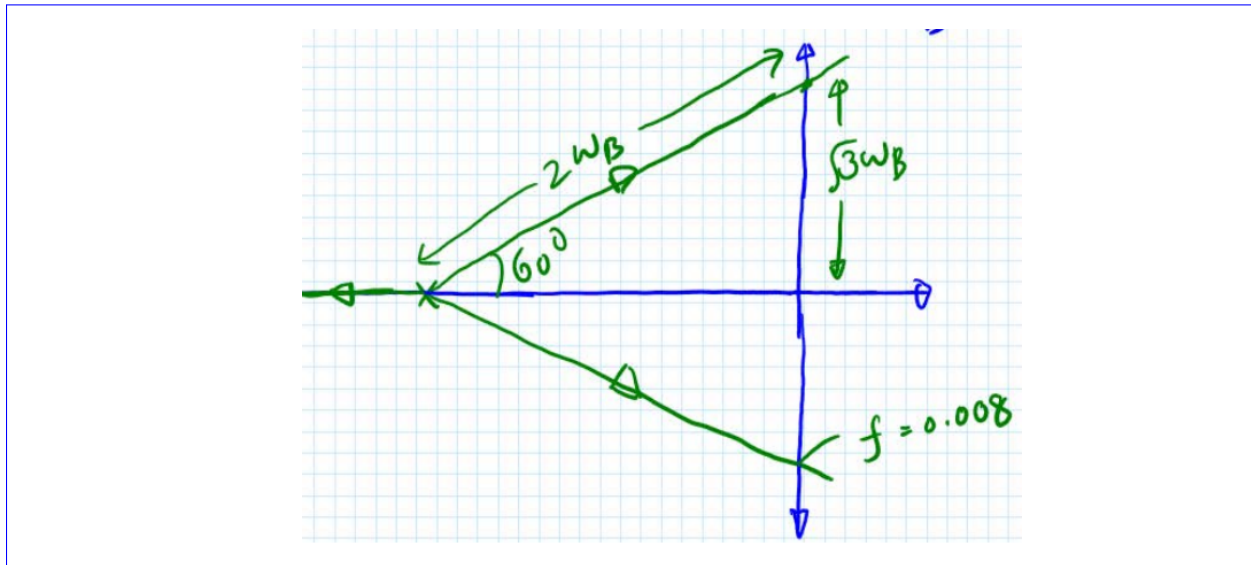where the portion of the expression above with the complex exponential gives the angle and magnitude of the vector which progresses from the initial pole location.



Rubric: (9 Points)

- +1: Calculated correct pole location in terms of f ($\times 3$)
- +1: Correct starting point when $f = 0$ ($\times 3$)
- +1: Correct angle of trajectory for each pole as f changes ($\times 3$)

- (b) At the point where the poles cross the $j\omega$ axis, annotate the plot with the value of f that gives this pole location.

Solution:

Using our answer to the previous part and with some triangle geometry, at the $j\omega$ axis, the real part is 0, so

$$\begin{aligned} 2\omega_p &= \sqrt[3]{A_0 f \omega_p^3} \\ f &= \frac{8}{A_0} \\ &= 0.008 \end{aligned}$$

See the plot above for the annotation.


Rubric: (2 Points)

- +1: Set real portion to 0 in expression for poles in previous part (don't double-penalize yourself—even if your expression for the pole location earlier was incorrect, you should still give yourself credit if you went through the correct process here)
- +1: Correctly calculated f given the expression from the previous part

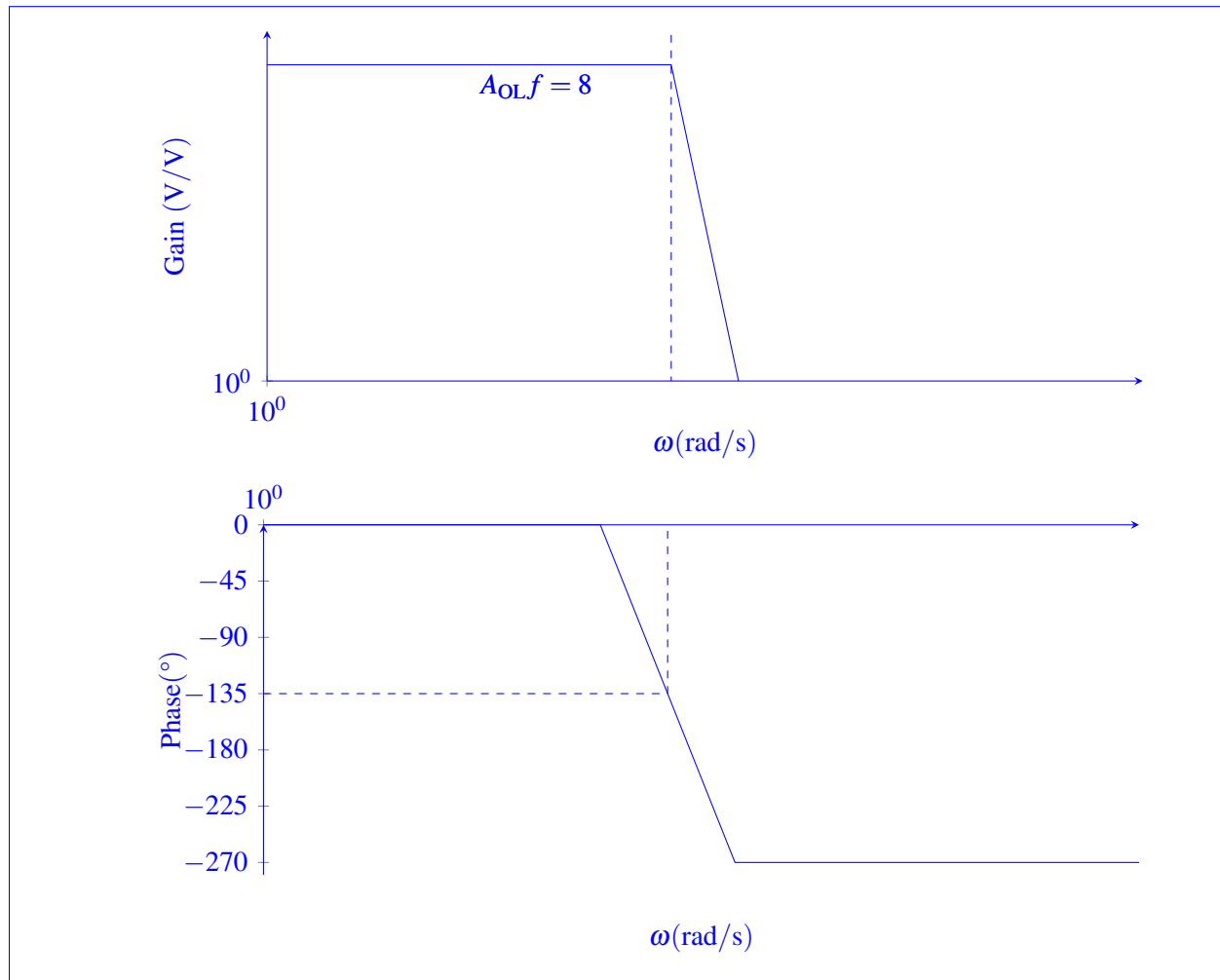(c) Using this value for f , draw a Bode plot of the loop gain Af

Solution:

$$A_{OL}f = \frac{8}{\left(1 + \frac{s}{\omega_p}\right)^3}$$




Rubric: (3 Points)

- +1: Correct DC Af
- +1: Correct pole location *and* -60 dB/decade slope
- +1: ω_u of $Af < 10^7 \frac{\text{rad}}{\text{s}}$

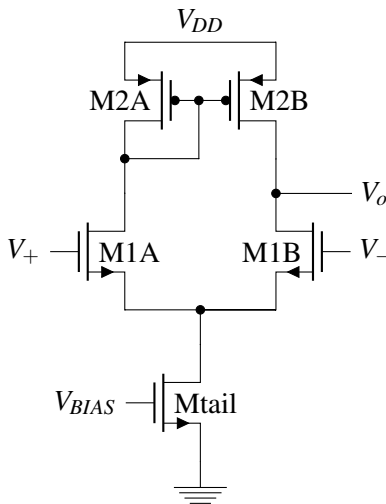4. Virtual Ground Doesn't Fly

Estimate the output resistance of a CMOS differential amplifier with current mirror load.



You may assume that $g_m r_o \gg 1$ for all combinations of g_m and r_o . The following steps may help:

- (a) Estimate the impedance seen looking into the source of M1A

Solution:

$$R_a = \frac{\frac{1}{g_{m2a}} + r_o}{1 + g_{m1a}r_o} \approx \frac{r_o}{g_{m1a}r_o}$$

$$R_a \approx \frac{1}{g_{m1a}}$$

Rubric: (1 Points)

- +1: Correct impedance estimate

- (b) Estimate the impedance seen looking down from the source of M1B

Solution:

$$R_b = \frac{1}{g_{m1a}} || r_{o3}$$

$$\approx \frac{1}{g_{m1a}}$$

$$R_b \approx \frac{1}{g_{m1a}}$$

Rubric: (1 Points)

- +1: Correct impedance estimate

(c) Estimate the impedance seen looking into the drain of M1B

Solution:

$$\begin{aligned} R_c &= R_b + r_o(1 + g_m R_b) \\ &\approx r_o(1 + g_m R_b) \\ &\approx 2r_o \end{aligned}$$

$$R_c \approx 2r_o$$

Rubric: (1 Points)

- +1: Correct impedance estimate

(d) For the R_o calculation, estimate i_{d1B} as a function of v_o .

Solution:

$$\begin{aligned} i_{d1B} &= \frac{v_o}{R_{out}} \\ &= \frac{v_o}{2r_{o1B}} \end{aligned}$$

$$i_{d1B} = \frac{v_o}{2r_{o1B}}$$

Rubric: (1 Points)

- +1: Correct relationship between i_{d1B} and v_o

(e) The current i_{d2B} is due to both the output resistance and the mirrored current. Estimate both parts.

Solution:

$$\begin{aligned} i_{d2B} &= (\text{mirrored current}) + (\text{current due to output resistance}) \\ &\approx i_{d1B} + \frac{v_o}{r_{o2B}} \\ &= \frac{3v_o}{2r_o} \end{aligned}$$

$$i_{d2B} = \frac{3v_o}{2r_o}, r_o = r_{o1B} = r_{o2B}$$

Rubric: (2 Points)

- +1: Correct mirrored current
- +1: Correct current due to output resistance

(f) Estimate the total output current $i_o = i_{d1B} + i_{d2B}$.

Solution:

$$\begin{aligned}
 i_o &= i_{d1B} + i_{d2B} \\
 &\approx \frac{v_o}{2r_{o1B}} + \frac{v_o}{2r_{o1B}} + \frac{v_o}{r_{o2B}} \\
 &= v_o \left(\frac{1}{r_{o1B} + r_{o2B}} \right)
 \end{aligned}$$

$$i_o \approx v_o \left(\frac{1}{r_{o1B} + r_{o2B}} \right)$$

Rubric: (1 Points)

- +1: Correct total output current given previous answers (don't double-penalize)

(g) Show that $R_o \approx r_{o1B} || r_{o2B}$. Magic!**Solution:**

$$\begin{aligned}
 R_o &= \frac{v_o}{i_o} \\
 &\approx \frac{1}{\left(\frac{1}{r_{o1B}} + \frac{1}{r_{o2B}} \right)} \\
 &= r_{o1B} || r_{o2B}
 \end{aligned}$$

$$R_o \approx r_{o1B} || r_{o2B}$$

Rubric: (1 Points)

- +1: Correct final calculation

5. (EE240A) More Poles

A single-stage op-amp has a low frequency gain of 200 and a dominant pole at 10Mrad/s.

- (a) Draw the s-plane with the real axis from -10^7 to 0, and the imaginary axis from 0 to 10^7 . Mark the pole location and draw a dot at $10^7 j$.

Solution: See the solution for part (c)**Rubric:** (2 Points)

- +1: Correct imaginary and real axes
- +1: Correct pole location

- (b) Draw the vector from the pole to $10^7 j$. Calculate the magnitude and phase of this vector.

Solution:

$$\text{magnitude} = \sqrt{2} \cdot 10^7$$

$$\begin{aligned} \text{phase} &= -\arctan\left(\frac{10^7}{-10^7}\right) \\ &= 45^\circ \end{aligned}$$

See the solution for part (c) for the plot.

$$\text{magnitude} = \sqrt{2} \cdot 10^7$$

$$\text{phase} = 45^\circ$$

Rubric: (3 Points)

- +1: Drew vector
- +1: Correct magnitude
- +1: Correct phase

(c) Draw a dot at $10^6 j$. Draw the vector from the pole to $10^6 j$. Calculate the magnitude and phase of this vector.


Solution:

$$\begin{aligned} \text{magnitude} &= \sqrt{(10^7)^2 + (10^6)^2} \\ &\approx 10^7 \end{aligned}$$

$$\begin{aligned} \text{phase} &= -\arctan\left(\frac{10^6}{10^7}\right) \\ &\approx 0.1 \text{ rad} \leftarrow \text{small angle approximation} \\ &\approx 5.73^\circ \end{aligned}$$

$$\text{magnitude} \approx 10^7$$

$$\text{phase} \approx 5.73^\circ$$

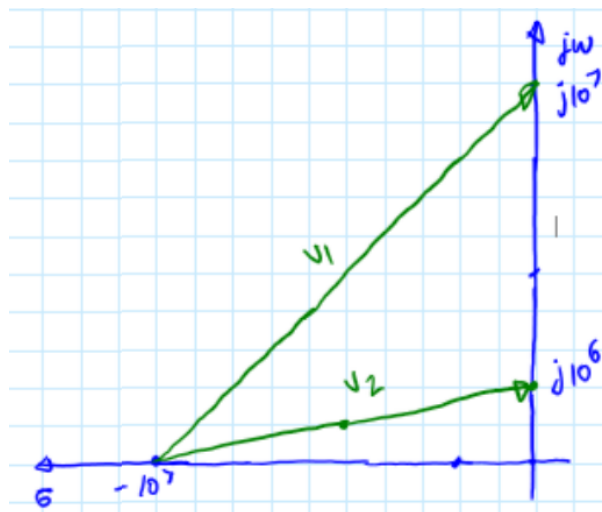

Rubric: (3 Points)


- +1: Drew vector and dot
- +1: Correct magnitude
- +1: Correct phase

(d) Repeat parts (a) and (b), but with the imaginary axis from 0 to 10^8 and the dot at $10^8 j$. Keep the pole in the same location.

Solution:

$$\text{magnitude} = \sqrt{(10^7)^2 + (10^8)^2} \\ \approx 10^8$$


$$\text{phase} = -\arctan\left(\frac{10^8}{10^7}\right) \\ \approx 1.47\text{rad} \\ \approx 84.3^\circ$$

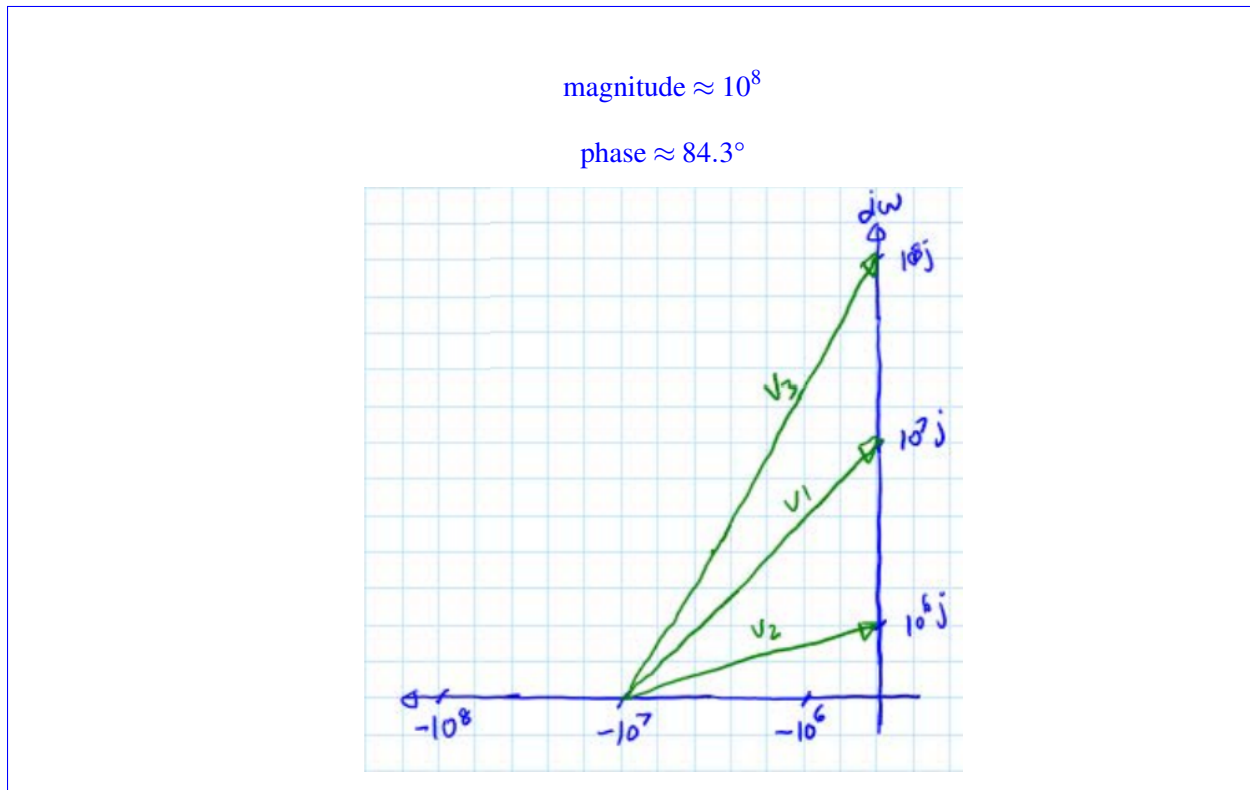**Rubric:** (3 Points)

- +1: Drew vector
- +1: Correct magnitude
- +1: Correct phase

(e) Draw a Bode plot of the gain of your amplifier, with frequency running from 10^5 to 10^9 rad/s. Use the straight-line approximations for the Bode plot, and then add dots showing the results of parts (b), (c), and (d).

Solution:

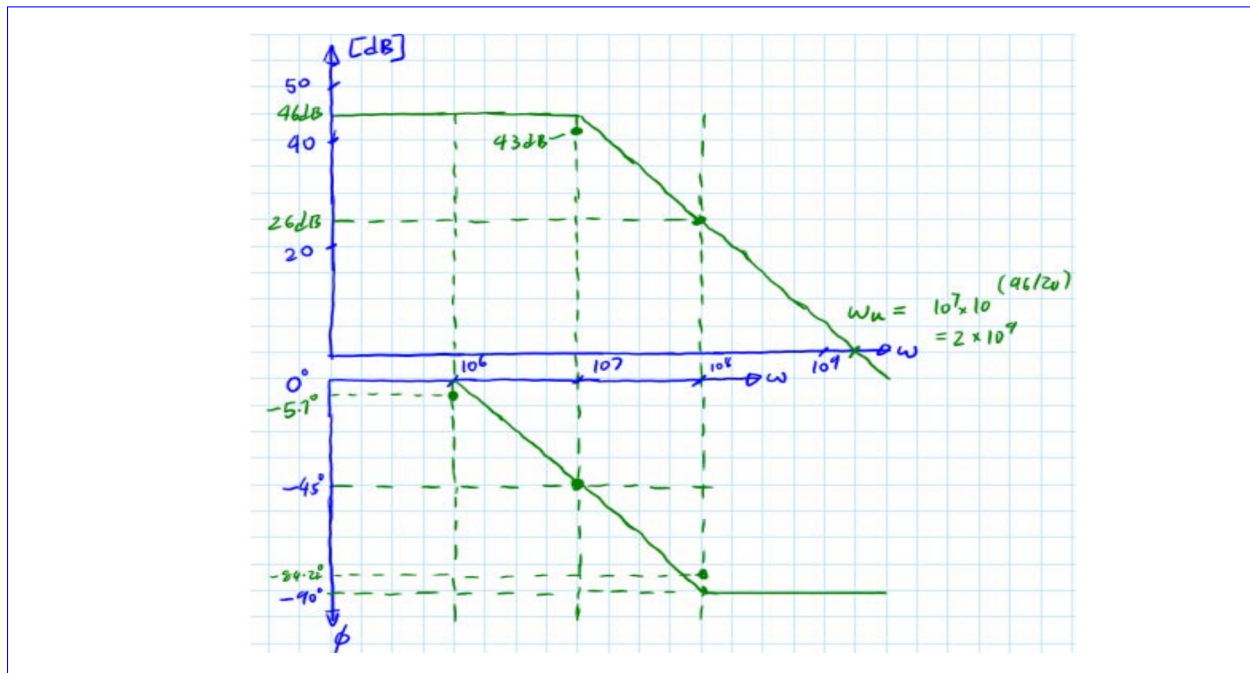**Rubric:** (4 Points)

- +1: Correct DC magnitude
- +1: Correct pole frequency
- +1: Correct magnitude slope
- +1: Correct phase start and end values

6. Compensating for Something

A two-stage CMOS op-amp running at a particular bias point has the following parameters:

- | | |
|------------------------------|--------------------------------|
| • $G_{m1} = 1\text{mS}$ | • $G_{m2} = 1\text{mS}$ |
| • $R_{o1} = 1\text{M}\Omega$ | • $R_{o2} = 100\text{k}\Omega$ |
| • $C_1 = 0.1\text{pF}$ | • $C_2 = 10\text{pF}$ |
| • $C_C = 0\text{pF}$ | |


(a) Plot the magnitude and phase of the overall gain of this uncompensated amplifier.

Solution:

$$\begin{aligned}\omega_{p1} &= \frac{1}{R_{o1}C_1} \\ &= 10^7 \frac{\text{rad}}{\text{s}}\end{aligned}$$

$$\begin{aligned}\omega_{p2} &= \frac{1}{R_{o2}C_2} \\ &= 10^6 \frac{\text{rad}}{\text{s}}\end{aligned}$$
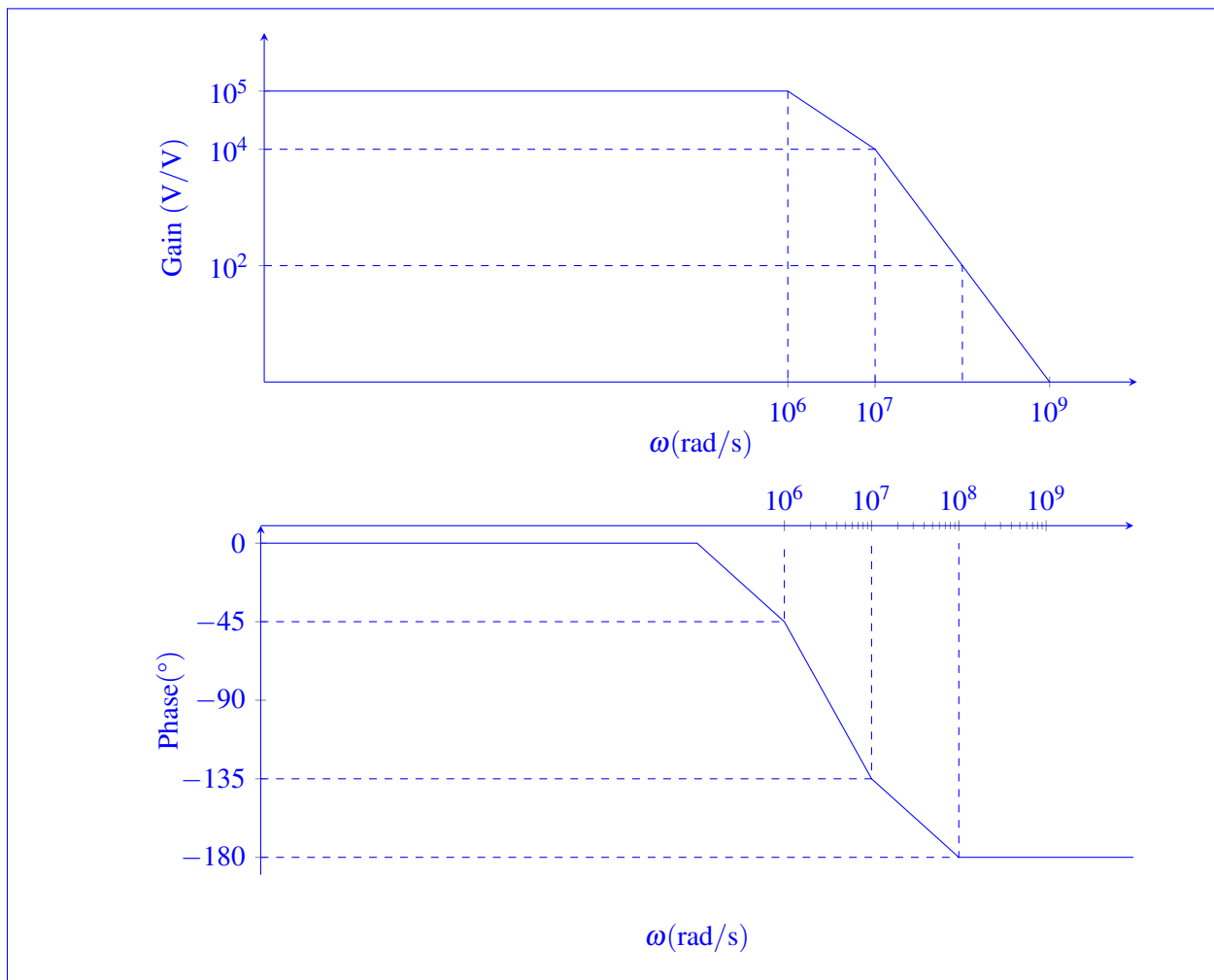
$$\begin{aligned}A_{v0} &= G_{m1}R_{o1}G_{m2}R_{o1} \\ &= 10^5 \frac{\text{V}}{\text{V}}\end{aligned}$$



Rubric: (6 Points)

- +1: Correct pole frequency (2×)
- +1: Correct DC gain
- +1: Correct phase relationship about pole frequencies (2×)
- +1: Correct unity gain frequency

(b) Where are the poles of the uncompensated amplifier? Is it unity-gain stable?

Solution: See the plot in part (a)

$$\omega_{p,1} = 10^7 \frac{\text{rad}}{\text{s}}, \omega_{p,2} = 10^6 \frac{\text{rad}}{\text{s}}$$

No, the amplifier is not unity gain stable.

Rubric: (1 Points)

- +1: Correct answer of if the amplifier is unity gain stable

7. Continuing... For the same amplifier above, we now add $C_C = 1\text{pF}$. You may ignore the RHP zero that this introduces. On the figures provided below,

(a) Plot the magnitude of the second stage gain vs. frequency.

Rubric: (3 Points)

- +1: Correct DC gain
- +1: Correct pole frequency
- +1: 20dB/decade drop-off

(b) Plot the magnitude of the input *capacitance* of the second stage (including C_C) vs. frequency.

Rubric: (4 Points)

- +1: Correct DC capacitance (if you didn't include C_1 that's fine)
- +1: Correct high-frequency capacitance (fine if you didn't include C_1)
- +1: Correct pole location for gain dropping the capacitance
- +1: Correct ω_{u2} location where C_C no longer Millerizes

(c) Plot the magnitude of the input *impedance* of the second stage vs. frequency. Add a line for the output impedance of the first stage.




Rubric: (4 Points)


- +1: Correct low frequency R_{o1}
- +1: Correct impedance line for Millerized C_C
- +1: Correct zero location in the impedance when Miller effect begins to decrease
- +1: Correct impedance line for non-Millerized C_C

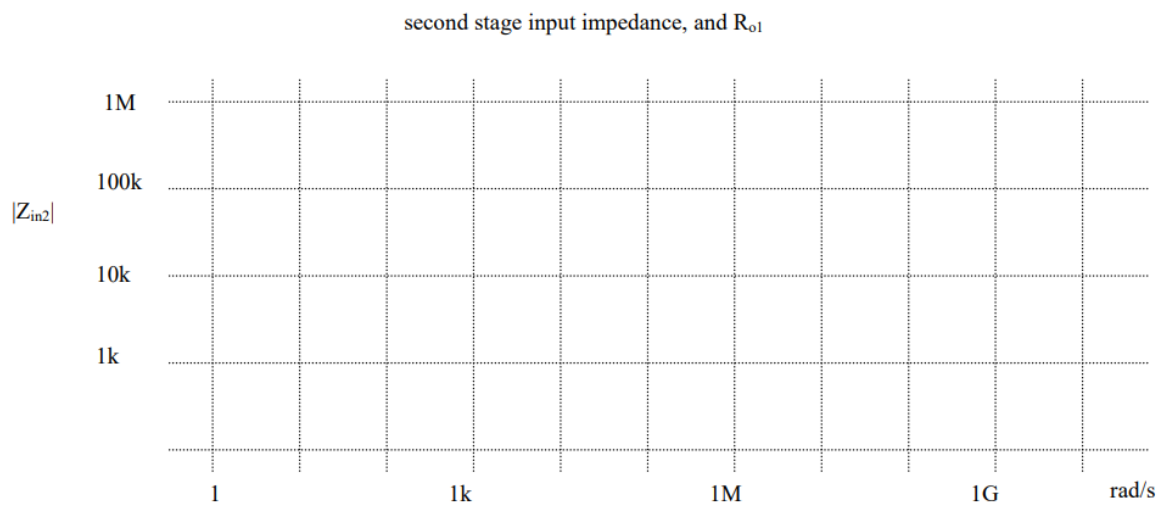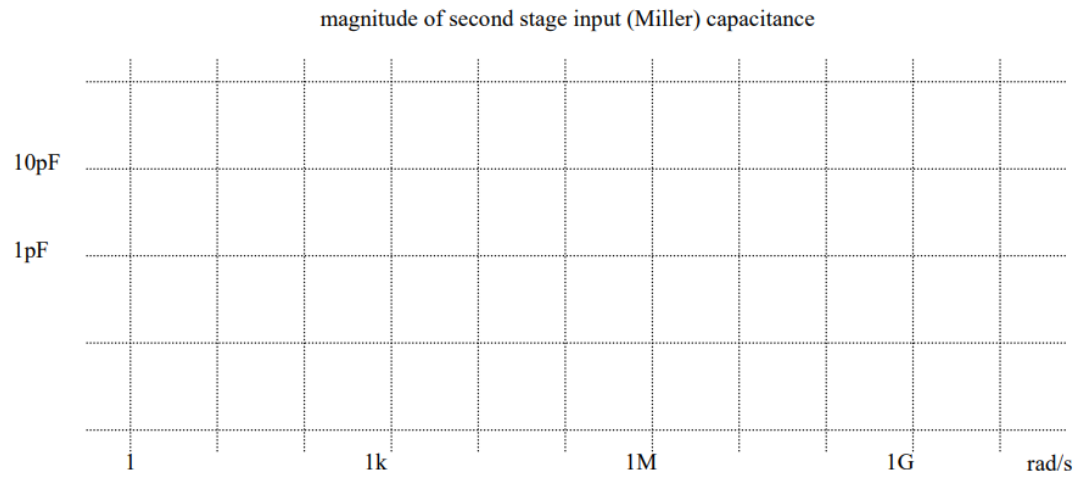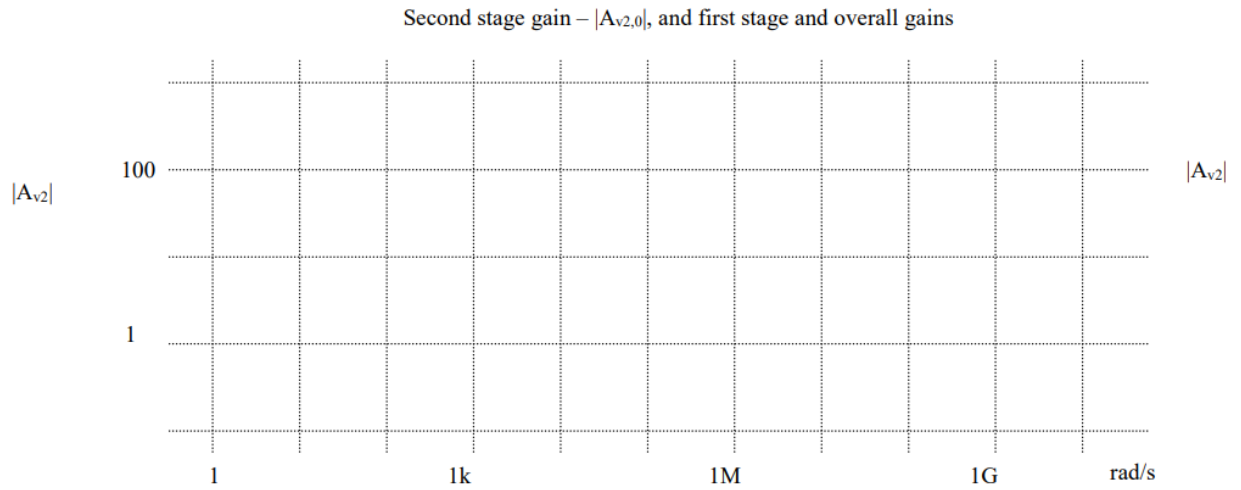(d) Now plot the magnitude of the gain of the first stage on the top plot, and the magnitude of the overall gain of the amplifier.

Rubric: (9 Points)

- +1: Correct DC gain of first stage
- +1: Correct pole and zero locations of the first stage gain ($3\times$)
- +1: Correct DC gain of combined stages
- +1: Correct pole locations and slope of combined stages ($4\times$)



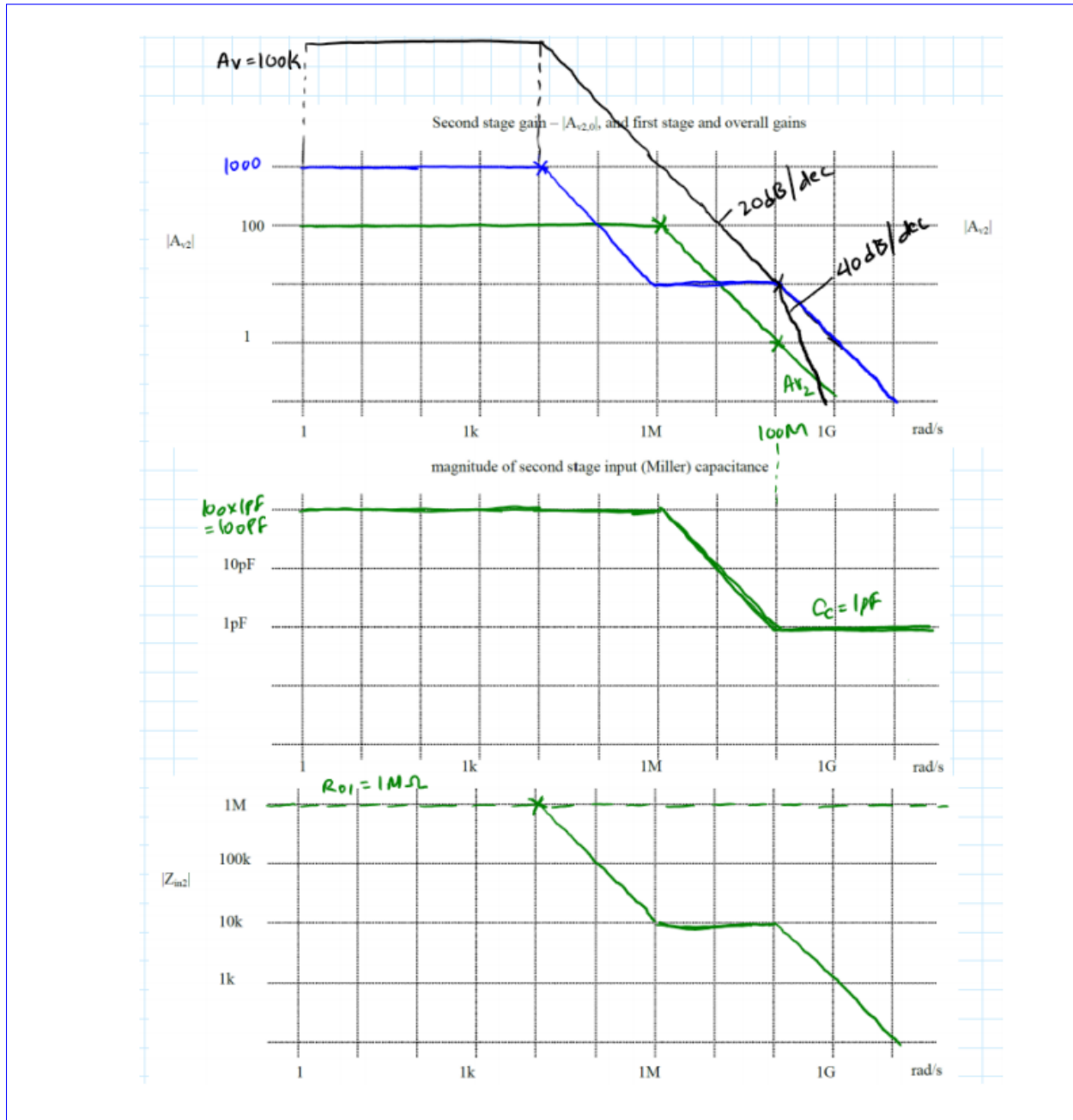Solution:

- (e) What are the compensated poles of the amplifier? If C_c were 0pF, where would the poles of the amplifier be?

Solution:

	ω_{p1} (rad/s)	ω_{p2} (rad/s)
Uncompensated	10^7	10^6
Compensated	10^4	10^8

Rubric: (4 Points)

- +1: Correct compensated poles of the amplifier ($2\times$)
- +1: Correct uncompensated poles of the amplifier ($2\times$)

8. Virtual Ground Is A Lie

(EE240A) For a standard 5 transistor CMOS differential amplifier show that the gain from a differential input to the (so called virtual ground!) tail voltage is $\frac{1}{4}$. You can assume that $g_m r_o \gg 1$ for all combinations of g_m and r_o . You can win bets with experienced IC designers with this knowledge!

Solution:

Estimating G_m :

$$\begin{aligned} v_{mirr} &\approx -\frac{v_i}{2} \\ v_d &\approx g_m v_i \left(\frac{r_o}{2} \right) \\ i_o &\approx -\frac{v_x}{r_o} - \frac{v_d}{r_o} \\ &\approx \frac{v_i}{2r_o} - \frac{g_m}{2} v_i \\ G_m &\approx -\frac{g_m}{2} \end{aligned}$$

Estimating R_o

$$\begin{aligned} R_o &\approx r_o \parallel \frac{r_o + \frac{1}{g_m}}{1 + g_m r_o} \parallel \frac{r_o + r_o}{1 + g_m r_o} \\ &\approx r_o \parallel \frac{1}{g_m} \parallel \frac{2}{g_m} \\ &\approx \frac{2}{3g_m} \\ &\approx \frac{1}{2g_m} \text{ if you ignore the additional } r_o \text{ on the non-diode connected branch} \end{aligned}$$

Rubric: (4 Points)

- +1: Correct G_m estimate with correct sign
- +1: Correct R_o estimate (using $\frac{2}{3g_m}$ is acceptable)
- +2: Correct gain with correct sign