

Homework Assignment #7

Due by online submission **Wednesday 10/23/2019** (9am Thursday)

1. You have a two-stage CMOS amplifier driving an output load of 10pF. The second stage has a transconductance of 10mS, an output resistance of 10k Ω , and an input capacitance of 1pF. The first stage has a transconductance of 1mS and an output resistance of 100k Ω . Assume $C_c=0$.
 - a. Draw a Bode plot of the gain and phase of the first and second stage individually, and the combined gain and phase.
 - b. Is the amplifier stable in unity gain feedback?
 - c. Estimate the largest feedback factor and corresponding gain for which the amplifier has 45 degree phase margin.Now we will add C_c to make the amplifier stable in unity gain feedback.
 - d. Assuming that C_c will be bigger than C_1 , estimate the second stage pole.
 - e. Ignoring the RHP zero from C_c and the pole/zero doublet from the current mirror, where do you need to put the unity gain frequency in order to get a 45 degree phase margin in unity gain feedback?
 - f. What is the value of C_c which achieves this? Was your assumption correct in part d?
 - g. Where is the compensated first stage pole?
 - h. Draw a Bode plot of the compensated amplifier.
2. Check out the “early op-amp” in Figure 2 on this page <https://www.maximintegrated.com/en/app-notes/index.mvp/id/4428>.
 - a. Circle and label the following components
 - i. differential pair with resistive load
 - ii. tail current sink
 - iii. common emitter gain stage with level-shifting diodes
 - iv. output stage with current-limiting resistors
 - v. Zener diode based voltage reference
 - b. Why is there a resistor in series with the Zener diode?
 - c. If the Zener has a reverse breakdown of 3.5V, and the tail resistor is 1k Ω , what is the tail current? Does it vary much with supply voltage?
 - d. If you were going to add a compensation capacitor to this op-amp, where would you put it? (draw it on the circuit)
3. You have three op-amp topologies: single stage active load (our standard 5 transistor opamp), the two stage version of that, and the current mirror op-amp (schematic below). Each topology can either have NMOS or PMOS inputs, for six different flavors. Which sketch the output swing vs. common mode input range for each flavor.
4. The LT1008 <http://cds.linear.com/docs/en/datasheet/1008fb.pdf> (also decades old, \$3.55 on digikey) is not internally compensated. This gives you higher performance (BW, slew rate) for higher gain, but means that you need to add external capacitance when using the amplifier in low-gain configurations. They give you two choices, either add a capacitor C_F that will be somewhat Millerized or add C_S that looks more like our C_2 .
 - a. with a closed loop gain of 1,000 and perfect feedback resistor matching,
 - i. estimate your gain error at 0.1 Hz
 - ii. estimate the closed-loop pole location with $C_S=10\text{pF}$ vs. $C_F=30\text{pF}$ (page 6, lower left)
 - b. With $C_F=3\text{pF}$ vs. 30pF, what is the maximum feedback factor (and corresponding minimum gain and max bandwidth) that will give a phase margin of 60? (page 6, lower right)
5. Figure 6.15 in Razavi is a model of a two-stage amplifier. [For ee247A students: Fig 9.18 in GHLM, and equations 9.27 and 9.33 for parts b and c]
 - a. re-draw it using our terminology from class: G_{m1} , G_{m2} , R_{o1} , R_{o2} , C_1 , C_2 , C_c .
 - b. Equation 6.30 is the transfer function of the amplifier. Re-write that with our terminology.

