

Due by online submission **Wednesday** 11/13/2019

-
- The circuit schematic illustrates a 2.5V CMOS differential amplifier. It features a Wilson current source at the tail, composed of NMOS transistors Mb1 (100/1), Mb2 (100/1), and Mb3 (200/1), and PMOS transistors Mb4 (200/1) and Mb5 (10/1). A 100uA current source is connected to the 2.5V supply. The differential pair consists of NMOS transistors M1A (200/1) and M1B (200/1), biased by a Wilson cascode structure made of PMOS transistors M2A (200/1), M2B (200/1), M3A (100/1), M3B (100/1), M4A (200/1), M4B (200/1), M5A (200/1), and M5B (200/1). The output voltage V_{OUT} is taken from the node between M4B and M5B. Biasing is provided by a 2.5V supply, a 0V supply, and a gate voltage V_{G3} for the cascode transistors. The schematic also shows a central differential pair M1A/M1B with biasing voltages V₊ and V₋.

- a. Calculate and tabulate:
 - i. the overdrive voltage and current in all devices. For this step you may assume that $\lambda=0$. The simplest order may be Mb1 through Mb6, then M1 through M5.
 - ii. Calculate the bias voltages on all nodes, assuming $V_{I,CM}=1V$. Specifically: tail, G2, G3, G5, G6, S3B, S4AB, and out.
 - iii. the g_m and r_o parameters for M1 through M5
- b. Calculate G_m , R_o , and A_v

- c. Calculate the input common mode range and output swing.
 - d. What is the minimum voltage that could be used on the gates of M3AB to still keep M2AB in saturation? If you used that voltage, what is the new input common mode range and output swing? How would you change the size of Mb5 to achieve that voltage?
 - e. If the load capacitance is 1pF (roughly the same as the input capacitance),
 - i. what are the pole and unity gain frequencies?
 - ii. What is the phase margin in unity gain?
 - iii. What are the frequencies of the pole/zero doublets from the current mirror?
6. To increase the positive output swing of the previous amplifier,
 - a. redraw the PMOS current mirror M4AB, M5AB as a high-swing cascode current mirror, as in Figure 5.18b in Razavi (5.13b in the 1st edition), but PMOS.
 - b. Generate V_b (V_{G4}) using something like Mb5 above, but PMOS. What current source do you use? What gate voltage biases it? What W/L do you use for all devices, and why?
 - c. [240A] generate V_b from the circuit suggested in 5.19b in Razavi. What value for $(W/L)_5$ in that figure is needed?
7. In Figure 2 of this Analog Devices discussion on voltage regulators
<http://www.analog.com/en/design-center/landing-pages/001/fundamentals-of-ldo-design-and-applications.html>
 - a. Estimate the low-frequency loop gain T in terms of the op-amp voltage gain A_0 , g_m of the pass transistor, and load resistance R_L (not shown in the figure).
 - b. Why does the SENSE value connect to the positive input of the op-amp? Is this positive feedback?
8. For the circuit in figure 13.43 in Razavi (6.9 in GHLM)
 - a. what ratios of C_2 to C_1 are needed to make a variable gain amplifier with gain equal to any integer between 1 and 8?
 - b. for a given open-loop op-amp gain A , which of the closed-loop gains above has the worst gain error? (you may assume that $C_P=0$)
 - c. if the desired closed-loop gain accuracy is 0.4% regardless of gain setting, what is the minimum open-loop gain necessary for the op-amp?
 - d. if the amplifier must settle to within 0.4% of the correct value within 10us, what is the minimum unity gain bandwidth of the op-amp?
9. [ee240A] For the folded cascode above, how does performance change
 - a. if the bias current drops to 1uA and all devices are biased at roughly $V_{gs}=V_t$?
 - b. if the bias current remains 100uA, but the length of all devices is changed to 14nm, and the widths vary from 200nm to 400nm as appropriate for a current density of 0.5mA/um? Assume that the load capacitance is comparable to the input capacitance (which is?).