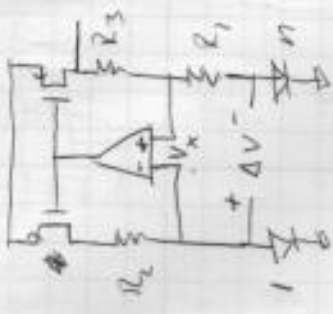


Mitcham Friday in class  
HW11-8  
Lect 1-3  
2 pages, 4 slides notes

Bandgap  
temp sensor  
Cascode



$$\Delta V = \frac{K_B \ln(n) T}{q}$$

86mV  
K



0.2mV/K if n=10

Driving  $V_x = 0$  enforces  $I_{D1} = I_{D2}$   
 $I R_1 = V_{TH} \ln(n) \frac{R_3}{R_1}$   
 $V_{D1} = V_{D2} + I R_1$   
 $V_{BG} = V_{D1} + I R_3$

$$= V_{D1} + V_{TH} \ln(n) \frac{R_3}{R_1}$$



M + choose

to sub 0 temp coeff

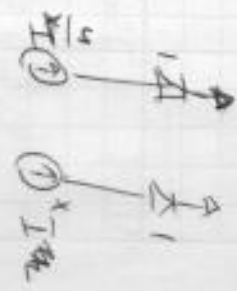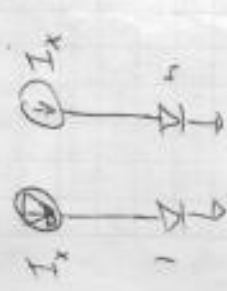

n=2?  
n=7?  
Both current and both diodes?

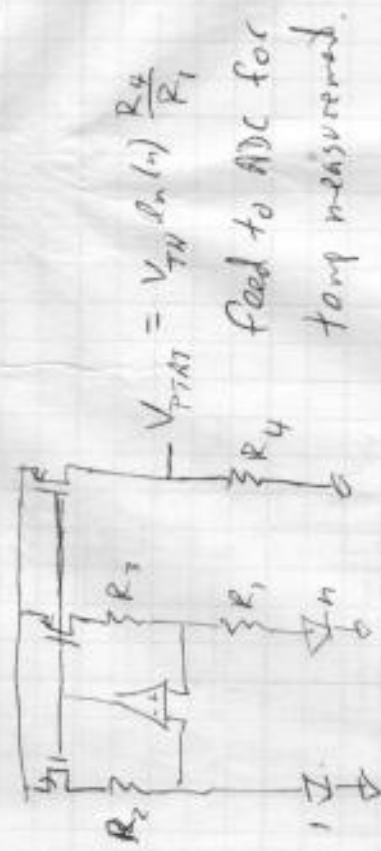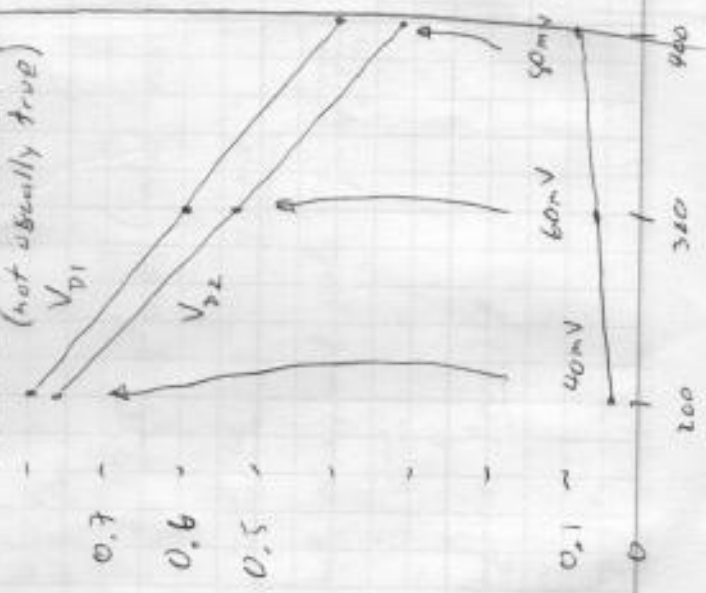assume  $I_x$  constant (not usually true)



$$V_{PTAT} = V_{TH} \ln(n) \frac{R_4}{R_1}$$


Feed to ADC for temp measurement.

what topology to use?  
 CMOS input & trouble w/ input common mode  
 PMOS input 5T: trouble w/ output swing.  
 2 stage? current mirror?  
 no  $V_{en}$  transistors?

One more op-amp topology family: cascode.  
 issues/goals: gain -  $g_m r_o$  often not enough  
 stability simple stage is nice  
 I/O range prefer more flexibility

telescopic cascode: solves first 2  
 trouble w/ third

simplest bias

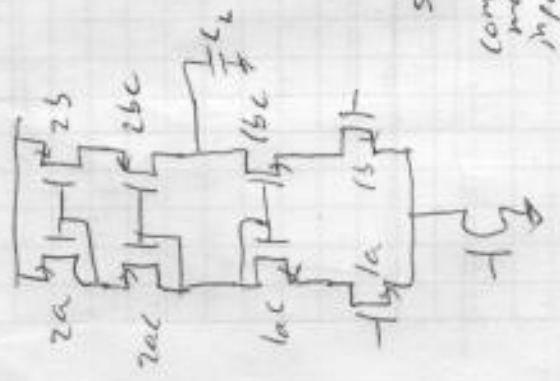

$$G_m = g_{m1}$$

$$R_o = (g_{m1} r_{o1})_{ic} r_{o1b} \parallel (g_{m1} r_{o1})_{2c} r_{o1b}$$

$$A_v \approx \frac{1}{2} (g_{m1} r_{o1})^2 \frac{g_{m00d}}{g_{m1}}$$

simple dominant pole  $\omega_p = \frac{1}{R_o C_o}$

$$\omega_u \approx \frac{g_{m1}}{C_o}$$


swing is terrible  
 common mode input range

v.s. resistor


high output impedance  $r_o$   
 easy biasing  
 $\approx 2 \times g_m$

want to add output resistance  
 cascode sort by  $(g_m r_o)_{case}$ .

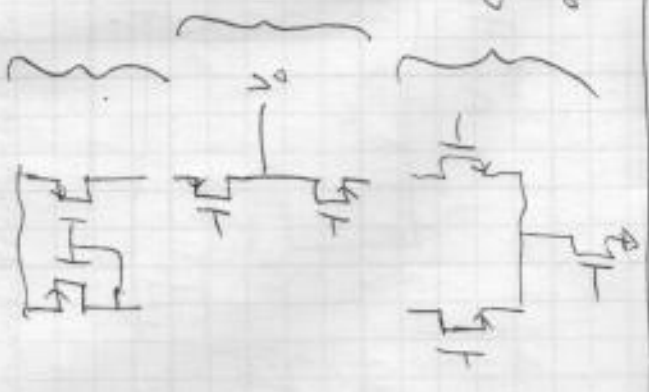
common mode rejection  
 differential output



with some tricks

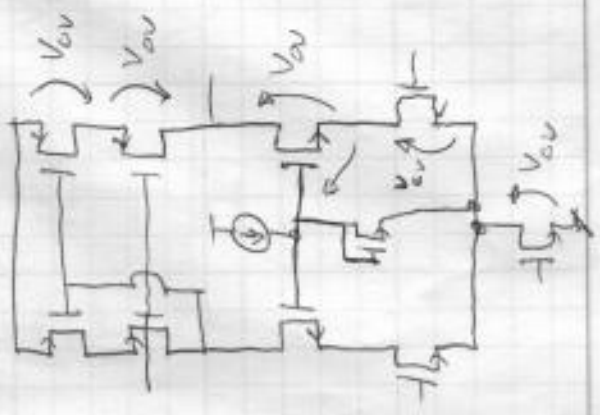


folding

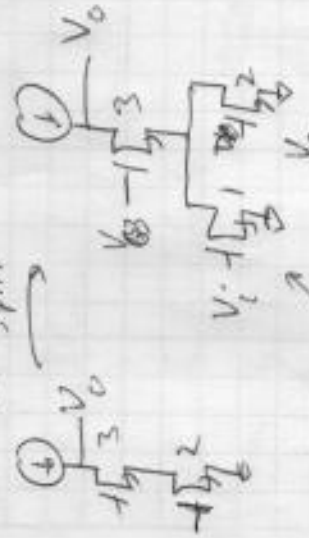

$G_m: i_o = g_m v_i$


fold

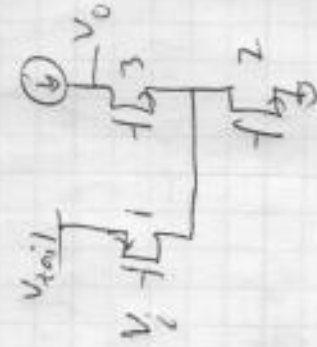

$G_m: i_o = g_m v_i$

differential

fewest transistor folded input stage

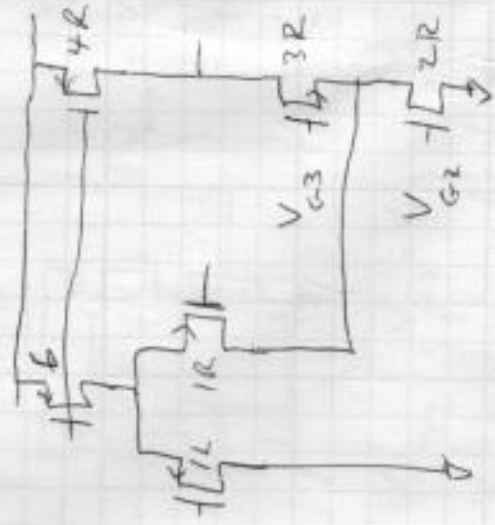


$G_m = g_{m1} R / 2$   
 $R_o = r_{o4R}$   
 (could cascade)

$V_{i,cm}$   
 $min = V_{ov2} - |V_{tp}|$   
 $typ < 0!$




works!

simplified folded cascode (self-biased)

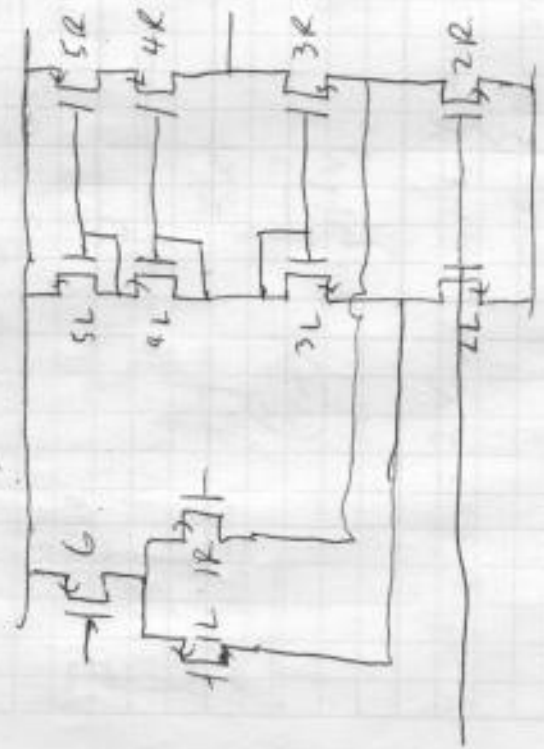

$V_{ov}$  possible, but often  $V_{i,cm,max}$  is not important.

p.s.

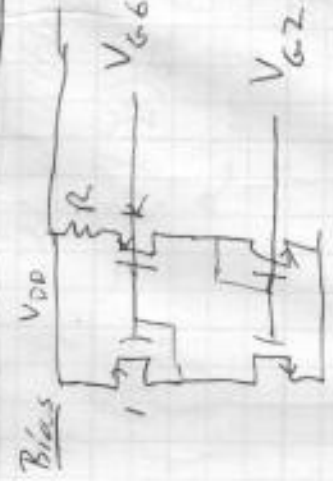

$$G_m = g_{m1}$$

$$R_o = R_{out} \parallel R_{outdown}$$

if  $I_{D1} = I_{D3 \& 5}$

then  $I_{D2} = 2I_{D1}$

$$r_{o2} = \frac{1}{2} r_{o1} \Rightarrow r_{o2} \parallel r_{o1} = \frac{1}{3} r_{o1} = \frac{1}{3} r_{o5}$$



if  $g_m$  same for all then

$$R_o = (g_{m1} r_{o1})_{3 \& 5} (r_{o5} \parallel \frac{1}{3} r_{o1}) = \frac{1}{4} (g_{m1} r_{o1})_{3 \& 5} r_{o5}$$

$$A_v = \frac{1}{4} (g_{m1} r_{o1})_{3 \& 5}^2 \text{ lots of "ifs"}$$


better biasing

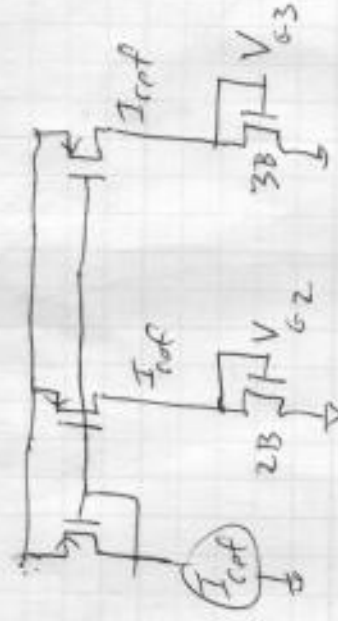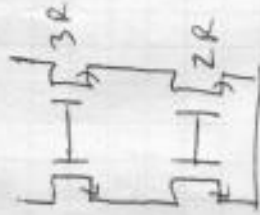like  $V_{G3} = V_{G3, \min} = V + V_{ov2}$



to set  $V_{ov3} = 2V_{ov2}$ , either  $\left\{ \begin{array}{l} 4 \times \text{current} \\ \text{or} \\ 4 \times \text{smaller } (\frac{W}{L}) \end{array} \right.$

output swing of self-biased:

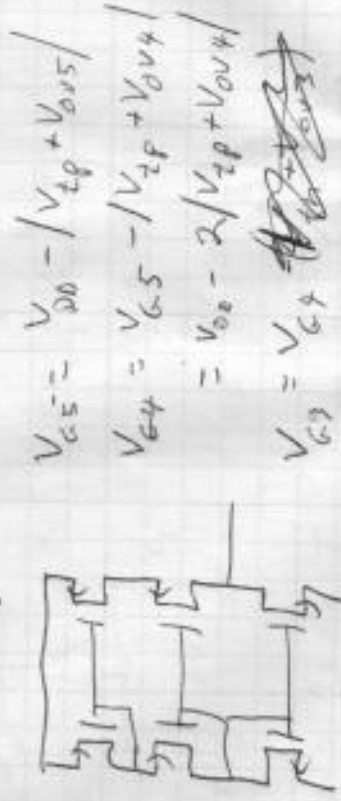

$$V_{G5} = V_{DD} - |V_{tp} + V_{ov5}|$$

$$V_{G4} = V_{G5} - |V_{tp} + V_{ov4}|$$

$$= V_{G5} - 2|V_{tp} + V_{ov4}|$$

$$V_{G3} = V_{G4} - |V_{tp} + V_{ov3}|$$

$$V_{O, \min} = V_{G3} - V_{tn}$$

$$V_{O, \max} = V_{G4} + |V_{tp}|$$

typically add a little margin

$$\left(\frac{W}{L}\right)_{B3} = \frac{1}{5} \left(\frac{W}{L}\right)_{B2}$$

or  $\frac{1}{6}$  integer multiples  
(B2 is 5 or 6 copies of B3)