
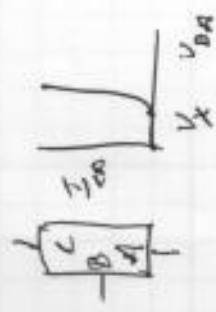


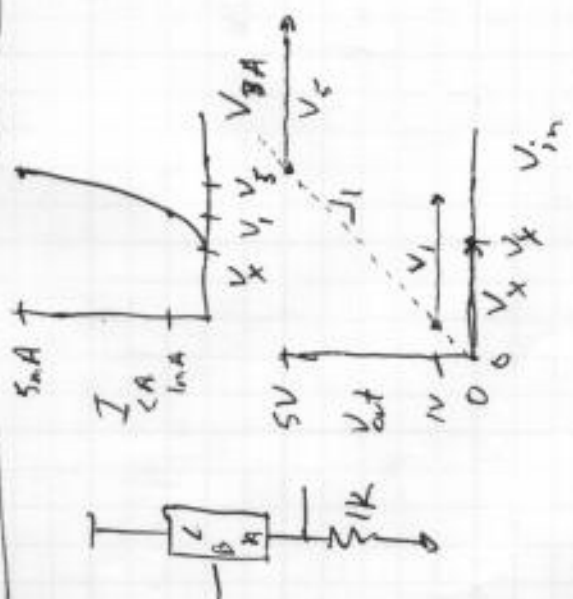piarra, sources, website
 section
 lab - LTSPICE





"normal" mode: $V_{BA} > V_X$
 BJT "forward active"
 $V_{BE} \approx$ roughly 0.5V
 $V_{CE} > V_{CE(sat)} \approx 0.3V$




cathode follower (1934)

emitter follower
 source follower

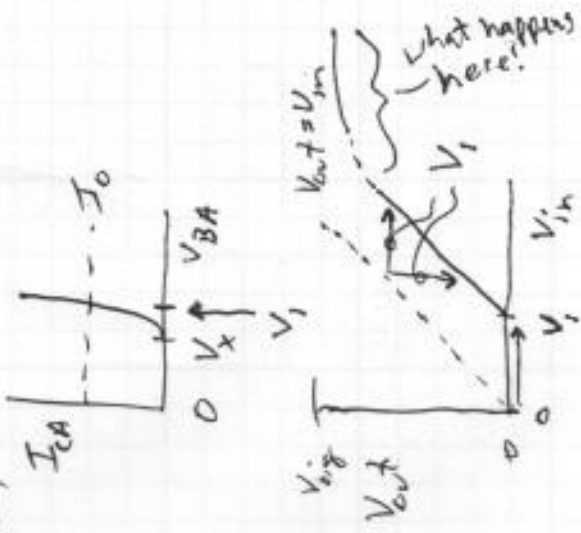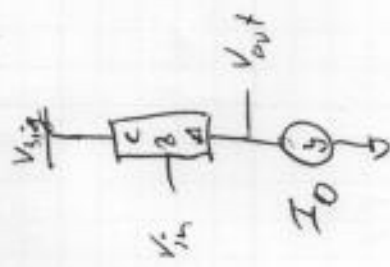


140/240A



195A W/LZ

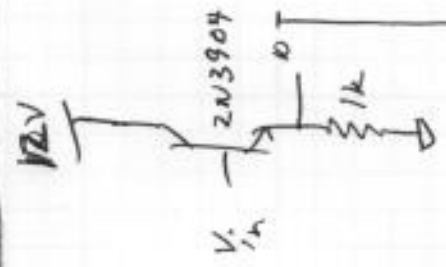



$V_i = 0.6V$
 $V_o = 0.66V$

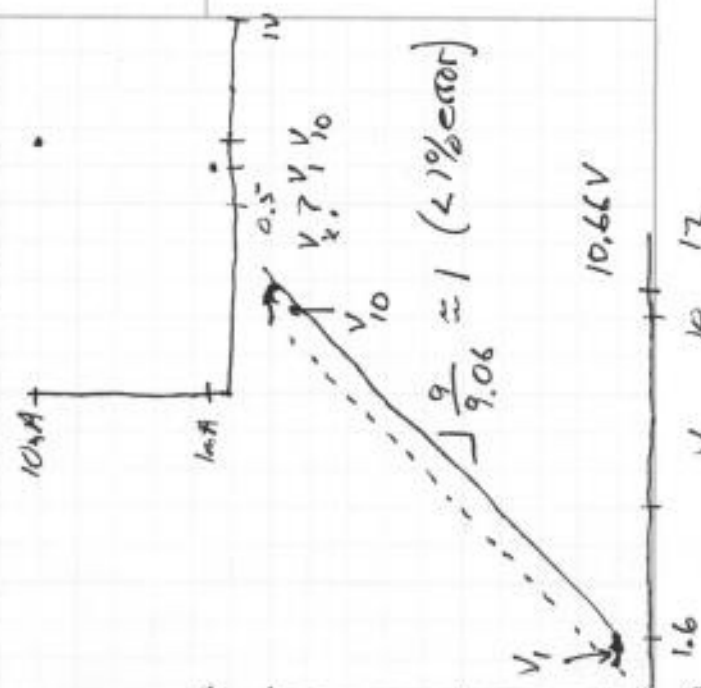




Diff pair (1936)

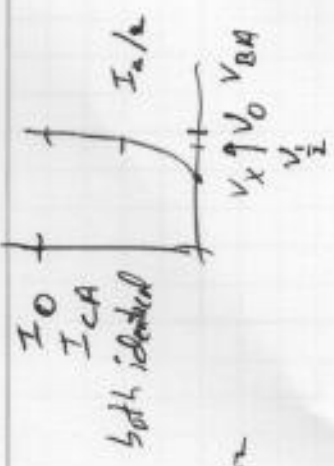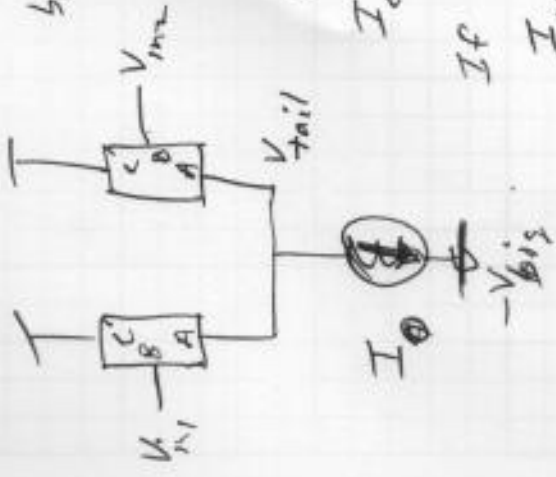


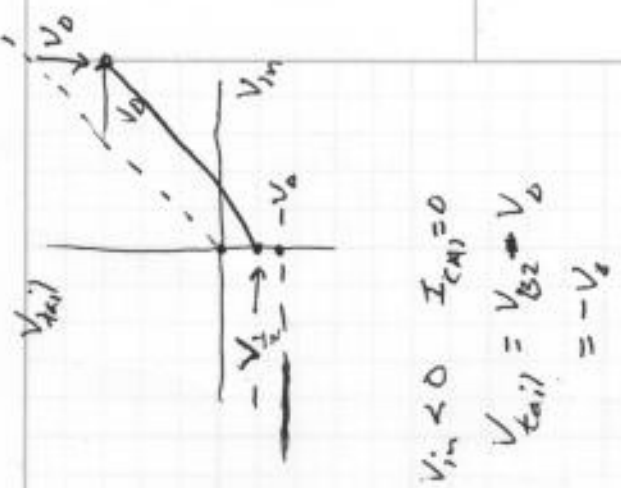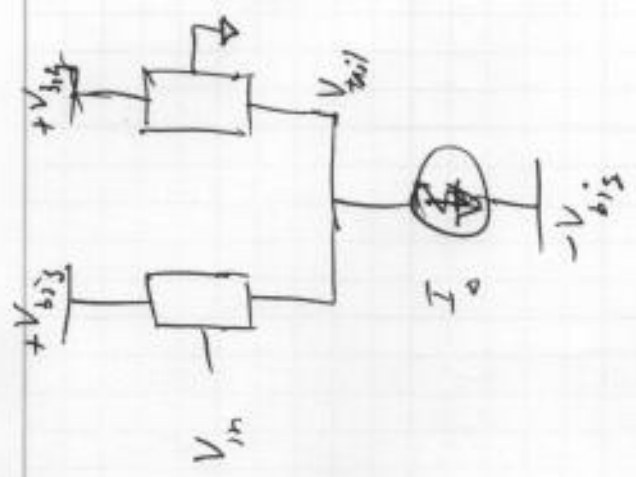both identical
 I_0
 I_{CA}
 if $V_{in1} = V_{in2}$
 $I_{CA1} = I_{CA2} = I_0/2$
 If $V_{in1} > V_{in2}$ $I_{CA1} < I_{CA2}$
 $I_{CA1} = I_0$ $I_{CA2} = 0$



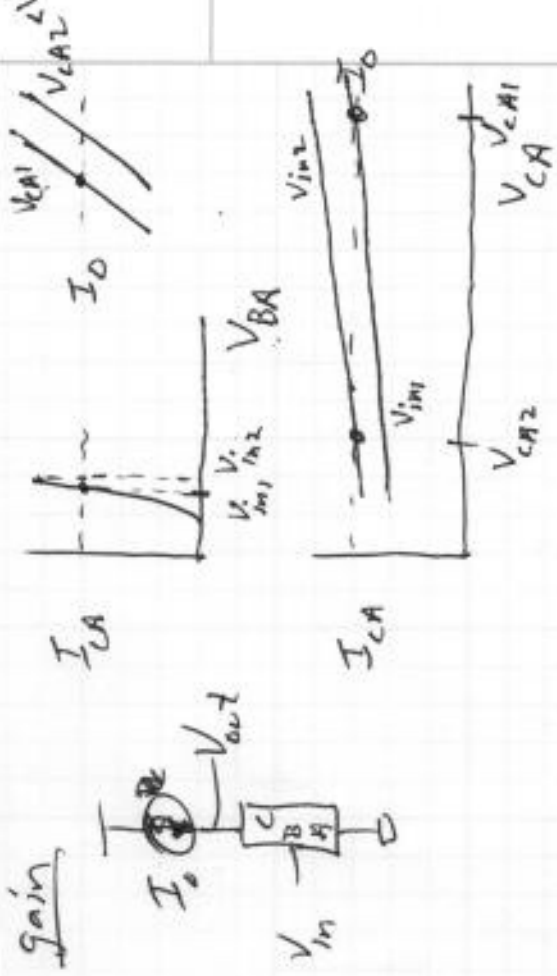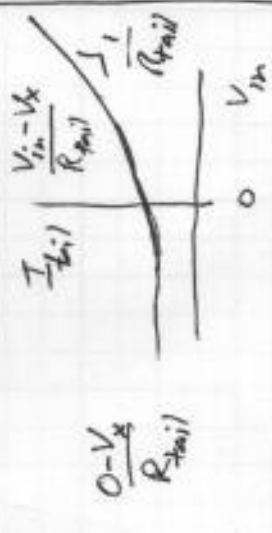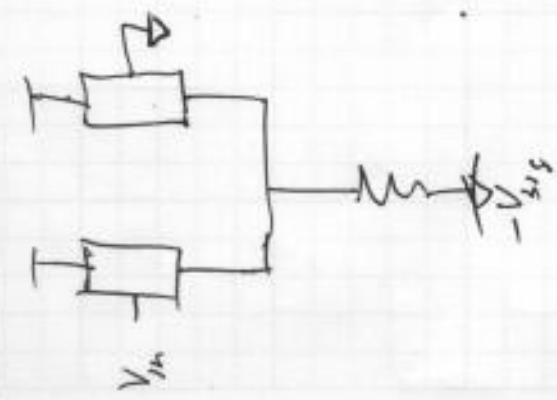$V_{in} < 0$ $I_{CA1} = 0$
 $V_{tail} = V_{B2} = V_0 = -V_0$



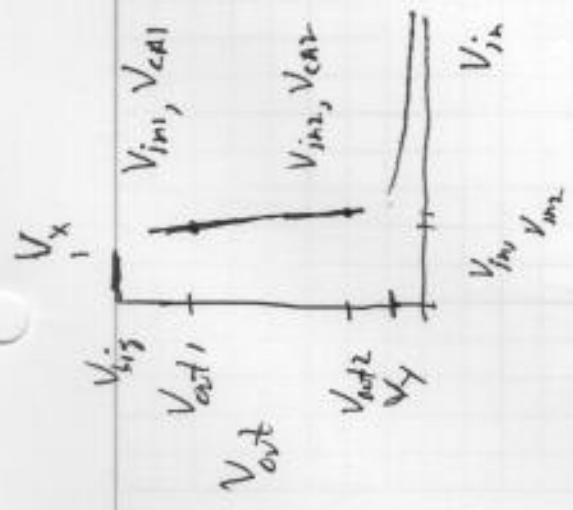

3 regions: too little, normal, too much

gain \Rightarrow input range is smaller than output range.

Why not just calculate directly?

$$V_0 = V_{CC} - I_C R$$

$$I_C = I_S \left(e^{\frac{V_{BE}}{V_{TH}}} - 1 \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$

$$V_0 = V_{CC} - R I_S \left(e^{\frac{V_{BE}}{V_{TH}}} - 1 \right) \left(1 + \frac{V_0}{V_{TH}} \right)$$

this you can solve by hand

What's the gain?

input: $\delta i_i = g_m \delta v_i$


output: $\delta i_o = g_o \delta v_o$

but I_o is const, so $\delta i_i + \delta i_o = 0$

$$\frac{\delta v_o}{\delta v_i} = -\frac{g_m}{g_o}$$



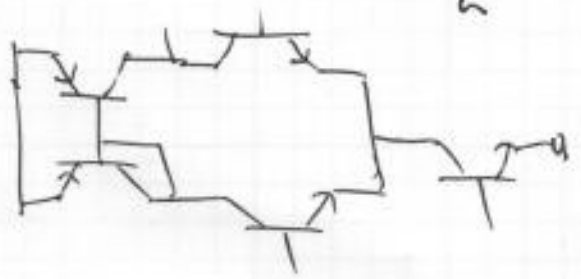essentially impossible to solve closed form by hand.
Easy for numerical soln.



linearization gives reasonable accuracy as long as you set the region of operation right

heavily depends on specs, but usually

Taylor

$$f(x, y) \text{ cont.}$$


$$f(x_0, y_0) = f_0$$

best approx near x_0, y_0 ?

$$f(x_0 + \delta x, y_0 + \delta y) = f(x_0, y_0) + \frac{\partial f}{\partial x} \delta x + \frac{\partial f}{\partial y} \delta y + \text{h.o.t.}$$

(Full non-linear) = (one D.C. operating point) + (small signal model) + h.o.t

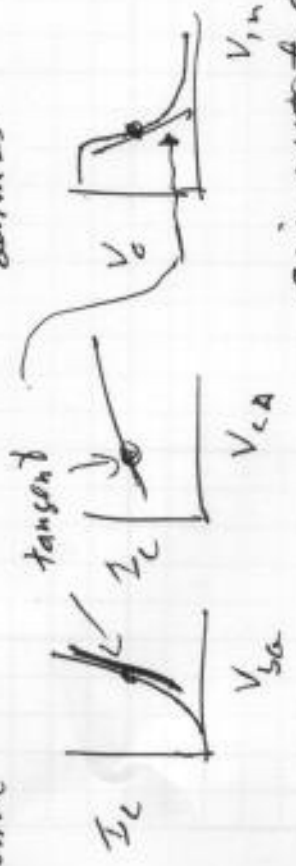hard to solve \rightarrow solve / nonlinear problem \rightarrow Taylor local derivatives \rightarrow error



gain ~~is~~ exact at that pt.

BREATH model

$$I_D = \frac{\mu C_{ox}}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

etc.


find some DC bias point $I_D(V_{GS}, V_{DS}) = I_{D0}$

$$I_D(V_{GS} + v_{gs}, V_{DS} + v_{ds}) = I_{D0} + \underbrace{\frac{\partial I_D}{\partial v_{gs}}}_{g_m} v_{gs} + \underbrace{\frac{\partial I_D}{\partial v_{ds}}}_{g_o} v_{ds} + \text{h.o.t.}$$

$$I_D = I_{D0} + i_{gs} + i_{ds}$$

$$i_{ds} = g_m v_{gs} + g_o v_{ds}$$

Back to lab:

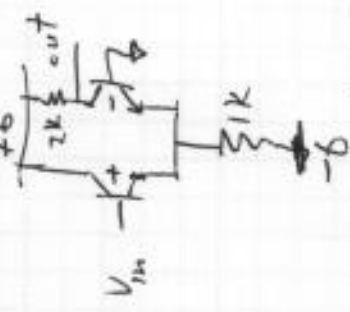

$V_{in} = 0$ DC bias point
what is V_{out} ?

looks great in feedback!
DC sweep awesome
when I build it... gah!

