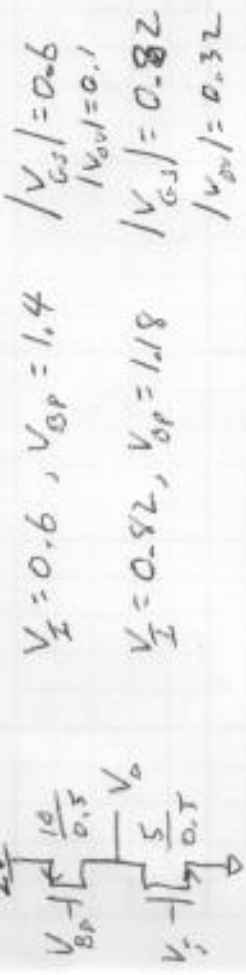


Midterm in three in class 1 page, 2 side notes
 CS amplifier
 No Silicon

Fixed division, varying bias
 scaling
 design problem

Midterm
 HW 1-4
 Lab 1

Let's try analysis of 2 quadrant bias point



today: sub- V_t "weak inversion"?

velocity ind.

and let's add $C_L = 1pF$

and calculate w_u, w_p , and C_{in}

$$C_{gs} = \frac{2}{3} (2.5 \mu m)^2 \frac{5 pF}{\mu m^2} = 8 pF + 2.5 pF$$

$$C_{gd} = 5 (0.5 \frac{\mu m}{2}) = 2.5 pF$$

140/240A 19FA W4LZ

Process: 0.5um CMOS $\mu_n C_{ox} = 200 \frac{\mu A}{V^2}$, $\mu_p C_{ox} = 100 \frac{\mu A}{V^2}$
 $V_{DD} = 2V$, $V_{th} = -V_{tp} = 0.5V$ $\lambda = \frac{1}{10V} \frac{0.5 \mu m}{L}$
 quadratic model good for $V_{ov} > 100mV$
 I_d in sub- V_t \approx quadratic model w/ $V_{ov} = 10mV$, $n = 2$
 velocity saturated when $V_{ov} > 500mV$

Quadratic

V_{ov}	100mV	320mV	0	1000mV
V_{I}	0.6	1.18	0.5	1.5
V_{DP}	0.82	1.18	1.5	0.5
V_{OUT}	1	1	1	1
I_D	10nA	100nA	10nA	2.5mA
g_m	200nS	600nS	2nS	2.5mS
r_O	500k	50k	100M	4k Ω
A_V	100	30	200	10
C_{in}	260fF	85fF	510fF	38fF
swish	(0.1, 1.9)	(0.32, 1.68)	(0.05, 1.78)	(1V, 1V)
w_p	2x10 ⁷	2x10 ⁷	10 ⁴ rad/s	250m rad/s
w_u	200x10 ⁶	600x10 ⁶	2x10 ⁶ rad/s	2.5x10 ⁶ rad/s

$V_I = 0.5 \Rightarrow V_{BP} = 1.5$ $V_{AVN} = 0 = V_{ovp}$

sub- V_T model

$I_d = I_s e^{V_{gs}/nV_T}$ $I_s = \frac{M_n C_{ox} (\frac{W}{L})}{2} (10 \text{ mV})^2 = 100 \text{ nA}$

$g_m = \frac{I_D}{nV_T} = \frac{10^{-7} \text{ A}}{50 \text{ mV}} = 2 \mu\text{S}$

$r_o = \frac{1}{\lambda I_D} = \frac{10 \text{ V}}{10^{-7} \text{ A}} = 100 \text{ M}\Omega$ (bad model)

$A_v = 200$

$\omega_p = \frac{1}{10^8 \cdot 10^{-12}} = 10^4 \text{ rad/s}$ } audio?
 $\omega_u = \frac{2 \times 10^6}{10^{-12}} = 2 \times 10^{18} \text{ rad/s}$ } bias circuits

$C_{in} = 510 \text{ fF}$

quadratic model scaling

w/ fixed $\frac{W}{L}$, if $V_{ov} \propto \beta \alpha$

- $I_d \propto \alpha^2$
- $g_m \propto \alpha$
- $r_o \propto \alpha^2$
- $A_v \propto \alpha$
- $\omega_p \propto \alpha^2$
- $\omega_u \propto \alpha$
- Power $\propto \alpha^2$

} bandwidth costs power

(Compare to vel sat. limited and sub- V_T)

USE $\sim 10 \times$ faster than $V_{ov} = 100 \text{ mV}$, but 250x more current! and low gain

Sub- V_T is slow, but good for power. & gain

$V_I = 1.5 \text{ V}$, $V_{BE} = 0.5 \text{ V}$ $E_{ch} = \frac{V_{ov}}{0.5 \mu\text{A}} = \frac{2 \text{ V}}{0.5 \mu\text{A}}$ vel. sat.

$I_D = W C_{ox} \mu_{se} \frac{V_{ov}}{L} (17 \lambda V_{ov})$

$= (5 \mu\text{m}) (\frac{5 \text{ fF}}{2 \mu\text{m}}) (10^5 \frac{1}{\text{s}}) (1 \text{ V}) = 25 \times 10^{-15+5+6} = 2.5 \text{ nA}$

$g_m = \frac{I_D}{V_{ov}} = \frac{2.5 \text{ nA}}{1 \text{ V}} = 2.5 \mu\text{S}$ $A_v = 10$

$r_o = \frac{10 \text{ V}}{2.5 \text{ nA}} = 4 \text{ K}\Omega$ } swing = (1V, 1V) 50%!

$C_{in} = C_{gs} + (1-10)C_{gs} = 10.5 \text{ fF} + 11(2.5 \text{ fF}) = 38 \text{ fF}$

$\omega_p = \frac{1}{(4 \times 10^3)(10^{-12})} = 0.25 \times 10^9 = 250 \text{ M rad/s}$

$\omega_u = \frac{2.5 \mu\text{S}}{10^{-12}} = 2.5 \times 10^6 \frac{\text{rad}}{\text{s}} (\approx 400 \text{ MHz})$

$\omega_T = \frac{2.5 \mu\text{S}}{10 \text{ fF}} = 0.25 \times 10^{12} = 250 \text{ G rad/s} (\approx 40 \text{ GHz})$

Design Ex: Spec: $A_{v0} = 50$, $A(\text{at } 1 \text{ kHz}) = 2$, $C_L = 100 \text{ fF}$

Pick $L_n = L_p \Rightarrow r_{on} = r_{op} \Rightarrow A_v = \frac{1}{\lambda V_{ov}}$

$A_v = \frac{10 \text{ V}}{V_{ov}} \frac{0.5 \mu\text{A}}{L}$ pick $L_n = 0.5 \mu\text{m}$

$A_v = \frac{10 \text{ V}}{V_{ov}}$ Calc $V_{ov} = 200 \text{ mV}$

Calc $g_m = W_n C_{ox} = 2 \times 10^9 \cdot 10^{-13} = 200 \mu\text{S}$ assume $C_{ox} = C_L$

Calc $(\frac{W}{L})_n^2 = \frac{5 \mu\text{A}}{M_n C_{ox} V_{ov}} = \frac{200 \mu\text{S}}{200 \mu\text{A} (0.2 \text{ V})} = 5$ Calc $W_n = 5 L_n = 2.5 \mu\text{m}$

Pick $V_{ovp} = V_{ovn}$

$I_{Dn} = M_n C_{ox} (\frac{W}{L})_n V_{ovn}^2 = M_n C_{ox} (\frac{W}{L})_p V_{ov,p}^2$

$I_{D0} = I_{OP}$, $L_n = L_p$, $M_{Cox} = 2M_p C_{ox} \Rightarrow W_p = 2W_n = 5\mu m$
 $C_{in} = C_{SSn} + C_{SDn}(1-A)$
 $= \frac{2}{3}WL C_{ox} + 2W C_{oe}(1-50)$ Miller
 $= \frac{2}{3}(2.5\mu m)(0.5\mu m) \frac{5FF}{\mu m^2} + 52(2.5\mu m)(0.5\mu m)$
 $= 4FF + 65FF$
 $= 70FF$
 $I_0 = \frac{M_{Cox} W}{2} V_{ov}^2 = \frac{500\mu A}{2} (0.1V)^2 = 20\mu A$
 $\sqrt{I_0} = 4.5 \mu A^{0.5}$
 $\sqrt{I_0} = 2.5 / 0.5$

What if spec said $A_v = 500$?
 pick $L_n = L_p$
 $A_v = \frac{10V}{V_{ov}} \left(\frac{L}{0.5\mu m} \right)$
 $= 100 \left(\frac{L}{0.5\mu m} \right)$
 calc $L = 2.5\mu m$
 $g_m = 200\mu A/V = M_n C_{ox} \left(\frac{W}{L} \right) (V_{ov})$
 $= 200\mu A/V \left(\frac{W}{L} \right) (0.1V)$
 calc $\left(\frac{W}{L} \right) = 10$ $W_n = 25\mu m$

$C_0 = 100FF?$
 $C_{SDn} = (2.5\mu m)(0.5\mu m) = 1.25FF$
 $C_{SDp} = 2C_{SDn} = 2.5FF$
 $C_0 = C_L + C_{SDn} + C_{SDp} = 103.75FF$ noise

$C_{in} = \frac{2}{3}WL C_{ox} + (1-A)W C_{oe}$
 $= \frac{2}{3}(2.5\mu m)(2.5\mu m)(5\frac{FF}{\mu m^2}) + 50(2.5\mu m)(0.5\frac{FF}{\mu m})$
 $= 200FF + 6.3PF$
 big problem for input cap spec!
 Solutions:
 1) 2 stages
 2) cascode
