

HW6 Due Friday 10/18
 HW7 Due Wed 10/23
 HW8 Due Wed 10/30

Midterm Nov 1 in class on HW1-8

Feedback & stability

why "jw"?

graphical (HG) and (HG)

Phase margin

Poles move in feedback

1 pole
2 poles

In the time domain

negative feedback looks good

$$A_{cl} = \frac{A}{1 + Af}$$

positive feedback generally not



buffer



latch (permanent?)



inverter w/ hysteresis

if phase around loop = ±180°, positive feedback!



Feedback is great

- set stable gain w/ ratio of components

- build math operations

- raise/lower input/output impedances [later] appropriately

but

there be dragons!

Sometimes feedback systems oscillate

need to understand poles, Heaviside transform

output derivatives introduce negative phase. in HG

$$v_i = -w \int \frac{v_o}{f} dt$$

$$i_o = C \frac{dv_o}{dt}$$

$$RC \frac{dv_o}{dt} + v_o = v_i$$

$$i_o = \frac{v_i - v_o}{R}$$


say $v_o = A \sin wt$

$$\frac{dv_o}{dt} = wA \cos wt$$

$$\frac{d^2 v_o}{dt^2} = -w^2 A \sin wt$$

$$\frac{d^3 v_o}{dt^3} = -w^3 A \cos wt$$


$$d^4 v_o = w^4 A \sin wt$$

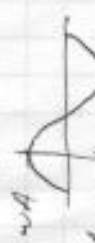

$RC \frac{dv_o}{dt} + v_o = v_i$ $v_i = V_i \sin(\omega t)$

$v_o = A \sin \omega t + B \cos \omega t =$

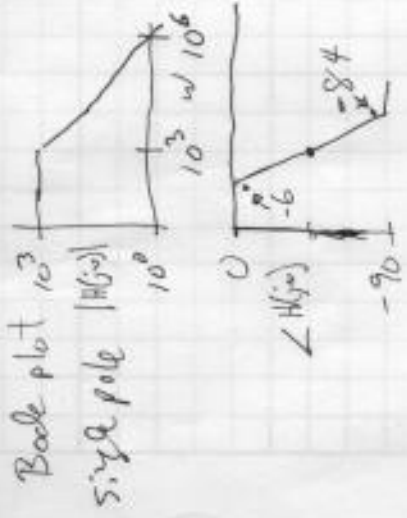$RC \frac{dv_o}{dt} = RC \omega A \cos \omega t - RC \omega B \sin \omega t$



$H(s) = \frac{1}{1 + s/\omega_p}$

$H(j\omega) = \frac{1}{1 + j\omega/\omega_p}$

$H(j\omega) \approx \begin{cases} 1 & \omega \ll \omega_p \\ \frac{1}{1+j} & \omega = \omega_p \\ \frac{\omega_p}{j\omega} & \omega \gg \omega_p \end{cases}$

$j\omega$ just looks like derivatives effect on \sin, \cos
 at high freq, derivative of output dominates, w/ 90° positive phase shift relative to output
 but that derivative term is approx v_i'
 so output must lag v_i'




$H(s) = \frac{1}{1 + s/\omega_p} = \frac{\omega_p}{s + \omega_p}$

$|H(j\omega)| = \frac{|\omega_p|}{|j\omega + \omega_p|} = \frac{|\omega_p|}{\sqrt{\omega^2 + \omega_p^2}}$

$|H(j\omega)| = \frac{|\omega_p|}{R}$

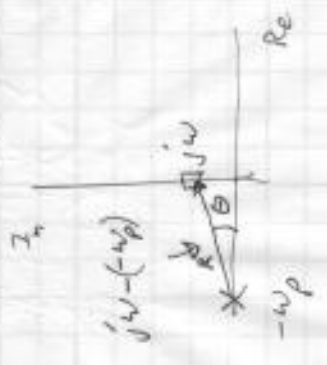$\angle H(j\omega) = \angle \omega_p - \angle R e^{j\theta} = -\theta$





Above $10^4 \frac{\text{rad}}{\text{s}}$
 $\angle H(jw) = -180$

looks like positive feedback!
 amplifier sings!
 (rings in oscillation)



error = 2 * 60

Bode plot of open loop amplifier tells you about the stability of the closed loop amplifier.

What about the closed loop transfer function?

$$A_{CL} = \frac{A}{1+AF}$$

$$= \frac{N(s)}{D(s)} \frac{1}{1 + \frac{N(s)F}{D(s)}} = \frac{N(s)}{D(s) + FN(s)}$$

Roots of characteristic polynomial are poles of CL sys
 roots depend on N, D, F - everything.

peaks what if $f = 0.001$? 0.005 ? 0.01 ?

need a measure of how close we are to trouble, defined as when

$$\angle H(jw) = -180$$

$$|H(jw)| \geq 1$$

phase margin

$$PM = \angle H(jw) - (-180)$$

PM desired varies
 30-80° spec
 45-60 typ. EE128



1 pole, passive feedback (f near 0. f < 1)

$$A = \frac{A_0}{1+s/w_p}$$

$$A_{CL} = \frac{1}{1 + \frac{s}{w_p(1+A_0f)}} \approx \frac{1}{f} \frac{1}{1 + \frac{s}{w_{pCL}}}$$

$$w_{pCL} = w_p(1+A_0f)$$



s-plane

w, store name