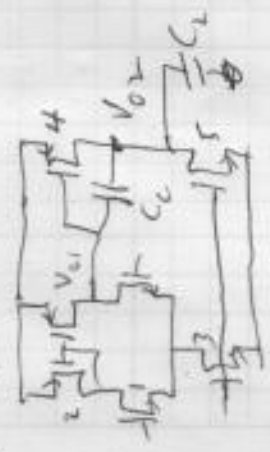


2 stage



$$\begin{aligned}
 G_{m1} &= g_{m1} \\
 R_{O1} &= r_{O1} || R_{O1b} \\
 G_{m2} &= g_{m2} \\
 R_{O2} &= r_{O2} || R_{O2b} \quad (|| R_{load}) \\
 C_{O1} &\approx C_{SS4} \\
 C_{O2} &\approx C_L \\
 C_C &=? \quad N_{O2}
 \end{aligned}$$



what about  $C_C$ ?

Miller multiplied

$$C_{Miller} = C_C (1 - A_{v2}(s))$$

Can push  $\omega_p$  to lower frequency with

less capacitance than just adding to  $C_{O1}$

$\Rightarrow$  good. Smaller caps are cheaper (die area)

Magically, it also pushes  $\omega_p$  to higher freqs

$\Rightarrow$  great. More bandwidth

"pole splitting"

If  $C_C = 0$  (it doesn't,  $C_{gd}$  at least, but if)

$$A_{v1} = \frac{A_{v1DC}}{1 + s/\omega_{p1}}$$

$$A_{v1DC} = -G_{m1} R_{O1}$$

$$\omega_{p1} = \frac{1}{R_{O1} C_{O1}}$$

$$A_{v2} = \frac{A_{v2DC}}{1 + s/\omega_{p2}}$$

$$A_{v2DC} = -G_{m2} R_{O2}$$

$$\omega_{p2} = \frac{1}{R_{O2} C_{O2}}$$

2 poles

mathematically never unstable  $\angle A(j\omega) \rightarrow -180$   
phase margin sets to 0 threshold

Compensation

Changing freq response of the open loop amplifier (typically by adding capacitor)

to improve closed-loop performance

e.g. 1) to make it stable

2) to achieve desired phase margin (settling properties)


2-stage examples

$$A_r = \frac{10^3}{(1 + s/\omega_p)^2}$$

set PM to  $-45^\circ$

1) add cap to  $C_1$

2) add cap to  $C_2$

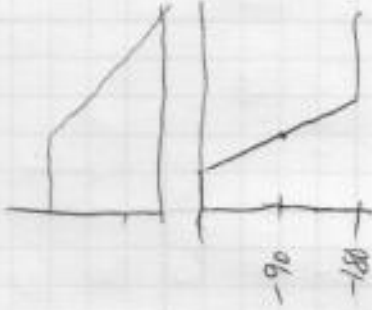

to move 1 pole  $10^3$  lower freq, need

$10^3$  times as much capacitance.

- So 1) increase  $C_{01}$  by  $1000\times$
- 2) increase  $C_{02}$  by  $1000\times$

problem: might not know  $C_L$

solution #1 tricky - need bounds on  $C_L$

solution #2 OK, but may unnecessarily

compromise performance.

if we separate poles a lot




to set PM =  $45^\circ$  need  $\omega_{p2} \gg \omega_{p1}$

to set PM =  $70^\circ$  need  $\omega_{p2} \gg 3\omega_{p1}$

what is  $\omega_{min}$  CL gain w/ no

compensation?

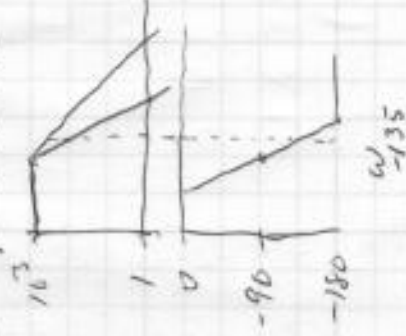


need  $|AF| \leq 1$

when  $\angle AF = -135^\circ$

$$|A|_{\omega_{135}} \approx 100$$

need  $f \leq 0.01$

$$A_{CL} \geq \frac{1}{f} = 100$$

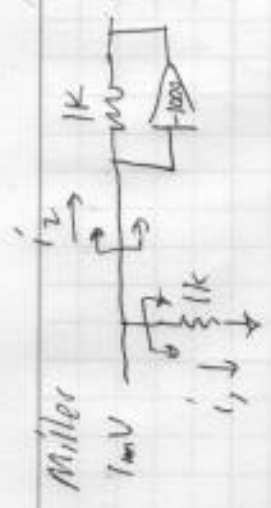

$$i_1 = \frac{1mV}{1k} = 1\mu A$$


$$i_2 = \frac{1000(1mV - 1000mV)}{1k} = 1.001mA$$

$$Z_{in2} = \frac{1k}{1-A} \approx 1\Omega$$

$$i = C \frac{d(v_{in} - 1000v_{in})}{dt} = 40001C \frac{dv_{in}}{dt} \quad C_{eq} = (1-A)C$$


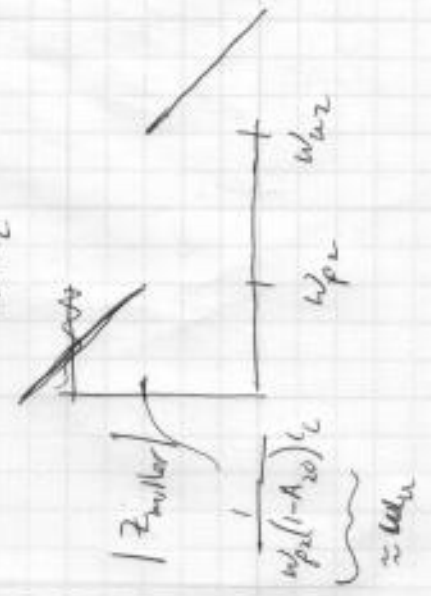
$$Z_{miller} = \begin{cases} \frac{1}{\omega(1-A_{20})C_c} & \omega < \omega_{p2} \\ \frac{1}{\omega C_c} & \omega > \omega_{a2} \end{cases}$$



$$A = \frac{A_{2DC}}{1 + \omega/\omega_{p2,u}}$$

$$A_{2,DC} = -G_{m2}R_{o2}$$

$$C_{miller} = \begin{cases} (1 + G_{m2}R_{o2})C_c & \omega < \omega_{p2,u} \\ C_c & \omega \gg \omega_{p2,u} \end{cases}$$





$\omega_{p2,u}$

$$\begin{aligned}
 Z_{\text{Miller}} &= \frac{1}{S \left[ 1 + \frac{A_{v2,0}}{1 + \frac{S}{\omega_{p2}}} \right]} C_c \\
 &= \frac{1 + \frac{S}{\omega_{p2}}}{S \left[ 1 + \frac{S}{\omega_{p2}} + A_{v2,0} \right]} C_c \\
 &= \frac{1 + \frac{S}{\omega_{p2}}}{S (1 + A_{v2,0}) \left( 1 + \frac{S}{\omega_{p2}} \right)} C_c
 \end{aligned}$$

$$\omega_{\text{PZM}} = \omega_{p2} (1 + A_{v2,0}) \approx \omega_{u2}$$


$$Z_{\text{Miller}} = \begin{cases} \frac{1}{j\omega(1+A_{v2,0})C_c} & \omega < \omega_{p2} \\ \frac{1}{j\omega_{p2}(1+A_{v2,0})C_c} & \omega_{p2} < \omega < \omega_{u2} \\ \frac{1}{sC_c} & \omega_{u2} < \omega \end{cases}$$

constant, real

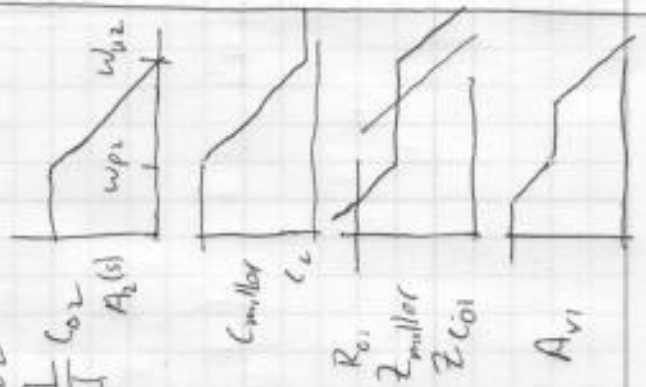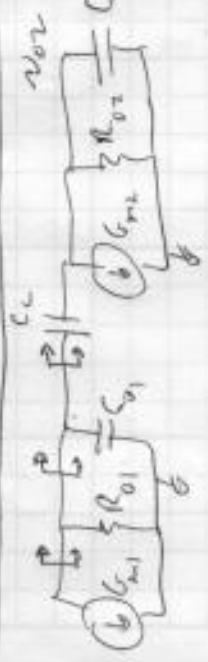

No virtual ground


$G_m$  calc

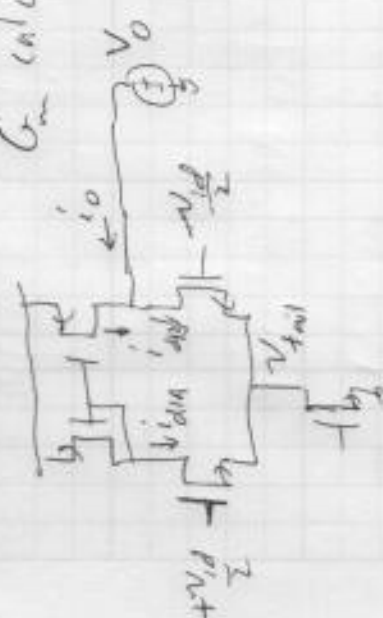

$$i_o = i_{d1b} - i_{d1a} = g_{m1} \left( \frac{v_{id}}{2} - v_{tail} \right) = -g_{m1} v_{id}$$

$$G_{m1} = g_{m1}$$

$R_o$  calc

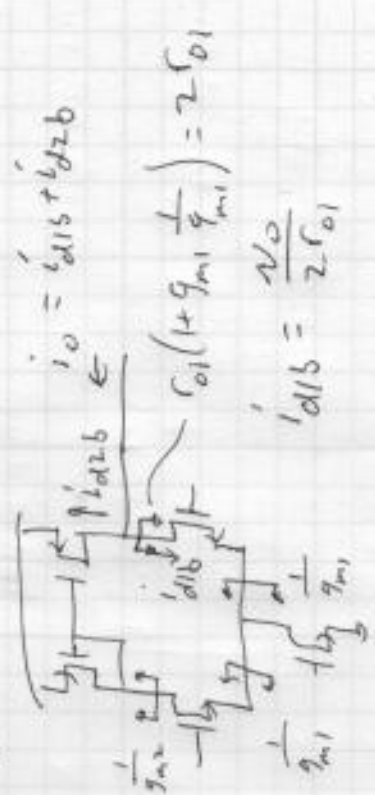

$$i_o = i_{d1b} + i_{d2b}$$

$$i_{d1b} = \frac{v_o}{2r_{o1}} + \left( \frac{v_o}{2r_{o1}} + \frac{v_o}{r_{o2}} \right) = v_o \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right)$$

$$i_{d2a} = i_{d1b}$$

$$i_{d2b} = i_{d1b} + \frac{v_o}{r_{o2}}$$

$$i_o = \frac{v_o}{2r_{o1}} + \left( \frac{v_o}{2r_{o1}} + \frac{v_o}{r_{o2}} \right) = v_o \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right)$$

$$R_{o1} = r_{o1} || r_{o2}$$