

2 stage w/comp
 Poles & zeros
 Common mode gain
 slow rate
 current mirror op-amp

Uncompensated Compensated w/c_c

$$\omega_{p1} = \frac{1}{C_{M2} R_{M2}}$$

$$\omega_{p2} = \frac{G_{m2}}{C_1 + C_2 + R_{M2}^2 C_c}$$

$$\omega_{pm} = \frac{G_{m2}}{2C_{SS2}}$$

$$\omega_{zm} = 2\omega_{pm}$$

$$\omega_{zc} = \left(\frac{G_{m2}}{C_{M2}} \right) \frac{RA}{RA}$$


$$\frac{G_{m2}}{C_c} \text{ if present}$$

$$\omega_{uc} = \frac{G_{m2}}{C_c}$$

iff so designed

but low gain, output swing issues
 so, add 2nd stage = gain swing
 but stability & paino

Some options: current mirror op-amp.

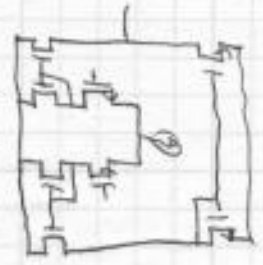

good swing

low gain

telescopic cascode
 good gain, terrible swing

Cascode current mirror

folded cascode



± single pole

PM ≈ 90

unity gain
 stable

Feedback

2 stage, uncomp.



oscillates



ok if f < 1

2 stage, comp or single pole

looks like



$$A_{CL} \approx \frac{1}{A_F}$$


$$\text{error} \approx \frac{1}{A_F}$$

$$\omega_{p,CL} = f \omega_{uc}$$


$$= \frac{\omega_{uc}}{A_{CL}}$$

$$\omega_{u,CL} = \omega_{uc}$$

Common mode

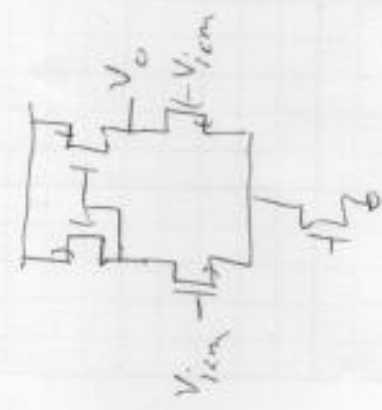


1/2 circuit

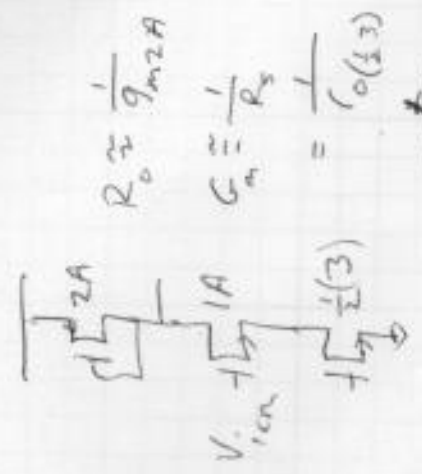

$$A_{v_{cm}} = -g_m R_o = \frac{-1}{2g_{m2A} r_{o3}} \quad C_{MRR} = \frac{A_{v_{cm}}}{A_{v_{cm}}}$$

2 stage

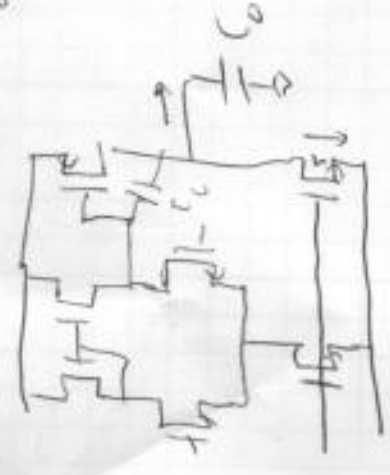

$$v_{o2} = v_{o1} + v_{c_c}$$


$$\frac{dv_{o2}}{dt} = \frac{dv_{o1}}{dt} + \frac{dv_{c_c}}{dt}$$

$$\left. \frac{dv_o}{dt} \right|_{\min} = \frac{-I_{D5}}{C_o}$$

$$\left. \frac{dv_o}{dt} \right|_{\max} = \frac{I_{D5}}{C_o} \gg \frac{I_{D5}}{C_o}$$

Right? what about C_c ?

slow rate

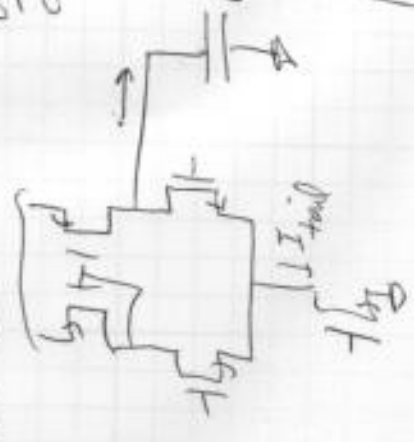

$$\frac{dv_o}{dt} = \frac{i_c}{C_o}$$

max $\frac{dv_o}{dt}$ is called min slow rate

Non linear behavior
H(s) no longer applies

$$i_c \max = I_{tail}$$

$$i_c \min = -I_{tail}$$

$$v_{o2} = A_{v2} v_{o1}$$

$$\frac{dv_{o1}}{dt} = \frac{1}{A_{v1}} \frac{dv_{o2}}{dt}$$

$$\frac{dv_{o2}}{dt} \left(1 - \frac{1}{A_{v1}}\right) = \frac{dv_{c_c}}{dt} = \frac{i_c}{C_c}$$

need to check both caps C_{o2} and C_c and their currents

$$\text{slow rate low} = \min\left(\frac{-I_{tail}}{C_c}, -\frac{I_{D5}}{C_{o2}}\right)$$

$$\text{slow rate high} = \frac{I_{tail}}{C_c}$$

PMOS-independent biasing

and temp sensing - and voltage reference


$$I_{ref} = \frac{V_{DD} - (V_{th} + V_{ov})}{R}$$

would like a stable reference over changes in

Process V_{th} (max, λ , ...)

Voltage $V_{DD} = 0.8 - 1.6V$

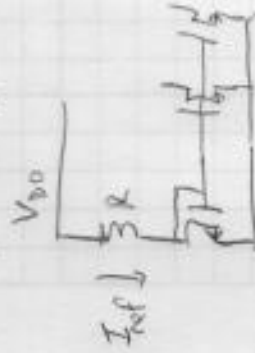T $-40 - +95C$, $0 - 70C$, $-55 + 125C$
industrial consumer auto mil



$$V_{th} = V_{th0} - \frac{2mV}{K} \Delta T$$

Enforce that $I_{D2} = I_{D1}$



$$K(V_{ov1} - I_{D2}R)^2 = V_{ov1}^2$$

$$V_{ov1} = \sqrt{K} (V_{ov1} - I_{D2}R)$$


$$\frac{V_{ov1}}{\sqrt{K}} - V_{ov1} = -I_{D2}R$$

$$I_{D2}R = (1 - \frac{1}{\sqrt{K}}) V_{ov1}$$

$$I_{D2}R = \frac{1}{2} V_{ov1}$$

$$V_{ov2} = V_{ov1} - \frac{1}{2} V_{ov1} = \frac{1}{2} V_{ov1}$$

Pick $K=4$

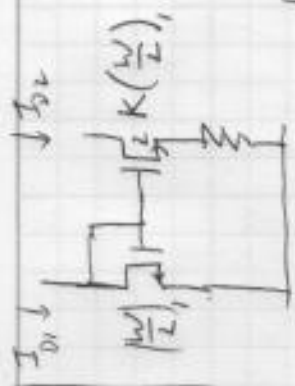

if quadratic $(\frac{V_{ov}}{L} < \frac{1V}{\mu m})$

$$I_{D1} = \frac{2I_{D1}}{V_{ov1}}$$

$$= \frac{2I_{D1}}{2I_{D1}R}$$

$$= \frac{1}{R} !$$

"const gm bias"

but we ignored λ - use log channels

ignored $I_{D1} = I_{D2} = 0$

$$I_{D1} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{ov1})^2$$

$$I_{D2} = K \left(\mu_n C_{ox} \left(\frac{W}{L}\right)_2\right) (V_{ov2} - I_{D2}R)^2$$


K is an integer. $K=4$ common

← looks like a source follower at some point

$$V_{ov1} = 2I_{D2}R$$

$$I_{D1} = I_{D2}$$

indep of $V_{DD}, V_{th}, \mu_n, \tau$


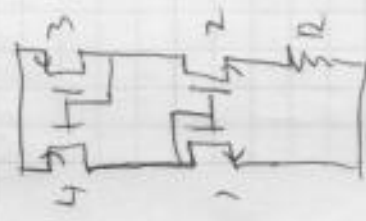


$$\frac{\partial I_{02}}{\partial V_{D0}} = \frac{I_0}{V_{D0}} = \frac{1}{r_{04}(2k-1)}$$

(much vlsly algebra)

so use long-channel, or cascode or LDC.

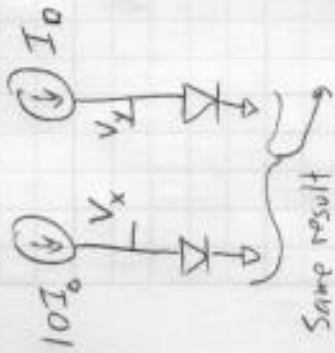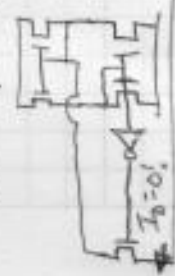
Startup - what if $I_{D1} = I_{D2} = 0$ $V_{GS1} \approx 0$



$$V_x = V_{TN} \ln \frac{10I_0}{I_S}$$

$$V_y = V_{TN} \ln \frac{I_0}{I_S}$$
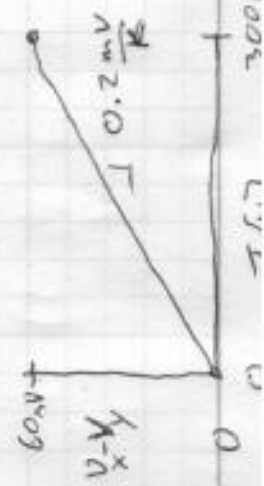
$$V_x - V_y = V_{TN} \left(\ln \frac{10I_0}{I_S} - \ln \frac{I_0}{I_S} \right) = V_{TN} \ln(10)$$



More fun: Dardar's reference, P141

$$I_0 = I_S \left(e^{\frac{V_D}{V_{TN}}} - 1 \right) \approx I_S e^{\frac{V_D}{V_{TN}}}$$

$$V_D = V_{TN} \ln \frac{I_0}{I_S} \quad \frac{60mV}{\text{decade}} @ R.T. \quad \text{decade } 300K$$

$$V_{TN} = \frac{k_B T}{q}$$

V_{TN} is Proportional To Absolute Temperature



$$V_b = V_{TN} \ln \frac{I_{fixed}}{I_S}$$

temp response?

$$V_{TN} = \frac{k_B T}{q} \quad \text{Contributor, positive coeff.}$$


factor of ≈ 2 over automotive temp.

I_S increases by 10^5 from -40 to $+85$ C

result: at const current, V_b has a

negative temp coeff $\approx -2mV/K$

Same result

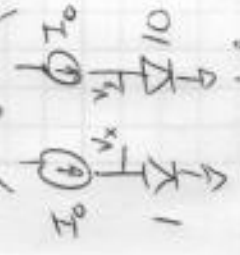

true even if T changes w/