

Midterm Friday

- NW1-8
- labs 1-3
- 2 pass, 4 sides 100g
- Supply indep biasing
- Bandgap
- temp sensor

Simplist fix - V_{th} reference

$$I_{ref} = \frac{V_{GT}}{R_2}$$



$$V_{th} + V_{ov1} = V_{th} + \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} (\frac{W}{L})_1}}$$

can have much smaller variation
 still get 3x variation in I_{D1} from 1.6 \rightarrow 0.9, but

0.9-1.6

Bad. Why do I care?

$\pm 3x$ variation
 supply variation
 Affects bias currents




$\Rightarrow g_m, r_o, C_j (C_{db}, \dots)$
 \Rightarrow performance specs

\rightarrow overdesign to meet the worst case, waste power elsewhere

Stability i complicates compensation


temp-indep

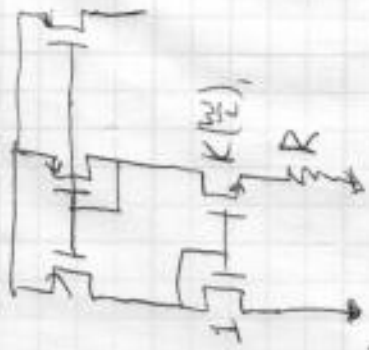

$K=4$
 $V_{ov1} = 2V_{ov2}$
 $V_{ov2} = I_{D2} R$



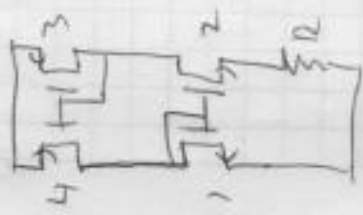Stable equilibrium
 I_{D1}
 I_{D2}
 nominally unstable equilibrium
 BUT not always





$$\frac{\partial I_{D2}}{\partial V_{D0}} = \frac{I_0}{V_{D0}} = \frac{1}{r_{D4}(2k-1)}$$

(much vlsly algebra)

so use long-channel, or cascode or both.

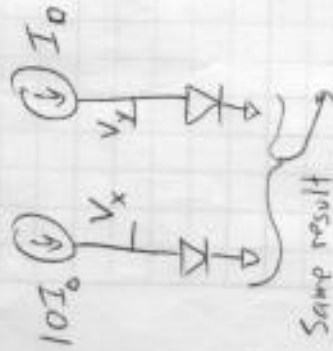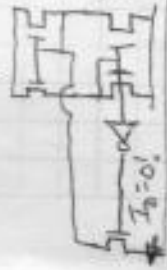
startup: what if $I_{D1} = I_{D2} = 0$ $V_{GS1} \approx 0$




$$V_x = V_{TH} \ln \frac{10I_0}{I_S}$$

$$V_y = V_{TH} \ln \frac{I_0}{I_S}$$
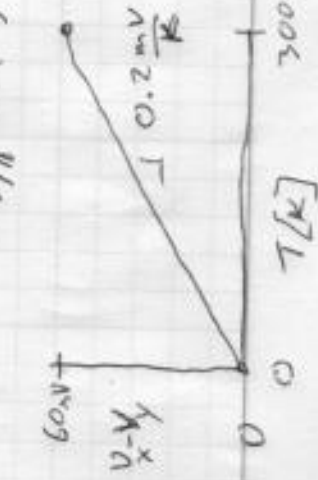
$$V_x - V_y = V_{TH} \left(\ln \frac{10I_0}{I_S} - \ln \frac{I_0}{I_S} \right) = V_{TH} \ln(10)$$



Same result

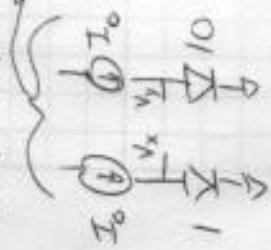

have even if I_0 changes w/ temp.

More fun: Bandgap reference PTAT

$$I_0 = I_S \left(e^{\frac{V_{D1} - V_{D2}}{V_T}} - 1 \right) \approx I_S e^{\frac{V_{D1} - V_{D2}}{V_T}}$$

$$V_D = V_{TH} \ln \frac{I_0}{I_S} \quad 60mV \text{ @ R.T. divide } 300K$$

$$V_{TH} = \frac{k_B T}{q}$$

V_{TH} is Proportional To Absolute Temperature



$$V_D = V_{TH} \ln \frac{I_{fixed}}{I_S}$$

temp response?

$$V_{TH} = \frac{k_B T}{q} \text{ contributes positive coeff.}$$

factor of ≈ 2 over automotive temp.


I_S increases by 10^5 from -40 to $+85$ C

result: at const current, V_D has a

negative temp coeff $\approx -2mV/K$

depends on current density
may decrease w/ decrease in current

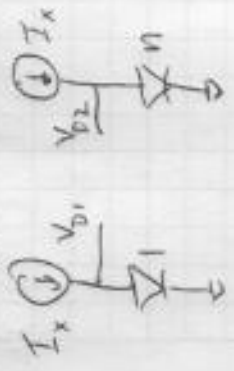Say V_{D1} temp. $\approx -2 \frac{mV}{K}$
 $V_{D1} = 0.6V$ at $300K$



if I_x constant

$$V_{D1} = V_{D1}(300K) - \left(\frac{2mV}{K} \right) \Delta T$$

$$V_{D1} - V_{D2} = V_{TH} \ln(n)$$

say $n=10$




goal: $V_{D1} + M(V_{D1} - V_{D2}) = V_{out}$
 $V_{out} = V_{D1}(300K) - \frac{2mV}{K} \Delta T + M \left(\frac{2mV}{K} \right) T$
 choose $M=10$

$$V_{out} = 0.6V - \frac{2mV}{K} \Delta T + \frac{2mV}{K} (300 + \Delta T)$$

$$= 1.2V + \left(-\frac{2mV}{K} + \frac{2mV}{K} \right) T$$

$= 1.2V$ indep. of $T!$
 "bandgap reference"

How?

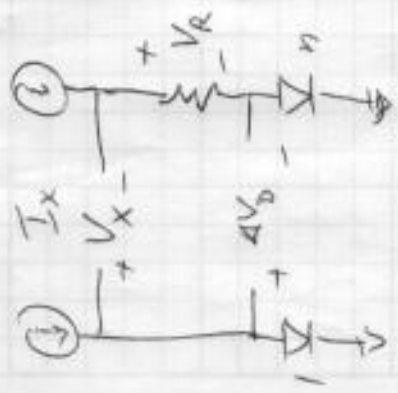

Increase I_x until $V_x = 0$

$$V_R = I_x R_1$$

if $V_x = 0$ then

$$V_R = 4V_D = V_{TH} \ln(n)$$


= PTAT!



$$V_{out} = V_{D2} + I_x (R_1 + R_3)$$

$$= V_{D2}(300K) + \alpha \Delta T + \underbrace{V_{TH} \ln(n) \frac{R_1 + R_2}{R_1}}_{\frac{R_1 + R_2}{R_1} \frac{k_B}{q} \ln(n) T}$$

choose to be $-\alpha$

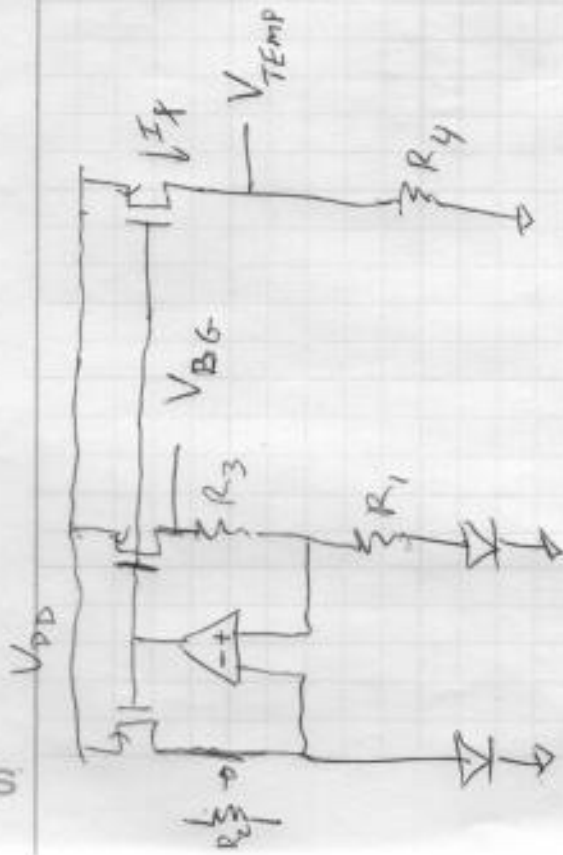

$$V_{TEMP} = I_x R_4 = V_{TH} \ln(n) \frac{R_4}{R_1}$$

Result

1.2V



300K 400K
-40C 25C 125C

10s of mV of variation over temp.