

PROBLEM SET #6

Issued: Tuesday, March 3, 2009

Due: Tuesday, March 10, 2009, **5:00 p.m.** in the EE 140 homework box in 240 Cory

1. For the high-swing cascode mirror shown in Figure PS6-1 answer the following questions:
 - (a) Calculate W such that the minimum output voltage for which both M_1 and M_2 are in saturation is $0.5V$. Assume that M_3 - M_5 can provide appropriate gate biases for M_1 and M_2 .
 - (b) Calculate W_5 in order to achieve the minimum output voltage calculated in (a).
 - (c) Briefly explain the function of M_4 .
 - (d) What is the output resistance of this current source?
 - (e) What is the change in I_{OUT} for $\Delta V_{OUT}=1V$?
 - (f) What is the resistance seen by the ideal current source I_{IN} that biases M_3 and M_4 ?
 - (g) Calculate input voltages V_{IN1} and V_{IN2} .
 - (h) Replace transistors M_5 and M_6 with one diode connected device. What is the W of the new device?

$$I_{IN} = 100\mu A, \quad L = 1\mu m \quad C_{ox} = 5 \frac{fF}{\mu m^2}, \quad \mu_n = 450 \frac{cm^2}{Vs}, \quad V_{th0} = 0.6V, \quad \lambda = 0.02V^{-1}, \quad \gamma = 0$$

 


Figure PS6-1

2. Use half-circuit concepts to determine the differential-mode and common-mode gain of the circuit shown in Figure PS6-2. Neglect r_o , r_u and r_b . Then calculate the differential-mode and common mode input resistance.

 


Figure PS6-2

 


Figure PS6-3

3. Use half circuit analysis to determine (i) the differential-mode gain A_{dm} , (ii) the common-mode gain A_{cm} , (iii) the common-mode input to differential-mode output gain A_{cm-dm} , and (iv) the differential-mode input to common-mode output gain A_{dm-cm} for a resistively loaded differential pair shown in Figure PS6-3 with mismatched resistive loads, R_1 and R_2 . Assume that $R_1=10.1\text{k}\Omega$, $R_2=9.9\text{k}\Omega$, also assume $r_{o1}=r_{o2}=\infty$, and $R_{tail}=1\text{M}\Omega$. Use the following process parameters: $t_{ox}=8\text{ nm}$, $\mu_n=450\text{ cm}^2/\text{VS}$, $L_d=0.09\text{ }\mu\text{m}$, $W=10\text{ }\mu\text{m}$, $L=1\text{ }\mu\text{m}$. Then calculate the input offset voltage assuming a W/L mismatch of 2 percent besides the resistive load mismatch. Ignore the difference of the device threshold in your offset calculation.

4. This problem concerns the actively loaded MOS amplifier shown in Figure PS6-4.

- (a) Design the amplifier to achieve a differential small signal gain of 200. Bias M_1 and M_2 with $100\text{ }\mu\text{A}$ of current each. The maximum output swing should be 2V peak-to-peak. Do not use overdrive voltages lower than 150mV . Choose W_5 and W_6 so that the bias currents of M_5 and M_6 are exactly the same at the quiescent point. Use the smallest channel lengths that satisfy the gain requirements. All transistors should have the same channel lengths.
- (b) If the desired output voltage at the quiescent point is in the middle of output signal range, what is the systematic input referred voltage offset of this amplifier?
- (c) Due to manufacturing imperfections threshold voltages, channel widths and channel lengths can differ from designed by ΔV_{th} , ΔW , ΔL , where $|\Delta V_{th}| < 10\text{mV}$, $|\Delta W| < 5\text{nm}$, $|\Delta L| < 5\text{nm}$. What is the worst case input referred voltage offset due to mismatches?

$$V_{DD} = 1.8\text{V}, V_{SS} = -1.8\text{V}, V_{th0,n} = V_{th0,p} = 0.5\text{V}, \alpha_N = \frac{dX_d}{dV_{DS}} = 0.02 \frac{\mu\text{m}}{\text{V}}, \alpha_P = \frac{dX_d}{dV_{SD}} = 0.04 \frac{\mu\text{m}}{\text{V}},$$

$$\mu_n C_{ox} = 250 \frac{\mu\text{A}}{\text{V}^2}, \mu_p C_{ox} = 100 \frac{\mu\text{A}}{\text{V}^2}, \gamma = 0, L_d = 0$$

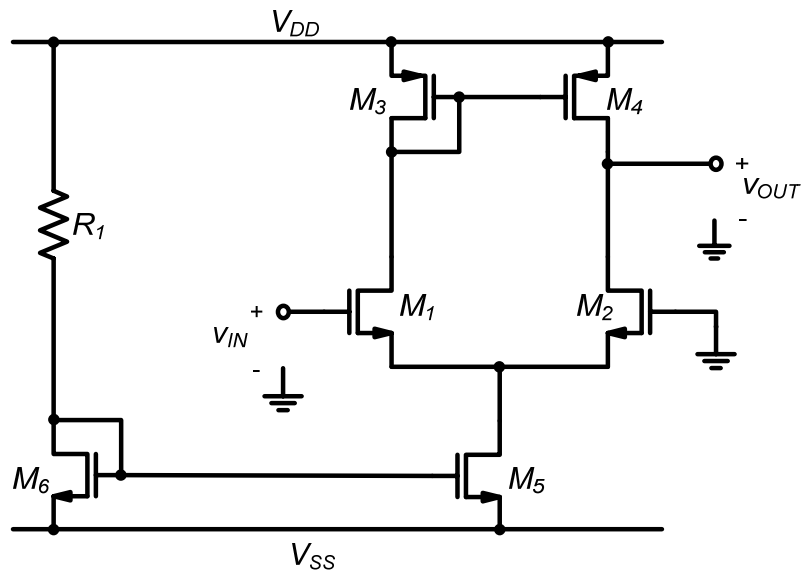


Figure PS6-4