

Lecture 10: High Swing Current Sources

• Announcements:



- ↳ Monday Labs: due to holiday next week, shift to the following Monday
- ↳ Monday Lab#1's are due in the 140 Box on Tuesday next week (per Travis's email)

• Lecture Topics:

- ↳ Output Swing (Headroom) (cont.)
- ↳ High Swing Current Sources
- ↳ Current Source Matching Considerations

• Last Time:

Issue: Output Swing (Headroom)

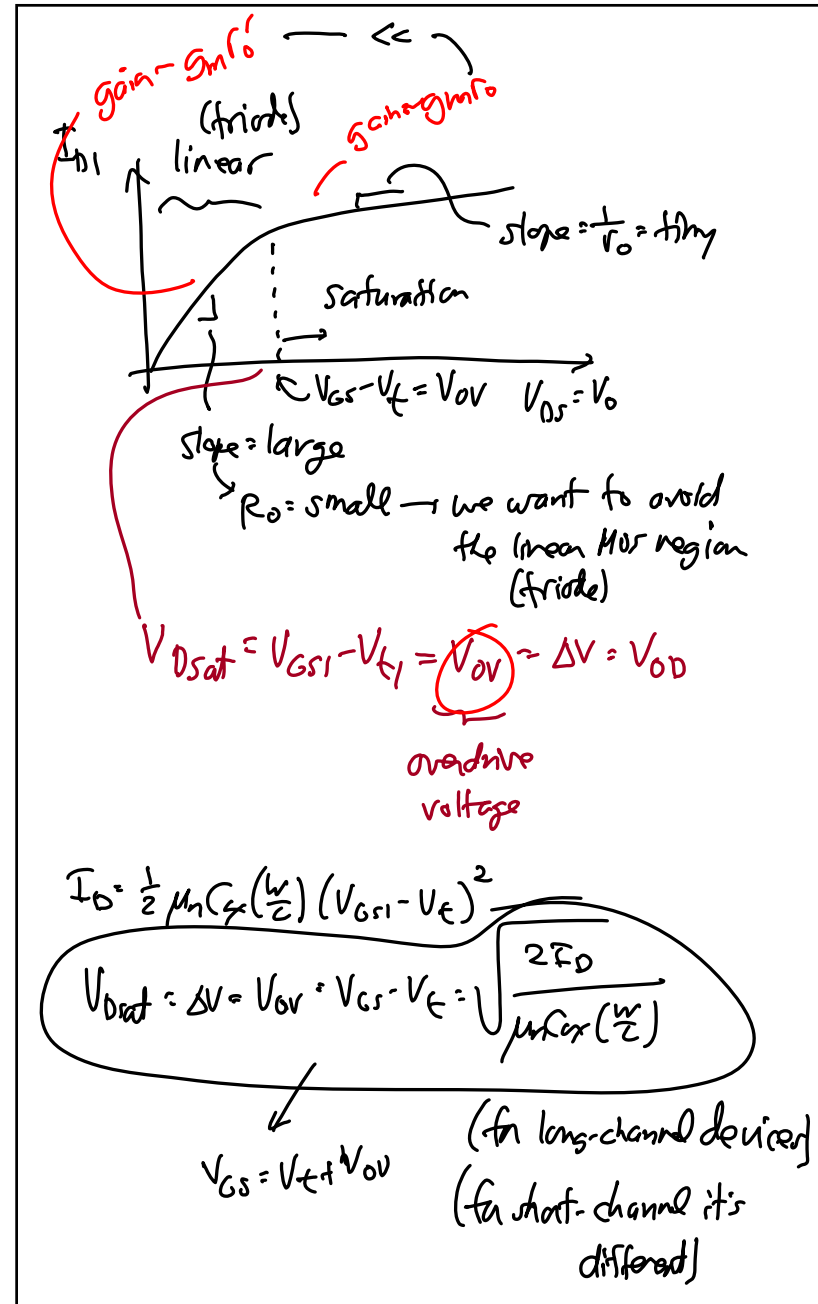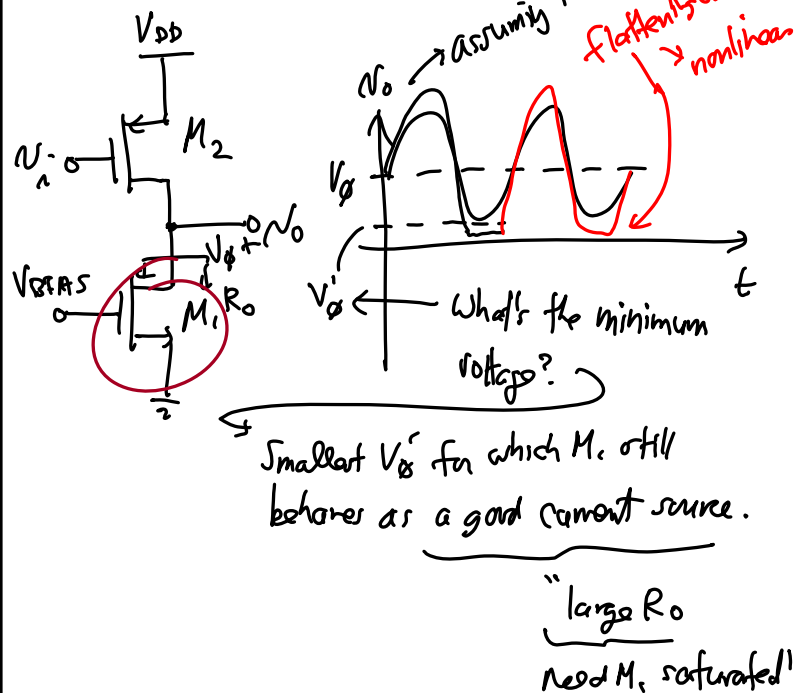


The min. voltage that still keeps M_1 as a good current source:

$$V_{omh} = V_{psat} = V_{ov}$$

\therefore the output swing is:

$$V_{swing, pp} = V_{DD} - V_{psat1} - V_{psat2} = V_{DD} - 2V_{ov}$$

↑
peak-to-peak

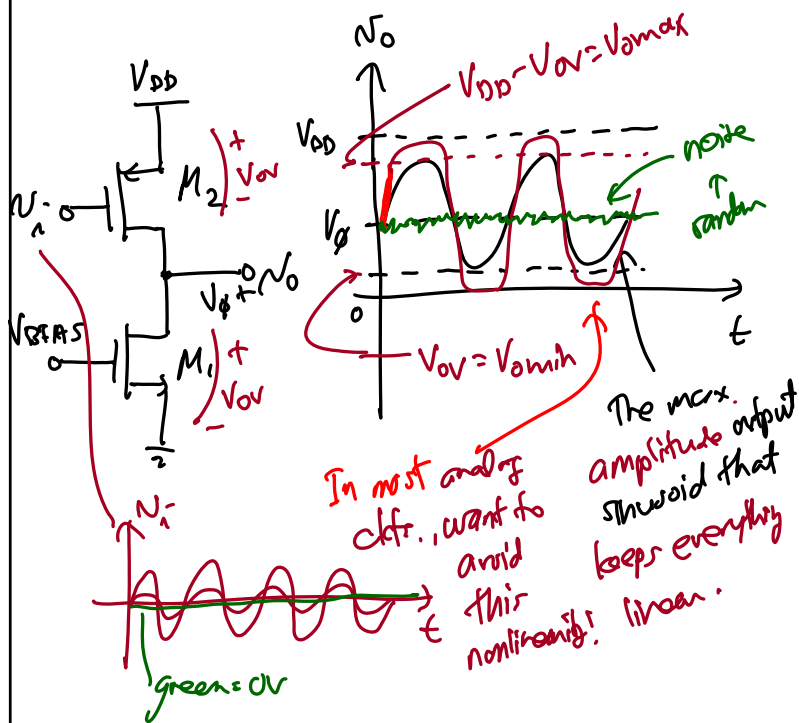

Dynamic Range = DR = $\frac{\text{maximum output signal}}{\text{minimum input signal}}$


↑
Want to max. this!



↑
Determined by Output Swing!


↑
Determined by Noise!

← we care about this a lot!

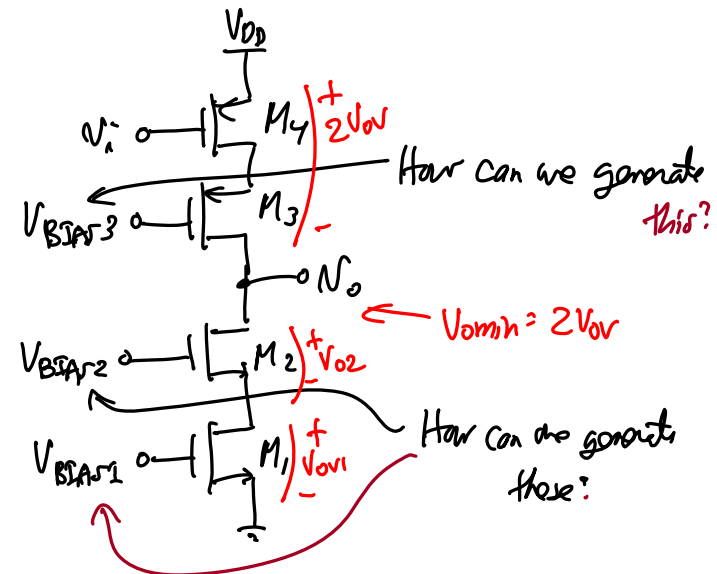What about a ckt. with a better current source, like a cascode current source?



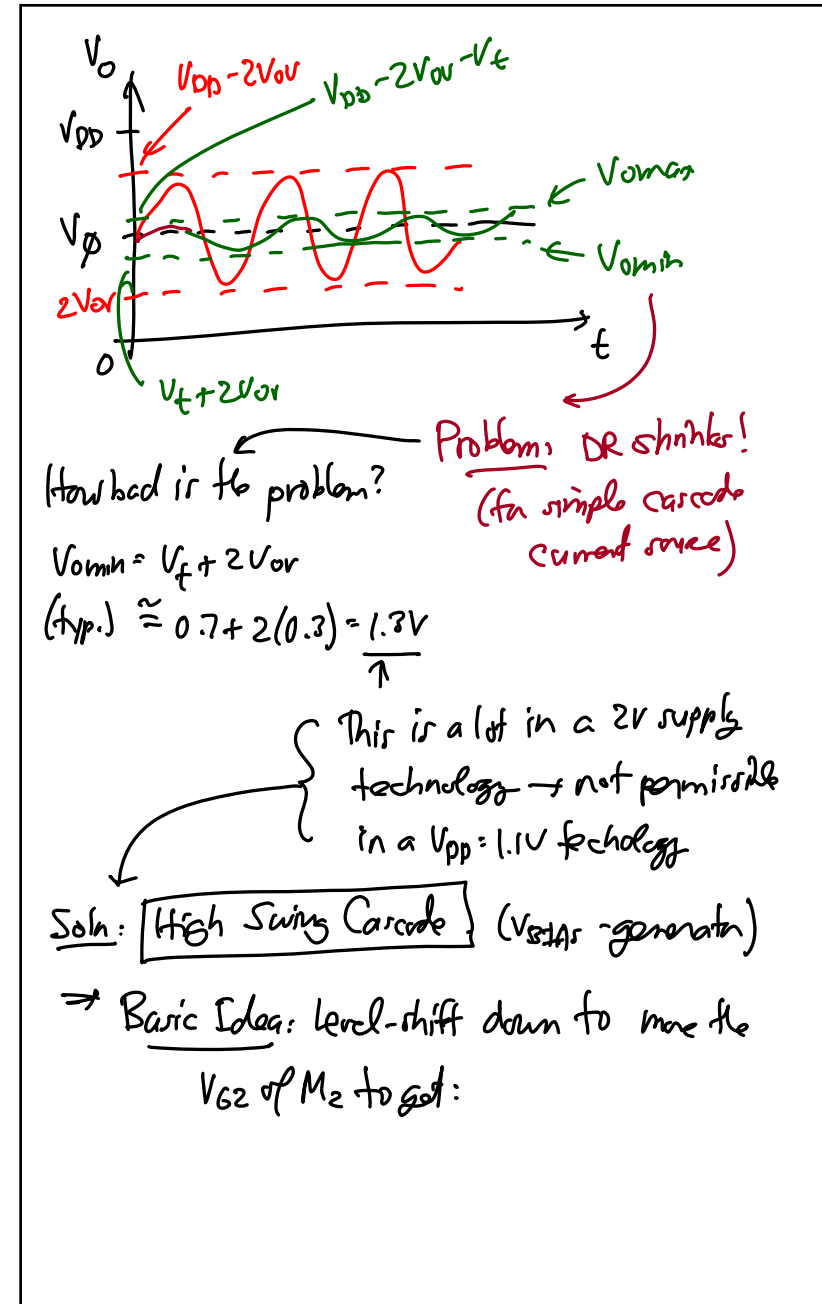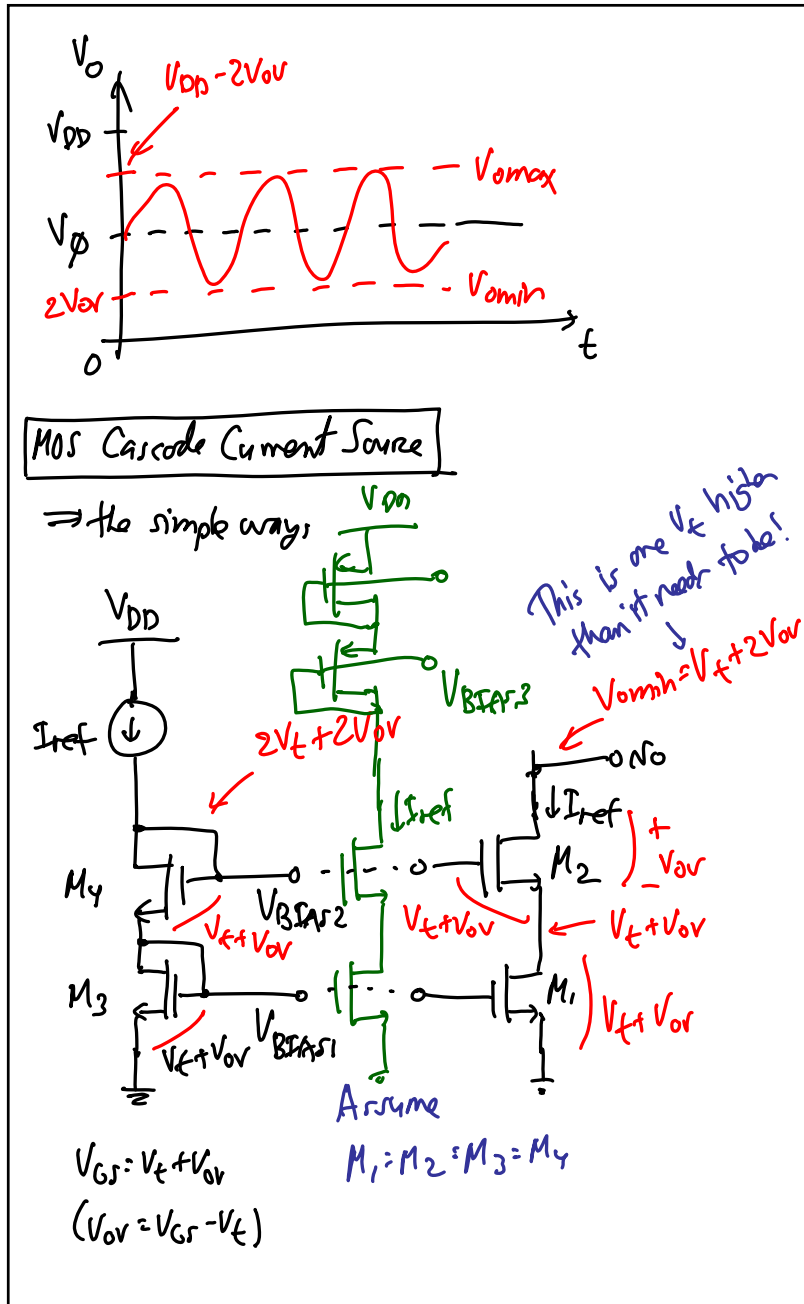

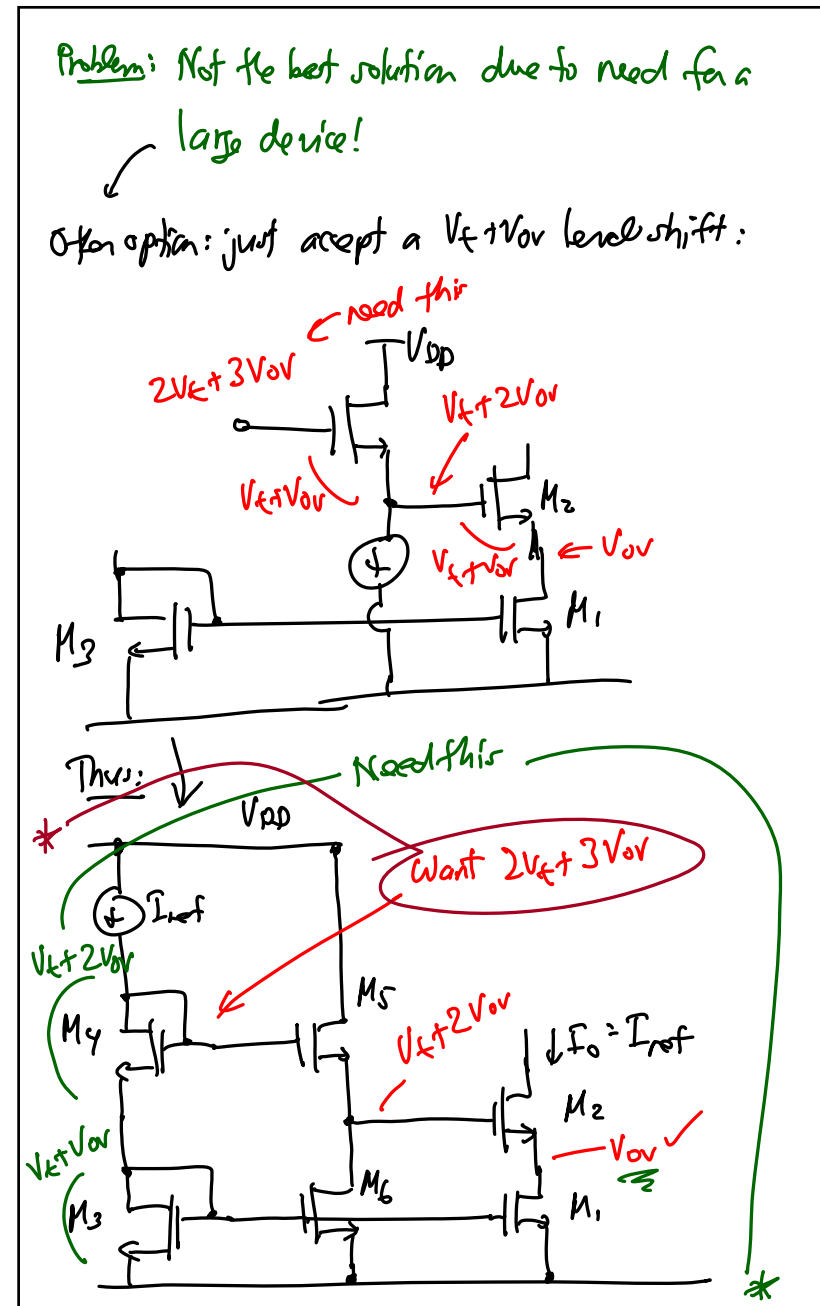

* — To get this, must size M_4 accordingly:

$$I_{D3} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{ov3})^2$$

$$I_{D4} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 (2V_{ov3})^2$$

$V_{ov4} = 2V_{ov3}$

$$I_{D3} = I_{D4} = I_{ref}$$


~~$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{ov3})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 (2V_{ov3})^2$$~~

$$\left(\frac{W}{L}\right)_4 = \frac{1}{4} \left(\frac{W}{L}\right)_3$$

... and $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6$

Problem Body effect in M_4, M_5, M_2 .

→ will increase their V_{t_i} 's!

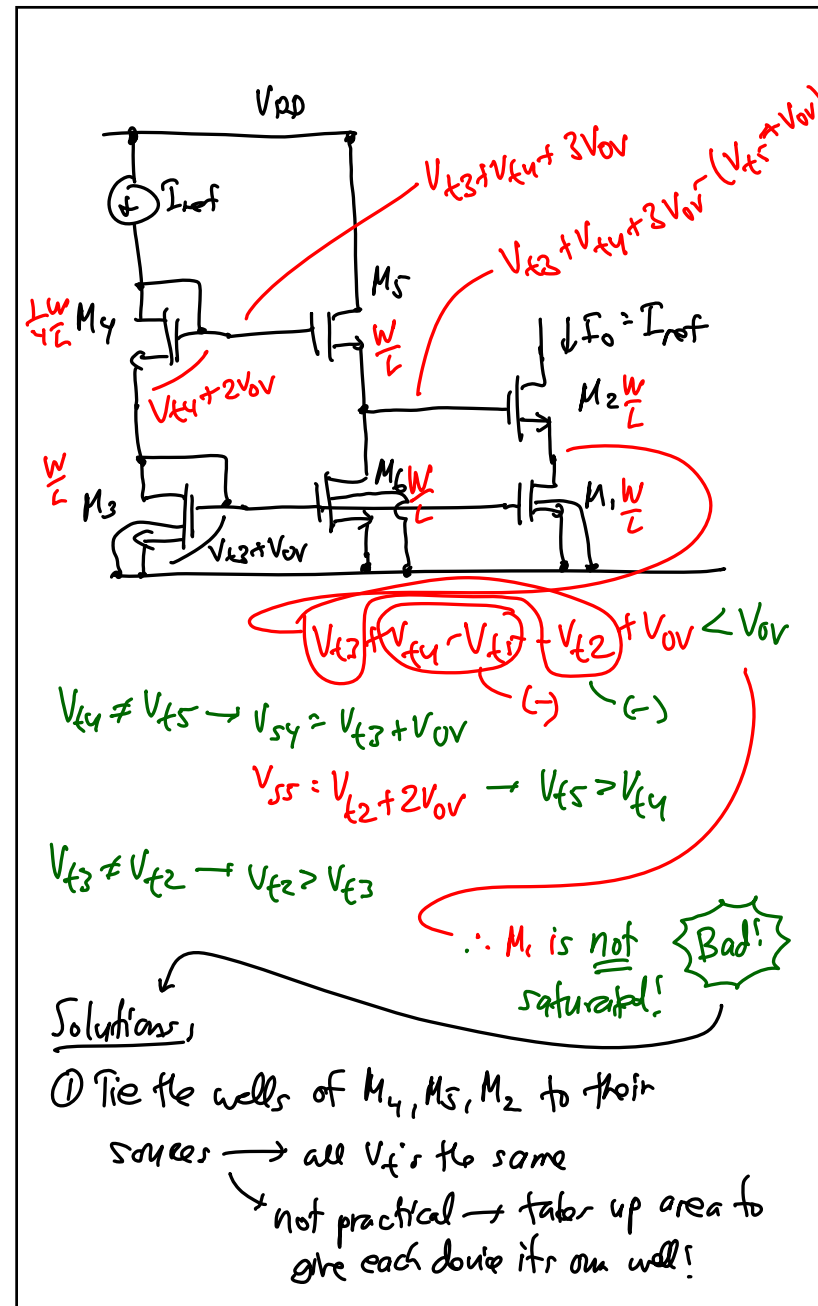

② Bias M_4 so that $V_{GS4} > V_t + 2V_{ov}$,

(e.g., $V_{GS4} = V_t + 3V_{ov}$)

make M_4 smaller than $\frac{1}{4}(\frac{W}{L})_1$

$$(W/L)_4 = \frac{1}{4}(W/L)_1$$

Issue: $V_{DS1} \neq V_{DS3} \rightarrow I_0 = \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS3})} I_{ref}$

\downarrow
 $I_0 \neq I_{ref}$

Solution: → next time.