

Lecture 11: High Swing Current Sources II

• Announcements:

↳ HW#5 online


• Lecture Topics:

↳ High Swing Current Sources (cont.)

↳ Current Source Matching Considerations

↳ Op Amp Review

• Last Time: V_{DD}

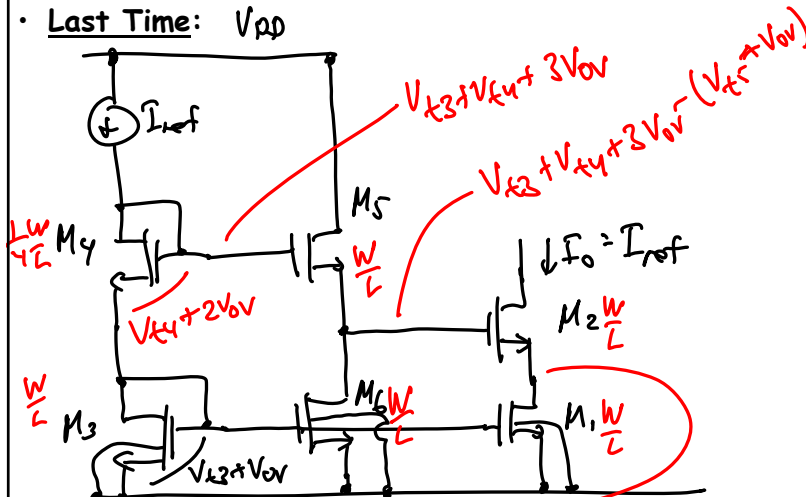

$$V_{t3} + V_{t4} - V_{t3} + V_{t2} + V_{ov} < V_{ov}$$

$$V_{t4} \neq V_{t5} \rightarrow V_{s4} = V_{t3} + V_{ov}$$

$$V_{s5} = V_{t2} + 2V_{ov} \rightarrow V_{t5} > V_{t4}$$

$$V_{t3} \neq V_{t2} \rightarrow V_{t2} > V_{t3}$$

$\therefore M_6$ is not saturated! Bad!

Solutions,

① Tie the wells of M_4, M_5, M_2 to their sources \rightarrow all V_t 's the same
 \rightarrow not practical \rightarrow takes up area to give each device its own well!

② Bias M_4 so that $V_{gs4} > V_t + 2V_{ov}$,

(e.g., $V_{gs4} = V_t + 3V_{ov}$)


make M_4 smaller than $\frac{1}{4}(\frac{W}{L})_1$

$$(W/L)_4 = \frac{1}{4}(W/L)_1$$

Issue: $V_{DD1} \neq V_{DD3} \rightarrow I_0 = \frac{(1 + \lambda V_{DD1})}{(1 + \lambda V_{DD3})} I_{ref}$

$$I_0 \neq I_{ref}$$


Soln: Use an alternative biasing scheme.

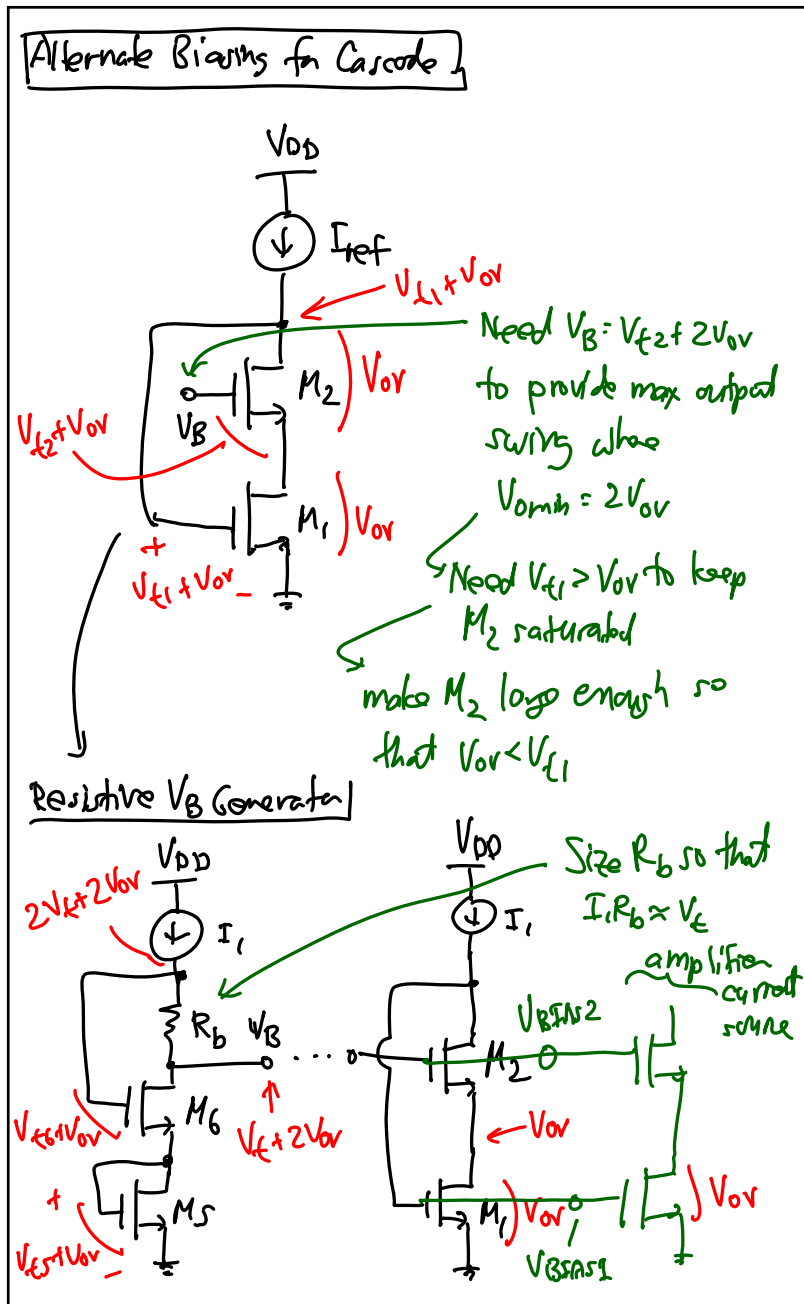

Issues:

① $I_1 R_b$ not all that well-controlled.

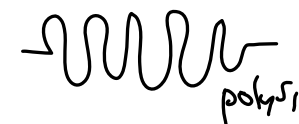can hit the right value of R_b only to 20% (in an IC process)




R_b = big \rightarrow costs too much...

② Must still account for Body Effect.

So really need: $I_1 R_b = V_{G5} + V_{G6} - V_{G2}$

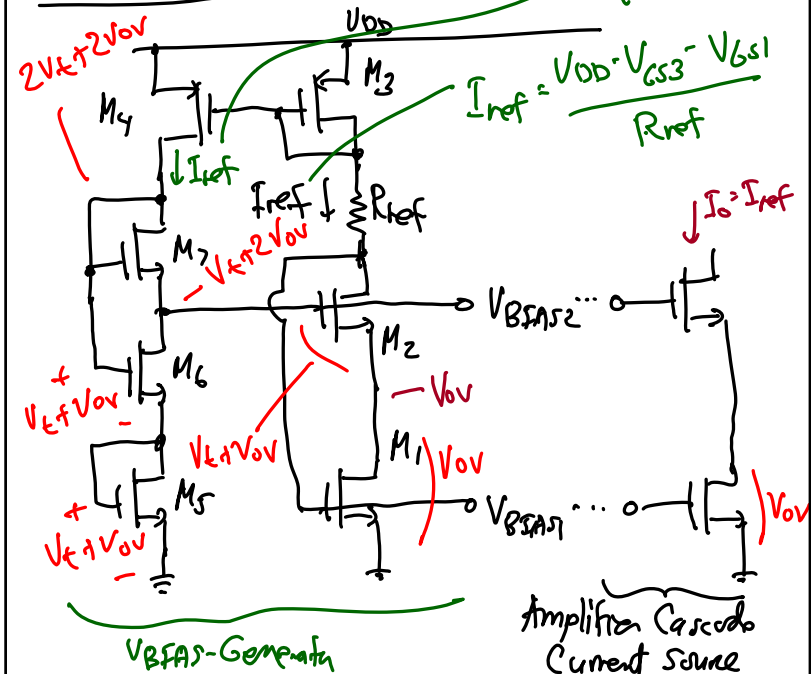Replace R_b w/ transistor level-shift: w/ $(\frac{W}{L})_1 = (\frac{W}{L})_3$



Design: (for now, ignore body effect)


Approach 1: insist that all devices are saturated
want $V_{DS6} = V_{OV} \rightarrow$ need $V_{GS7} = V_t$

Normally, $V_{GS7} = V_t + V_{OV}$
Can make $V_{OV} \approx 0V$ if make

$$V_{OV} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)_7}}$$

M_7 huge! $\left(\frac{W}{L}\right)_7 = \text{large}$
takes chip area
 $\left(\frac{W}{L}\right)_7 \uparrow \rightarrow V_{OV} \downarrow \rightarrow 0V$ problem! \rightarrow cutoff too much

Creating I_{ref} :

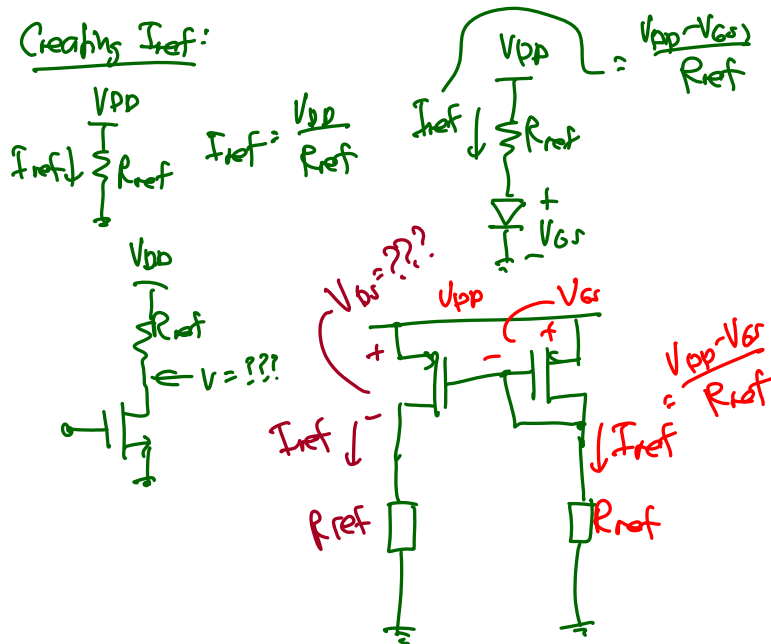


Approach 2: recognize that devices in the V_{GS} -Generator need NOT be saturated \rightarrow some can be in the triode region!

- ① Allow M_7 to drop $V_{GS7} = V_t + V_{OV}$
- ② Still need $V_{DS6} = V_{OV}$
- ③ Can get this by operating M_6 in the triode region.

$$M_7 \text{ saturated: } I_{D7} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_7 (V_{GS7} - V_t)^2$$

$$M_6 \text{ triode: } I_{D6} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_6 [2(V_{GS6} - V_t)V_{DS6} - V_{DS6}^2]$$

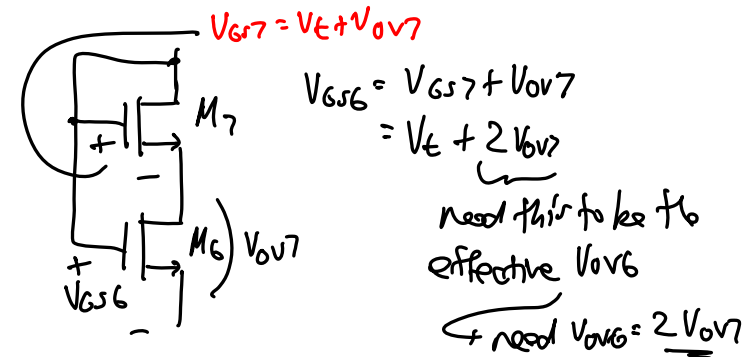Want: When $V_{GS7} = V_t + V_{OV}$ \rightarrow want



$$\text{Thus: } I_{D7} = I_{D6}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_7 (V_{OV7})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_6 [2(2V_{OV7})V_{OV7} - (V_{OV7})^2]$$

$$\left(\frac{W}{L}\right)_7 = 3 \left(\frac{W}{L}\right)_6$$

Problem We're using too much voltage to do this!

[illegible]

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (2V_{ov3})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_3 (V_{ov3})^2$$

Copyright © 2011 Regents of the University of California