

Lecture 13: Op Amps & ECP

• Announcements:

- ↳ SPICE 3f3 manual online
- ↳ This is the original manual for Berkeley SPICE
- ↳ It might be the only version we can post without violating any licenses
- ↳ ~~Problem 5 on HW#5 will be moved to HW#6~~
- ↳ HW#6 will be online tonight *→ actually, we'll just*
- ↳ I will miss next week's Thursday lecture
- ↳ Will inform you how we will make it up; perhaps by special software that records directly off my computer

• Lecture Topics:


- ↳ Op Amp Review
- ↳ Emitter Coupled Pair (ECP)

→ cancel problems, since there are already many problems on HW#6

• Last Time:

- Started op amp review

Ex:

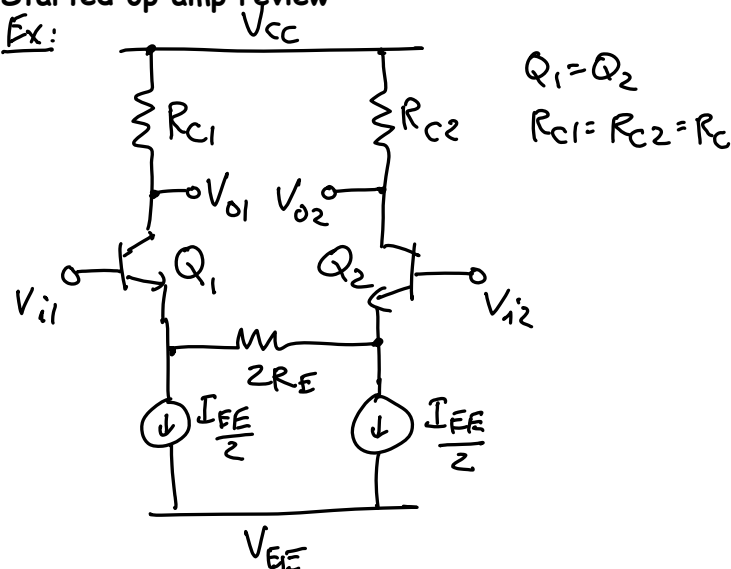

Properties of Ideal Op Amps:

① $R_{in} = \infty$

leads to

④ $i_+ = i_- = 0$

② $R_o = 0$

③ $A = \infty$

leads to

⑤ $V_+ = V_-$, assuming $N_o = \text{finite}$

Why? Because for $\infty(N_+ - N_-) = N_o = \text{finite}$

$$\therefore \underbrace{N_+ - N_-}_{\frac{N_o}{\infty}} = 0 \rightarrow N_+ = N_-$$


virtual short ckt.
(virtual ground)

Big assumption! ($N_o = \text{finite}$)

How can we assume this? \Rightarrow only when there is an appropriate negative feedback path!

Negative Feedback

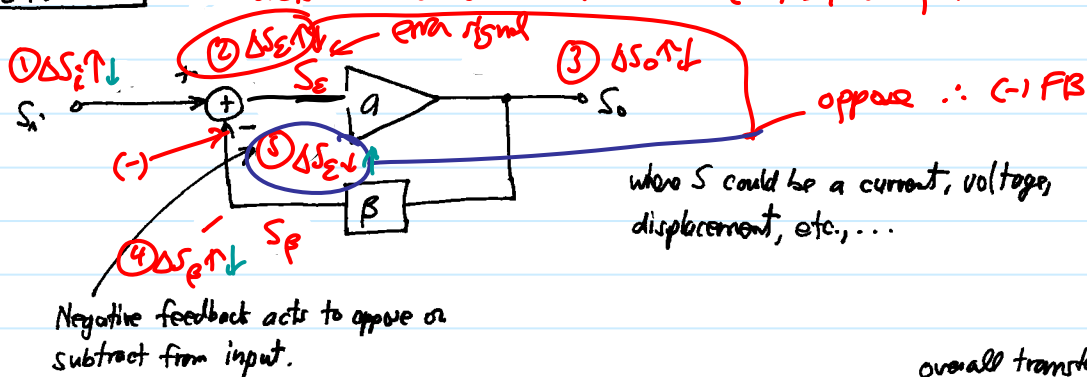\rightarrow to determine whether a circuit has (-) FB, do a perturbation analysis:



$$\left. \begin{aligned} S_o &= a S_\varepsilon \\ S_\varepsilon &= S_i - \beta S_o \end{aligned} \right\} \Rightarrow S_o = a(S_i - \beta S_o)$$

$$S_o(1 + a\beta) = a S_i \rightarrow$$

$$\boxed{\frac{S_o}{S_i} = \frac{a}{1 + a\beta}}$$

overall transfer function

 $a\beta = \text{loop gain}$ $\beta \triangleq \text{feedback factor}$


$$[a \rightarrow \infty] \Rightarrow \frac{S_o}{S_i} \approx \frac{a}{a\beta} = \frac{1}{\beta} = \text{finite!}$$

$$\therefore S_o = \frac{1}{\beta} S_i = \text{finite} \checkmark$$


(when there is neg. FB around the amplifier)

In Summary:① Neg. FB can insure $S_o = \text{finite}$ even with $a = \infty$.② ^{overall} Gain dependent (or overall T.F.) dependent only on external components. (e.g., β)③ Overall (closed-loop) gain $\frac{S_o}{S_i}$ is independent of amplifier gain a .

\nwarrow very important! \Rightarrow as you'll see, when designing amplifiers using transistors, it's easy to get large gain, but it's hard to get an exact gain.
i.e., if you're shooting for $a = 50,000$, you might get 47,000 or 60,000 instead.

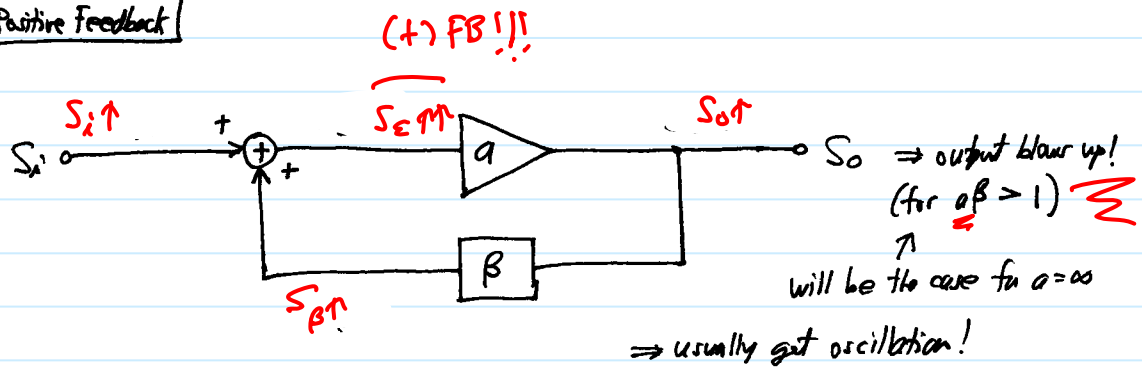
Contrast w/ Positive Feedback

Thus, for a bounded, controllable function, need negative FB around an op amp.

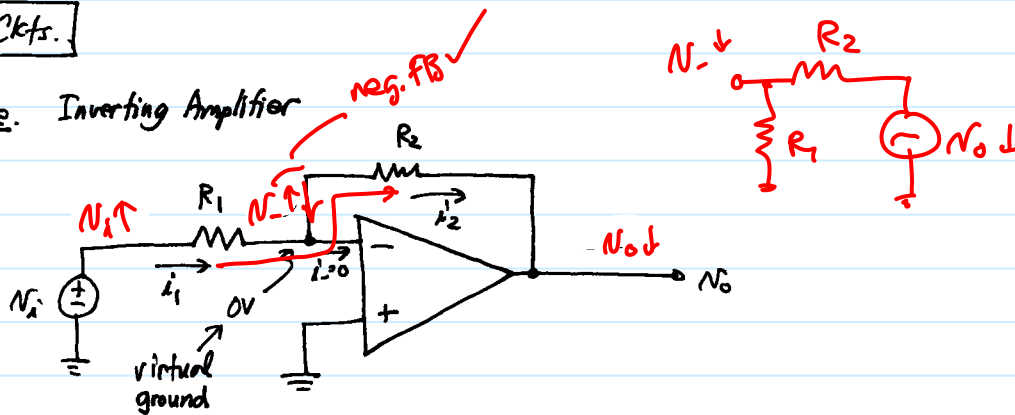Op Amp Ckts.Example. Inverting Amplifier \rightarrow ① Verify that there is negative FB. ✓② $\therefore N_o = \text{finite} \rightarrow N_+ = N_- \rightarrow$ node attached to (-) terminal is virtual ground③ $i_- = 0 \therefore i_1 = i_2$ \leftarrow virtual ground

$$\left. \begin{aligned} i_1 &= \frac{N_i - 0}{R_1} = \frac{N_i}{R_1} = i_2 \\ N_o &= 0 - i_2 R_2 = -i_2 R_2 \end{aligned} \right\} \Rightarrow N_o = -\left(\frac{N_i}{R_1}\right) R_2 = -\frac{R_2}{R_1} N_i \therefore \boxed{\frac{N_o}{N_i} = -\frac{R_2}{R_1}}$$

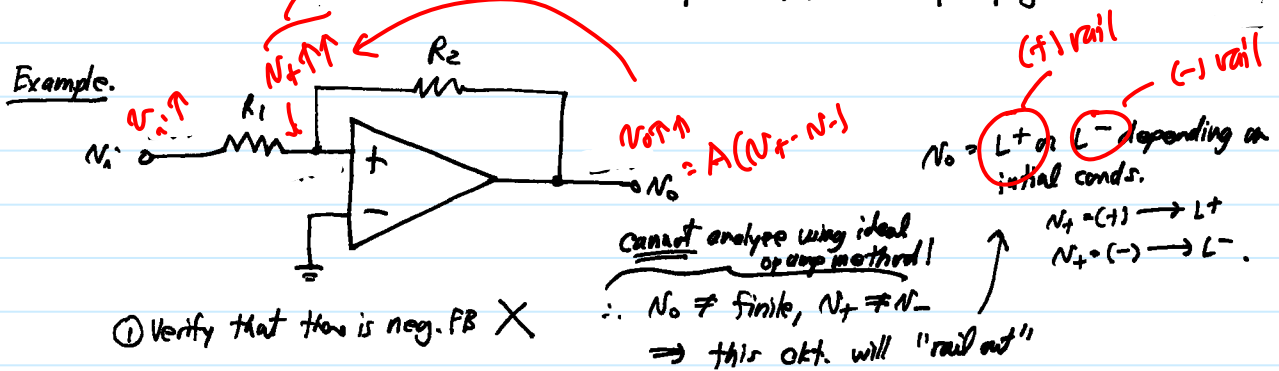$(+) \text{ FB} \times$ Note: Gain dependent only on R_1 & R_2 (external components), not on the op amp gain.




How does one make an op amp? (It turns out, you already know!)

⇒ Basic Needed Attributes:

- ① Gain (voltage gain).
- ② Two inputs, (+) and (-).
- ③ One output equal to the difference of the inputs multiplied by some gain.


In fact, the differential pair you studied in EE 105 can by itself serve as an op amp!

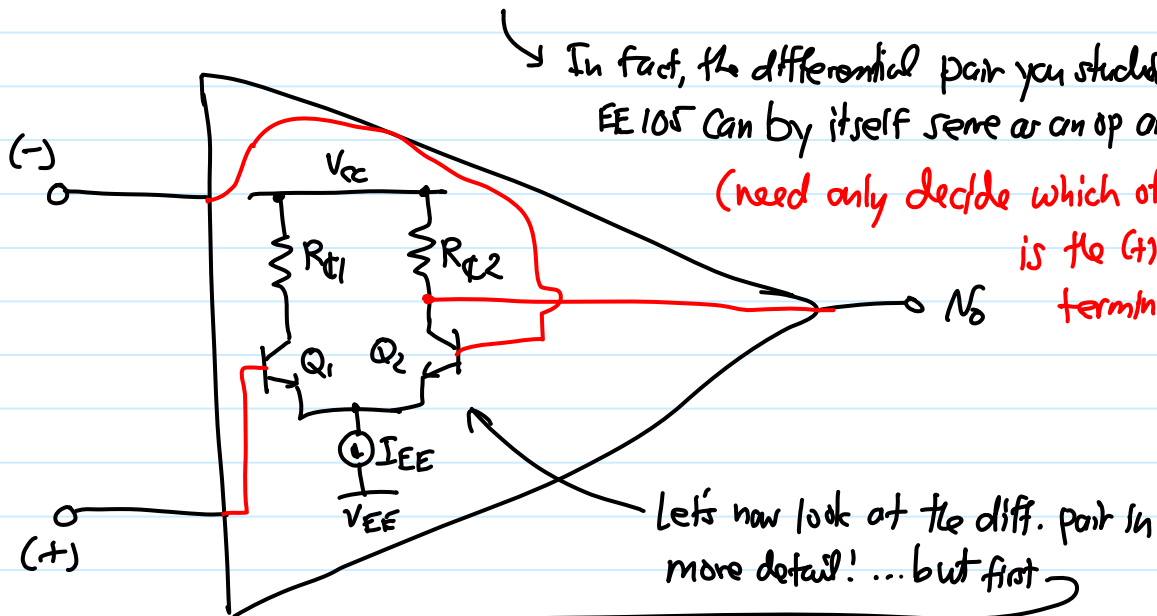(need only decide which of the inputs is the (+) and (-) terminals)





Why have 2 inputs?

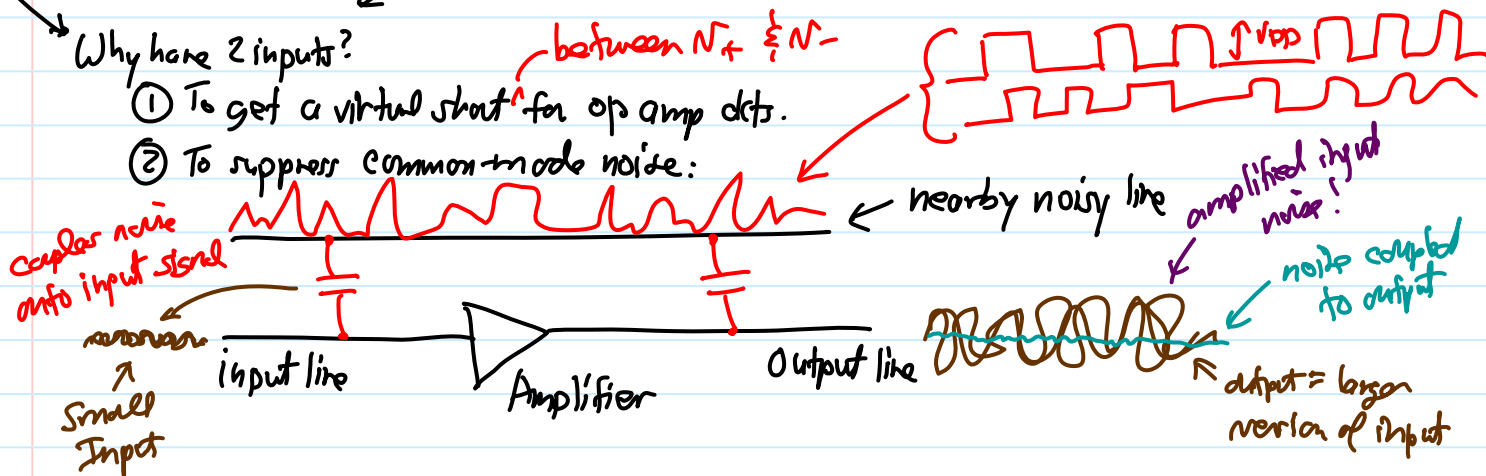- ① To get a virtual short for op amp dets.
- ② To suppress common-mode noise:



Can avoid this w a differential input:

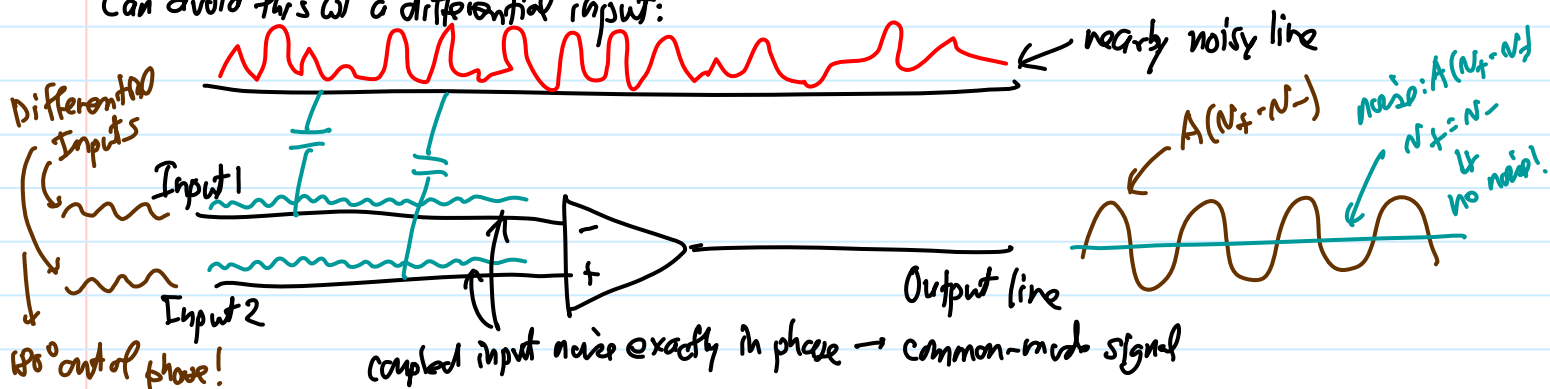

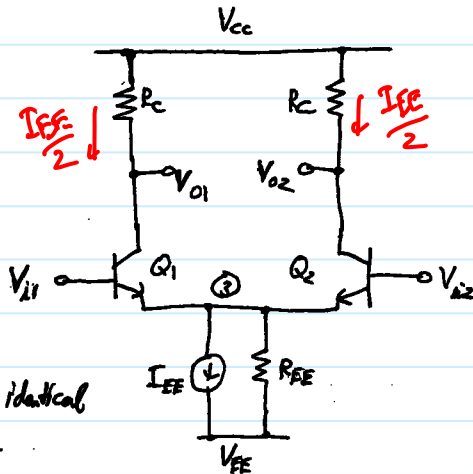Differential Pair (Emitter-Coupled Pair)

Assume:
 $Q_1 \neq Q_2$ identical
 $R_{C1} = R_{C2}$

Purpose: Amplify the difference between two signals regardless of their common-mode DC values (or their common-mode values in general)

Definition: $V_{id} = V_{i1} - V_{i2}$ (differential input)
 $V_{icm} = \frac{V_{i1} + V_{i2}}{2}$ (common-mode input)

$$\Rightarrow \begin{cases} V_{i1} = V_{icm} + \frac{V_{id}}{2} \\ V_{i2} = V_{icm} - \frac{V_{id}}{2} \end{cases}$$

Differential Gain = $A_d = \frac{V_{o1} - V_{o2}}{V_{id}} = \frac{V_{od}}{V_{id}}$ (want this to be large for this differential amplification)

Common-Mode Gain = $A_{cm} = \frac{V_{o1}}{V_{cm}} \approx \frac{V_{o2}}{V_{cm}}$ (want this to be small so that the amp rejects common-mode signals)

Common-Mode Rejection Ratio = $CMRR = \frac{A_{dm}}{A_{cm}}$ (should be very high to favor the differential mode and reject the common-mode)

\Rightarrow we also want a high Common-Mode Input Range to reject DC input offsets

\Rightarrow Note: No need for bypass capacitors (large) to the inputs or outputs \rightarrow can just use direct coupling!

Biased & Large Signal Common-Mode Behavior


Case: $R_{EE} = \infty \rightarrow$ ideal current source biasing $\rightarrow I_{E1} = I_{E2} = \frac{I_{EE}}{2} \rightarrow V_{o1} = V_{o2} \Rightarrow V_{od} = 0$

\uparrow If $V_{cm} \uparrow \rightarrow V_{B1} \uparrow$, but current draw from I_{EE} stays constant $\therefore I_{C1}$ & I_{C2} stay constant \rightarrow bias pt. doesn't change
 Ideal $g_{m1} = \frac{1}{2} \frac{I_{EE}}{V_T}$ ideal current source \times $R_{EE} = \infty$

Case: $R_{EE} = \text{finite}$


\uparrow If $V_{icm} \uparrow \rightarrow V_{B1} \uparrow \rightarrow I_{E1} = I_{E2} \uparrow$ (current draw = $I_{EE} + \frac{V_{od}}{R_{EE}}$)

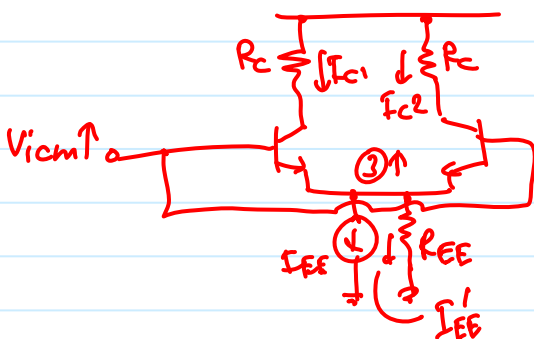\Rightarrow in general, R_{EE} will be large, so this component won't be large, and the bias pt. won't Δ much




If $V_{icm} \uparrow \rightarrow I_{EE}' \uparrow \rightarrow I_{E1} = I_{E2} \uparrow \rightarrow I_{C1} = I_{C2} \uparrow$
 \downarrow
 $V_{ocm} \downarrow$

Small-Signal Analysis of Diff. Pair

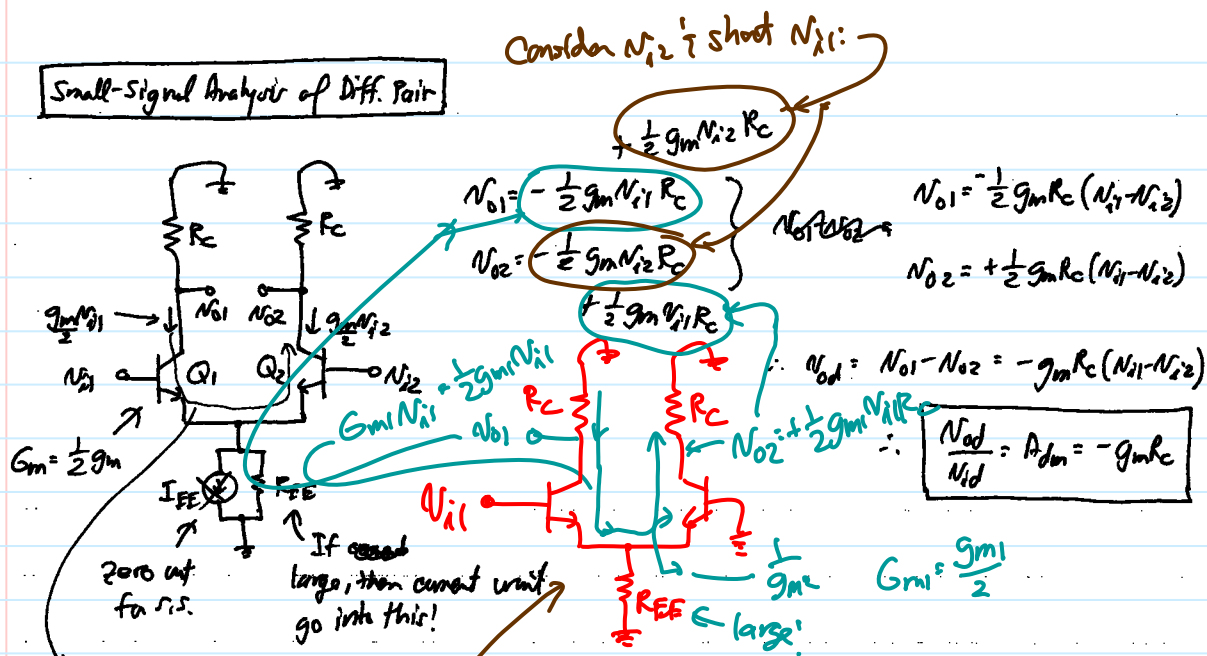


⇒ Easiest to see this happening using the T-model: (for those who must see the model ckt.)

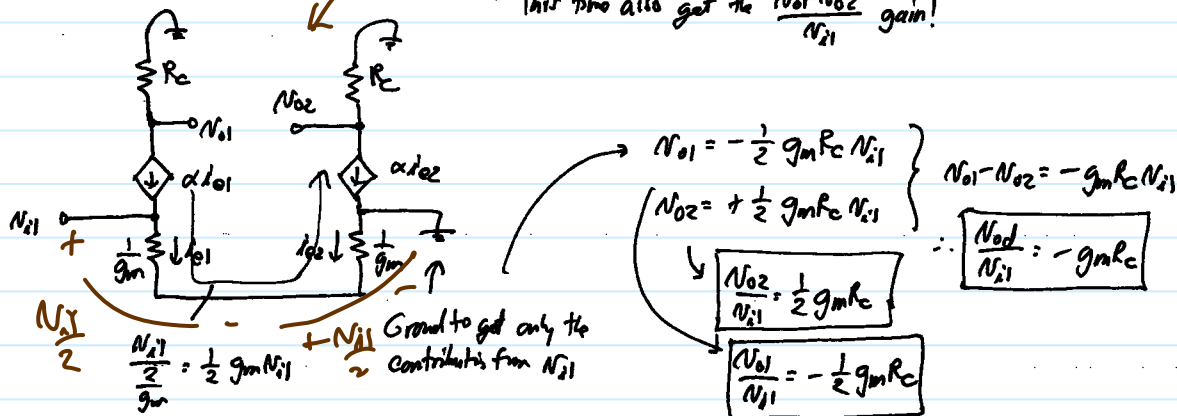↳ This time also get the $\frac{N_{o1} - N_{o2}}{N_{i1}}$ gain!



Diff. Mode Analysis

Assume a ckt. w/ only diff. input:

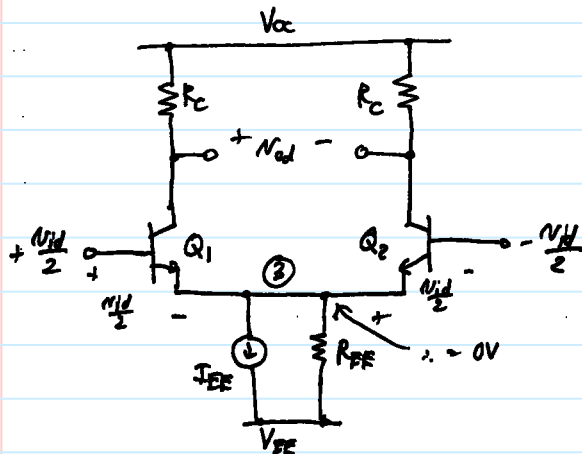

Total current thru I_{EE} = const.

→ V_E = const. as input changes

→ ③ act as an incremental ground! → $V_3 = 0V$ (always!)

∴ we can ground ③, and then have

a **Differential Half Ckt.**

Note: Can really only make this for a purely symmetrical ckt!