

Ex:

V_{CC}

R_{C1} R_{C2}

V_{01} V_{02}

Q_1 Q_2

V_{id}

$2R_E$

$\frac{I_{EE}}{2}$ $\frac{I_{EE}}{2}$

V_{EE}

$S.S. Ckt.$

V_{x1} V_{x2} V_x

R_{C1} R_{C2}


Q_1 Q_2

V_{x1} V_{x2} V_x

R_E R_E

I_x

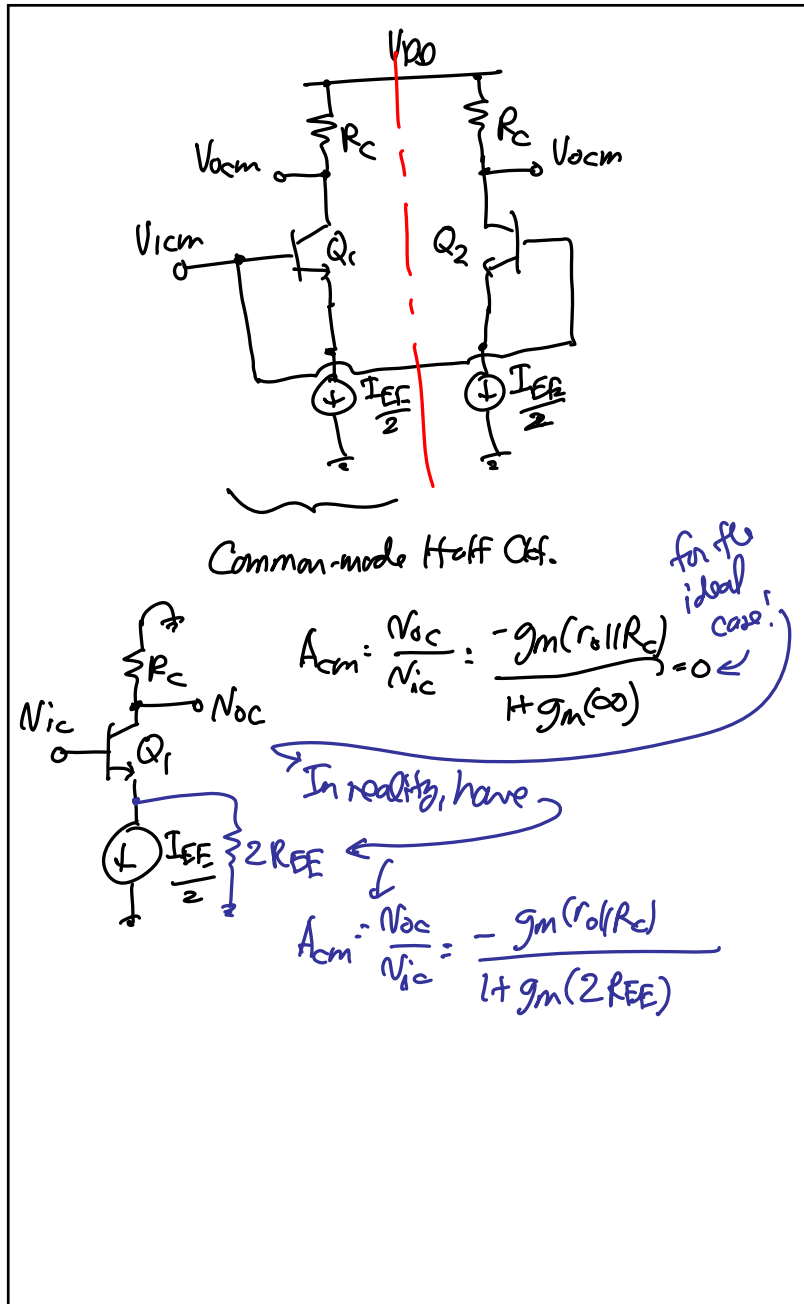How much current goes through this resistor?
 $\hookrightarrow \lambda = 0 \therefore$ the resistor effectively isn't there!



If there is a mismatch in the ckt., e.g., $R_{c1} \neq R_{c2}$,
then we can define:

$$A_{cm-dm} \triangleq \text{common-mode input to differential-mode output gain}$$

$$= \frac{V_{od}}{V_{ic}} = \frac{V_{o1} - V_{o2}}{V_{i1}} = \frac{V_{o1} - V_{o2}}{V_{i2}} \quad (\text{w/ } V_{i1} = V_{i2})$$

$$A_{dm-cm} \triangleq \text{differential-mode input to common-mode output gain}$$

$$= \frac{V_{oc}}{V_{id}} = \frac{V_{oc}}{V_{i1} - V_{i2}} \quad [\text{w/ } V_{oc} = \frac{1}{2}(V_{o1} + V_{o2})]$$

You'll will be experiencing these in your HW!

- Now go back to the handout, to the source coupled pair (SCP) section
- Go through this until you get to "What is R_o ?"
- Then ...



What is R_o ?

Handwritten notes on the diagram:


- r_{o4} (red)
- R_o (red)
- $2r_{o2} = r_{o2}(1 + g_m(\frac{1}{g_m}))$ (red)
- g_m (red)
- i_x (green, circled)
- N_x (red, circled)
- r_{o2} (green, underlined)
- $\underbrace{\hspace{1cm}}_{\text{mirrored}}$ (green)

$$i_x = \frac{N_x}{r_{o4}} + \underbrace{\frac{N_x}{2r_{o2}} + \frac{N_x}{2r_{o2}}}_{\text{mirrored}}$$

$$\frac{N_x}{i_x} = R_o = \frac{1}{\frac{1}{r_{o2}} + \frac{1}{r_{o4}}} = (r_{o2} || r_{o4}) \checkmark$$

- Now go back to the handout, at the current mirror loaded SCP section

Consider N_{i2} & shoot N_{i1} :

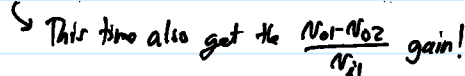

$N_{02} = + \frac{1}{2} g_m R_c N_{A1}$

\downarrow

N_{02}

$\therefore \frac{N_{02}}{N_{A1}} = -g_m R_c$

$$\frac{N_{02}}{N_{01}} = \frac{1}{2} g m R_c$$

Assume a def. w/ only diff. input:



→ $V_E = \text{const.}$ as input changes


→ ③ act as an incremental ground! → $V_3 = 0V$ (always!)

∴ we can ground ③, and then, have

a Differential Half. Ctg.

Note: Can really only make this for a purely symmetrical obs.!

Differential Half Ckt.

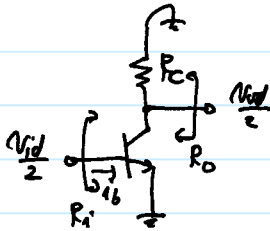

By inspection: $\frac{v_{od}/2}{v_{id}/2} = \frac{v_{od}}{v_{id}} = A_{dm} = -g_m R_c$


$\frac{v_{id}/2}{i_b} = r_{\pi} \rightarrow R_{id} = \frac{v_{id}}{i_b} = 2r_{\pi} = R_{id}$

$\frac{v_{od}/2}{i_o} = r_o || R_c \rightarrow R_{od} = \frac{v_{od}}{i_o} = 2(r_o || R_c) \approx 2R_c = R_{od}$

S.S. params. determined w/ $I_c = \frac{I_{EE}}{2}$

Common-Mode Analysis

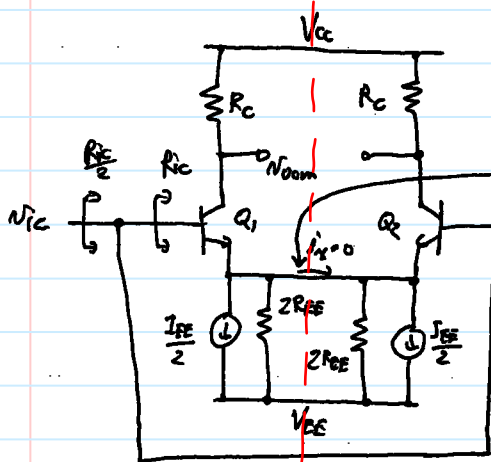Assume a pure CM input \rightarrow tie inputs together




By symmetry, $i_x = 0 \Rightarrow$ thus, really have to equivalent of an open ckt. here

$\therefore \Rightarrow$ can split the ckt. into CM half-ckt.!

S.S. CM Half-Ckt.

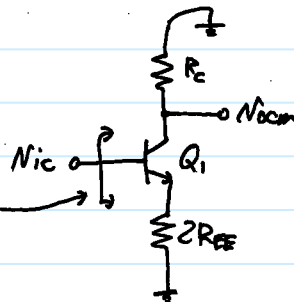$R_{ic} = r_{\pi} + (\beta+1)(2R_{EE})$
@ each input




$A_{cm} = \frac{v_{ocm}}{v_{ic}} = -\frac{g_m R_c}{1 + g_m (2R_{EE})} \approx -\frac{R_c}{2R_{EE}}$

Want small for large CMRR \therefore want $R_{EE} \rightarrow$ large!

Common-Mode Rejection Ratio = $CMRR = \frac{A_{dm}}{A_{cm}} = \frac{-g_m R_c}{-\frac{R_c}{2R_{EE}}} \Rightarrow CMRR = 1 + 2g_m R_{EE}$

Having looked at S.S. parameters, we now turn to large signal performance. Here, we'll be particularly interested in the linear range of the ECP.

Large Signal ECP Performance

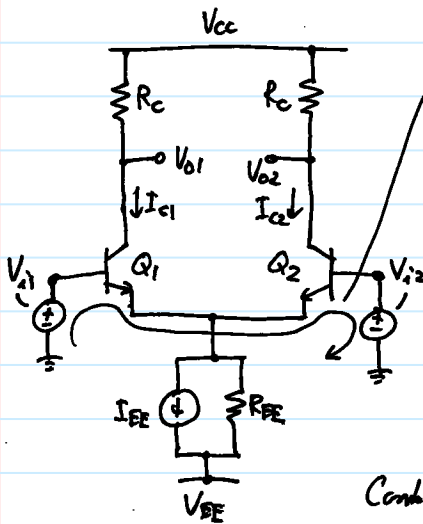Find I_{C1} & I_{C2} :

$$\text{KVL: } V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$$

$$I_{C1} = I_{S1} \exp\left(\frac{V_{be1}}{V_T}\right) \rightarrow V_{be1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right), \quad V_{be2} = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right)$$

$$V_{i1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) - V_{i2} = 0 \rightarrow \ln \frac{I_{C1}}{I_{C2}} = \frac{V_{i1} - V_{i2}}{V_T} = \frac{V_{id}}{V_T}$$

$$\frac{I_{C1}}{I_{C2}} = \exp\left(\frac{V_{id}}{V_T}\right) \quad (1)$$

$$I_{EE} = I_{C1} + I_{C2} = \frac{1}{\alpha} (I_{C1} + I_{C2}) \quad (2)$$

Combine (1) & (2) to get:

$$I_{C1} = \frac{\alpha I_{EE}}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)}, \quad I_{C2} = \frac{\alpha I_{EE}}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} \quad (3)$$

Find V_{od} :

$$\left. \begin{aligned} V_{O1} &= V_{CC} - I_{C1} R_C \\ V_{O2} &= V_{CC} - I_{C2} R_C \end{aligned} \right\}$$

$$V_{od} = V_{O1} - V_{O2} = (I_{C2} - I_{C1}) R_C$$

using (3)

$$= \alpha_F I_{EE} R_C \left\{ \frac{1}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} - \frac{1}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)} \right\}$$

$$\times \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right)} \quad \times \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right)}$$

$$= \alpha_F I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} - \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right) + \exp\left(-\frac{V_{id}}{2V_T}\right)} \right\}$$

$$= \alpha_F I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right) - \exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} \right\} = \alpha_F I_{EE} R_C \frac{\sinh\left(-\frac{V_{id}}{2V_T}\right)}{\cosh\left(-\frac{V_{id}}{2V_T}\right)}$$


$$\left\{ \begin{aligned} \sinh u &= \frac{1}{2} (e^u - e^{-u}) \\ \cosh u &= \frac{1}{2} (e^u + e^{-u}) \end{aligned} \right\} \quad u = -\frac{V_{id}}{2V_T}$$

$$\therefore V_{od} = \alpha_F I_{EE} R_C \tanh\left(-\frac{V_{id}}{2V_T}\right)$$

From our knowledge of the Taylor series for

$$\tanh x \approx x - \frac{x^3}{3} + \frac{2}{15} x^5 - \dots$$


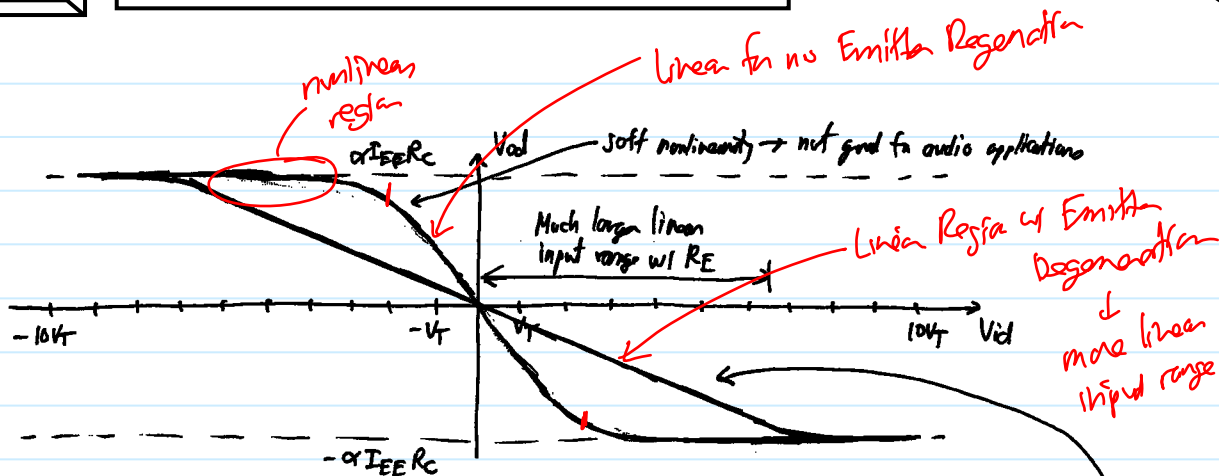
This is fairly linear for small V_{id} , but gets nonlinear abruptly when V_{id} approaches a threshold value!



In the above curve, the $\frac{V_{out}}{V_{in}}$ Xfer function is really only linear for $V_{in} \ll V_T \rightarrow$ beyond V_T , start to enter the nonlinear realm of curve \rightarrow causes signal distortion: eg, phone breaking up, television static

To linearize: add emitter degeneration (same trick as used before for single Xfer amplifiers)

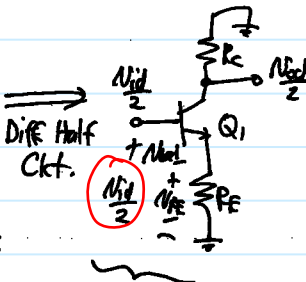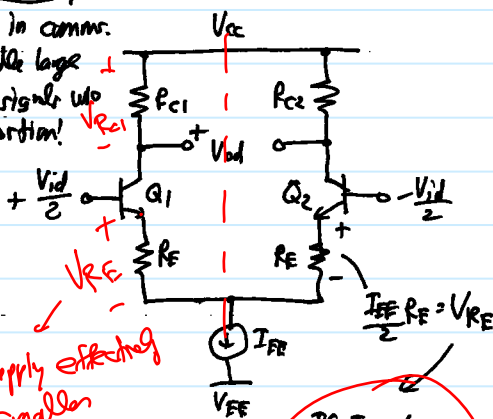Needed in comm. to handle large input signals w/o distortion!





$$A_{dm} = -\frac{g_m R_C}{1 + g_m R_E}$$

\Rightarrow s.s. gain reduced, but the linear range is increased

If I_{EE} is large, then this can force large supply voltages


$\frac{V_{in}}{2} = V_{be1} + V_{RE}$
This can still be $V_{be1} \ll V_T$ if this absorbs some of the input voltage!

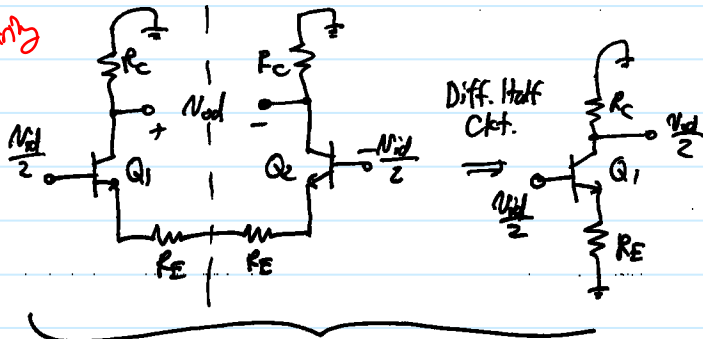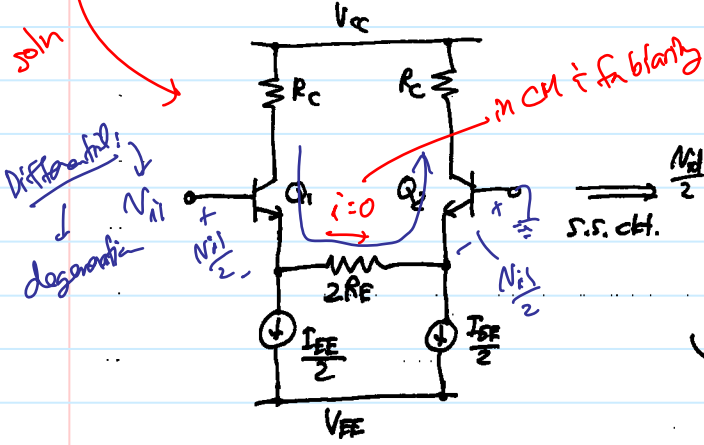Alternative Biasing Technique if Need Larger DC Currents:-



Same S.S. performance w/o the need to drop a DC voltage across $R_E \rightarrow$ get better
Can use lower V_{CC} & V_{EE} .

MOSFET Source-Coupled Pair

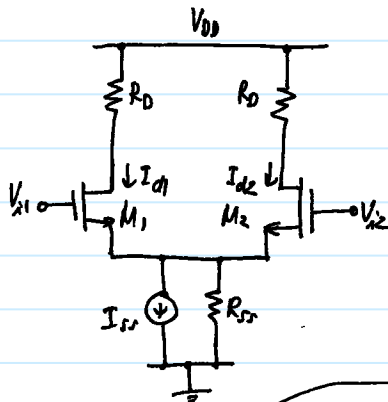

Assume: M_1 & M_2 are identical.

Find $\Delta I_d = I_{d1} - I_{d2} = f(V_{id})$.

\Rightarrow approach: get $V_{id} = f(\Delta I_d) \rightarrow$ then invert to get $\Delta I_d = f(V_{id})$

$$I_{d1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{gs1} - V_t)^2 \Rightarrow V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$$

$$\therefore V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}}$$

Define:

$$\begin{cases} \Delta I_d = I_{d1} - I_{d2} \\ I_d = \frac{I_{d1} + I_{d2}}{2} \end{cases} \Rightarrow \begin{cases} I_{d1} = I_d + \frac{\Delta I_d}{2} \\ I_{d2} = I_d - \frac{\Delta I_d}{2} \end{cases}$$

$$V_{id} = \sqrt{\frac{2(I_d + \frac{\Delta I_d}{2})}{k}} - \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_d + \frac{\Delta I_d}{2} - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2} + I_d - \frac{\Delta I_d}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_d - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2}$$

\Rightarrow Now rearrange to get ΔI_d (algebra)

Solve for ΔI_d :

$$\Delta I_d = \frac{k}{2} V_{id}^2 \left(\frac{2I_{ss}}{k/2} - V_{id}^2 \right)^{\frac{1}{2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left(\frac{2I_{ss}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_d$$

Large Signal Equation for Differential Output Current

Valid so long as the devices stay saturated:


$$|V_{id}| \leq \sqrt{\frac{2I_{ss}}{k}} = \sqrt{\frac{2I_{ss}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

V_{GS} for $I_D = \frac{I_{ss}}{2}$

if true then input devices are both saturated

Thus, to extend the linear input range:

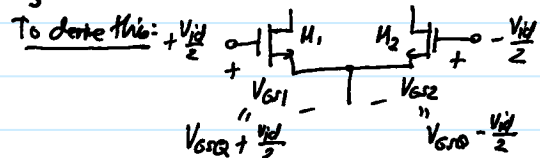- ① $I_{ss} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ② W/L
- ③ $L \uparrow$




When $V_{id} \geq V_{GSQ} - V_t = \Delta V$ then M_2 will cut-off

$\therefore V_{id} \leq 2(V_{GSQ} - V_t) \rightarrow$ to maintain saturation

$$V_{GSQ} - V_t = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$

Then plug in ΔI_d & solve for V_{id}

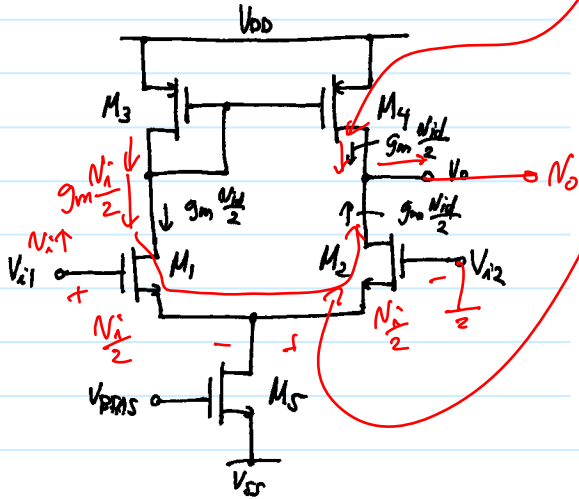MOS Differential Stage w/ Current Mirror Load



from bottom from top

$$V_o = \left(\frac{g_m}{2} V_{i1} + \frac{g_m}{2} V_{i2} \right) R_o = \frac{V_o}{V_{i1}} = g_m R_o$$

$$= g_m (r_{o2} || r_{o4}) = \frac{V_o}{V_{i1}}$$


Adm

What is R_o ?

Go to the main lecture page

$R_o = (r_{o2} || r_{o4}) \dots$ but not by inspection!

CMRR-

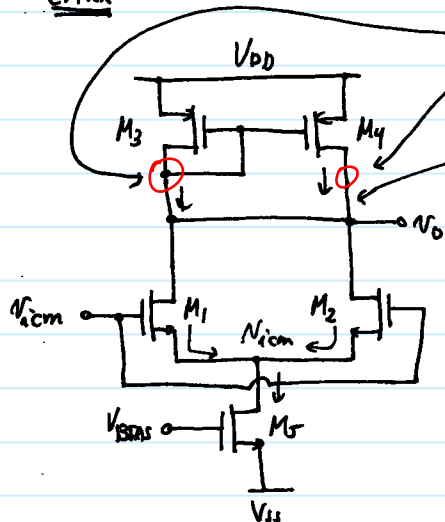


for $M_1 = M_2$ & $M_3 = M_4$

$V_{D3} = V_{D4}$ (they track each other)

⇒ Thus, can short the drains of M_3 & M_4

provided the ckt. is completely symmetrical.

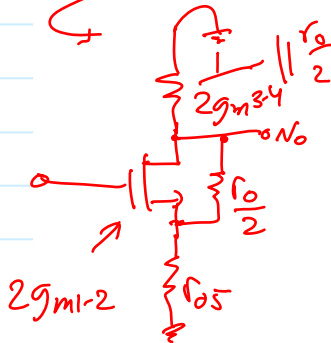truly symmetric → we can draw a half ckt.
or just combine the two ckt. together!



$$A_{cm} = - \frac{2g_{m1-2} \left(\frac{1}{2g_{m3-4}} \right)}{1 + 2g_{m1-2} r_{o5}}$$

Thus:

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1-2} (r_{o1-2} || r_{o3-4}) (1 + 2g_{m1-2} r_{o5}) \left(\frac{g_{m3-4}}{g_{m1-2}} \right)$$

$$CMRR = (1 + 2g_{m1-2} r_{o5}) g_{m3-4} (r_{o1-2} || r_{o3-4})$$

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep M_5 saturated

$$V_{icm(min)} = CMR^- = V_{SS} + V_{ovs5} + V_{GS1,2} = V_{SS} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} (W/L)_5}} + V_{t1,2} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox} (W/L)_{1,2}}}$$