

Lecture 15: Vos & Finite Gain-BW

• Announcements:

- ↳ HW#7 will be online soon
- ↳ Pre-Lecture materials for this lecture (on Vos) are already online
- ↳ Lab#2 will be due the week AFTER Spring Break; this should give ample time to write up a good lab report
- ↳ I will miss Thursday's lecture
- ↳ We will make it up on Friday, at 3 p.m., in the Hogan Room \Rightarrow it will be recorded via software on my computer
- ↳ Midterm Exam next week, Thursday, March 17, in 213 Wheeler (this room), during the regular class period

• Lecture Topics:


- ↳ Midterm Exam Info
- ↳ Offset Voltage (Vos)
- ↳ Finite Gain-BW Product

• Last Time:

- Going through prepared notes on op amps ... almost finished ... finish the notes
- Then go to the Vos notes

Vos of a Mismatched SCP

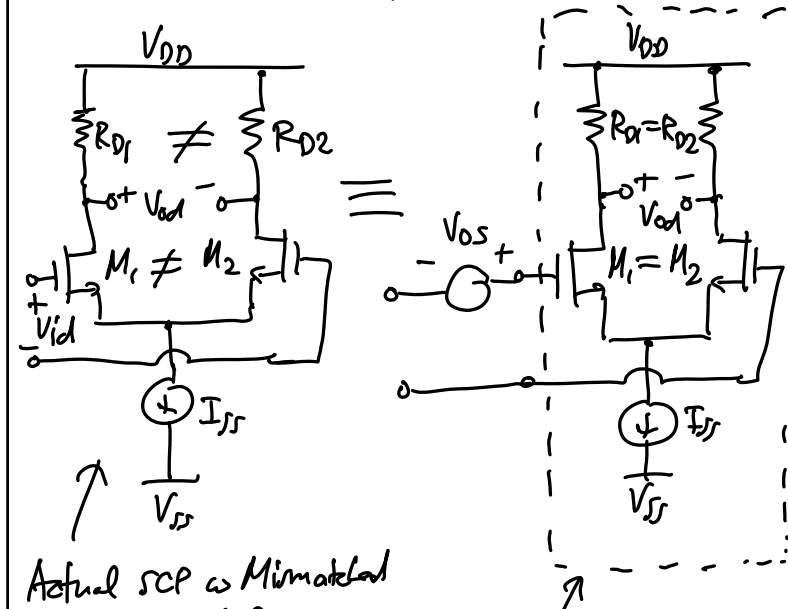Objective: Derive an expression for V_{os} .




Actual SCP w/ Mismatched
X'sistors & R's

Ideal SCP w/
matched $M_1=M_2$
& $R_{D1}=R_{D2}$

V_{os} enters due to variations in:

- ① X'sistors $M_1 \neq M_2 \rightarrow \frac{W}{L} \neq V_{t, \text{var}}$
- ② $R_{D1} \neq R_{D2} \rightarrow$ cause variations in gain

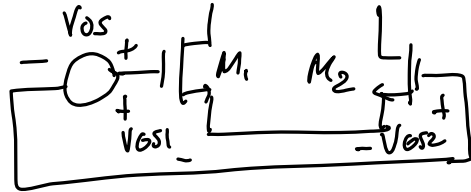Definition. $V_{os} = V_{id}$ needed to get $V_{od} = 0V$ in this ckt:



→ KVL: $V_{os} - V_{GS1} + V_{GS2} = 0$

$\therefore V_{os} = V_{GS1} - V_{GS2}$

$$= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{os} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\begin{array}{l|l} \Delta I_D = I_{D1} - I_{D2} & \Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2 \\ I_D = \frac{I_{D1} + I_{D2}}{2} & \left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right] \end{array}$$

$$\begin{array}{l|l} \Delta V_t = V_{t1} - V_{t2} & \Delta R_D = R_{D1} - R_{D2} \\ V_t = \frac{1}{2}(V_{t1} + V_{t2}) & R_D = \frac{1}{2}(R_{D1} + R_{D2}) \end{array}$$

Rearranging:

$$\begin{array}{l|l|l} I_{D1} = I_D + \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} & V_{t1} = V_t + \frac{\Delta V_t}{2} \\ I_{D2} = I_D - \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} & V_{t2} = V_t - \frac{\Delta V_t}{2} \end{array}$$

Substituting into (1): $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{os} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}}$$

$$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox}(W/L)}} \right] \rightarrow \frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right]$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

→ Binomial Theorem:

$$(1+mx)^m \rightarrow 1+mnx \quad \eta = \text{small}$$

$$V_{os} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}} - \cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{os} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1}R_{D1} = I_{D2}R_{D2}$


mismatch in I_D must be opposite that of R_D
 $\therefore \frac{\Delta I_D}{I_D} = -\frac{\Delta R_D}{R_D}$ *Pay no attention to these signs!*

$$V_{os} = \Delta V_t + \frac{1}{2}(V_{GS} - V_t) \left\{ -\frac{\Delta R_D}{R_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Mismatch

Geometric Variations (eg, lithography limitations)

Scale w/ overdrive

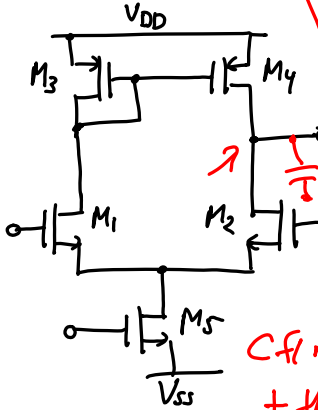

$\frac{\Delta R_D}{R_D} \approx \pm 1, \frac{\Delta(W/L)}{(W/L)} \approx \pm 1$
 can easily be the case!


Cfl next stage + those fl M_2 & M_4

Freq. Response: $\omega_H = \frac{1}{(r_{o2} || r_{o4})C_L}$ ← dominant pole

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.

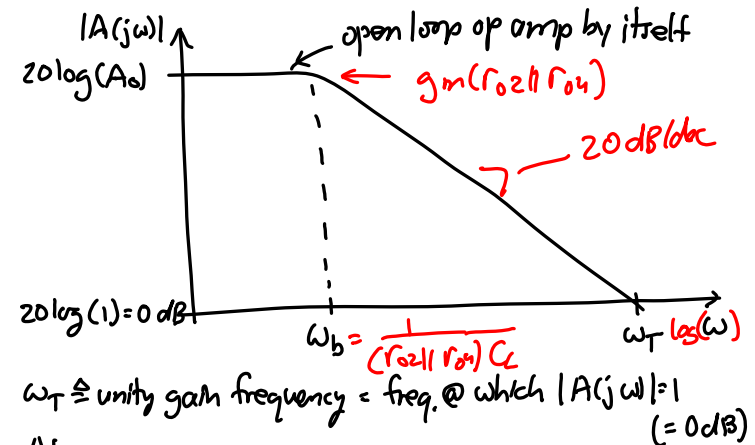In reality, the gain is given by: $A(s) = \frac{A_0}{1 + s/\omega_b}$



At ω_T :

$$|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}}$$

$$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \boxed{\omega_T = A_0 \omega_b}$$

Gain-Bandwidth Product


For $\omega \gg \omega_b$:

$$A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f} \left[\begin{array}{l} \text{Integrates w/ time} \\ \text{Constant } \tau = \frac{1}{\omega_T} \end{array} \right]$$

The unity gain bandwidth f_T is usually specified on op amp data sheets. Knowing f_T , one can easily determine the op amp gain at a given frequency f .

Frequency Response of Closed Loop Amplifiers

Example. Non-Inverting Amplifier

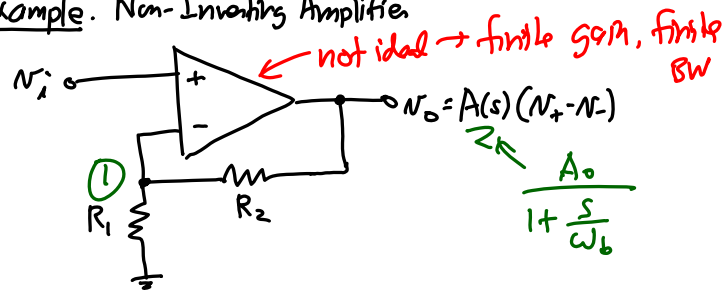

Find an expression for the gain as a function of frequency.

① Brute force derivation:

$$\text{KCL @ ①: } \frac{N_o - N_-}{R_2} = \frac{N_-}{R_1} \rightarrow \frac{N_o}{R_2} = N_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$



$$\frac{N_o}{R_2} = \left(N_i - \frac{N_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{N_o(s)}{N_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$$

$$\left[A(s) = \frac{A_o}{1 + \frac{s}{w_b}} \right] \rightarrow \frac{N_o(s)}{N_i(s)} = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_o w_b \left(\frac{R_1}{R_1 + R_2} \right)}}$$

(after algebra)


Neg. FB Block Diagram

② More insightful way to do this:

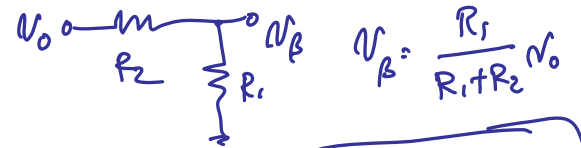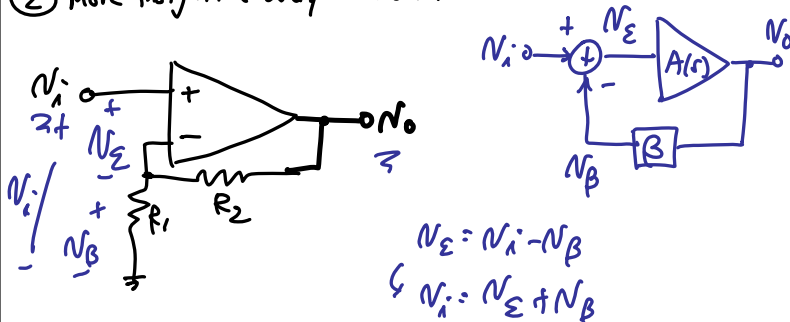

$$B = \frac{N_\beta}{N_o} = \frac{R_1}{R_1 + R_2}$$

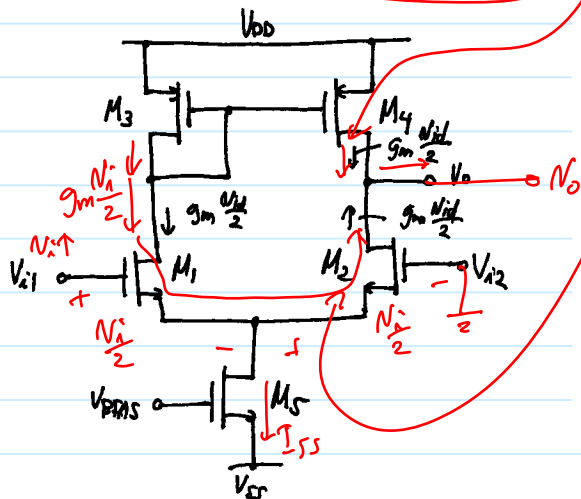MOS Differential Stage w/ Current Mirror Load



from bottom from top

$$V_o = \left(\frac{g_m}{2} V_i + \frac{g_m}{2} V_i \right) R_o = \frac{V_o}{N_i} = g_m R_o$$

$$= g_m (r_{o2} || r_{o4}) = \frac{V_o}{N_i}$$


Adm

What is R_o ?

Go to the main lecture page

$R_o = (r_{o2} || r_{o4}) \dots$ but not by inspection!

CMRR-

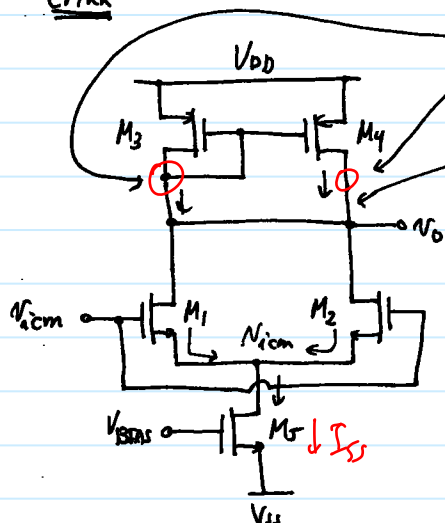


for $M_1 = M_2$ & $M_3 = M_4$

$V_{DS} = V_{DS}$ (they track each other)

⇒ Thus, can short the drains of M_3 & M_4

provided the ckt. is completely symmetrical.

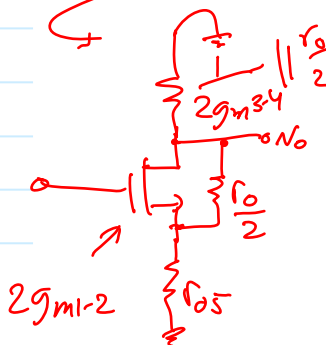truly symmetric → we can draw a half ckt.
or just combine the two ckt. together!



$$A_{cm} = - \frac{2g_{m1-2} \left(\frac{1}{2g_{m3-4}} \right)}{1 + 2g_{m1-2} r_{o5}}$$

Thus:

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1-2} (r_{o1-2} || r_{o3-4}) (1 + 2g_{m1-2} r_{o5}) \left(\frac{g_{m3-4}}{g_{m1-2}} \right)$$


$$CMRR = (1 + 2g_{m1-2} r_{o5}) g_{m3-4} (r_{o1-2} || r_{o3-4})$$

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep M_5 saturated

$$V_{icm(min)} = CMR^- = V_{SS} + V_{ovs5} + V_{GS1,2} = V_{SS} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} (W/L)_5}} + V_{t1,2} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox} (W/L)_{1,2}}}$$

High End - keep M_1, M_2 saturated

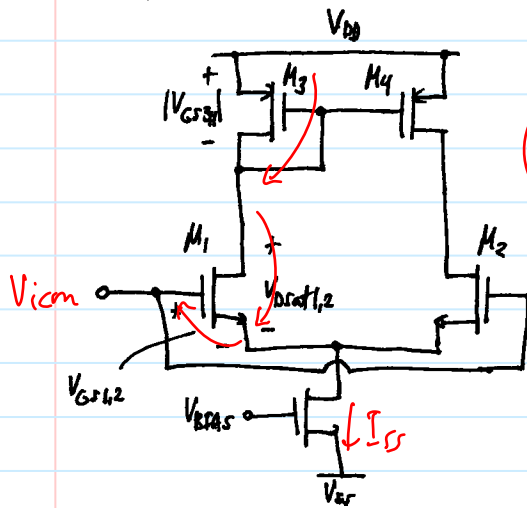

$$V_{icm(max)} = CMR + = V_{DD} - |V_{GS3,4}| - V_{ov1,2} + V_{GS1,2}$$

$$V_{icm(max)} = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{3,4}}} - |V_{t3,4}| + V_{t1,2}$$


Device Mismatch Effect in Diff. Amplifiers

⇒ up to this point, we assumed that Q_1 & Q_2 are perfectly matched

⇒ in actual ckt., got device mismatches due to processing variations

The Result:

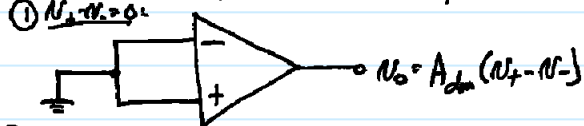① $N_+ \neq N_-$ → Output not zero when Input is zero → $N_{od} \neq 0$ when $N_{id} = 0$!



Ideal Case: $N_o = 0$

Reality: $N_o \neq 0$, even w/ $(N_+ - N_-) = 0$!

② Input $I_{B1} \neq I_{B2}$ if Q_1 & Q_2 not matched. (for BJT & JFET only.)


To model these effects, introduce:

① Input Offset Voltage, V_{os}


② Input Offset Current, I_{os}

Typ. $I_{os} = 10 \text{ nA}$ for BJT

Typ. 1-5 mV for BJT

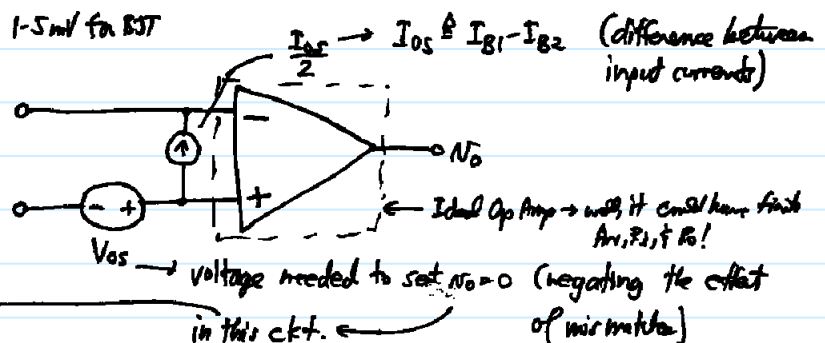Effect of V_{os} on Op Amp Ckt. -

Example. Integrator

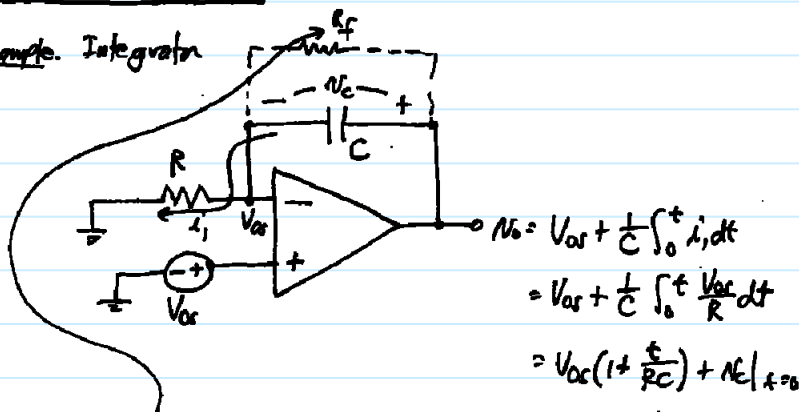

Fix: Place an R_F in shunt w/ the C


→ then $N_o = V_{os}(1 + \frac{R_F}{R})$, and railing doesn't happen

→ but, usually R_F is large to allow the C to dominate

the integrator Xfer Function $\therefore N_o = V_{os}(1 + \frac{R_F}{R})$ can be quite large → still want $V_{os} = \text{small}$

will continue to increase until op amp hits the voltage rails

V_{os} is even more important in setting the resolution of AD converters and other precision ckt.

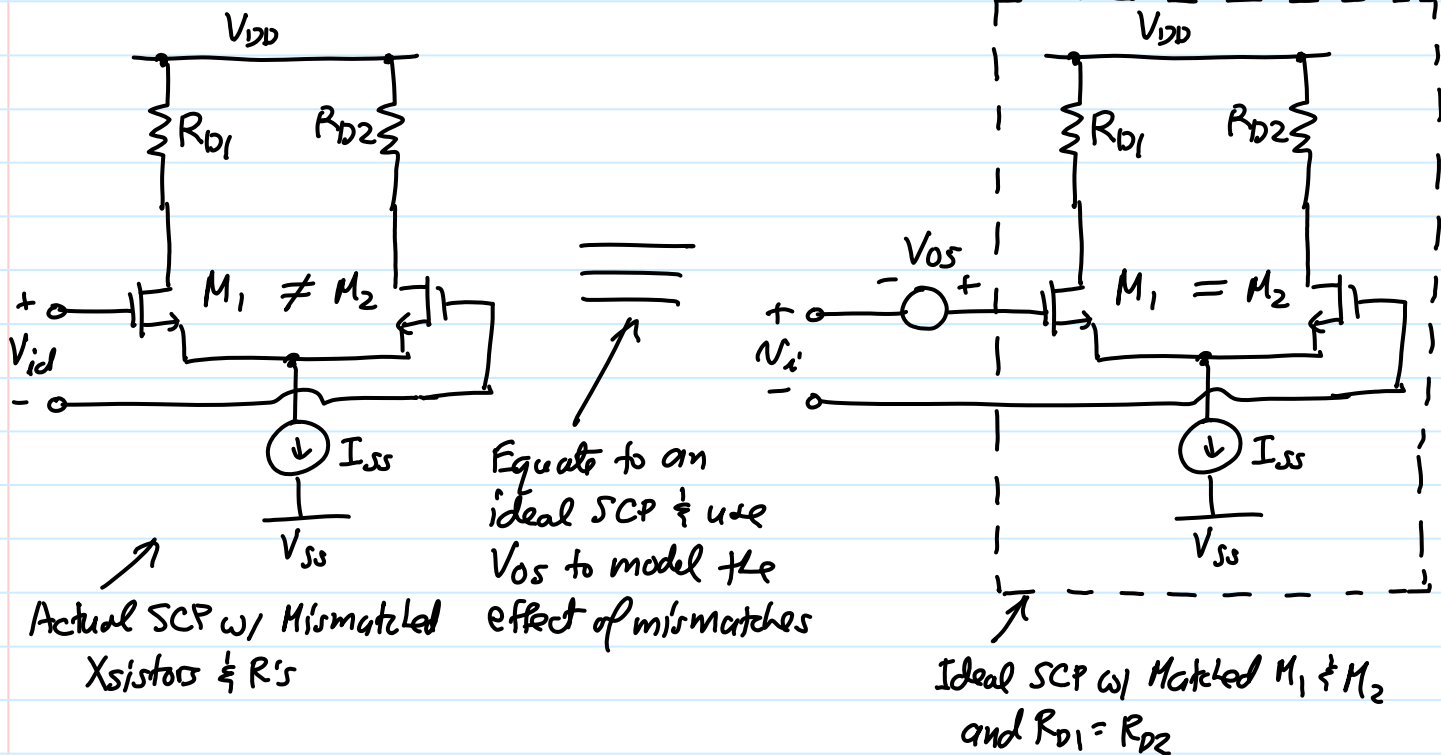V_{OS} of a Mismatched SCPObjective: Derive an expression for V_{OS} .Input offset voltage V_{OS} arises due to variations in:

- ① Xsistors, $M_1 \neq M_2 \rightarrow \frac{W}{L}$ and V_t vary
- ② $R_{D1} \neq R_{D2} \rightarrow$ causes gain variation

Definition. $V_{OS} = V_{id}$ to get $V_{od} = 0$ in this ckt.

$$\text{KVL: } V_{OS} - V_{GS1} + V_{GS2} = 0$$

$$\therefore V_{OS} = V_{GS1} - V_{GS2} = V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\begin{array}{l} \rightarrow \Delta I_D = I_{D1} - I_{D2} \\ \rightarrow I_D = \frac{I_{D1} + I_{D2}}{2} \end{array} \quad \left| \quad \begin{array}{l} \Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2 \\ \left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right] \end{array} \quad \left| \quad \begin{array}{l} \Delta V_t = V_{t1} - V_{t2} \\ V_t = \frac{V_{t1} + V_{t2}}{2} \end{array} \quad \left| \quad \begin{array}{l} \Delta R_D = R_{D1} - R_{D2} \\ R_D = \frac{R_{D1} + R_{D2}}{2} \end{array} \right.$$

Rearranging:

$$I_{D1} = I_D + \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} \quad V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} \quad V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Substituting into (1):

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \frac{\Delta I_D}{2})}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right) \right]}} - \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right) \right]}}$$

$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right] \rightarrow \frac{2I_D(1 + \frac{\Delta I_D}{2I_D})}{\frac{W}{L} [1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}]} - \frac{2I_D(1 - \frac{\Delta I_D}{2I_D})}{\frac{W}{L} [1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}]}$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \sqrt{\frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}}} - \sqrt{\frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}}} \right\}$$

Binomial Theorem:

$$(1 + nx)^m \xrightarrow{n \text{ small}} 1 + mn x$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{OS} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2} \rightarrow$ mismatch in I_D must be opposite

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ -\frac{\Delta R}{R} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

that of R_D

$$\frac{\Delta I_D}{I_D} = -\frac{\Delta R_D}{R_D}$$

Threshold
Mismatch


Geometric (i.e., Layout)
Variation

scale w/ overdrive


bias independent

V_{OS} in a Mismatched ECP

Objective: Derive an expression for V_{OS} .

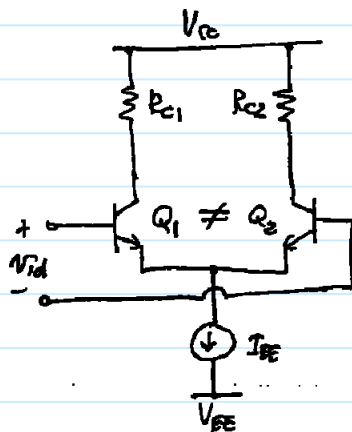Actual ECP w/ Mismatched Q_1 & Q_2 & R 's

Equivalent to an ideal ECP + use V_{OS} & I_{SS} to model the effect of mismatches

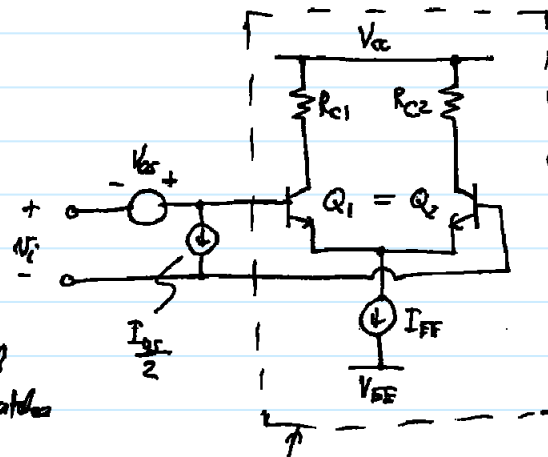Ideal ECP w/ Matched Q_1 & Q_2 and $R_{c1} = R_{c2}$

Input Offset Voltage V_{OS} arises due to variations in:

① $Q_1 \neq Q_2 \rightarrow I_S \neq \beta$ vary:

$$I_S = \frac{q n_i^2 D_n A}{N_A W_B (V_{CB})}$$

"function of"

$I_{S1} \neq I_{S2}$ can be caused by:

- (i) $A_1 \neq A_2$ (etching tolerance limits)
- (ii) $N_{A1} \neq N_{A2}$ (doping variations of base)
- (iii) $W_B \neq f(V_{CB})$ (width variations exacerbated by V_{CB} diff)

② $R_{c1} \neq R_{c2} \rightarrow$ cause gain variation

Definition: $V_{OS} = V_{id}$ to get $V_{od} = 0$, which occurs when:

$$KVL: V_{OS} - V_{be1} + V_{be2} = 0$$

$$V_{OS} = V_{be1} - V_{be2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}} = V_T \ln \left(\frac{I_{C1}}{I_{C2}} \frac{I_{S2}}{I_{S1}} \right)$$

Find $\frac{I_{C1}}{I_{C2}}$ in terms of design elements:

$$[\text{When } V_{id} = V_{OS} \rightarrow V_{od} = 0] \rightarrow V_{od} = (V_{CC} - I_{C1} R_{c1}) - (V_{CC} - I_{C2} R_{c2}) = 0$$

$$I_{C1} R_{c1} = I_{C2} R_{c2} \rightarrow \frac{I_{C1}}{I_{C2}} = \frac{R_{c2}}{R_{c1}}$$

$$V_{OS} = V_T \ln \left(\frac{R_{c2}}{R_{c1}} \frac{I_{S2}}{I_{S1}} \right)$$

This is an exact equation for V_{OS} . It's often more useful & intuitive to express this in terms of percent variations (and eventually standard deviations).

Convert to Percent Variation Form -

Define: $R_c = \frac{R_{c1} + R_{c2}}{2}$, $\Delta R_c = R_{c1} - R_{c2}$ } Objective: Express Var in terms of percent variations $\frac{\Delta R_c}{R_c} \neq \frac{\Delta I_s}{I_s}$.

$I_s = \frac{I_{s1} + I_{s2}}{2}$, $\Delta I_s = I_{s1} - I_{s2}$ }

In general: $\Delta X = X_1 - X_2$ } $X_1 = X + \frac{\Delta X}{2}$ } \Rightarrow Thus: $R_{c1} = R_c + \frac{\Delta R_c}{2}$, $R_{c2} = R_c - \frac{\Delta R_c}{2}$

$X = \frac{X_1 + X_2}{2}$ } $X_2 = X - \frac{\Delta X}{2}$ } $I_{s1} = I_s + \frac{\Delta I_s}{2}$, $I_{s2} = I_s - \frac{\Delta I_s}{2}$

With these formulations:

$$V_{OS} = V_T \ln \left[\frac{R_{c2}}{R_{c1}} \frac{I_{s1}}{I_{s2}} \right] = V_T \ln \left\{ \frac{R_c - \frac{\Delta R_c}{2}}{R_c + \frac{\Delta R_c}{2}} \frac{I_s + \frac{\Delta I_s}{2}}{I_s - \frac{\Delta I_s}{2}} \right\} = V_T \ln \left\{ \frac{1 - \frac{\Delta R_c}{2R_c}}{1 + \frac{\Delta R_c}{2R_c}} \frac{1 + \frac{\Delta I_s}{2I_s}}{1 - \frac{\Delta I_s}{2I_s}} \right\}$$

$$\left[\ln(1+x) \approx x - \frac{x^2}{2} + \frac{x^3}{3} - \dots \right] \Rightarrow V_{OS} \approx V_T \left\{ -\frac{\Delta R_c}{2R_c} - \frac{\Delta R_c}{2R_c} - \frac{\Delta I_s}{2I_s} - \frac{\Delta I_s}{2I_s} \right\}$$

taking the first term assuming $\Delta R \ll R_c$ & $\Delta I_s \ll I_s$

$$V_{OS} = V_T \left\{ -\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s} \right\}$$

Since $\frac{\Delta R_c}{R_c}$ and $\frac{\Delta I_s}{I_s}$ are statistically ^{varying} parameters for


given process run & layout, one usually expresses terms in the form of variances when specifying V_{OS} :

\rightarrow since $\frac{\Delta R_c}{R_c} \neq \frac{\Delta I_s}{I_s}$ are uncorrelated, their variances add like power:

$$\sigma_{Var} = V_T \sqrt{\sigma_{\Delta R_c/R_c}^2 + \sigma_{\Delta I_s/I_s}^2}$$

Ex: Typ. $\sigma_{\Delta R_c/R_c} \sim 0.01$, $\sigma_{\Delta I_s/I_s} \sim 0.05$
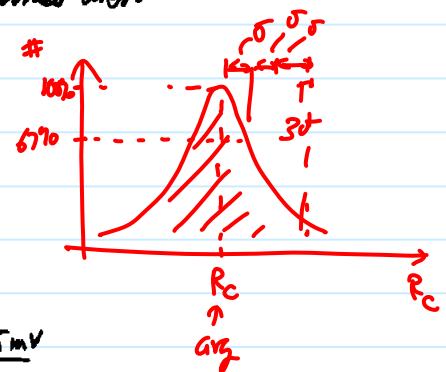
$$\therefore \sigma_{V_{OS}} = (26m) \sqrt{(0.01)^2 + (0.05)^2} = 1.3mV \quad \text{Typ. Var for BJT} \sim 1-5mV$$



V_{OS} Drift w/ Temperature

$$\frac{dV_{OS}}{dT} = \frac{kT}{q} \left\{ -\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s} \right\} \frac{1}{T} = \frac{Var}{T}$$

indep. w/ T [in Kelvin]

Ex: $\frac{dV_{OS}}{dT} = \frac{1.3m}{300K} = 4.3 \mu V/K$ ^{drift} around $T = 300K$.

I_{OS} in a Mismatched ECP

By Definition: $I_{OS} = I_{B1} - I_{B2} = \frac{I_{C1}}{\beta_1} - \frac{I_{C2}}{\beta_2} = I_{OS}$

To express in percent variations:

$$\begin{cases} I_{C1} = I_C + \frac{\Delta I_C}{2} \\ I_{C2} = I_C - \frac{\Delta I_C}{2} \end{cases} \quad \begin{cases} \beta_1 = \beta + \frac{\Delta \beta}{2} \\ \beta_2 = \beta - \frac{\Delta \beta}{2} \end{cases}$$

$$\therefore I_{OS} = \frac{I_C + \frac{\Delta I_C}{2}}{\beta + \frac{\Delta \beta}{2}} - \frac{I_C - \frac{\Delta I_C}{2}}{\beta - \frac{\Delta \beta}{2}} = \frac{I_C}{\beta} \left\{ \frac{1 + \frac{\Delta I_C}{2I_C}}{1 + \frac{\Delta \beta}{2\beta}} - \frac{1 - \frac{\Delta I_C}{2I_C}}{1 - \frac{\Delta \beta}{2\beta}} \right\}$$

$$\left[\frac{1}{1+x} \approx 1 - x + x^2 - \dots \right] \rightarrow = \frac{I_C}{\beta} \left\{ \left(1 + \frac{\Delta I_C}{2I_C}\right) \left(1 - \frac{\Delta \beta}{2\beta}\right) - \left(1 - \frac{\Delta I_C}{2I_C}\right) \left(1 + \frac{\Delta \beta}{2\beta}\right) \right\}$$

$$= \frac{I_C}{\beta} \left\{ 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} - \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} - 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} + \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} \right\}$$

$$I_{OS} = \frac{I_C}{\beta} \left\{ \frac{\Delta I_C}{I_C} - \frac{\Delta \beta}{\beta} \right\}$$


But for $V_{od} = 0V \Rightarrow \frac{I_{C1}}{I_{C2}} = \frac{R_{C2}}{R_{C1}} \rightarrow \frac{\Delta I_C}{I_C} = - \frac{\Delta R_C}{R_C}$

$$\therefore I_{OS} = - \frac{I_C}{\beta} \left(\frac{\Delta R_C}{R_C} + \frac{\Delta \beta}{\beta} \right)$$

Ex. Typ: $\sigma_{\Delta R_C} = 0.1$, $\sigma_{\Delta \beta} = 0.01$

$$\Rightarrow I_{OS} = - \frac{I_C}{\beta} \left[\sigma_{\Delta R_C}^2 + \sigma_{\Delta \beta}^2 \right]^{1/2} \approx -0.1 \frac{I_C}{\beta} \approx -0.1 I_B = I_{OS}$$

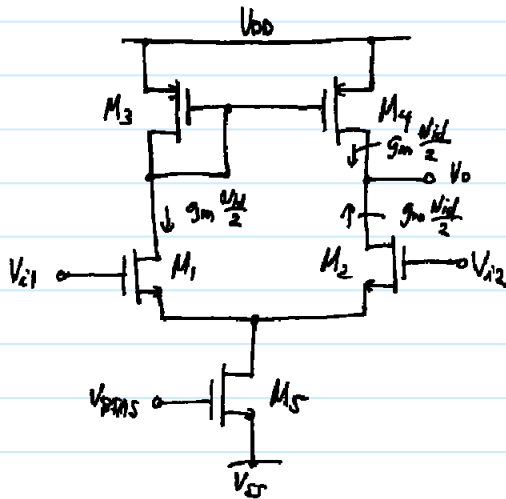MOS Differential Stage w/ Current Mirror Load



Small-Signal Gain: (similar to BJT)

$$\frac{V_o}{V_{id}} = g_{m2}(r_{o2} \parallel r_{o4}) = \frac{g_{m2}}{g_{ds2} + g_{ds4}} = \frac{\sqrt{2\mu_n C_{ox} (\frac{W}{L})_2 I_{D2}}}{\lambda_2 I_{D2} + \lambda_4 I_{D4}}$$

$$= \frac{\sqrt{\mu_n C_{ox} (\frac{W}{L})_2 I_{D2}}}{\frac{I_{D2}}{2} (\lambda_2 + \lambda_4)} \Rightarrow \frac{V_o}{V_{id}} = \frac{2}{\lambda_2 + \lambda_4} \sqrt{\frac{\mu_n C_{ox} (W/L)_2}{I_{D2}}}$$

$$\left[\frac{\Delta(W/L)_{1,2}}{(W/L)_{1,2}} - \frac{\Delta(W/L)_{3,4}}{(W/L)_{3,4}} \right]$$

Offset Voltage - $V_{OS} = V_{GS1} - V_{GS2}$ when $V_{od} = 0V$

$$V_{OS} = \Delta V_{t1,2} + \Delta V_{t3,4} \left(\frac{g_{m3,4}}{g_{m1,2}} \right) + \frac{(V_{GS} - V_t)_{1,2}}{2} \left[\frac{\Delta k_{1,2}}{k_{1,2}} + \frac{\Delta k_{3,4}}{k_{3,4}} \right]$$

For small V_{OS} : ① small $(V_{GS} - V_t)$

$$\text{② } g_{m3,4} < g_{m1,2} \rightarrow k_{3,4} < k_{1,2} \text{ } \frac{1}{2} \left(\frac{W}{L} \right)_{3,4} < \left(\frac{W}{L} \right)_{1,2}$$

Via similar derivation to what we just did