

Lecture 17: Compensation & Slew Rate

• Announcements:

- ↳ Video and sound of the make-up lecture are available online; the pdf of the notes were emailed last Friday
- ↳ 1<sup>st</sup> 5 min. of video is corrupt → just advance through this to get to good stuff
- ↳ Lab#2 will be due the week AFTER Spring Break; this should give ample time to write up a good lab report
- ↳ Midterm Exam, Thursday, March 17, in 213 Wheeler (our regular room), during the regular class period

• Lecture Topics:

- ↳ High Gain Op Amps (cont.)
- ↳ Lab#2 Compensation (a 1<sup>st</sup> pass)
- ↳ Slew Rate

• Last Time:

- Covered the telescopic op amp

Problem / Issue:

① Limited output swing:

$$V_{omax} = V_{DD} - (|V_{t7}| + |V_{ov7}| + |V_{t5}| + |V_{ov5}| + |V_{t6}| + |V_{ov6}| - |V_{ov6}|)$$



$$V_{omin} = V_{ovss} + V_{ov2} + V_{ov4}$$

↑  
from tail current source

$$V_{swing} = V_{omax} - V_{omin}$$


Swing not enough!  
↓  
problem!

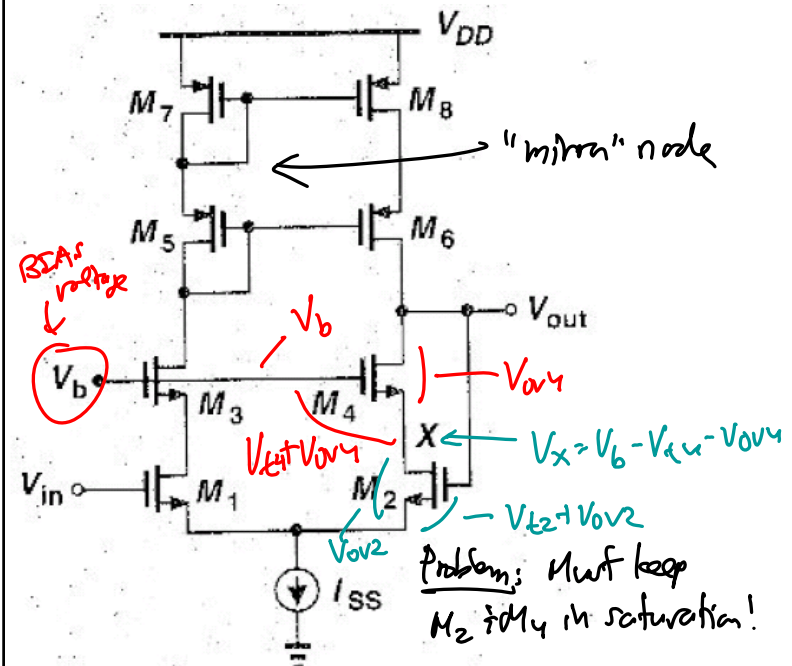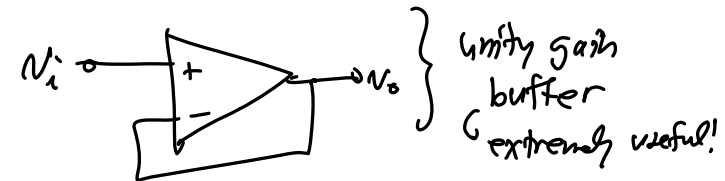Problem ②: Difficult to tie the input to the output!



M<sub>4</sub>: Need  $V_{out} \geq V_b - V_{t4} - V_{ov4}$   
 $\therefore V_{out} \geq V_b - V_{t4}$

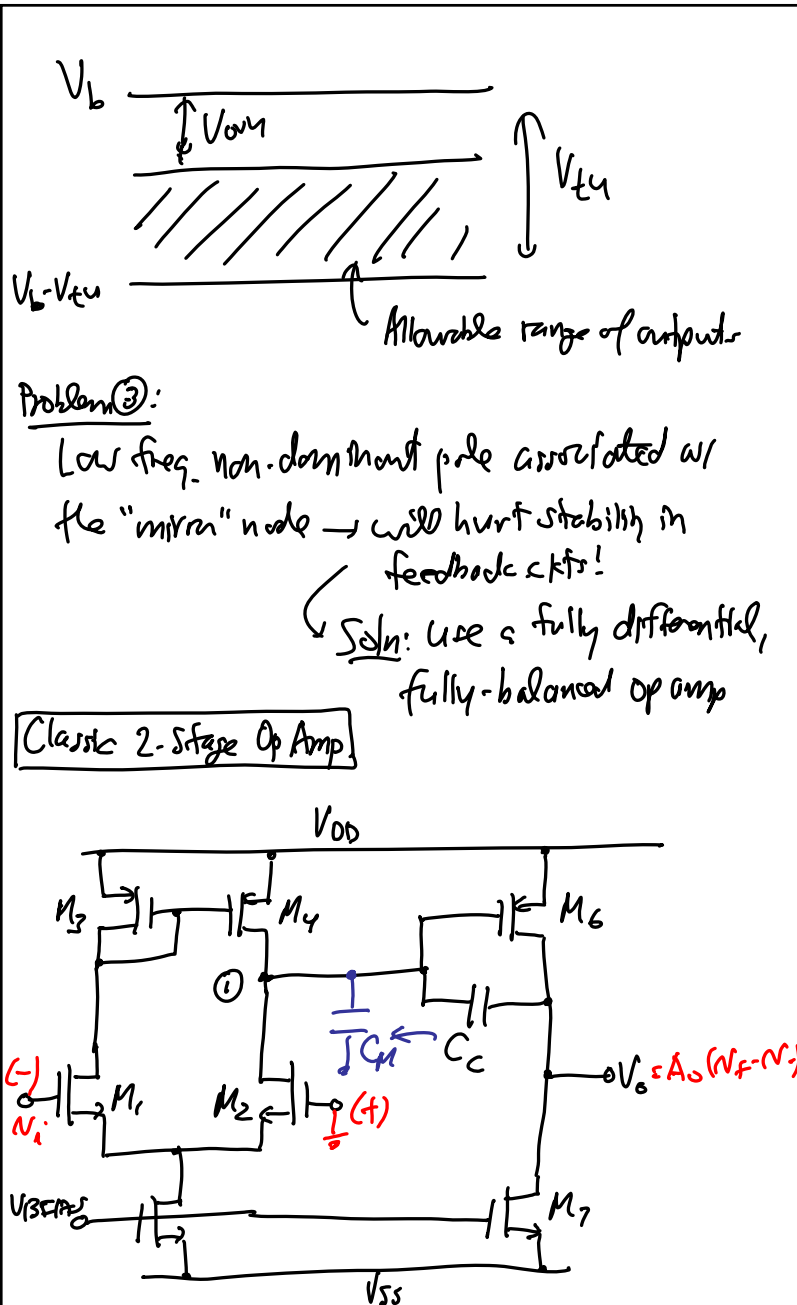M<sub>2</sub>: Need  $V_{out} \leq V_x - V_{ov2} + V_{t2} + V_{ov2}$   
 $V_{out} \leq V_b - V_{t4} - V_{ov4} + V_{t2} \approx V_b - V_{ov4}$   
 $V_{t2} \approx V_{t4}$



Gain -

1<sup>st</sup> stage:  $A_{v1} = \frac{V_O}{V_i} = g_{m1}(r_{o2} || r_{o4})$


2<sup>nd</sup> stage:  $A_{v2} = \frac{V_O}{V_O} = -g_{m6}(r_{o6} || r_{o7})$


$A_v = A_{v1} A_{v2} = -g_{m2}(r_{o2} || r_{o4}) g_{m6}(r_{o6} || r_{o7})$

Output Swing:

$V_{o,swing} = V_{DD} - V_{DS} - |V_{ov6}| - V_{ov7}$

Freq. Response:

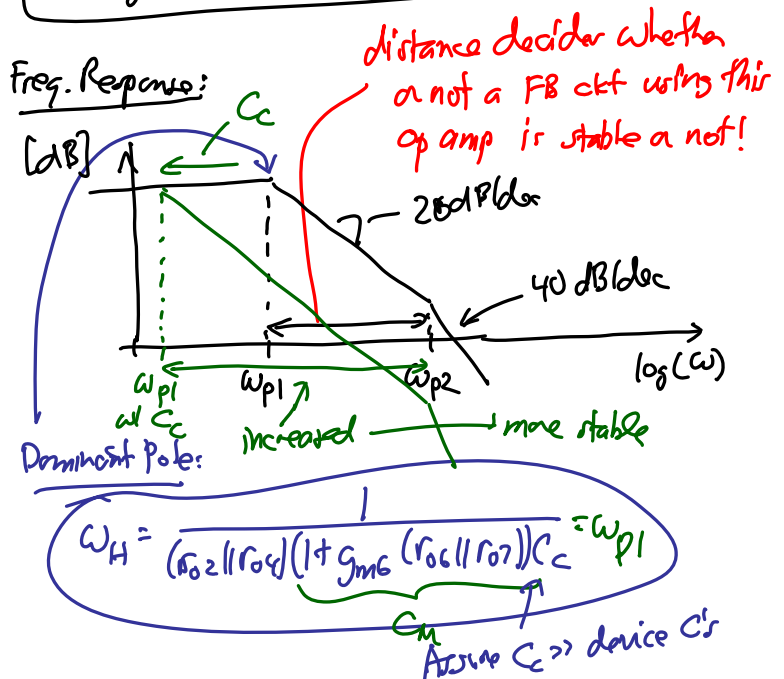


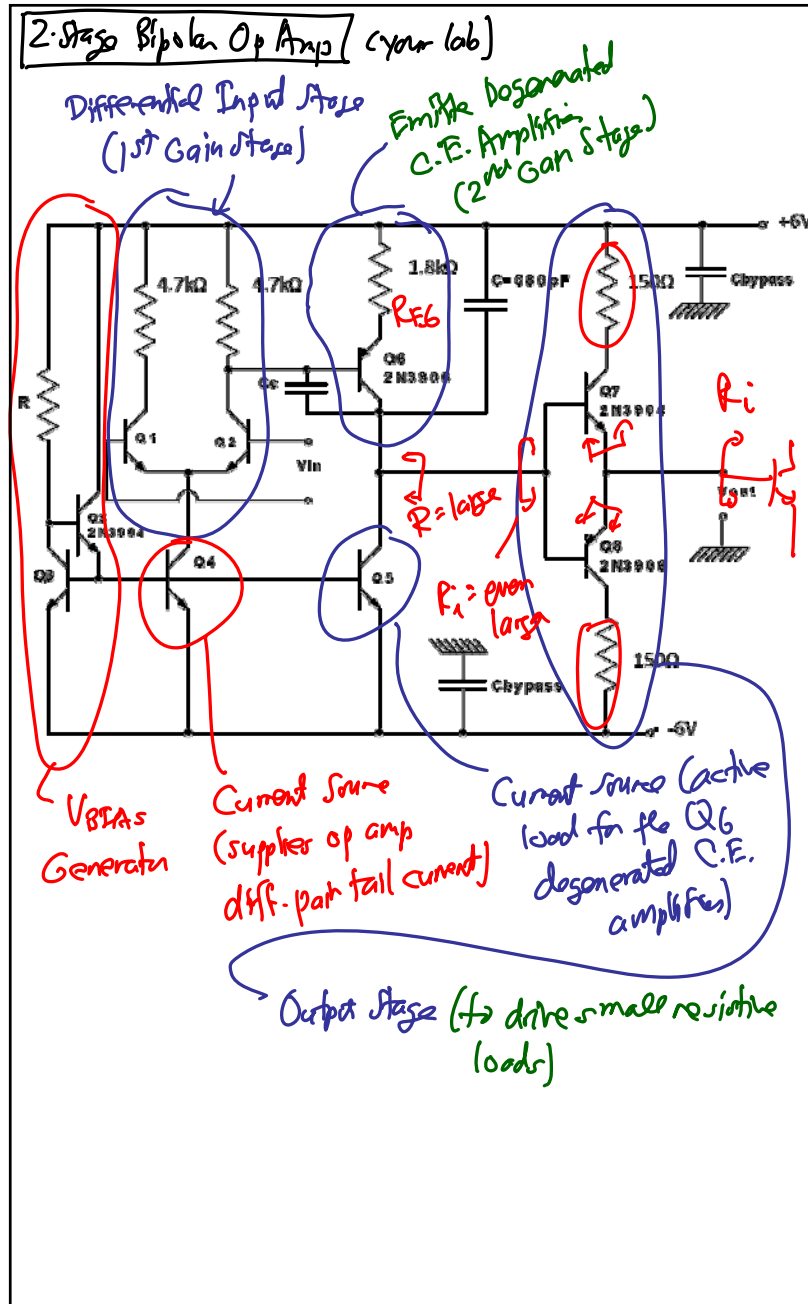

Remarks.

- ① You analyze this in Lab#2.
- ② Usually, the resistively-loaded diff. pair is replaced w/ an active current mirror load for more gain.
- ③  $R_{E6}$  raises the input R of  $Q_6$  (of the 2<sup>nd</sup> gain stage), plus helps w/ biasing.
- ④ Same comment as ③ for the output stage.
- ⑤ Output stage needed when driving a resistive load

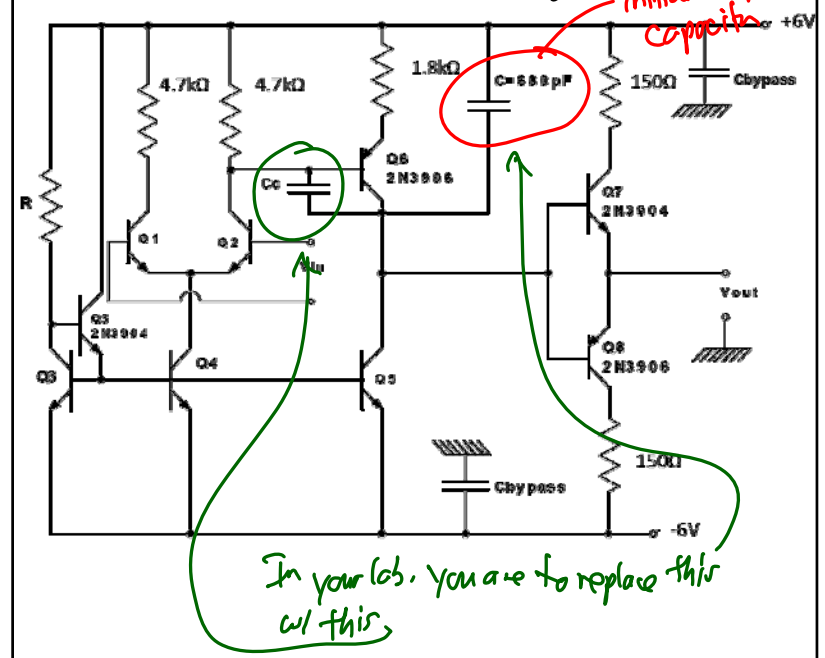often the case for bipolar  
not often the case for MOS, where a capacitive load  $C_L$  is often more relevant → MOS op amps often don't need output stages!





In your lab, simply choose  $C_c$  so that it generates the same  $\omega_{p1}$  as the original  $C = 680$  pF.

(again, all for stability reasons)

all related to keeping  $\omega_{p1}$  &  $\omega_{p2}$  as far apart as needed for stability.

### Slew Rate

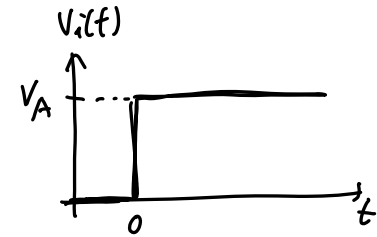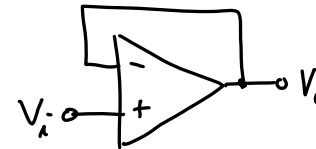

Using Laplace Xform Theory:

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + \frac{s}{\omega_1}} = \frac{1}{1 + s\tau_1}$$


single (dominant) pole

$$V_i(s) = \frac{V_A}{s}$$


$$V_o(s) = \frac{V_A}{s(1 + s\tau_1)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_1}}$$

Inverse Laplace Xform

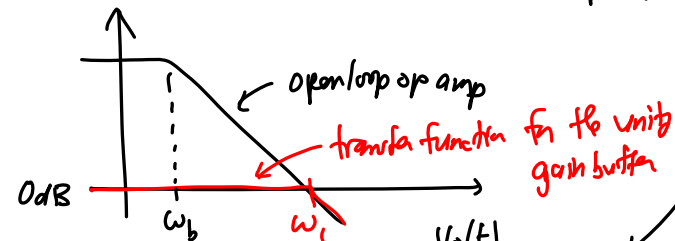
$$V_o(t) = V_A(1 - e^{-t/\tau_1}) \leftarrow \text{expected response}$$





Expectation

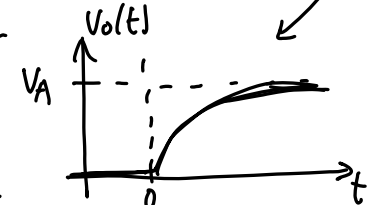

Actually:  
Why this slow rise?

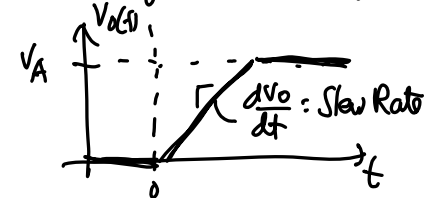

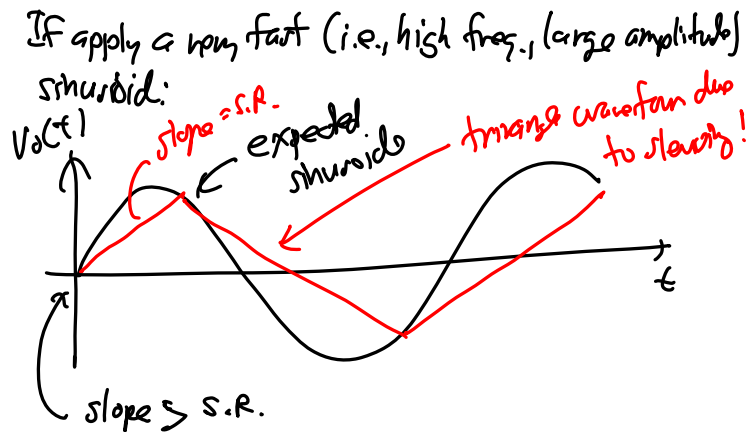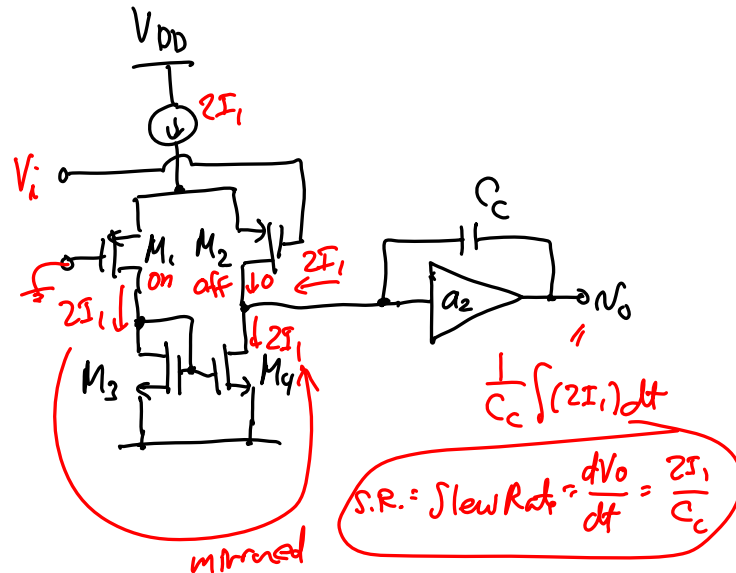Reason 1<sup>st</sup> or 2<sup>nd</sup> stage of an op amp cannot source enough current to mimic the slope (or speed) of a fast rising signal



If compensate w  $C_c$ :

