

## Lecture 21: Choosing Cc

### Announcements:

- ↳ Your project cannot use ideal current sources; all you have is Vdd and Vss
- ↳ You need to design your own current sources if you need them
- ↳ You should also try to minimize area, as usual (e.g., a design using an enormous resistor will not be as good as one using a much smaller one, or no resistor at all)


### Lecture Topics:

- ↳ Narrowbanding
- ↳ Pole-Splitting
- ↳ Choosing Cc

### Last Time:
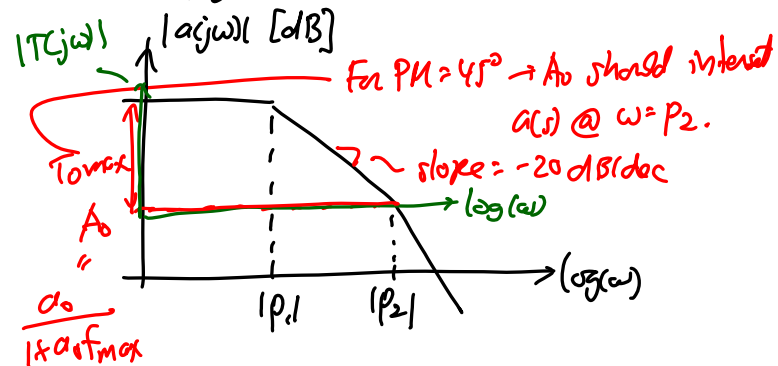
#### Compensation of Op Amps

To compensate need the distance between  $p_1$  &  $p_2$  to be large enough to accommodate the largest desired loop gain.



$$20(\log |p_2| - \log |p_1|) = 20 \log(T_{\max})$$

$$\frac{|p_2|}{|p_1|} = T_{\max} \rightarrow |p_2| = |p_1| T_{\max}$$

largest desired loop gain

provided  $|p_3| \gg |p_2|$

Need for stability w/  $PM = 45^\circ$  @  $A_0$   
desired closed loop gain

Basically, there is a minimum separation needed betw.  $p_1$  &  $p_2$ !


### Two Ways to Compensate:

- ① Narrowbanding
- ② Pole-Splitting

#### Narrowbanding

introduce a pole  $p_0$  so that there is sufficient separation between  $p_1$  &  $p_2$

dominant pole

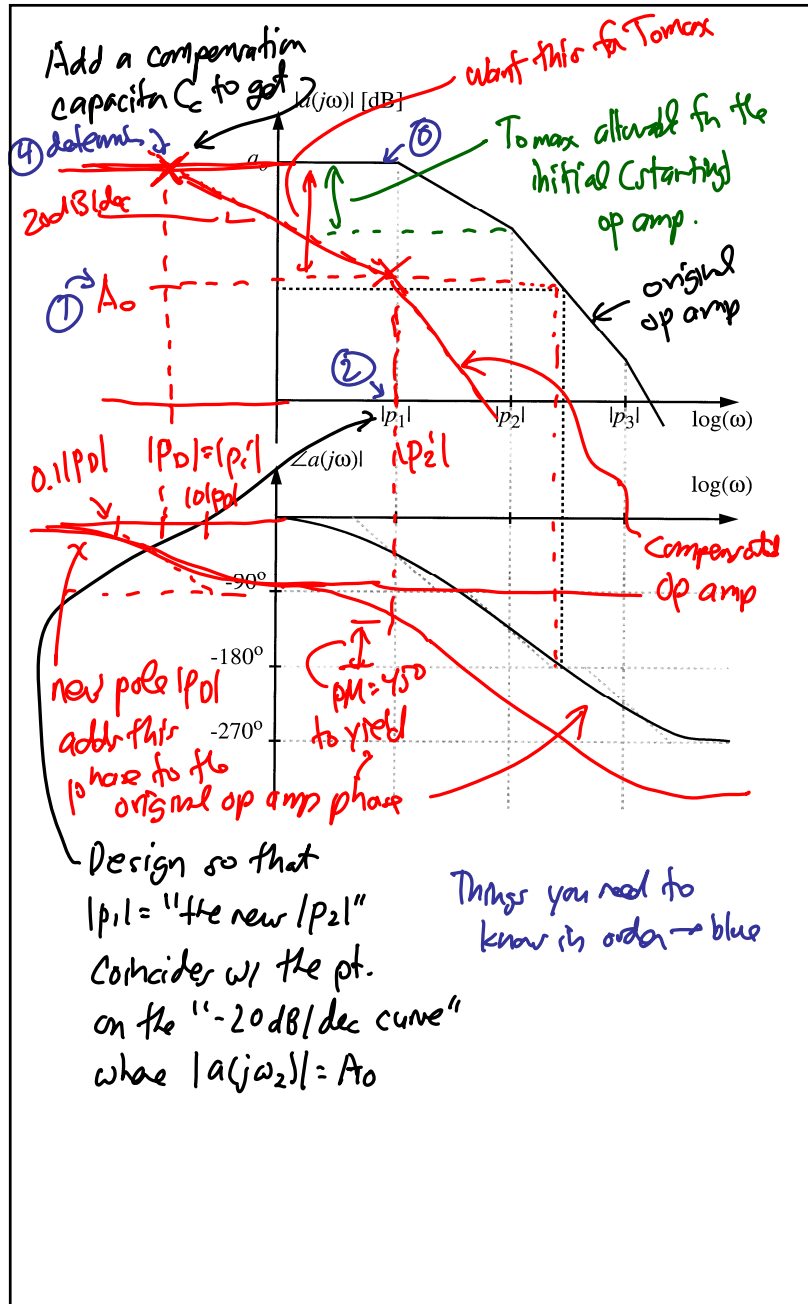

### Remember on Narrowbanding]


- ① Assumption:  $p_1, p_2, p_3$  don't move when  $p_0$  is introduced (often not true, but that's normal isn't that big)
- ② Summarize choose  $p_0$  such that  $|T(j\omega)| = 0 \text{ dB} = 1$
- ③ Why do this? Isn't pole-splitting much better?  
 ↓  
 Do it when you have no other choice, e.g., when you have a packaged op amp & have access to only a few terminals (not to the optimum compensation node)  
 @  $p_1$  (which becomes the 2nd most dominant pole)  
 original ( $|p_2| \gg |p_1|$ )
- ④  $|p_0| = \frac{|p_1|}{T_{0\max}}$  ← maximum expected/needed loop gain

### Problem:

- ① often,  $|p_0| < |p_1| \therefore f_{3\text{dB}}$  BW of the op amp will be very small
- ②  $\omega_{\text{closed loop}} = |p_1|$  which isn't that large

### Solution: Pole-Splitting

- move  $|p_1|$  down & either keep  $|p_2|$  still or move  $|p_2|$  up simultaneously!
- ①  $\omega_{3\text{dB}} = |p_1|$
  - ②  $\omega_{\text{closed loop}} = |p_2|$

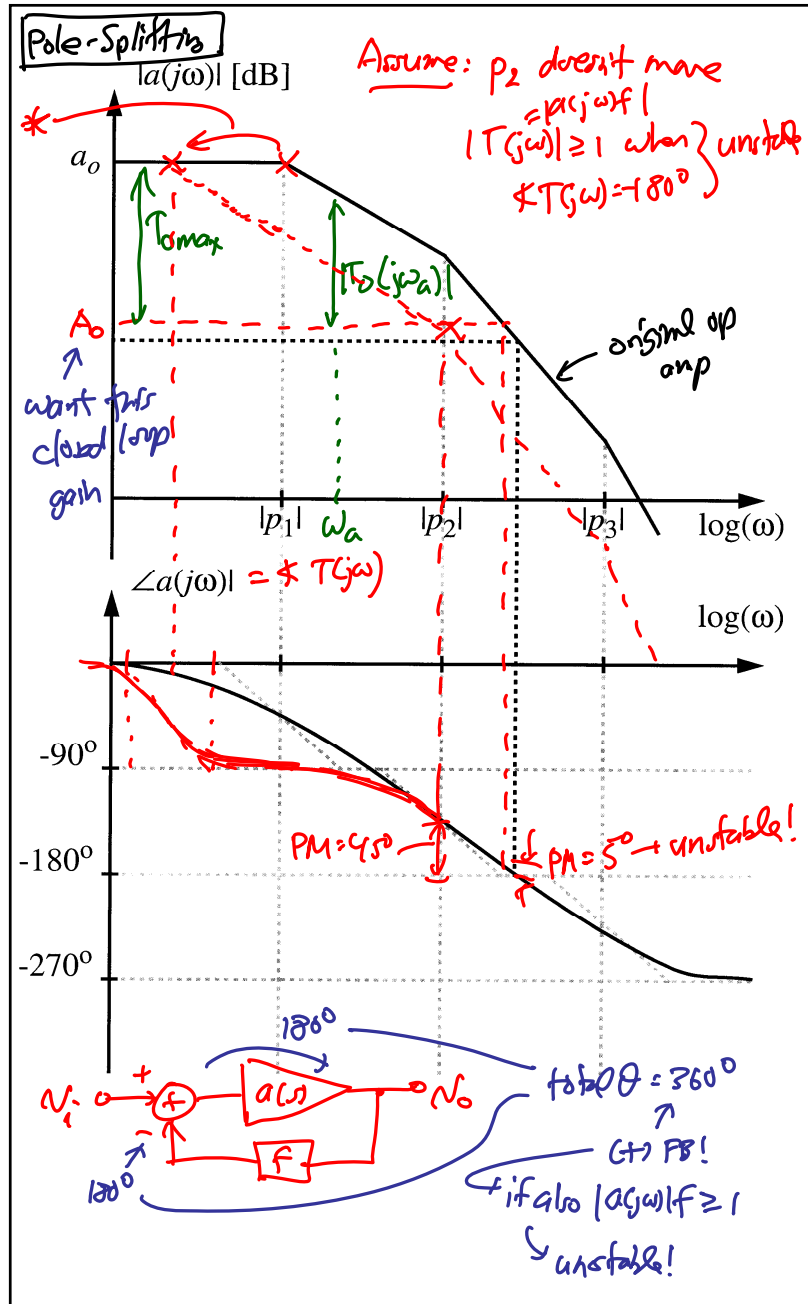

\* push  $p_1$  down so that the "20 dB/dec" portion of  $a(j\omega)$  intersects the " $|T(j\omega)| = 1$  pt." at  $|a(j\omega)| = A_0 \rightarrow$  gives  $45^\circ$  phase margin


Remark for Pole-Splitting 1

① For pole-splitting,  $|p_1'| = \frac{|p_2|}{T_{\max}}$

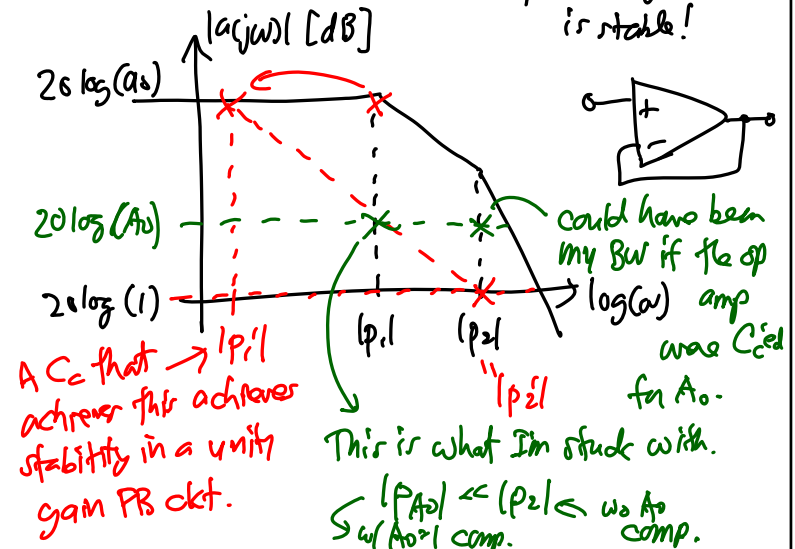**Unity Gain Stable Op Amps**

(e.g., 741 op amp)

If it's compensated monolithically so that even a unity FB ckt. is stable  $\rightarrow$  i.e., a voltage follower is stable!



Choosing  $C_c$  (assume no RHP zero &  $|p_3| \gg |p_2|$ )  
 $\Rightarrow$  assume  $\frac{1}{sC_c} \ll$  (surrounding impedance) @ high freq.

① Case: Two-Stage Amplifier, Miller Compensation

of op amp  
 of the transconductance:  $V \rightarrow i$  gain  
 $i_o = -G_{m1}V_i$   
 $R_D = \text{very large!}$   
 $R_S = 0$  (ideal)  
 $R_S = \infty$  (ideal)  
 $N_{eff} \text{ Equiv. (ideal, } R_S = \infty)$

$V_o = \frac{i_{ix}}{sC_c}$   
 $i_{ix} = G_{m1}V_i$   
 $V_o = \frac{G_{m1}}{sC_c} V_i \rightarrow \frac{V_o}{V_i}(s) = \frac{G_{m1}}{sC_c}$

$| \frac{V_o}{V_i}(j\omega) |_{dB}$   
 $A_0$   
 $(p_2)$   
 $\log(\omega)$   
 for PM = 45°  
 does not apply here

$\left| \frac{V_o}{V_i}(j\omega) \right| = \frac{G_{m1}}{\omega C_c} \Rightarrow$  this should equal  $A_0$  @ the freq  $\omega$  corresponding to the target phase margin

For PM = 45°:

$\omega_{ult} = \omega @ |T(j\omega)| = 1$

"unity loop transmission"

For PM = 45°  $\rightarrow \omega_{ult} = \omega_2$

freq. of the 2nd pole in the  $a(j\omega)$  transfer fn.

$\left| \frac{V_o}{V_i}(j\omega) \right| = A_0 = \frac{G_{m1}}{\omega_2 C_c}$

$C_c = \frac{G_{m1}}{\omega_2 A_0}$


For PM = 45° (provided high order poles are far away, i.e.,  $|p_3| \gg |p_2|$ )

PM = 60°:

$\omega_{ult} = \frac{\omega_2}{1.73} \rightarrow \left| \frac{V_o}{V_i}(j\frac{\omega_2}{1.73}) \right| = A_0 = \frac{G_{m1}}{(\frac{\omega_2}{1.73})C_c}$

$C_c = \frac{1.73 G_{m1}}{\omega_2 A_0} \leftarrow$  for PM = 60°

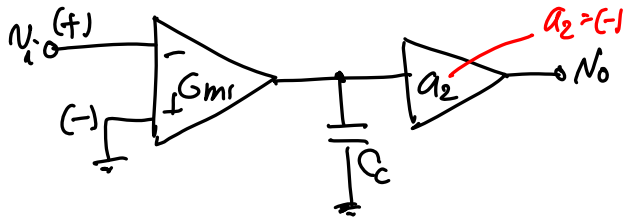② Case: Two-Stage Amplifier, Shunt  $C_c$  Compensation



After Lecture Discussion (Narrowbanding)

