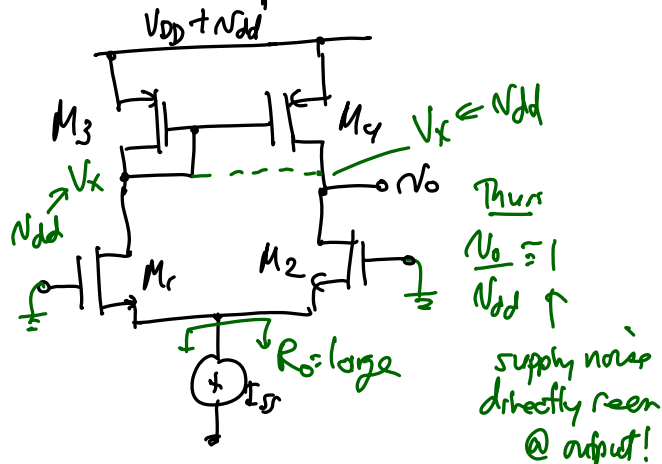


Lecture 25: Feedback Configurations

- Announcements:
- Design Project Checkpoint:
 - ↳ Due Monday, April 25, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (or linear if an MOS resistor)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
- Lecture Topics:
 - ↳ Power Supply Rejection Ratio (PSRR) - finish w/ an example
 - ↳ Advantages of Feedback (revisited)
 - ↳ Feedback Configurations
 - ↳ Effect of FB on Z_i and Z_o

• Last Time: PSRR

Ex. CMOS Diff. Input Stage w/ Current Source Load



Definition Power Supply Rejection Ratio (PSRR)

$$PSRR \triangleq \frac{\text{Gain from Input to Output}}{\text{Gain from Supply to Output}} = \frac{A_v|_{N_{dd}=0}}{A_{dd}|_{V_i=0}}$$


Thus, for the above example: $PSRR \approx \frac{g_{m2}(r_{o2}||r_{o4})}{1}$

$$PSRR \approx g_{m2}(r_{o2}||r_{o4})$$

For more complicated ckt's, much more is involved.

↳ to make it easier, use a unity gain config.

↳ can also get $PSRR = f(\omega)$

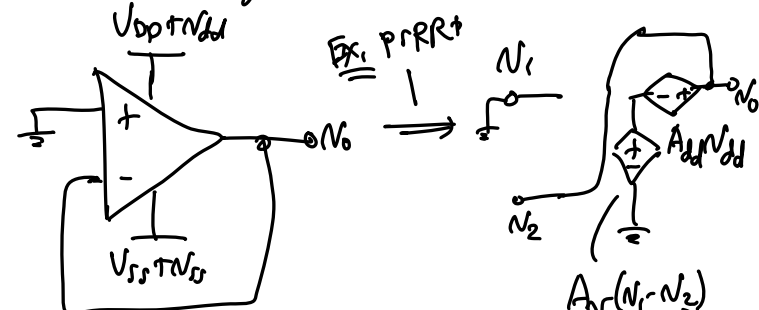

$$N_o = A_v(N_1 - N_2) + A_{dd}N_{dd}$$

$$PSRR^+ = \frac{N_{dd}}{N_o}$$

$$N_o(1 + A_v) = A_{dd}N_{dd}$$

$$\frac{N_o}{N_{dd}} = \frac{A_{dd}}{1 + A_v} = \frac{1}{A_{dd} + \frac{A_v}{A_{dd}}} \approx \frac{1}{PSRR^+} = \frac{N_o}{N_{dd}}$$

Two-Stage Op Amp PSRR⁺ Want $PSRR^+ = f(\omega)$ \uparrow freq.

Do brute force network analysis:

KCL[Ⓐ]: $G_I N_{dd} = (G_I + sC_c + sC_f) N_1 - (g_{mI} + sC_c) N_o$
KCL[Ⓑ]: $(g_{mII} + g_{ds6}) N_{dd} = (g_{mII} - sC_c) N_1 + (G_{II} + sC_c + sC_{II}) N_o$

$G_I = g_{ds1} + g_{ds4} = g_{ds2} + g_{ds4}$
 $G_{II} = g_{ds6} + g_{ds7}$
 $g_{mI} = g_{m1} = g_{m2}$
 $g_{mII} = g_{m6}$

$[g_{ds} = \frac{1}{r_o}]$ \uparrow for saturated device.

math & rearranging

Def: $\left. \frac{N_{dd}}{N_o} \right|_{\text{closed-loop}} = \frac{N(s)}{D(s)} = \left(\frac{\text{numerator}}{\text{denominator}} \right)$ polynomial

Then use: $N(s) = 1 + \left(\frac{s}{z_1} + \frac{s}{z_2} \right) + \frac{s^2}{z_1 z_2} \approx 1 + \frac{s}{z_1} + \frac{s^2}{z_1 z_2}$

$PSRR^+ = A_{No}^+ \left[\frac{(1 + \frac{s}{GB})(1 + \frac{s}{\omega_{p1}})}{(1 + \frac{s}{GB/A_{No}^+})} \right]$



where $GB = \text{Gain BW Product} = \frac{g_{mI}}{C_c}$
 $A_{No}^+ = \text{DC PSRR}^+ = \frac{g_{mI} g_{mII}}{G_I g_{ds6}}$
 $|p_1| = \frac{g_{mII}}{C_{II}} \quad \omega_p^+ = \frac{GB}{A_{No}^+}$

To maximize PSRR⁺ (@dc) decrease g_{ds6} , raise g_{mII}

$PSRR^- = A_{No}^- \left[\frac{(1 + \frac{s}{GB})(1 + \frac{s}{\omega_{p2}})}{(1 + \frac{s}{\omega_{p-}})} \right]$

where $A_{No}^- = \frac{g_{mI} g_{mII}}{G_I g_{ds7}}$
 $GB = \frac{g_{mI}}{C_c} \quad \omega_p^- = \frac{G_I}{C_c + C_{II}} \approx \frac{G_I}{C_c}$
 $|p_2| = \frac{g_{mII}}{C_{II}}$

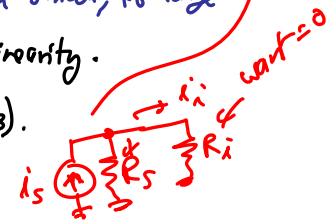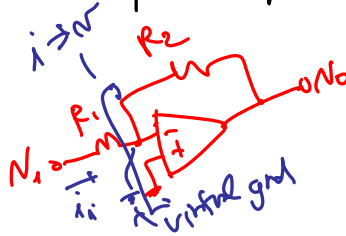To maximize PSRR⁻: ① decrease g_{ds7}
 ② increase $g_{mII} = g_{m6}$



$$A = \frac{a}{1+af} \rightarrow \frac{dA}{da} = \frac{(1+af) - af}{(1+af)^2} = \frac{1}{(1+af)^2}$$
$$\frac{\partial A}{\partial a} = \frac{1}{(1+af)^2} \rightarrow SA = \frac{\partial a}{(1+af)^2}$$

↑
much smaller than Sq

The fractional change:


$$\frac{\frac{\Delta A}{A}}{\frac{1 + af}{a} \frac{\frac{\Delta g}{g}}{(1 + af)^2}} \Rightarrow \frac{\frac{\Delta A}{A}}{1 + af} \frac{8a}{9}$$

ortion Reduction via FB

The graph illustrates the relationship between the output S_0 and the input S_E or S_1 . The black curve represents the system's response, and the blue line represents the feedback path. The graph is annotated with various labels and arrows:

- $f(S_E)$ is labeled at the top right, with an arrow pointing to the blue line.
- $a_3 = 0$ is labeled near the top right, with an arrow pointing to the blue line.
- $\text{slope} = a_2$ is labeled at the top left, with an arrow pointing to the upper part of the black curve.
- $\text{slope} = a_1$ is labeled in the middle left, with an arrow pointing to the lower part of the black curve.
- $\text{slope} = \frac{1}{f}$ is labeled twice on the right side, with arrows pointing to the blue line.
- S_0 is labeled at the top of the vertical axis.
- S_{02} and S_{01} are labeled on the vertical axis.
- $\frac{S_{01}}{a_1}$ and $-S_{01}$ are labeled on the horizontal axis.
- $-S_{02}$ is labeled on the horizontal axis.
- $S_E \text{ or } S_1$ is labeled at the bottom right, with an arrow pointing to the horizontal axis.
- own meters is labeled at the bottom right, with an arrow pointing to the horizontal axis.
- input value is labeled at the bottom right, with an arrow pointing to the horizontal axis.


Now, close the loops
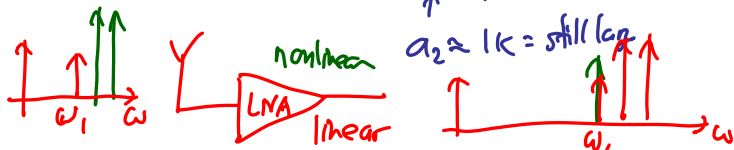
$$0 < s_0 < s_{0f}: A_i = \frac{a_i}{1 + af} \approx \frac{1}{f} \quad \leftarrow \text{for } a_i \text{ large}$$
$$\underline{S_{01} < S_0 < S_{02}}: A_2 = \frac{a_2}{1+a_2 f} \approx \frac{1}{f}$$


↓ starts with...

Series Connection - FB network in series w/ the amplifier port

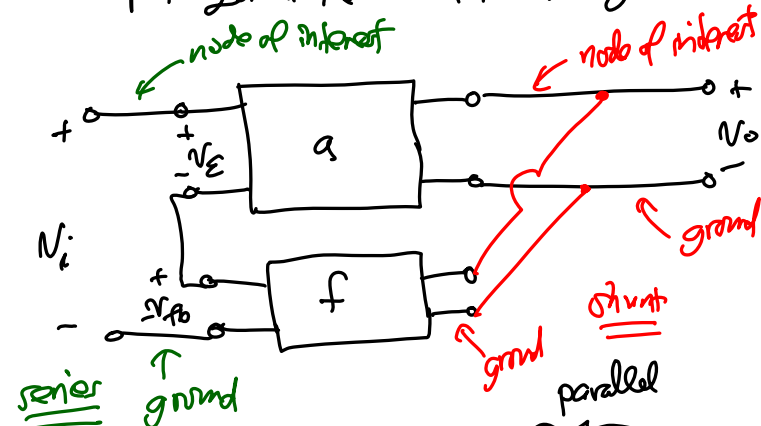→ must go through both the FB part & the amplification part to get fr the node of interest to ground



Shunt Connection: FB network part in shunt at the amplification part

→ Can get fr the node of interest to ground via either FB network part or the amplifier part


sender-shunt FB

The diagrams illustrate four basic op-amp feedback configurations:

- The Basic Amplifier:** A standard inverting amplifier configuration with input S_i and output S_o .
- Series-shunt configuration:** Features a voltage divider at the input (resistors R_E and R_F) and a voltage divider at the output (resistors R_E and R_F). The feedback signal is taken from the output and fed back to the inverting input. The input signal is applied to the non-inverting input. The output is labeled S_o .
- Shunt-series configuration:** Features a current divider at the input (resistors R_E and R_F) and a current divider at the output (resistors R_E and R_F). The feedback signal is taken from the output and fed back to the inverting input. The input signal is applied to the non-inverting input. The output is labeled S_o .
- Shunt-shunt configuration:** Features a current divider at the input (resistors R_E and R_F) and a current divider at the output (resistors R_E and R_F). The feedback signal is taken from the output and fed back to the inverting input. The input signal is applied to the non-inverting input. The output is labeled S_o .



Feedback Configurations

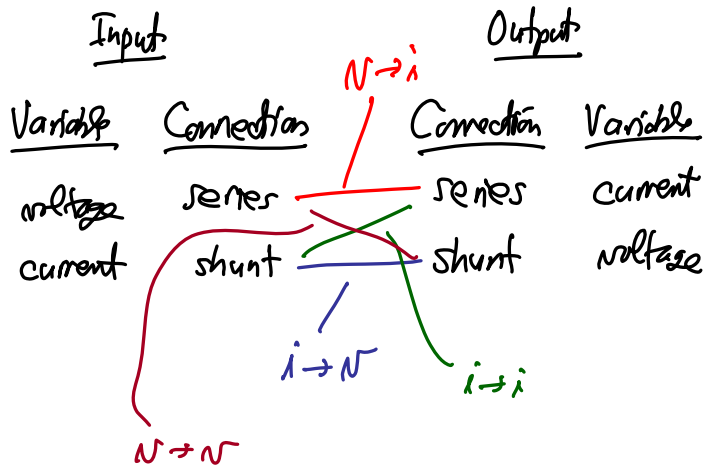


Effect of FB on Z_i & Z_o

Ex: series-shunt FB

Assumption: FB network has ideal impedances
 i.e., it does not load the amplifier

Basic Amplifier: $N_E \rightarrow N_O$

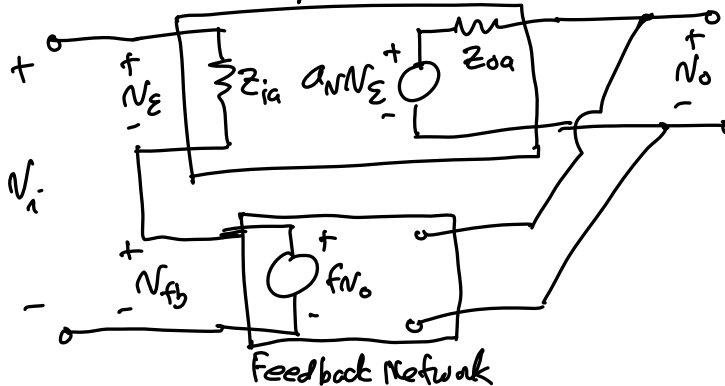

Find the T.F.:

$$\begin{aligned}
 N_E &= N_i - N_{fb} \\
 N_O &= a_N N_E \\
 N_{fb} &= f N_O
 \end{aligned}
 \left. \vphantom{\begin{aligned} N_E &= N_i - N_{fb} \\ N_O &= a_N N_E \\ N_{fb} &= f N_O \end{aligned}} \right\}
 \begin{aligned}
 N_O &= a_N (N_i - f N_O) \\
 \Rightarrow \frac{N_O}{N_i} &= \frac{a_N}{1 + a_N f} \quad \checkmark \\
 &\text{(as expected)}
 \end{aligned}$$