

Lecture 26: Feedback Impedance


• Announcements:

- ↳ Last HW#12 online (due during RRR week)
- ↳ Yes, I know, but it'll help you on the Final

• Lecture Topics:

- ↳ Effect of FB on  $Z_i$  and  $Z_o$
- ↳ Feedback Loading

• Last Time: Feedback Configurations

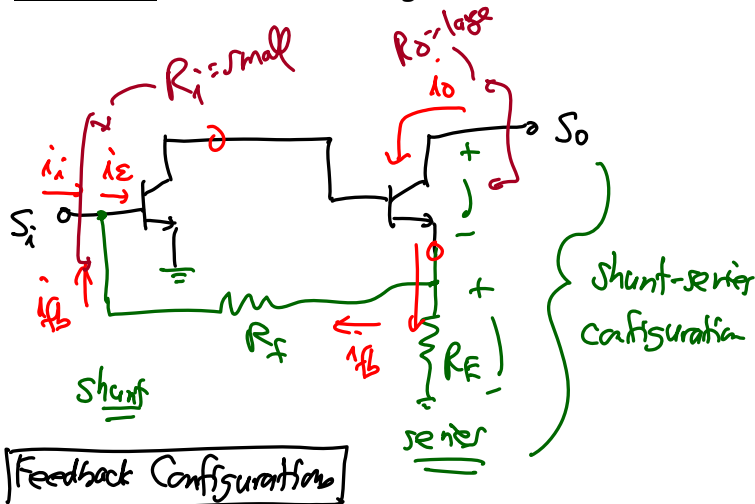

<u>Input</u>		<u>Output</u>	
<u>Variable</u>	<u>Connection</u>	<u>Connection</u>	<u>Variable</u>
voltage	series	series	current
current	shunt	shunt	voltage


$V \rightarrow V$     $i \rightarrow V$     $V \rightarrow i$     $i \rightarrow i$

Effect of FB on  $Z_i$  &  $Z_o$

Ex: series-shunt FB

Assumption: FB network has ideal impedances  
i.e., it does not load the amplifier

Basic Amplifier:  $V_E \rightarrow V_O$

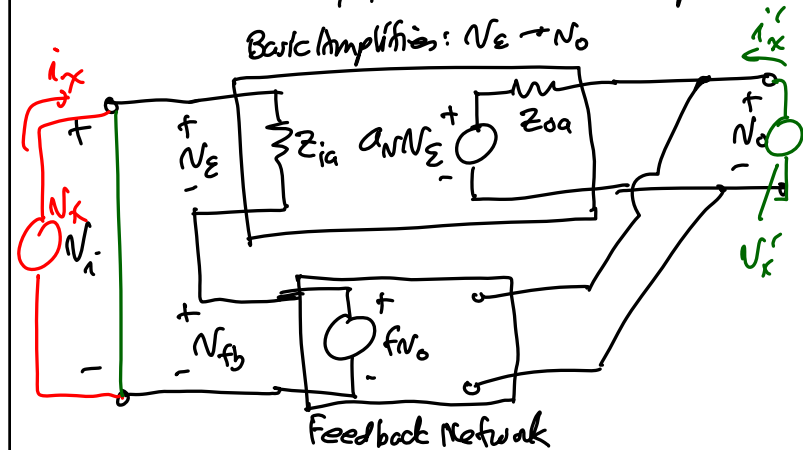

Find the T.F.:

$$\left. \begin{aligned} V_E &= V_i - V_{fb} \\ V_o &= a_v V_E \\ V_{fb} &= f V_o \end{aligned} \right\} \Rightarrow \frac{V_o}{V_i} = \frac{a_v}{1 + a_v f} \quad \checkmark$$

(as expected)

find  $z_i = \frac{N_x}{i_x}$ :

$N_x = N_\Sigma + N_{fb}$

$= N_\Sigma + fN_o = N_\Sigma + a_n f N_\Sigma = N_\Sigma (1 + a_n f)$  *loop gain!*

$i_x = \frac{N_\Sigma}{z_{ia}}$

$z_i = \frac{N_x}{i_x} = \frac{N_\Sigma (1 + a_n f)}{\frac{N_\Sigma}{z_{ia}}} = z_{ia} (1 + a_n f) = z_i$  *amplifier alone input impedance*

When use series connectin @ input: Input impedance raised by  $(1 + a_n f)$ !  $\rightarrow$  makes for a better voltage amplifier!

Find  $z_o = \frac{N_x'}{i_x'}$ : (w/ input shorted)

$N_\Sigma + N_{fb} = N_\Sigma + fN_x' = 0 \rightarrow N_\Sigma = -fN_x'$

$i_x' = \frac{N_x' - a_n N_\Sigma}{z_{oa}} = \frac{N_x' + a_n f N_x'}{z_{oa}}$

$\frac{N_x'}{i_x'} = \frac{z_{oa}}{1 + a_n f} = z_o$


Output impedance lowered by a factor of  $(1 + a_n f)$

Overall, series-shunt FB improves the impedance characteristics favorable to a  $v \rightarrow v$  amplifier:  $z_i \uparrow, z_o \downarrow$  due to series-shunt FB

Again, makes for a better voltage amplifier!

Ex. Shunt-Series FB

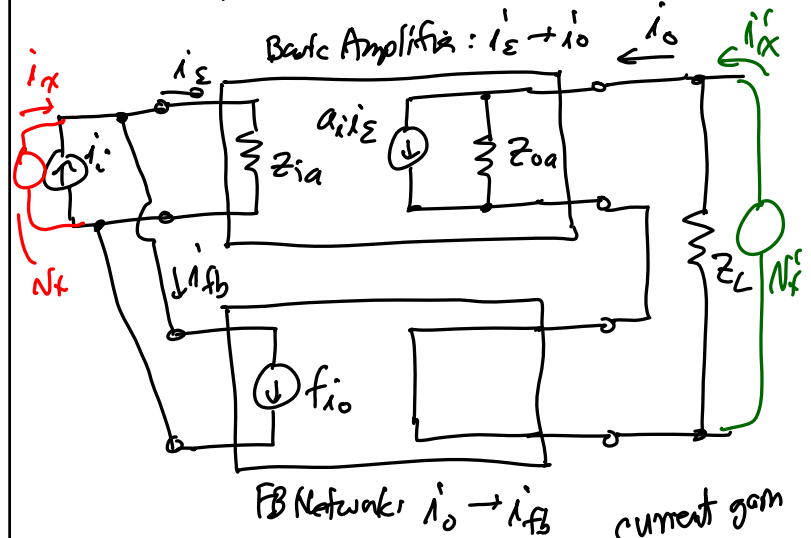$\Rightarrow$  Again, around FB network does not load the amplifier



Find T.F. -

$i_o = a_i i_\epsilon$

$i_\epsilon = i_i - i_{fb} = i_i - f i_o$

$\frac{i_o}{i_i} = \frac{a_i}{1 + a_i f}$  *current gain of amp alone*

$\uparrow$  *loop gain*

Same form as  $v \rightarrow v$  amp. This is a universal form!

Find  $Z_i = \frac{V_x}{I_x}$ :

$$\frac{V_x}{I_x} = \frac{Z_{is}}{1 + a_i f}$$

$\Rightarrow$  again, a shunt connection reduces the impedance by  $(1 + a_i f)$ !

Find  $Z_o = \frac{V_x}{I_x}$ :

$$\frac{V_x}{I_x} = Z_{oa}(1 + a_i f) = Z_o$$

series connection raises the impedance by  $(1 + a_i f)$

All together  $\rightarrow$  makes for a better  $i \rightarrow i$  amp  
(when using shunt-series FB)

Summary:


① series connection:  $Z \rightarrow Z(1 + T)$

② shunt connection:  $Z \rightarrow \frac{Z}{(1 + T)}$

$T = \text{loop gain}$

Determine the FB loading of an Amplifier

Example: Non-Inverting Amplifier

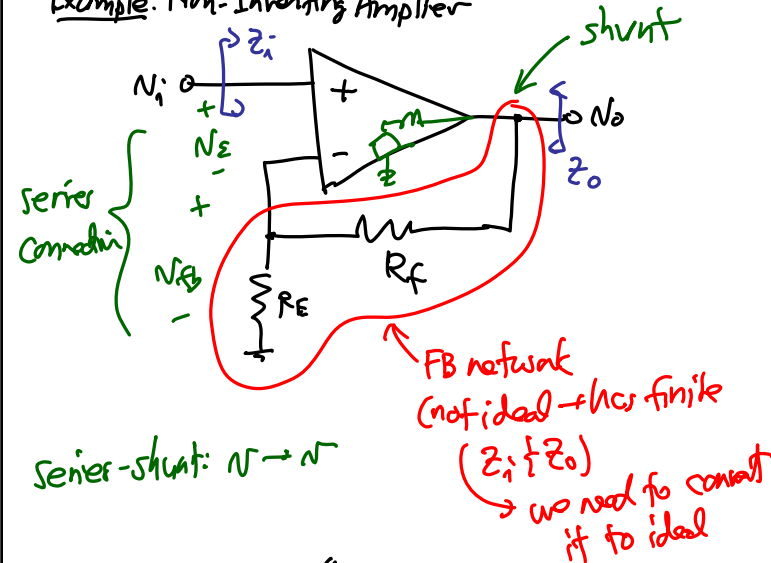

Series-shunt:  $V \rightarrow V$


Objective: Use  $A_o = \frac{a_v}{1 + a_v f}$  to get  $A_o$ .

In order to use this equation, we must know


(i)  $a_v \triangleq$  gain of the amplifier

(ii)  $f \triangleq$  gain of the feedback (also, called the feedback factor)  $\leftarrow$  gain of interest

In general:

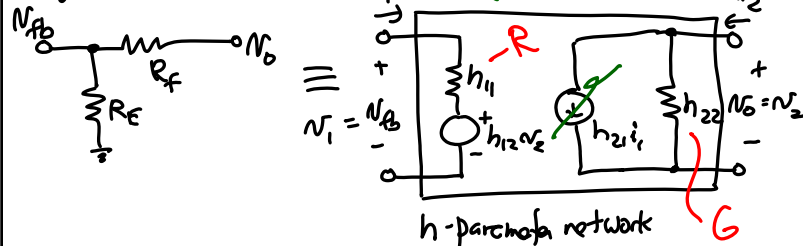


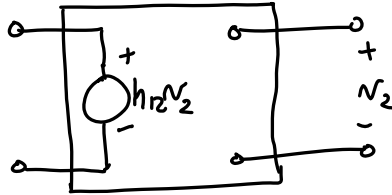But to simplify things,  
we would like to be able to represent the feedback network by  
just:




- Where: ① The small  $h_{21}$  is neglected.  
② All impedances have been moved out of the  
f-network and moved to the a<sub>n</sub>-network.)


Pictorially:

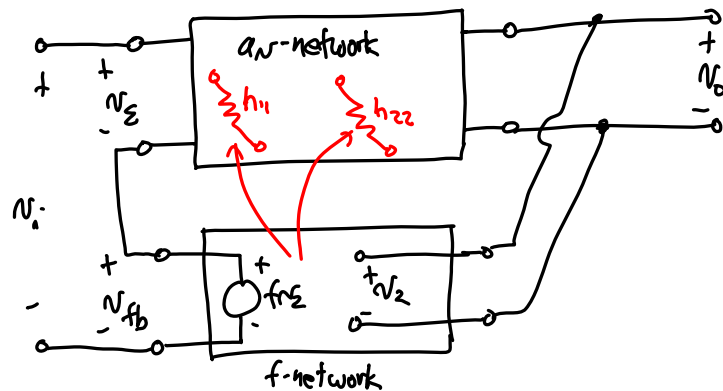

The FB Network:

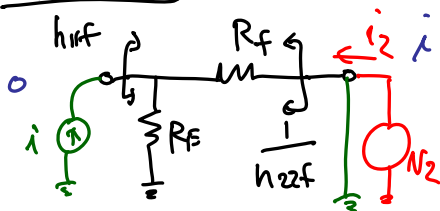

h-parameter Network (just a reminder)

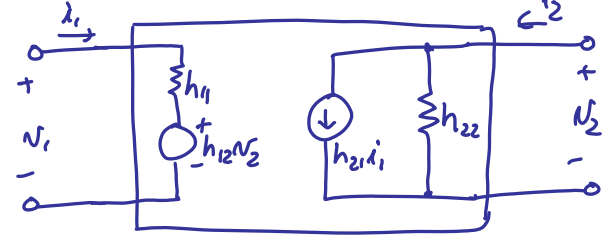

Port Equations:

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$i_2 = h_{21}i_1 + h_{22}V_2$$

Elements:

$$h_{11} = \left. \frac{V_1}{i_1} \right|_{V_2=0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$h_{21} = \left. \frac{i_2}{i_1} \right|_{V_2=0} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$

$$h_{22f} = \left. \frac{i_2}{V_2} \right|_{i_1=0} = \frac{1}{R_E + R_F} \quad \text{(this is the loading @ port 2, i.e., the amplifier output port)}$$

↑  
This is a conductance.

$$h_{12f} = \left. \frac{V_1}{V_2} \right|_{i_1=0} = \frac{R_F}{R_E + R_F} = f \quad \text{(feedback gain factor)}$$

$$h_{11f} = \left. \frac{V_1}{i_1} \right|_{V_2=0} = R_E || R_F \quad \text{(this is the loading at port 1, i.e., at the amplifier input port)}$$

The new simpler  
PB network:  $f = \frac{R_F}{R_E + R_F}$

$$\therefore \left( \frac{N_o}{N_i} \right)_{PB \text{ load}} = \left( \frac{Z_i'}{Z_i' + R_E \parallel R_F} \right) a \left( \frac{(R_E \parallel R_F) \parallel Z_L}{(R_E \parallel R_F) \parallel Z_L + Z_o'} \right) = a_{PF}$$