

Lecture 27: Feedback Inspection



• Announcements:

- ↳ Lab#3 (your project) due on Friday, May 6, at 5 p.m.
- ↳ Passed out Feedback Inspection Handout
- ↳ Passed out Final Information Sheet and sample Final Exam (from 2009)

• Lecture Topics:

- ↳ Feedback Loading
- ↳ Open-Loop Amp w/ Feedback Loading
- ↳ Feedback By Inspection
- ↳ Final Exam Info & Course Wrap Up

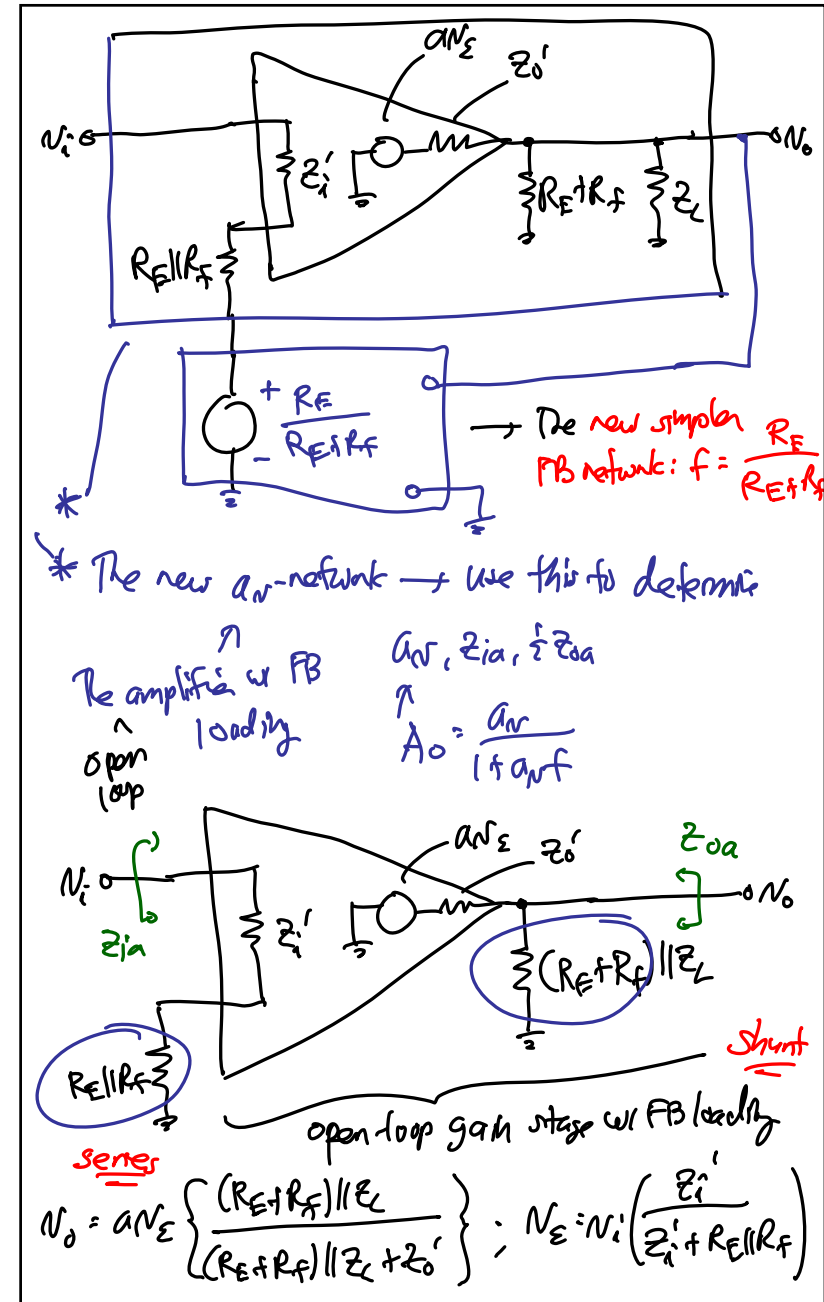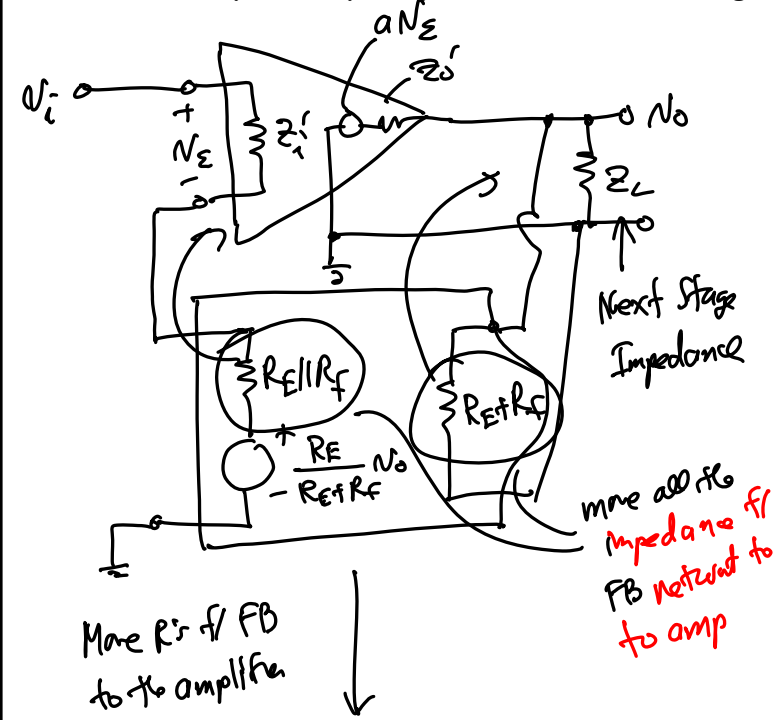• Last Time: Open-Loop Amp w/ Feedback Loading



$$\left. \frac{N_o}{N_i} \right|_{\text{FB loading}} = \left(\frac{Z_i'}{Z_i' + R_E \parallel R_F} \right) a \left(\frac{(R_E + R_F) \parallel Z_L}{(R_E + R_F) \parallel Z_L + Z_o'} \right) = a_{NF}$$

We know f : $f \cdot \frac{R_F}{R_E + R_F}$

Get closed loop gain: A_o

$$A_o \cdot \frac{N_o}{N_i} = \frac{a_{NF}}{1 + a_{NF} f} \approx \frac{1}{f} = 1 + \frac{R_F}{R_E}$$

What about R_i & R_o ?

for the open-loop amplifier w/ FB loading:

$Z_{ia} = Z_i' + R_E \parallel R_F \xrightarrow{\text{closed loop}} Z_i = (Z_i' + R_E \parallel R_F)(1 + a_{NF} f)$

$Z_{oa} = Z_o' \parallel (R_E + R_F) \parallel Z_L \xrightarrow{\text{closed loop}} Z_o = \frac{Z_o' \parallel (R_E + R_F) \parallel Z_L}{1 + a_{NF} f}$

$\omega_{-3dB} \big|_{\text{closed loop}} = \left[\omega_{-3dB} \big|_{\text{open-loop amp w/ FB loading}} \right] \times (1 + a_{NF} f)$

To determine loading by FB:

Input Loading

Output Loading

Example: Transresistance Amplifier

Want a current input

shunt

FB Network

shunt

$r_{\pi} \gg R_{E2}$

① Determine the type of FB: \rightarrow then determine the input & output variables

② Biases:

$I_{FB} = I_{B1} \leftarrow i_{in} \approx 0$

$I_{C2} \approx I_{E2} = \frac{V_{BE(on)}}{R_{E2}}$

$I_{C1} = \frac{V_{CC} - 2V_{BE(on)}}{R_{C1}}$

Note: Shouldn't do this if R_f is very big...

③ What kind of gain?

shunt-shunt FB $\rightarrow i \rightarrow v$ gain

\therefore we're looking for $R_m = \frac{V_o}{i_i} = \frac{r_m}{1 + r_m f_k}$

closed-loop gain Ω open-loop gain w/ FB loading

④ Determine r_m :


Get Gain: $\frac{N_o}{i_i} = \frac{N_{o1}}{i_i} \cdot \frac{N_{o2}}{V_{o1}} \cdot \frac{V_{o2}}{N_{o2}} = \frac{N_o}{i_i} \Big|_{OL w/ FB loading} = r_m$

$N_{o1} = i_i (r_{\pi1} || R_f) \rightarrow \frac{N_{o1}}{i_i} = r_{\pi1} || R_f$

$\frac{N_{o2}}{V_{o1}} = -g_{m1} (R_{C1} || (r_{\pi2} + (\beta+1)(R_{E2} || R_f || R_L)))$

$\frac{N_{o2}}{N_{o1}} \approx 1$

$r_m = \frac{N_o}{i_i} \Big|_{OL w/ FB loading} = -g_{m1} (r_{\pi1} || R_f) [R_{C1} || (r_{\pi2} + (\beta+1)(R_{E2} || R_f || R_L))] = r_m$

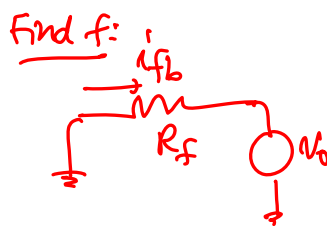

$$f = \frac{i_B}{v_O} = -\frac{1}{R_F}$$

Thus: $T = r_{mf} = (-g_{m1}(r_{\pi1} || R_F)) [R_{C1} || \overset{\text{large}}{C}] (-\frac{1}{R_F})$

$$T \approx g_{m1} R_{C1} \left(\frac{r_{\pi1} || R_F}{R_F} \right)$$

⑤ Finally, get all parameters

$$R_m: \frac{r_m}{1 + r_{mf}} \approx \frac{1}{f} = -R_F \Rightarrow R_m = -R_F$$

if $r_m = \text{large}$


$$R_i = \frac{R_{ia} | \omega / \text{FB loading}}{1 + r_{mf}} = \frac{r_{\pi1} || R_F}{1 + g_{m1} R_{C1} \left(\frac{r_{\pi1} || R_F}{R_F} \right)} = R_i$$

large \therefore this = $r_{\pi1}$

$$R_o = \frac{R_{oa} | \omega / \text{FB loading}}{1 + r_{mf}} = \frac{\frac{r_{\pi2} + R_{C1}}{\beta + 1} || R_{E2} || R_F || R_L}{1 + g_{m1} R_{C1} \left(\frac{r_{\pi1} || R_F}{R_F} \right)} = R_o$$

Find ω_{-3dB} :

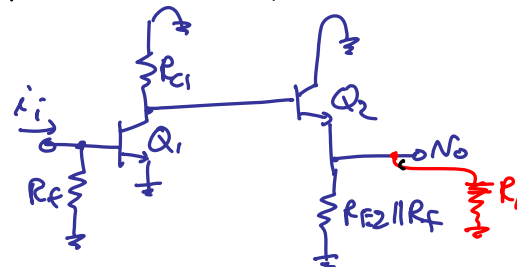① Find the ω_{-3dB} of the open-loop amplifier w/ FB loading, i.e., of this: \rightarrow use OCTC analysis



② Multiply by $(1+T)$:

$$\omega_{-3dB} |_{\text{closed-loop}} = (1+T) \times \omega_{-3dB} |_{\text{OL w/ FB loading}}$$

- What's next?
- **EE 240: Advanced Analog Integrated Circuits**
- Analysis and optimized design of integrated analog systems and building blocks. Specific topics include operational and wide-band amplifiers, gain-bandwidth and power considerations, analysis of noise in integrated circuits, low noise design, feedback, precision passive elements, analog switches, comparators, CMOS voltage references, non-idealities such as matching and supply/IO/substrate coupling. The course will include a significant design project applying the techniques taught in class to implement the analog front-end of a high-speed serial link.
- **EE 142: Integrated Circuits for Communication**
- Analysis and design of electronic circuits for communication systems, with an emphasis on integrated circuits for wireless communication systems. Analysis of noise and distortion in amplifiers with application to radio receiver design. Power amplifier design with application to wireless radio transmitters. Radio-frequency mixers, oscillators, phase-locked loops, modulators, and demodulators.
- **EE C245: Introduction to MEMS**
- Physics, fabrication, and design of micro-electromechanical systems (MEMS). Micro and nanofabrication processes, including silicon surface and bulk micromachining and non-silicon micromachining. Integration strategies and assembly processes. Transduction strategies and mechanical circuits. Electronic position-sensing circuits and electrical and mechanical noise. CAD for MEMS. Design project is required.