

EE 140

Inspection Analysis

CTN

1


EE 140

ANALOG INTEGRATED CIRCUITS

SPRING 2011
 C. Nguyen

Useful Inspection Formulas

The General Case (Midband)

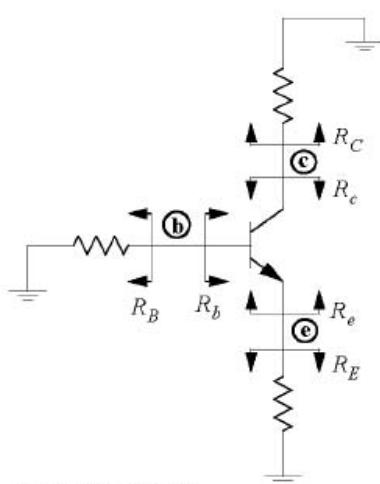

$$R_b = (r_e + R_E)(\beta + 1) = r_\pi + (\beta + 1)R_E$$

$$R_e = \frac{r_\pi + R_B}{\beta + 1} \cong \frac{1}{g_m} + \frac{R_B}{\beta + 1}$$

$$R_c = r_o \left[1 + \frac{g_m R_E}{1 + (R_B/r_\pi)} \right]$$

$$\frac{\alpha}{g_m} \approx \frac{1}{g_m}$$

Hybrid- π :

$$B$$

$$N\pi$$

$$G_m\pi$$

$$r_o$$

Base-to-Collector Gain:


$$\frac{v_c}{v_b} = -G_m R_C \quad G_m = \frac{g_m}{1 + g_m R_E}$$

Emitter-to-Collector Gain:

$$\frac{v_c}{v_e} = -G_m R_C \quad G_m = -\left(\frac{r_\pi}{r_\pi + R_B}\right) g_m$$

Base-to-Emitter Gain:
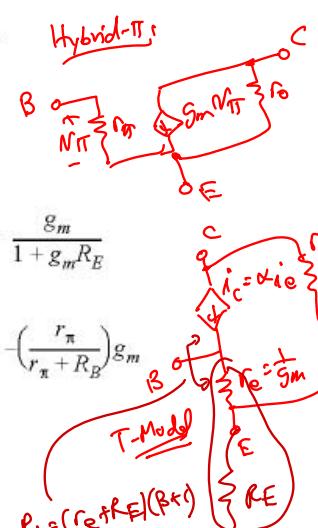
$$\frac{v_e}{v_b} = \frac{R_E \parallel r_o}{R_E \parallel r_o + r_e}$$




Node Resistances:

$$R_{(a)} = R_C \parallel R_e$$

$$R_{(b)} = R_E \parallel R_o$$

$$R_{(c)} = R_B \parallel R_b$$

High Frequency Analysis

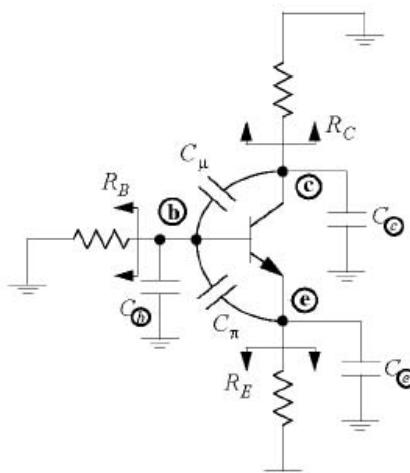

$$\omega_H = \frac{1}{\tau_b + \tau_{(a)} + \tau_{(b)} + \tau_{\mu o} + \tau_{\pi o}}$$

$$\tau_b = C_{(a)} R_{(a)}$$

$$\tau_{(a)} = C_{(a)} R_{(a)}$$

$$\tau_{(b)} = C_{(b)} R_{(b)}$$

$$\tau_{\pi o} = C_\pi R_{\pi o}$$

$$\tau_{\mu o} = C_\mu R_{\mu o}$$

$$R_{\pi o} = r_\pi \parallel \frac{R_B + R_E}{1 + g_m R_E}$$

$$R_{\mu o} = R_{(a)} + R_{(b)} + G_m R_{(a)} R_{(b)}$$