

Lecture 6: Frequency Response Inspection Analysis

- Announcements:
- This is our make-up lecture
- We will have lecture tomorrow (Tuesday), as well, at our regular time and place
- Lecture Topics:
 - ↳ Amplifier Bode plot
 - ↳ Open Circuit Time Constant (OCTC) Analysis
 - ↳ Frequency Response Inspection Analysis
 - ↳ Frequency Response Examples
- -----
- Last Time:

MOS Inspection Formulas w/ Substrate Grounded or well or tied to V_{DD}

$B \rightarrow \infty$
 $r_{\pi} = \frac{\beta}{g_m} \rightarrow \infty$
 \downarrow
 $g_m \rightarrow g_m + g_{mb}$

only difference from substrate tied to source? Case is that g_m is replaced by $g_m + g_{mb}$ in some of the formulas particularly over where the source is involved!

$R_g = \infty$
 $R_s = \frac{1}{g_m + g_{mb}}$
 $R_d = r_o [1 + (g_m + g_{mb}) R_s]$

over


$$\frac{N_d}{N_g} = -G_m R_d, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_s}$$



$$\frac{N_d}{N_s} = -G_m R_d, \quad G_m = -(g_m + g_{mb})$$

$$\frac{N_s}{N_o} = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s}$$

Remark: When the substrate is tied to the source, $g_{mb} = 0$.

Effect of g_{mb} (one more example)

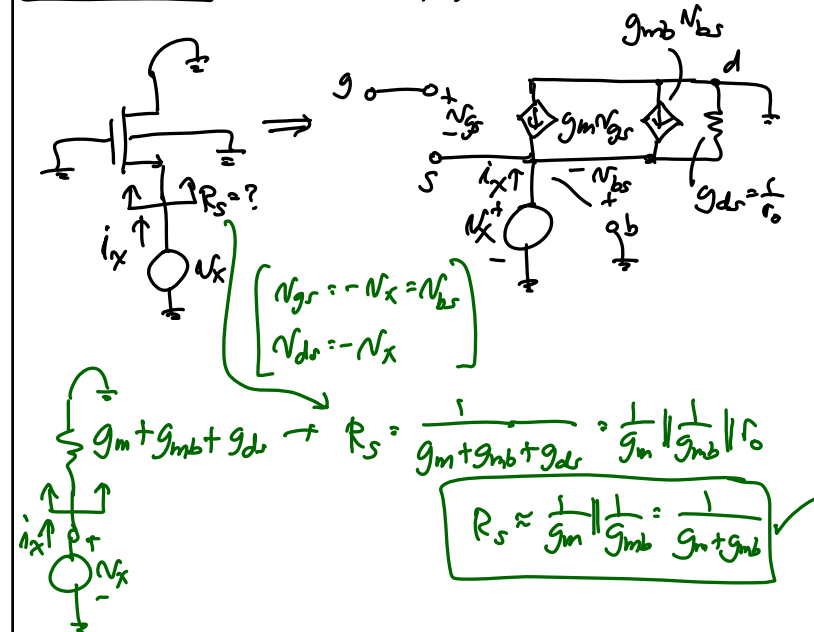

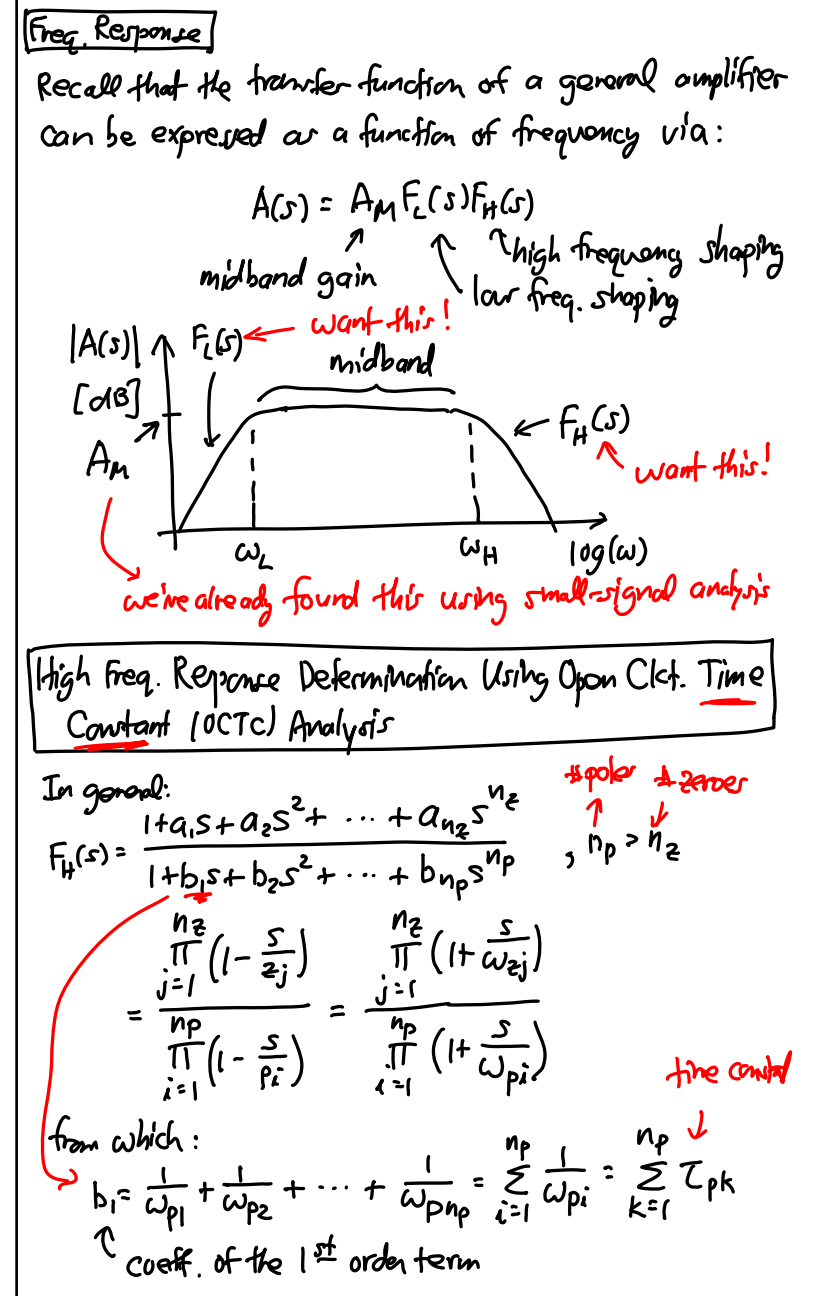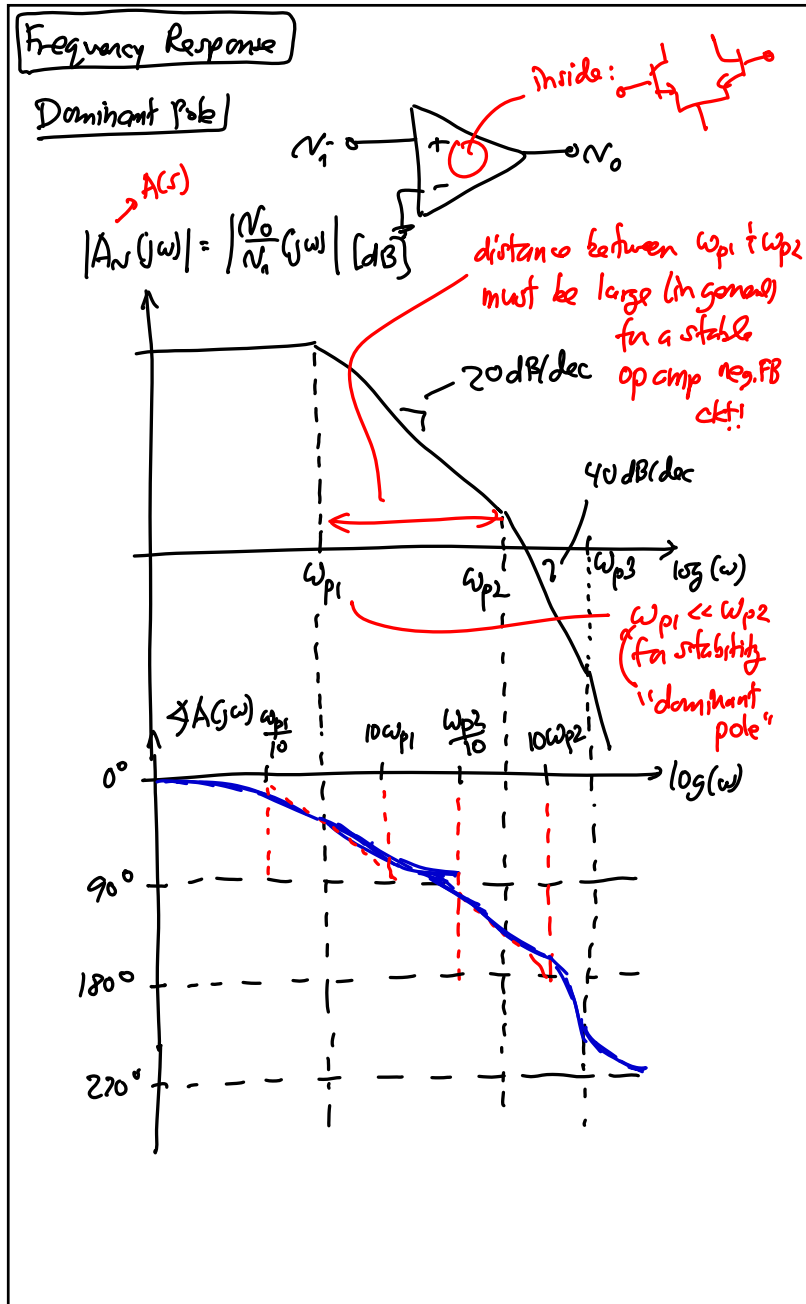

Lecture 6w: Frequency Response Inspection Analysis I

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{np} \tau_{pi} = \sum_j C_j R_{j0} = \sum_j \tau_{j0}$$

where C_j are capacitors in the H.F. ckt., i.e., small ones
 $R_{j0} \triangleq$ driving pt. resistance seen between the terminals of C_j determined with

- ① all small ($< 1nF$) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e., $> 1\mu F$ or $> 1nF$)

In calculating the H.F. response, we use the dominant pole approximation:

(i) $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pnp}$ ← # pole

$$F_H(s) \cong \frac{1}{1 + \frac{s}{\omega_H}}$$


(ii) $b_1 \cong \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \cong \frac{1}{b_1} = \frac{1}{\sum_j \tau_{j0}} = \frac{1}{\sum_j C_j R_{j0}}$

When there is no dominant pole, an approximate expression for ω_H is:

$$\omega_H \approx \frac{1}{\sqrt{\frac{1}{\omega_{p1}^2} + \frac{1}{\omega_{p2}^2} + \dots - \frac{1}{\omega_{z1}^2} - \frac{1}{\omega_{z2}^2} - \dots}}$$


(just FYI)

Example: H.F. Analysis of a C.E. Ckt.

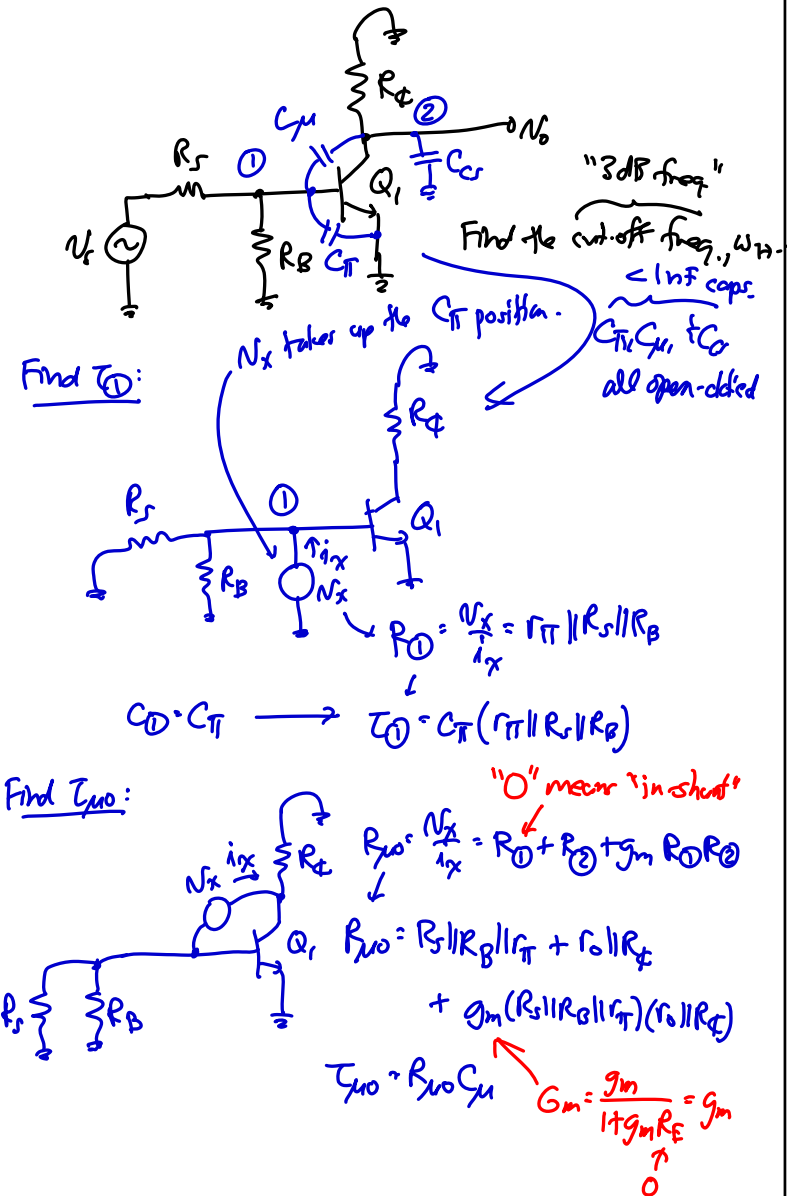


Find τ_2 : $\tau_2 = (r_o \parallel R_F) C_{cs}$
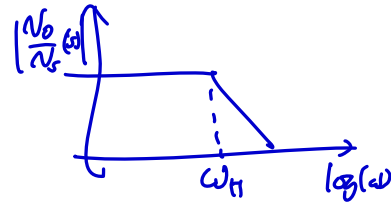
$$\omega_H = \frac{1}{\tau_0 + \tau_{m0} + \tau_2}$$



Now, use Miller's Theorem:

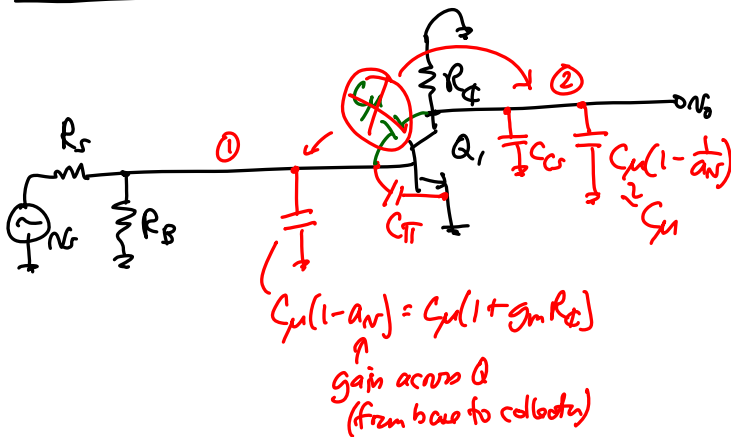


$$\tau_0 = (r_{\pi} \parallel R_S \parallel R_B) (C_{\pi} + C_{\mu}(1 + g_m R_F))$$

$$\tau_2 = (R_F \parallel r_o) (C_{\mu} + C_{cs})$$

$$\omega_H = \frac{1}{\tau_0 + \tau_2}$$

Multi-Stage Ex.

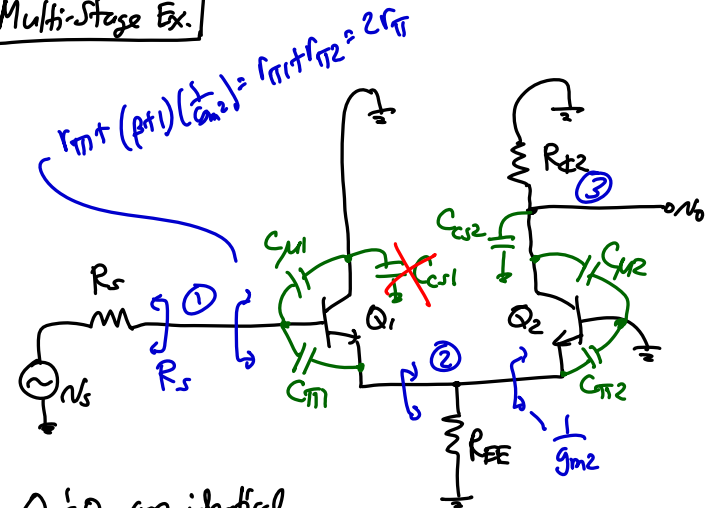

Q_1 & Q_2 are identical.

Find ω_H .

$$\tau_0 = (R_S \parallel (2r_{\pi})) C_{\mu 1}$$

$$\tau_{m1} = C_{m1} \left(r_{m1} \parallel \frac{R_S + \frac{1}{g_{m2}}}{1 + g_{m1} \left(\frac{1}{g_{m2}} \right)} \right)$$

$R_{EE} = \text{large!}$


↑
neg.

$$\tau_2 = C_{\pi 2} \left[\frac{1}{g_{m2}} \parallel R_{EE} \parallel \left(\frac{1}{g_{m1}} + \frac{R_S}{(\beta + 1)} \right) \right]$$

$$\tau_3 = (C_{\mu 2} + C_{cs2}) R_{F2}$$

$$\omega_H = \frac{1}{\tau_0 + \tau_{m1} + \tau_2 + \tau_3}$$

Aside:

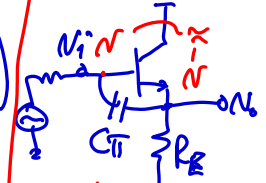

↑
if gain $\frac{V_o}{V_i} = 1$,
then can often neglect
the τ_{m0}

