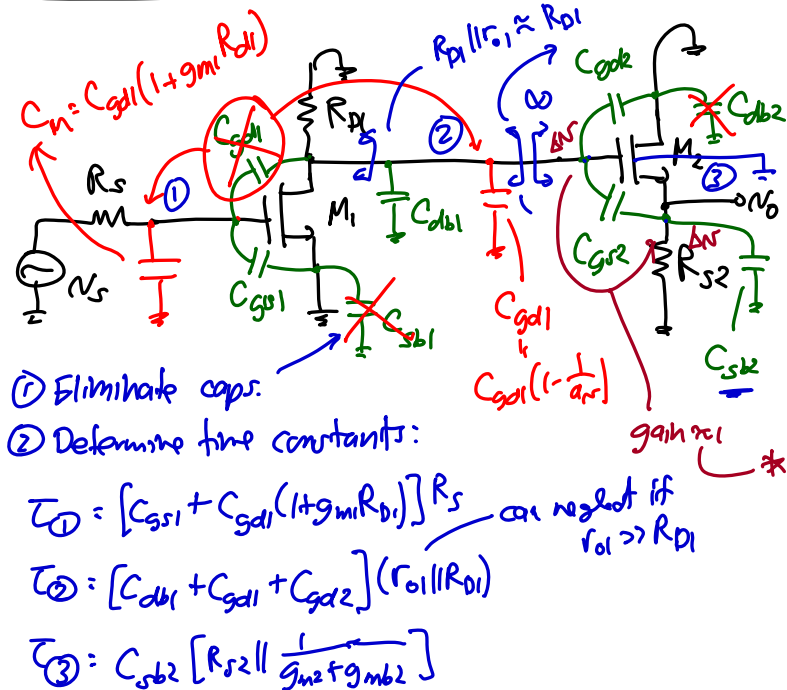


Lecture 7: Frequency Response Inspection Analysis II

- Announcements:
- HW#3 passed out in lecture and posted online
- HW#2 due today at 5 p.m.
- Lecture Topics:
 - ↳ Frequency Response Examples (cont.)
 - ↳ Short Ckt Time Constant (SCTC) Analysis
 - ↳ Example Low Freq. Response Determination
 - ↳ Start Active Loads

• Last Time:

MOS Two-Stage Amplifier




$$\tau_{gs2} = C_{gs2} \left(\frac{R_{D1} + R_{S2}}{1 + (g_{m2} + g_{mb2})R_{S2}} \right) \quad \text{if gain} \approx 1 \rightarrow \text{can neglect if there are other } \tau \text{ terms}$$

* and finally:

$$\omega_H = \frac{1}{\tau_1 + \tau_2 + \tau_3 + \tau_{gs2}}$$

Lecture 7w: Frequency Response Inspection Analysis II

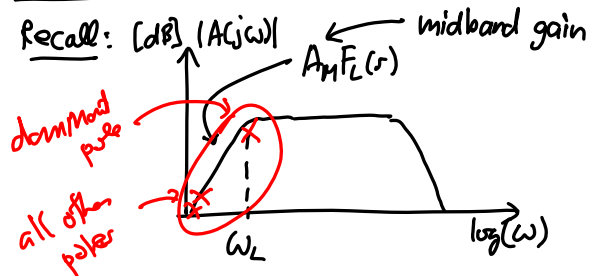Low Freq. Amplifier Response Using Short Circuit Time Constant Analysis (SCTC)



In general, for the low freq. response:

$$F_L(s) = \frac{s^{n_z} + d_1 s^{(n_z-1)} + \dots}{s^{n_p} + e_1 s^{(n_p-1)} + \dots}, \quad n_z = \# \text{ poles} = \# \text{ zeros}$$

We can express the coefficient e_1 by:

$$e_1 = \omega_{p1} + \omega_{p2} + \dots + \omega_{pn}$$

For the case of a dominant pole:

↳ i.e., the highest freq. pole

$$F_L(s) \approx \frac{s}{s + \omega_{p1}} = \frac{s}{s + e_1} \rightarrow e_1 \approx \omega_{p1} = \omega_L$$

$$\therefore \omega_L \approx e_1 = \sum_j \omega_{pj} = \sum_j \frac{1}{C_j R_{js}} = \sum_j \frac{1}{\tau_{js}}$$

where $C_j \triangleq$ various large ($> 10 \text{ nF}$) capacitors in the ckt. (e.g., the bypass caps.)

$R_{js} \triangleq$ driving point resistance seen between

the terminals of C_j determined with:

For reading, can go to Sedra & Smith

① all large capacitors short-circuited, except C_j , which is replaced by the test voltage source for R determination


② all independent sources eliminated (i.e., short voltage sources, open current sources)

③ open all H.F. capacitors (i.e., small caps in the pF range, or $< 1 \text{ nF}$)

Again, for the case where there are no dominant poles, a reasonable approximation is:

$$\omega_L \approx \sqrt{\omega_{p1}^2 + \omega_{p2}^2 - 2\omega_{z1}^2 - 2\omega_{z2}^2}$$

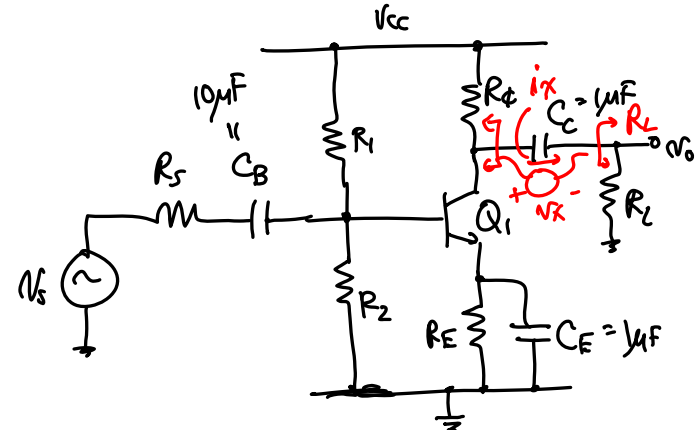Ex. Determine the L.F. Response of the C.E. amplifier



(a) τ_B due to C_B : short ckt. C_C & C_E driving pt. R associated w/ C_B

$R_B = \frac{V_x}{i_x} = \text{resistance in series w/ } V_x$

$\therefore R_B = R_S + R_1 \parallel R_2$

$\tau_B = R_B C_B = (R_S + R_1 \parallel R_2) C_B$

$\omega_{pB} = \frac{1}{\tau_B} = \frac{1}{(R_S + R_1 \parallel R_2) C_B}$

①

(b) T_C due to C_C : short def. $C_B \nmid C_E$
 again, N_X sees R in series

$$T_C = (R_L + r_{ol} \parallel R_E) C_C$$

$\sim R_E$ $\omega_{pc} = \frac{1}{T_C} = \frac{1}{(R_L + R_E) C_C}$

(c) T_E due to C_E : short $C_C \nmid C_B$

$R_{ES} = \frac{N_X}{i_X} = R_E \parallel \frac{r_{\pi} + R_S \parallel R_1 \parallel R_2}{\beta + 1}$

$\frac{1}{g_m} + \frac{R_S \parallel R_1 \parallel R_2}{\beta + 1} = \frac{r_{\pi} + R_S \parallel R_1 \parallel R_2}{\beta + 1}$

$T_E = R_{ES} C_E$
 $\omega_{pE} = \frac{1}{T_E} = \frac{1}{R_{ES} C_E}$

and finally:

$$\omega_L = \omega_{pB} + \omega_{pc} + \omega_{pE}$$

Active Load

\Rightarrow why use them?

Gain $= \frac{V_o}{V_i} = -g_m R_D$

load (resistive)

For $\frac{V_o}{V_i} \uparrow$, must:

① Raise $g_m \rightarrow$ raise I_D

problem: $V_{DD} \uparrow \rightarrow$ gets too large
 limited by V_{DD} !

supply limits the amount of gain you can have

② increase $R_D \rightarrow$ but same problem
 also, area

Layout:

poly-silicon resistor
 make lots & thin to get large R

1k resistor
 much larger than
 for bias!

\Rightarrow What would be ideal?

V_{DD}
 I_{B1AS}
 N_i
 N_o

to approximate this, use an active load!

