

## Lecture 9w: Current Sources

## Lecture 9: Current Sources


- Announcements: → Lab on Monday → shift to next Monday
  - ↳ HW#4 passed out today (and online)
  - ↳ Lab#2 passed out today (and online)
  - ↳ Monday Labs: due to holiday next week, shift to the following Monday
  - ↳ Monday Lab#1's are due in the 140 Box on Tuesday next week (per Travis's email)
- Lecture Topics:
  - ↳ Current Sources
  - ↳ Current Source  $V_{BIAS}$  Generators
  - ↳ Output Swing (Headroom)

---

 • Last Time:

Ex. Cascode Drive &amp; Load

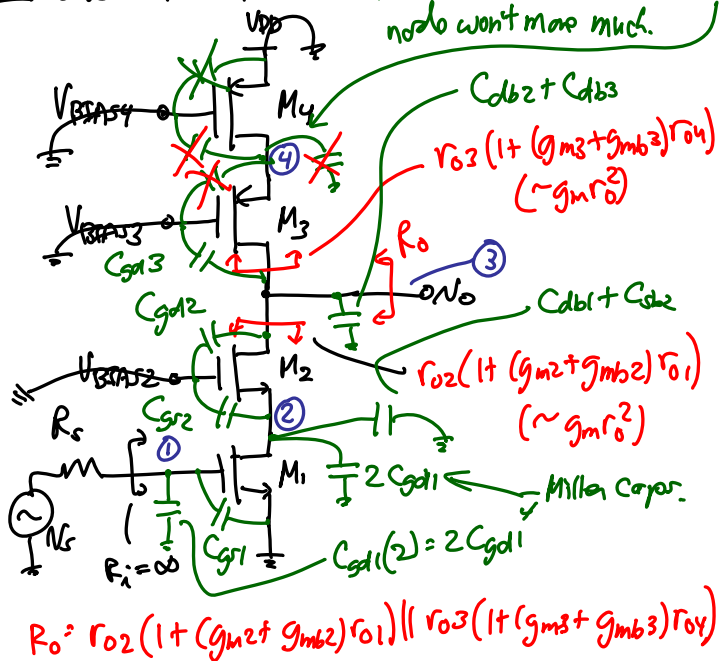For reason to be discussed, this node won't move much.



$$A_v = \frac{v_o}{v_s} = \frac{v_o}{v_i} \cdot \frac{v_i}{v_o} \cdot \frac{v_o}{v_i} \approx -1$$

$$= (1) (-g_{m1} \left( \frac{1}{g_{m2} + g_{mb2}} \right) (g_{m2} + g_{mb2}) R_o)$$

$$\therefore A_v = -g_{m1} R_o$$

Get the dominant pole: (use OCTC analysis)


$$\tau_0 = (2C_{gd1} + C_{gm1}) R_s$$


$$\tau_2 = (2C_{gd1} + C_{gr2} + C_{db1} + C_{db2}) \left( \frac{1}{g_{m2} + g_{mb2}} \right)$$

$$\tau_3 = (C_{gd2} + C_{db2} + C_{db3} + C_{gd3}) R_o \leftarrow \text{huge}$$

$$\omega_H = \frac{1}{\tau_0 + \tau_2 + \tau_3}$$

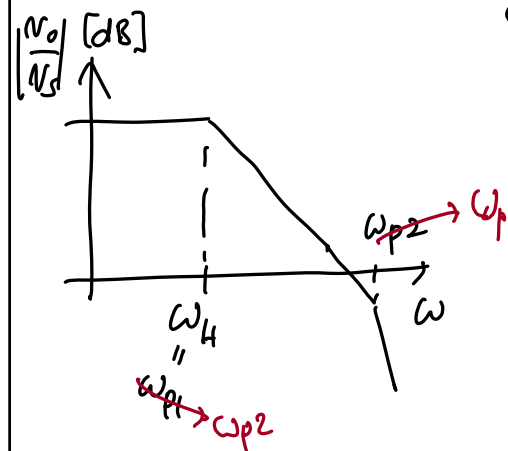⇒ this is accurate enough... but... can we be a bit smarter?



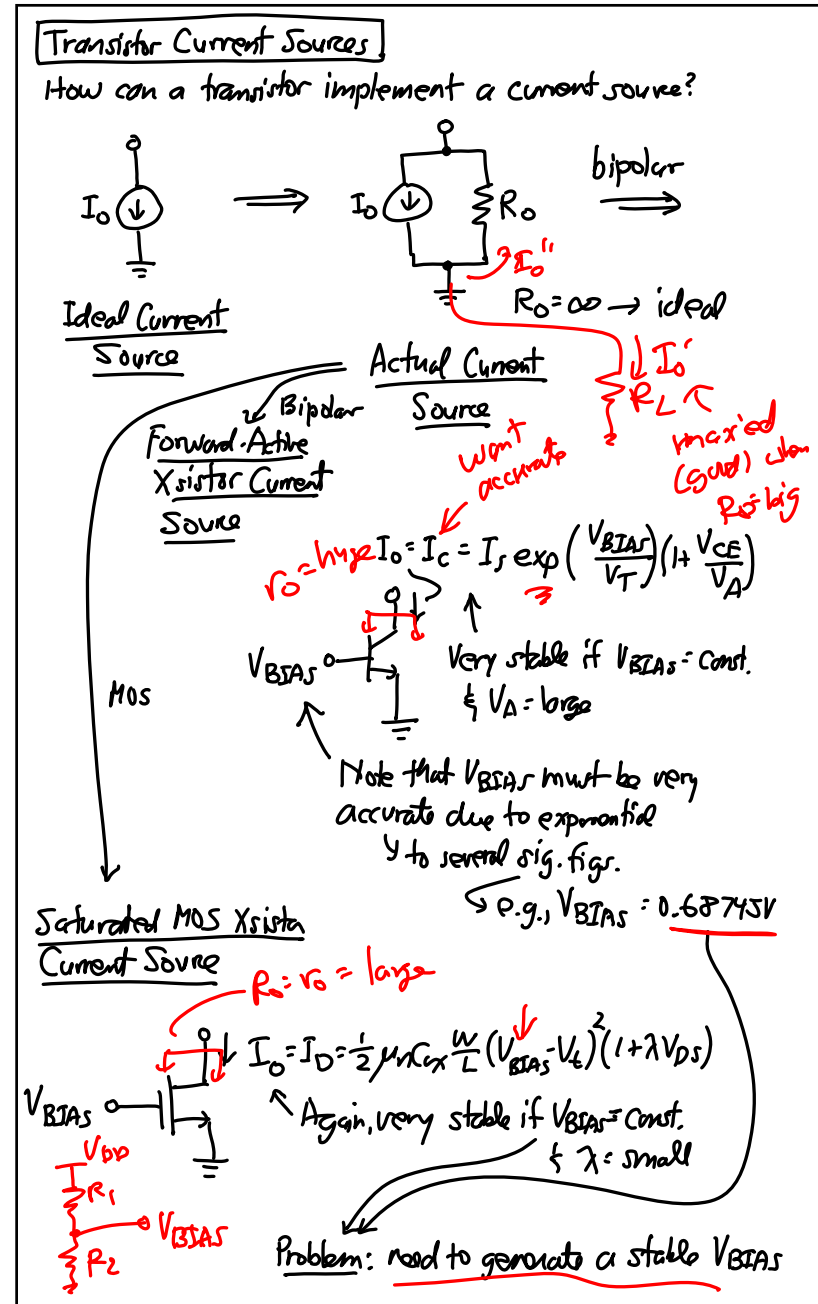


We now focus on methods for generating  $V_{BIAS}$ .  
But how do we get this degree of precision using a transistor ckt?

Solution:  $\rightarrow$

Replica Biasing (a simple & effective approach)

- ① Generate the desired current.
- ② Push the current through a Xsistor and allow it to reach a stable bias pt.
- ③ Use this stable bias pt. as  $V_{BIAS}$   
 $\rightarrow$  this can be very precise!

One simple approach:

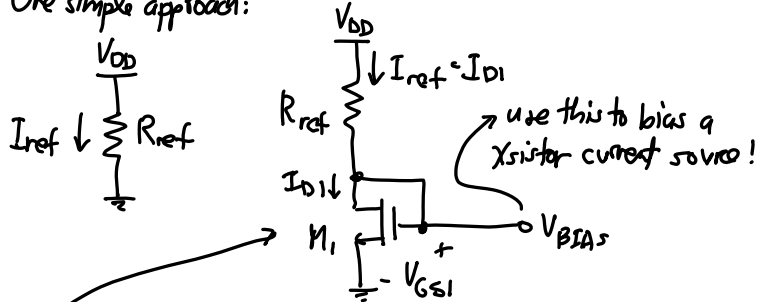


A diode-connected Xsistor is always in saturation and will basically bias itself to support the needed current!

$$I_{ref} = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS1} - V_t)^2 (1 + \lambda V_{DS1})$$

$\uparrow$   
 $V_{BIAS}$

Now, can distribute this  $V_{BIAS}$  to the gates of many MOS transistor current sources!

Ex. Simple MOS Current Source

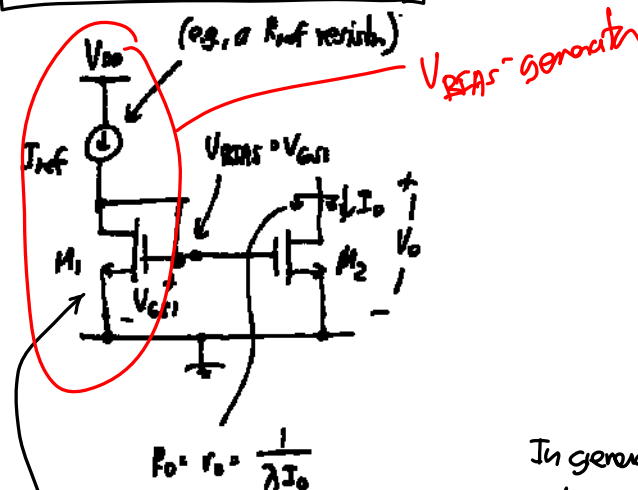

In general,  
Diode-connected Xsistor  $\rightarrow$  saturation:  
 $I_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{BIAS} - V_t)^2 (1 + \lambda V_{DS1})$   
 $I_{D2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{BIAS} - V_t)^2 (1 + \lambda V_{DS2})$   
In general,  $V_{DS1} \neq V_{DS2}$ , but if  $\lambda$  is small, then little difference in  $I_{D1}$  &  $I_{D2}$

① Case: matched  $M_1$  &  $M_2 \Rightarrow I_{D0} = I_{ref}$

② Case:  $M_1$  &  $M_2$  scaled w.r. to each other

$$\Rightarrow I_{D0} = I_{ref} \frac{(W/L)_2}{(W/L)_1}$$

$\Rightarrow$  use  $L_1 > L_2$  for better accuracy, then:

$$\frac{I_{D0}}{I_{ref}} = \frac{W_2}{W_1}$$

Note: for better accuracy, should use multiple copies of one device when setting currents  $\rightarrow$  reduces edge effects!

Ex: Layout for a Doubling Current Source

A single  $V_{BSAS}$  generator can now serve numerous current sources:

How about bipolar?

Simple Bipolar Current Source

Assume  $Q_1$  &  $Q_2$  are matched. ie.,  $V_A \rightarrow \infty$

$V_{BE1} = V_{BE2} \rightarrow I_{C1} = I_{C2} = I_O$  (neglecting  $V_A$ 's)

KCL:  $I_{ref} = I_{C1} + I_{B1} + I_{B2} = I_{C1} \left(1 + \frac{2}{\beta}\right)$

$\therefore I_{C1} = I_{C2} = I_O = \frac{I_{ref}}{1 + \frac{2}{\beta}} \rightarrow I_O \approx I_{ref}$

and  $I_{ref} = \frac{V_{CC} - V_{BE1}}{R_{ref}} \leftarrow 0.7V$  can say error  $\sim \frac{2}{\beta}$

$R_0 = r_{O2}$

Again, a single  $V_{BSAS}$  generator can serve many current sources throughout the IC chip:

$I_{ref} = I_{C1} + I_{B1} + I_{B2} + \dots + I_{Bn}$

[Identical  $V_{BSAS}$ 's]  $\Rightarrow I_{ref} = I_{C1} \left(1 + \frac{n}{\beta}\right)$

$\Rightarrow I_O = I_{C1} = \frac{I_{ref}}{\left(1 + \frac{n}{\beta}\right)}$

Problem: error  $\sim \frac{n}{\beta}$  increases as  $n$  (  $I_O$  divider from  $I_{ref}$ , and % deviation depends on  $n$ .)

This was not the case for MOS!

How can one reduce the error?

To reduce the error term, use a

Buffered  $V_{BE}$  Generator

Add a buffer Xsistor to attenuate base currents from Xsistor current sources.

This can now drive the base currents of many bipolar-transistor current sources (i.e., active loads).

$I_{ref} = I_{C1} + I_{B2}$

$I_{B2} = \frac{I_{E2} + I_{E3} + \dots + I_{En}}{\beta + 1} = \frac{n I_{E1}}{\beta(\beta + 1)}$  [Assuming identical Xsistors]

$I_{ref} = I_{C1} \left( 1 + \frac{n}{\beta(\beta + 1)} \right)$

$I_o = I_{C2} = \frac{I_{ref}}{1 + \frac{n}{\beta(\beta + 1)}} \approx I_{ref} \left( 1 - \frac{n}{\beta^2} \right)$

Note: Now,  $I_{ref} = \frac{V_{cc} - 2V_{BE(on)}}{R_{ref}}$

Problem: For power savings reasons, oftentimes very small bias currents are needed, on the order of  $\mu A$ . This might force for large an  $R_{ref}$  in the above bipolar  $V_{BE}$  generator.

Ex.

1 emitter } 1x device  
base  
↓  
10 emitter } 10x device  
base

i.e., larger emitter area: → Layout like this to get more accurate ratio.

If  $Q_1$  is 10x larger than  $Q_2$ .

$\therefore I_{C1} = 10 I_{C2} \rightarrow I_o \approx I_{ref}/10$

$\therefore I_o = \frac{(V_{cc} - V_{BE(on)})}{10 R_{ref}} \rightarrow R_{ref} = \frac{V_{cc} - V_{BE(on)}}{10 I_o}$

Ex.  $I_o = 5 \mu A$ ,  $V_{cc} = 30V$

$R_{ref} \approx \frac{30}{5 \mu A} = 600k\Omega$  ← That's way too big!  
(Yes, there's only one of them on the chip, but this takes up too much space!)

The Low Current Solution: Wilson Current Source

⇒ scale  $I_{C2} = I_o$  by reducing  $V_{BE2}$  (relative to  $V_{BE1}$ ):

Do this by emitter degenerating  $Q_2$  via  $R_2$

$R_o = r_{o2}(1 + g_m R_2)$

$V_{B1} = V_{B2} + V_{R2} = V_{B2} + \frac{1}{\alpha} I_{C2} R_2 \approx V_{B2} + I_{C2} R_2$   
 $I_{C2} R_2 = V_{B1} - V_{B2} = V_T \ln \frac{I_{C1}}{I_{C2}} - V_T \ln \frac{I_{C2}}{I_{C2}}$   
 $I_{C2} R_2 = V_T \ln \frac{I_{C1}}{I_{C2}}$  (Assuming  $Q_1$  &  $Q_2$  are matched.)  
 $I_{C2} R_2 = V_T \ln \frac{I_{ref}}{I_0}$   
 $I_0 R_2 = V_T \ln \frac{I_{ref}}{I_0}$

Rule of Thumb: $V_{B1} - V_{B2}$	$I_{C2} = I_0$
120mV	$\frac{1}{2} I_{ref}$
42mV	$\frac{1}{5} I_{ref}$
60mV	$\frac{1}{10} I_{ref}$
120mV	$\frac{1}{100} I_{ref}$

→ Set example again  
 Ex: scale by 100x using Widlar source  
 $V_{B1} - V_{B2} = 120mV \rightarrow R_2 = \frac{120mV}{5\mu A} = 24k\Omega$   
 $I_{ref} = 500\mu A \rightarrow R_{ref} = \frac{20V}{500\mu A} = 40k\Omega$   
 More accurate than 600kΩ before.  
 If want smaller, scale by 100x instead.

Another advantage of the Widlar: larger  $R_o \therefore$  a more ideal current source:  
 $R_o = r_{o2}(1 + g_{m2} R_2)$

Issue: Output Swing (Headroom)

Assuming the upper part is flat (not linear) → nonlinear  
 What's the minimum voltage?  
 Smallest  $V_{GS}$  for which  $M_1$  still behaves as a good current source.

Gain  $\sim g_{m1} R_o$  (fringe)  
 "large  $R_o$  need  $M_1$  saturated!"  
 slope  $= \frac{1}{r_o} = \frac{1}{\lambda I_D}$   
 slope = large  $\rightarrow R_o = \text{small} \rightarrow$  we want to avoid the linear MOS region (fringe)

$$V_{Dsat} = V_{GS1} - V_{t1} = \underbrace{V_{ov}}_{\text{overdrive voltage}} \approx \Delta V = V_{OD}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$V_{Dsat} = \Delta V = V_{ov} = V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left( \frac{W}{L} \right)}}$$

$\swarrow$   
 $V_{GS} = V_t + V_{ov}$  (for long-channel devices)  
 (for short-channel it's different)

The min. voltage that still keeps  $M_1$  as a good current source:

$$V_{om1n} = V_{Dsat1} = V_{ov}$$

$\therefore$  the output swing is:

$$V_{swing, pp} = V_{DD} - V_{Dsat1} - V_{Dsat2} = V_{DD} - 2V_{ov}$$

$\nearrow$   
 peak-to-peak