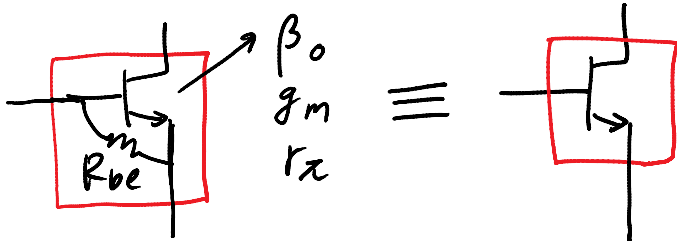


Discussion #2


Monday, February 06, 2012

4:21 AM

Problem: inspection formula for adding R_{be} parallel with r_π



What is the new β' , g_m' & r_π' ?

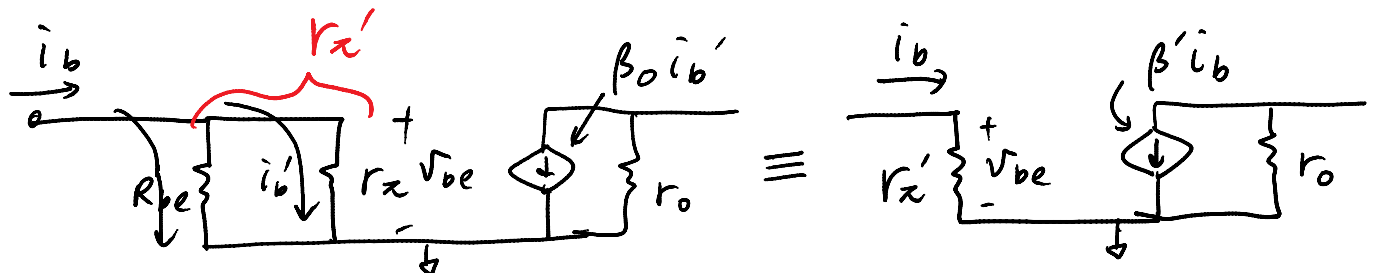

$$\beta' i_b = \beta_0 i_b' = \beta_0 \frac{R_{be}}{R_{be} + r_\pi} i_b$$

$$\Rightarrow \beta' = \frac{R_{be}}{R_{be} + r_\pi} \beta_0$$


$$r_\pi' = r_\pi \parallel R_{be}$$

$$= \frac{R_{be}}{R_{be} + r_\pi} \cdot r_\pi$$

$$g_m r_\pi = \beta_0 \Rightarrow g_m' r_\pi' = \beta' \Rightarrow g_m' = g_m$$

Ex:

Write the expression of R_{in} for

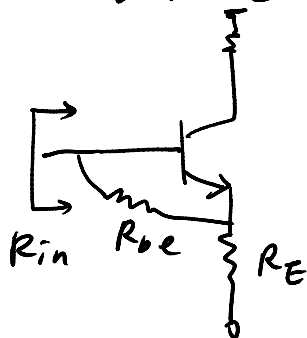


Method 1: small-signal analysis

Method 2: use inspection formulas

Wednesday, February 01, 2012
12:27 PM

Method 1 Use Small-signal model

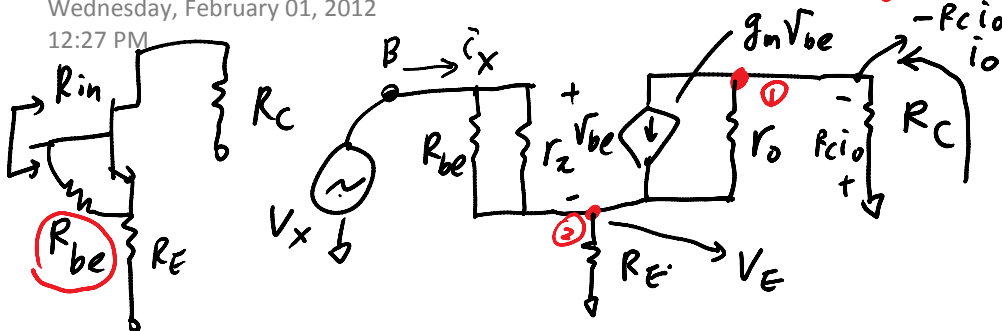

R_{in}'
 β'
 g_m'

$$\textcircled{1} \quad g_m V_{be} = i_o + (V_E + R_C i_o) g_o$$

$$\textcircled{2} \quad \frac{V_x - V_E}{r_{\pi}'} + i_o = \frac{V_E}{R_E}$$

$$\textcircled{2} \quad i_o = V_E g_E - (V_x - V_E) \cdot g_{\pi}' \quad \textcircled{3}$$

$$\Downarrow \quad V_E g_o + (R_C g_o + 1) [V_E g_o - (V_x - V_E) g_{\pi}'] = g_m (V_x - V_E)$$

$$\textcircled{V_E} [g_o + (1 + g_o R_C) g_E + (1 + g_o R_C) g_{\pi}' + g_m] =$$

$$R_{in} = \frac{V_x}{i_x} = \frac{V_x}{(V_x - V_E) g_{\pi}'}$$

$$V_E = \square V_x$$

$$= \frac{V_x}{(V_x - \square V_x) g_{\pi}'}$$

$$\square = \frac{g_m + g_{\pi}' (1 + g_o R_C)}{g_o + (1 + g_o R_C) R_E + (1 + g_o R_C) g_{\pi}'}$$

$$= \frac{1}{(1 - \square) g_{\pi}'}$$

$$1 - \square = \frac{\frac{g_o}{1 + g_o R_C} + g_E + g_m}{\frac{g_o + g_m}{1 + g_o R_C} + g_m + g_{\pi}'}$$


if $r_o \rightarrow \infty$
 $g_o \rightarrow 0$

$$\frac{g_E}{g_m + g_E + g_{\pi}'}$$

$$R_{in} = \frac{r_{\pi}'}{1-\alpha} = r_{\pi}' \cdot \frac{g_m + g_E + g_{\pi}'}{g_E}$$

$$= r_{\pi}' \left(\frac{g_m}{g_E} + 1 + \frac{g_{\pi}'}{g_E} \right)$$
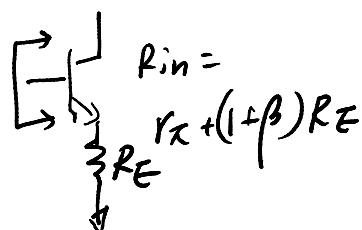
$$= r_{\pi}' (1 + g_m R_E + g_{\pi}' \cdot R_E)$$




$$= r_{\pi}' + g_m R_E r_{\pi}' + R_E$$

$$= r_{\pi}' + (1 + \underline{g_m r_{\pi}'}) R_E \quad (*)$$

where $r_{\pi}' = r_{\pi} \parallel R_{be}$


Method 2: use inspection formulas

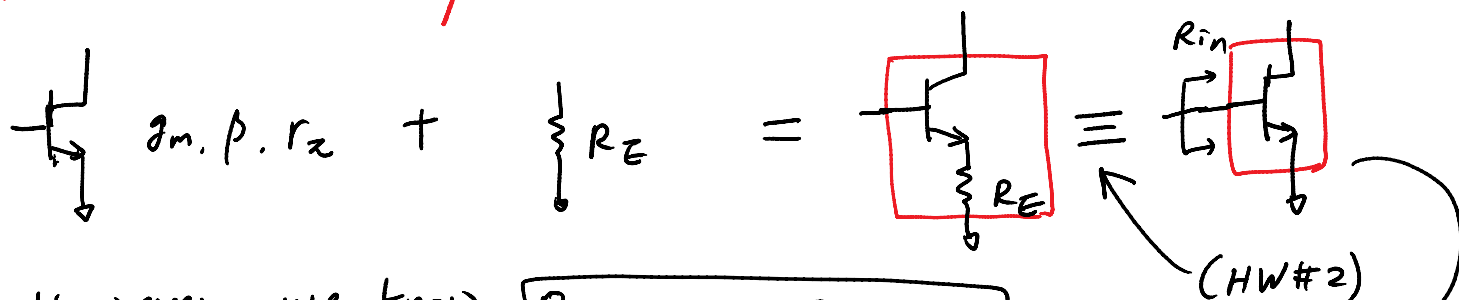

However, we know

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$


Then use

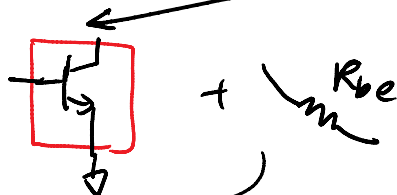

adding R_{be} yields

$$\left. \begin{aligned} \beta' &= \frac{R_{be}}{R_{be} + r_{\pi}} \beta_0 \\ r_{\pi}' &= \frac{R_{be}}{R_{be} + r_{\pi}} r_{\pi} \end{aligned} \right\} \text{inspection formulas}$$

actually is

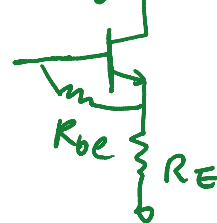

$$\Rightarrow R_{in} = r_{\pi}' + (1 + \beta') R_E \quad \text{--- same result as } (*)$$