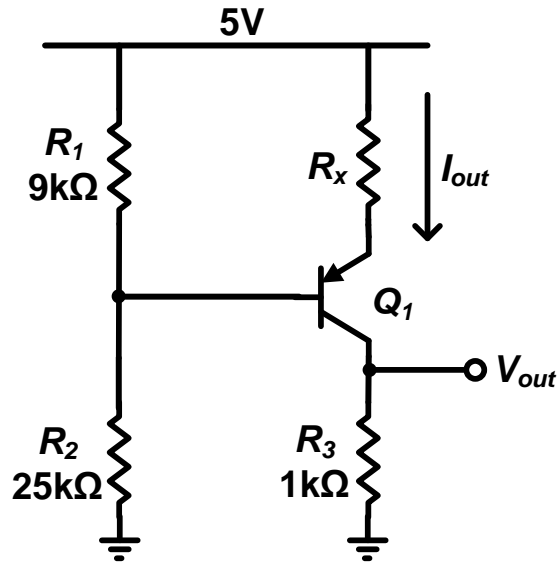


Issued: Thursday, Jan.24, 2013

Due (at 8 a.m.): Friday, Feb. 1, 2013, in the EE 140/240A HW box near 125 Cory.

1. Calculate the built-in potential, depletion layer depths, and maximum field in an abrupt pn junction in silicon with doping densities $N_A = 8 \times 10^{15}$ atoms/cm³ and $N_D = 10^{17}$ atoms/cm³. Assume that the edges of the depletion region are sharply defined.
 - (a) Assume a reverse bias of 4V.
 - (b) Repeat (a) for zero external bias and 0.4V forward bias.
2. Calculate the zero-bias junction capacitance for the example in Problem 1, and also calculate the value at 4V reverse bias and 0.4V forward bias. Assume a junction area of 2×10^{-5} cm².
3. Derive and sketch the complete small-signal equivalent circuit for a bipolar transistor biased so that $I_C = 0.2$ mA, $V_{CB} = 3$ V, $V_{CS} = 4$ V. Device parameters are: $C_{je0} = 20$ fF, $C_{\mu0} = 10$ fF, $C_{CS0} = 20$ fF, $\beta_0 = 100$, $\tau_F = 15$ ps, $\eta = 10^{-3}$, $r_b = 200\Omega$, $r_c = 100\Omega$, $r_{ex} = 4\Omega$, and $r_{\mu} = 5\beta_0 r_o$. Assume $\psi_0 = 0.55$ V for all junctions.
4. An NMOS transistor has parameters $W = 10\mu\text{m}$, $L = 1\mu\text{m}$, $k' = 190 \frac{\mu\text{A}}{\text{V}^2}$, $\lambda = 0.024\text{V}^{-1}$, $t_{ox} = 80\text{\AA}$, $\phi_f = 0.3$ V, $V_{t0} = 0.6$ V, and $N_A = 5 \times 10^{15}$ cm⁻³. Ignore velocity saturation effects.
 - (a) Sketch the $I_D - V_{DS}$ characteristics for V_{DS} from 0 to 3V and $V_{GS} = 0.5$ V, 1.5V and 3V assume $V_{SB} = 0$.
 - (b) Sketch the $I_D - V_{GS}$ characteristics for $V_{DS} = 2$ V as V_{GS} varies from 0 to 2V with $V_{SB} = 0$, 0.5V, and 1V.
 - (c) Derive and sketch the complete small-signal equivalent circuit for the device with $V_{GS} = 1$ V, $V_{DS} = 3$ V and $V_{SB} = 1$ V. Use $\psi_0 = 0.7$ V, $C_{sb0} = C_{db0} = 20$ fF, and $C_{gb} = 5$ fF. Overlap capacitance from gate to source and gate to drain is 2fF.
 - (d) Under the bias condition in (c), calculate the frequency of unity current gain of this device.
5. In the circuit shown below, find I_{out} and V_{out} for (a) $R_x = 4$ k Ω , (b) $R_x = 2$ k Ω , and (c) $R_x = 1$ k Ω . Assume $V_{BE(on)} = 0.7$ V, $V_{CE(sat)} = 0.2$ V, and $\beta \rightarrow \infty$.



6. Calculate the DC operating points including the current flowing through each branch and DC voltage at each node for the circuits shown:

$$V_{DD} = V_{CC} = 5V, \beta_f = 100, V_A \rightarrow \infty, r_b = 0, V_{BE(on)} = 0.7V, V_{CE(sat)} = 0.2V,$$

$$k'_n = 140 \frac{\mu A}{V^2}, V_{tn} = 0.7V, k'_p = 40 \frac{\mu A}{V^2}, V_{tp} = -0.8V, \lambda = 0$$

$$\left(\frac{W}{L}\right)_1 = \frac{10\mu m}{0.5\mu m}, \left(\frac{W}{L}\right)_2 = \frac{25\mu m}{0.5\mu m}, \left(\frac{W}{L}\right)_3 = \frac{10\mu m}{0.5\mu m}, \left(\frac{W}{L}\right)_4 = \frac{15\mu m}{0.5\mu m}$$

