

PROBLEM SET #10


Issued: Thursday, Apr. 11, 2013

Due (at 8 a.m.): Friday, Apr. 19, 2013, in the EE 140/240A HW box near 125 Cory.

1. Consider a two-pole op amp with open-loop transfer function $A(s) = \frac{a_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$. Assume that $a_0=60\text{dB}$, and ω_{p1} is the dominant pole located at $2\pi \times 100\text{kHz}$.
- Find the value of ω_{p2} so that the op amp would have a 45° phase margin in unity-gain feedback. Sketch the magnitude and phase Bode plots of the op amp's open-loop transfer function.
 - Let $\omega_{p2}=2\pi \times 10\text{MHz}$ for this and all remaining parts of this problem. Find the op amp's unity-gain frequency and unity-gain phase margin. Sketch the magnitude and phase Bode plots of the op amp's open-loop transfer function.
 - Given what you found in part (b), is it safe to put this op amp into unity-gain feedback? Explain why or why not.
 - We would like to compensate the op amp by using a zero to cancel ω_{p2} , so that its open-loop transfer function is now $A(s) = \frac{a_0(1+s/\omega_z)}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$, with $\omega_z=\omega_{p2}$. What is the compensated op amp's unity-gain frequency and unity-gain phase margin?
 - Realistically, we are unable to match ω_z and ω_{p2} exactly. Repeat part (d) for $\omega_z=2 \times \omega_{p2}$ and $\omega_z=0.5 \times \omega_{p2}$.

2. Consider an op amp whose open-loop transfer function is shown in Fig. PS10.2-a. Assume that the op amp circuit includes a stage such as that of Fig. PS10.2-b with $C_x = 100\text{pF}$, $C_y = 5\text{pF}$, and $g_m = 40\text{mA/V}$, that the pole at f_{P1} is caused by the input circuit of that stage, and that the pole at f_{P2} is introduced by the circuit output. Find the value of the compensating capacitor such that the closed-loop amplifier with resistive feedback is stable for any gain (i.e., for β up to unity) if the compensating capacitor is connected:

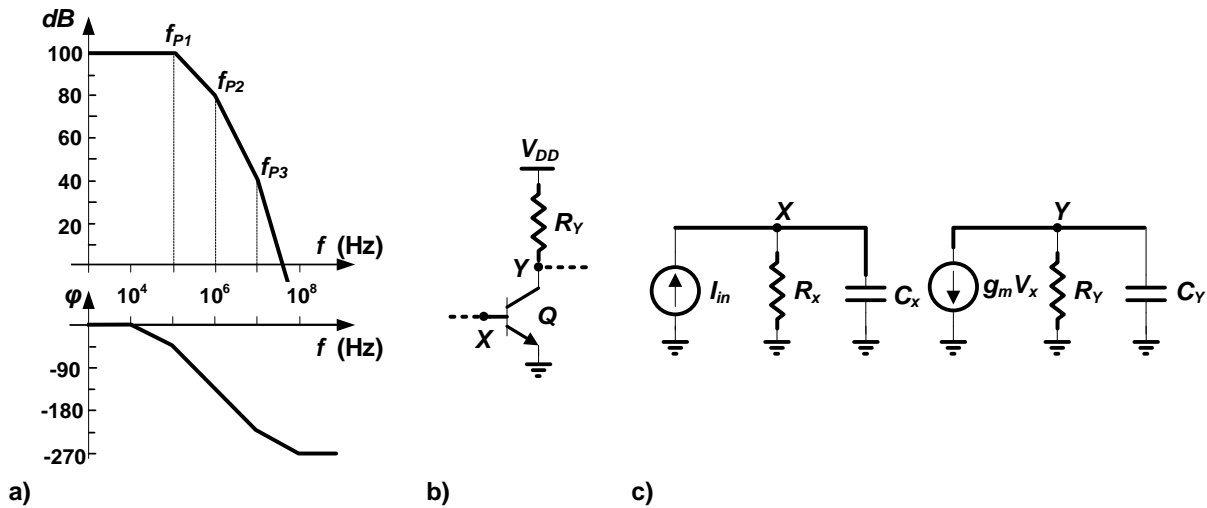- (a) between the input node X and ground,
- (b) between X and Y , in the feedback path of the transistor.



3. A two-stage op amp has a compensation capacitor connected between the input and the output of its second stage. Assume that the frequency of its second-pole is 60MHz and that this frequency stays constant with changes in the compensation capacitor. Assume the input stage generates a transconductance of 0.70mA/V, and the second stage provides a voltage gain of 100. With the feedback configuration shown in Fig. PS10.3, determine the maximum amplitude of the circuit's closed-loop gain due to frequency peaking for the following compensation capacitances:

- (a) 0.25pF
- (b) 0.50pF
- (c) 0.60pF

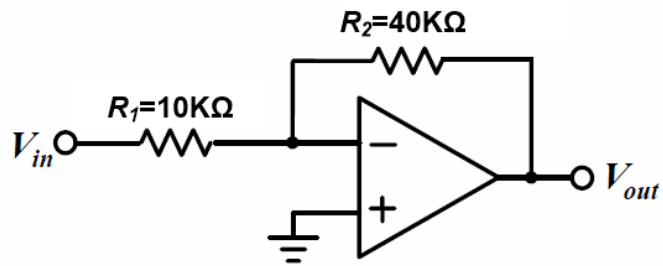


Figure PS10.3