

PROBLEM SET #3

Issued: Thursday, Feb. 7, 2013

Due (at 8 a.m.): Friday, Feb. 15, 2013, in the EE 140/240A HW box near 125 Cory.

1. Referring to the multistage amplifier circuit shown in Fig. PS3.1:

- Calculate the DC operating points including the current flowing through each branch and DC voltage at each node.
- Calculate transistor small-signal parameters (i.e. g_m , r_{π} , r_o , C_{π} , C_{μ} , C_{gs} , C_{gd})
- Provide expressions and calculate the numerical values for the input resistance, R_{in} ; output resistance, R_{out} ; first stage gain, v_{o1}/v_s ; second stage gain, v_{o2}/v_{o1} ; third stage gain, v_{out}/v_{o2} and total gain, v_{out}/v_s .
- Estimate the low frequency cut-off f_L and high frequency cut-off f_H of the amplifier.

BJT parameters:

$$\beta=100, V_A=50V, V_{BE(on)}=0.7V, V_{CE(SAT)}=0.2V, \tau_F=150ps, C_{je}=50fF, C_{\mu}=1pF, V_T=25mV.$$

MOS parameters:

$$V_{th0}=0.5V, k'=165.3\mu A/V^2, W/L=20\mu m/1\mu m, \lambda=0.05V^{-1}, C_{ox}=30\mu F/cm^2, C_{ol}=1pF, \gamma=0.$$

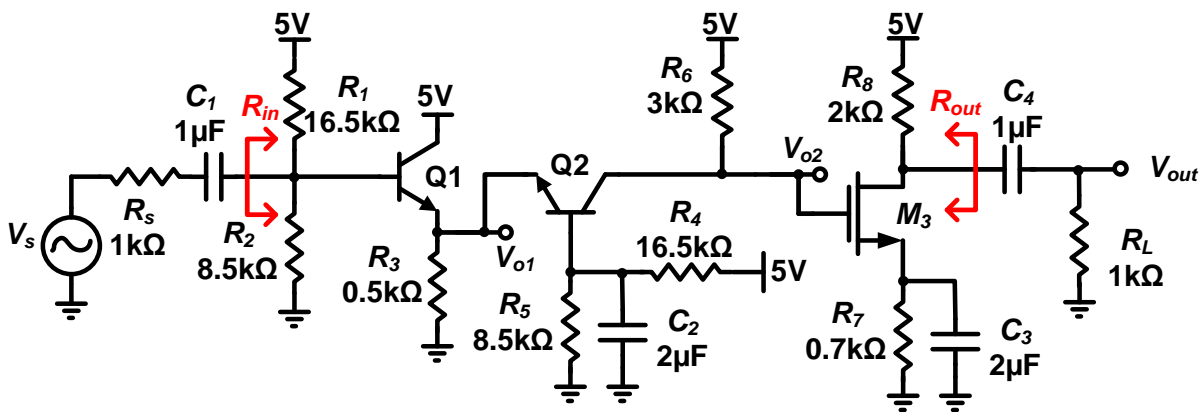


Fig. PS3.1

2. For the small-signal circuits shown in Fig. PS3.2, assume all transistors are identical and have the following parameters:

$$I_D = 2 \text{ mA}, W = 50 \mu\text{m}, L_{drwn} = 130 \text{ nm}, L_d = 15 \text{ nm}, X_d = 0, k_p' = 200 \mu\text{A}/V^2, \gamma = 0, \lambda = 0, C_{ox} = 15 \text{ fF}/\mu\text{m}^2, C_{sb} = C_{db} = 0.$$

Given $R_S = 500 \Omega$, $R_L = 1 \text{ k}\Omega$, and $C_L = 50 \text{ fF}$:

- Calculate the mid-band, small-signal voltage gain v_o/v_i for each circuit.
- Calculate and compare the high 3-dB cutoff frequencies of the two circuits.

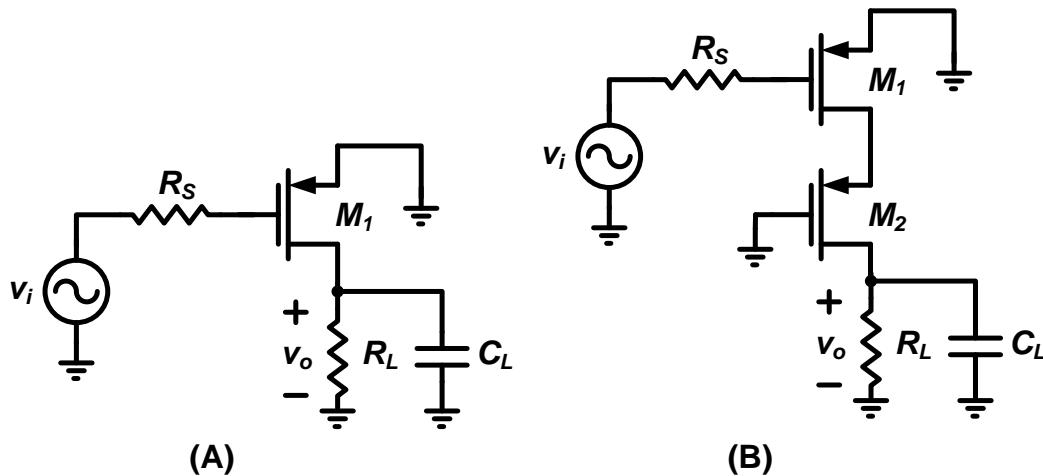


Fig. PS3.2

3. For the both circuits depicted in PS3.3, calculate the input impedance, output impedance, and voltage gain, v_{out}/v_{in} . Assume $\beta = 100$ and $V_A = 50V$. Repeat assuming $V_A = \infty$.

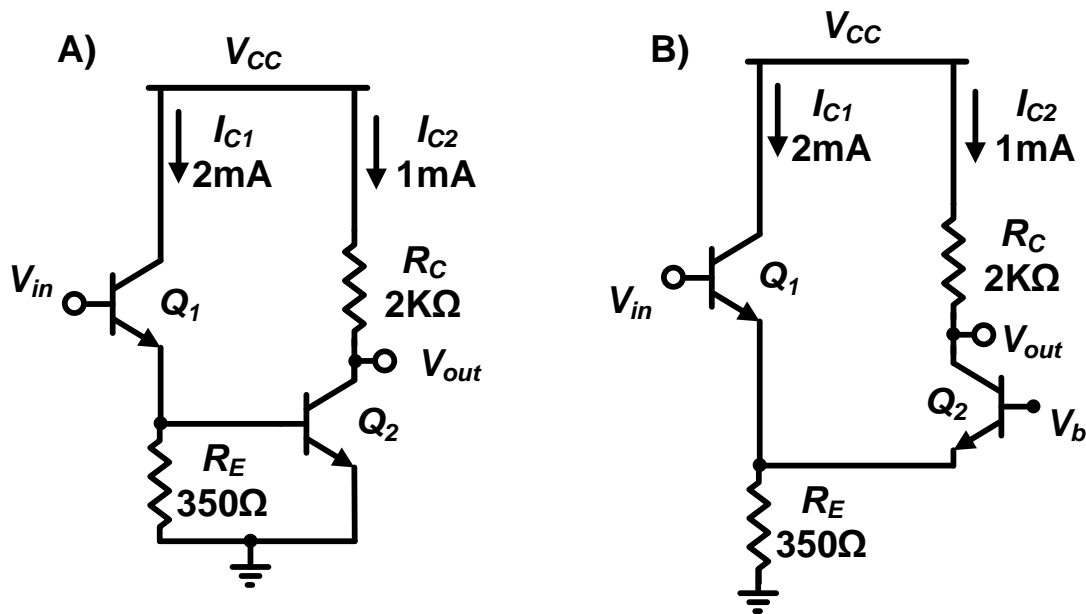


Fig. PS3.3

4. Design the common-base stage shown in Fig. PS3.4 for a voltage gain of 20 and an input impedance of 50Ω using a transistor with $\beta = 100$ and $V_A = 20V$. Assume a voltage drop of $10V_T = 260mV$ across R_E so that this resistor does not affect the input impedance significantly. Also, assume the current flowing through R_I is approximately 10 times the base current, and the lowest frequency of interest is 200Hz.

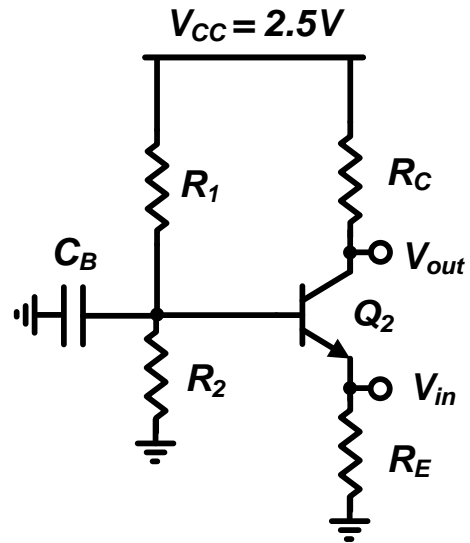


Fig. PS3.4